

# R2A20113A

R03AN0006EJ0100

Rev.1.00

## Application Note

Sep 13, 2011


### 1. Outline

The R2A20113A is the active power factor correction controller that operates in the critical conduction mode (CRM).

The R2A20113A is the voltage mode CRM, such that the Power MOSFET controlled by this IC is turned on when the current of the boost inductor reaches zero and also controlled to keep ON time of the Power MOSFET constant. So, the peak current of the boost inductor follows the input voltage waveform.

The voltage mode CRM PFC controller does not need the input voltage sense line. So, the power loss of the system can be reduced.

### 2. Block Diagram

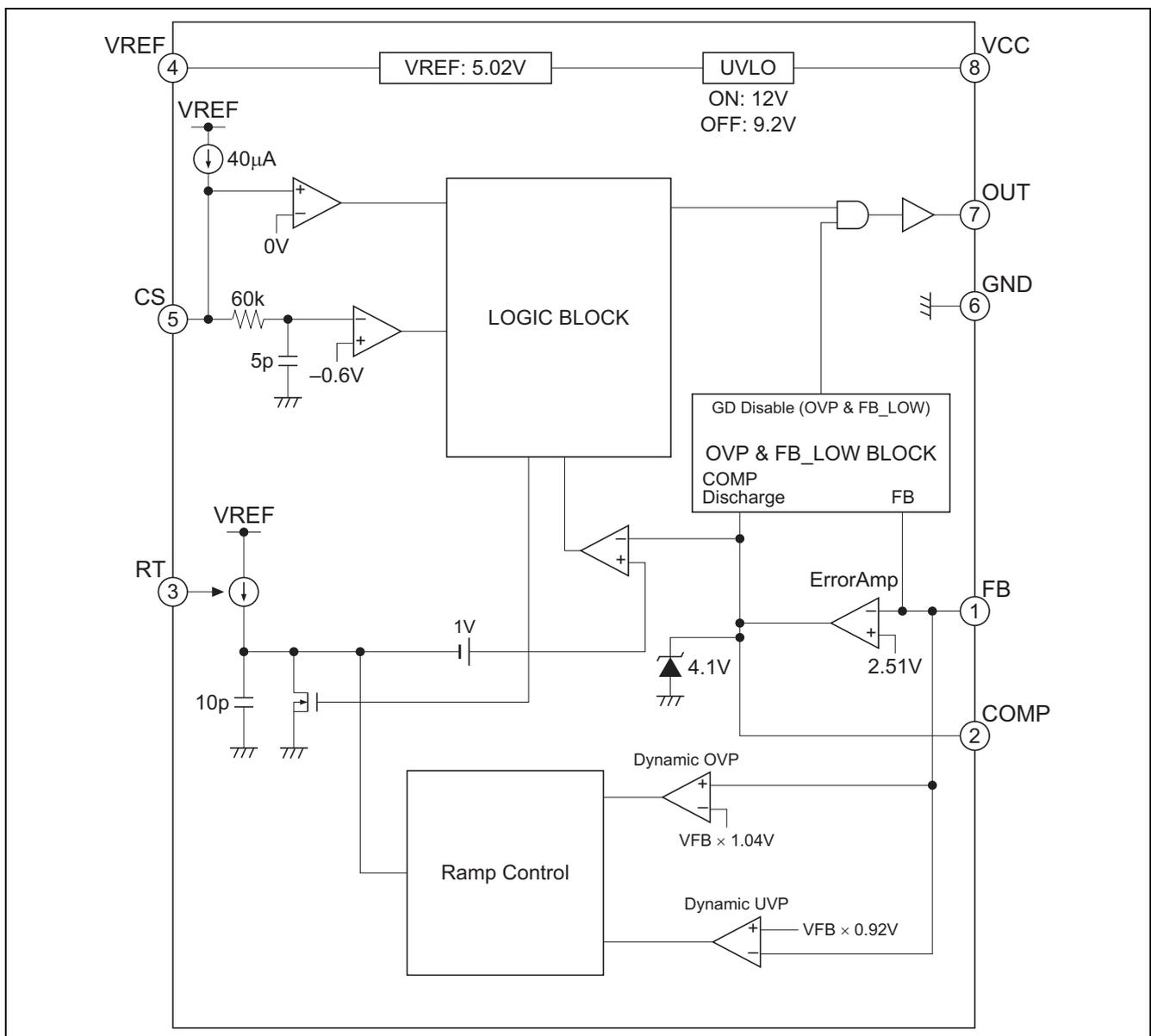

### 3. Descriptions of the R2A20113A Functional Blocks

#### 3.1 Reference Voltage Output (VREF)

R2A20113A has 5 V reference voltage output terminal (VREF). (accuracy:  $5.02 \text{ V} \pm 1.5\%$ )

VREF pin outputs 5 V when the UVLO protection is released.

If VREF output is used for an external circuit, the load should be under the current source capacity of 5 mA (Max).

#### 3.2 Zero-Current Detection

The Zero-Current Detection (ZCD) detects the zero-current of the inductor, and the Power MOSFET is turned on at that time. After being converted from the GND-current to the voltage by the sensing resistor  $R_{cs}$ , the ZCD signal is supplied to the CS-pin.

The threshold voltage for ZCD is 0 V (typ.). The delay time is set to  $0.44 \mu\text{s}$ , in which the drain voltage of the MOSFET decreases after the threshold voltage is detected.

Due to the offset of the zero-current, it is advised to tune the threshold voltage for ZCD to the negative side by inputting the resistor for the filtering between  $R_{cs}$  and the CS-pin.

Furthermore, as the threshold voltage of the ZCD is small, such as several mV, R2A20113A has the  $0.2 \mu\text{s}$  mask function to prevent erroneous operations due to noises. By the  $0.2 \mu\text{s}$  mask function, the output signal of the ZCD would be sent to the latter part, only when the zero current continues over the  $0.2 \mu\text{s}$  mask period.

The delay time is fixed and includes  $0.2 \mu\text{s}$  of the mask function.

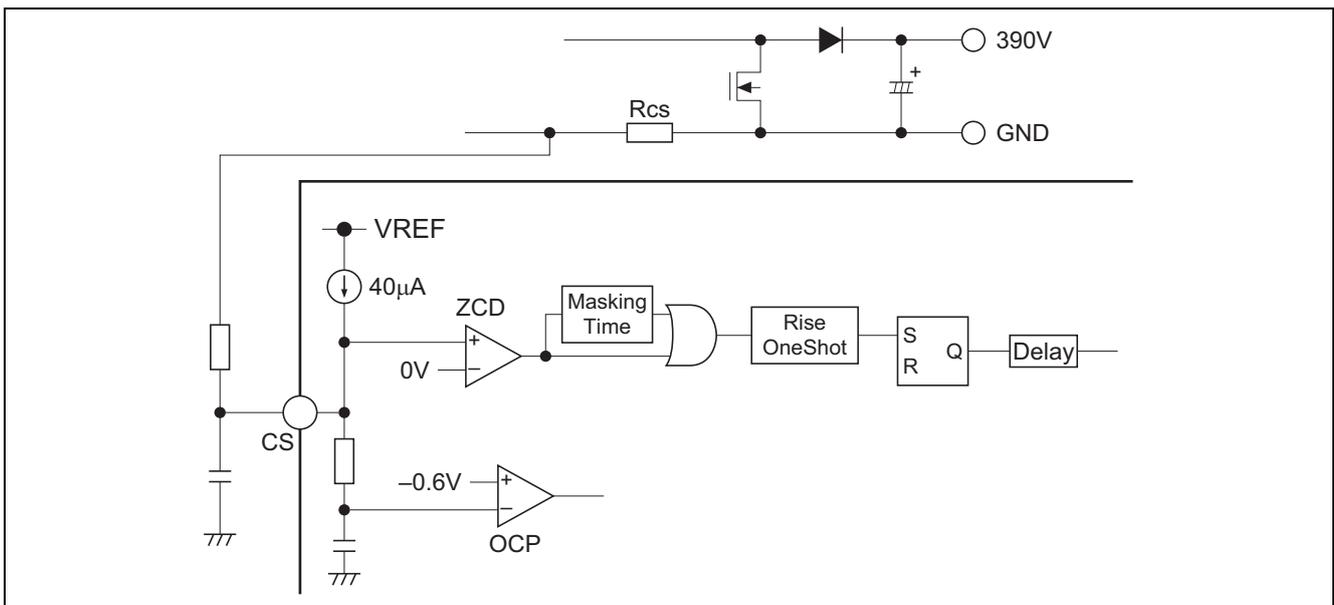


Figure 1

#### 3.3 Error Amplifier

The error amplifier of PFC control is a transconductance amplifier.

The output current changes according to a voltage difference between FB pin voltage and the internal reference voltage.

COMP pin which is output of error amplifier is clamped by 4.1 V (typ).

### 3.4 RAMP Slope (IC-Internal)

The slope at point RAMP within the chip depends on the current determined by the external resistor  $R_{RT}$  on the RT pin and on-chip 10-pF capacitor.

The resistor  $R_{RT}$  is connected between the RT pin and the GND level.

The maximum ON time,  $t_{onmax}$ , is determined when the output voltage of the error amplifier is 4.1 V (typ.). The RAMP circuit starts charging the RAMP capacitor when the ZCD circuit detects inductor zerocurrent and at the same time, the voltage at the point, "RAMP portion" is smaller than 0.2 V.

The RAMP circuit starts discharging the "RAMP portion" when the RAMP slope reaches COMP voltage.

And when the output voltage of the error amplifier is smaller than 1 V, the Power MOSFET ON time is zero, due to the built-in level shift voltage of 1 V.

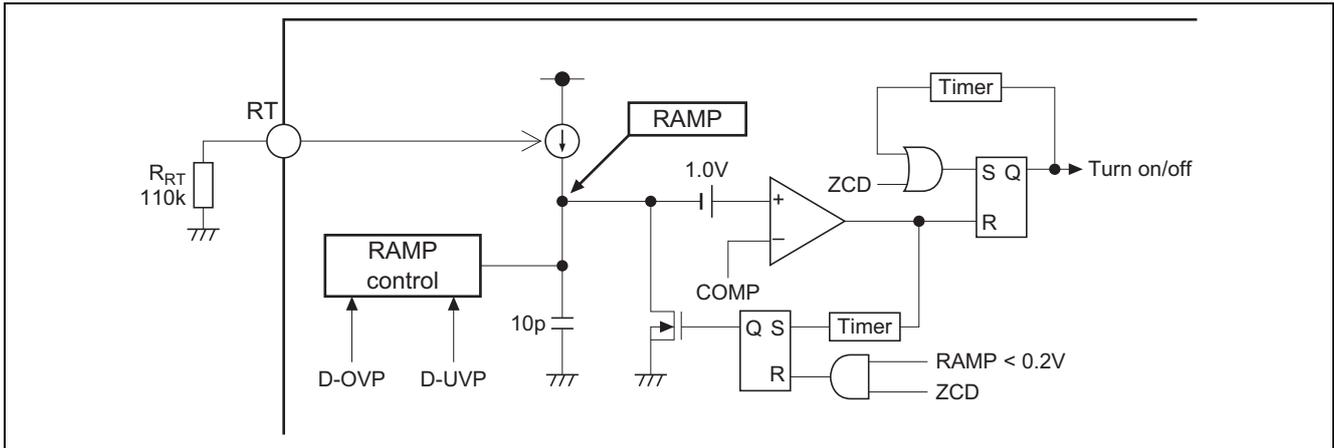


Figure 2

### 3.5 Output Stage

R2A20113A contains the single totem-pole output stage.

The drivability is +900 mA/-500 mA (peak). "+" means that the current flows into the IC.

Basically, direct driving of the power MOSFET is possible. However, please adjust drivability of the driver circuit on the board by selecting the appropriate parameters of the circuit according to the characteristics of the Power MOSFET to be used.

Due to zero-current switching, the speed of turning-off affects power loss more strongly than the speed of turning-on. The following figures show examples of driver circuits.

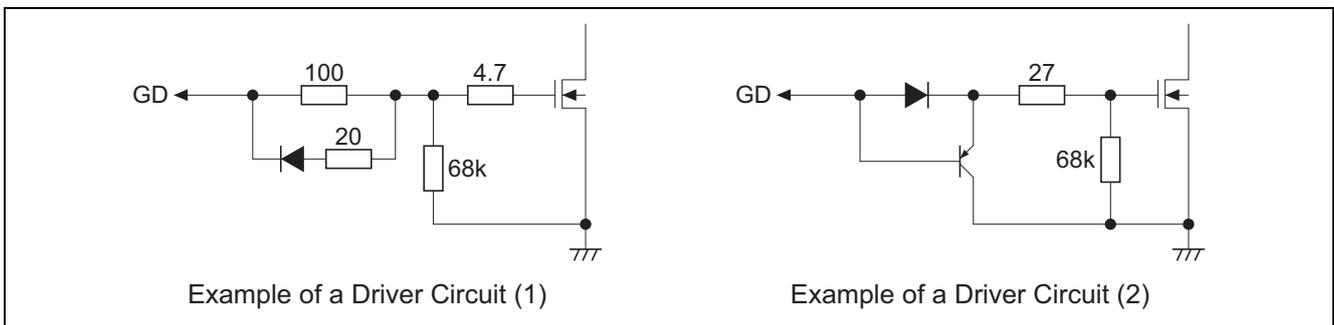


Figure 3

### 3.6 Protection

R2A20113A has the over voltage protection for PFC output voltage, feedback open loop protection, the over current protection, off time control function and so on.

#### 3.6.1 Static Over Voltage Protection (S-OVP)

Static Over Voltage Protection stops an OUT signal when FB pin voltage reaches  $1.08 \times V_{FB}$  (2.51 V typ).

A Power MOSFET turns off quickly and S-OVP keeps stopping an GD signal till FB pin voltage reaches  $1.08 \times V_{FB}$  (2.51 V typ) – 100 mV.

#### 3.6.2 Feedback Low Detection (FB-LOW)

The FeedBack LOW protection discharges COMP pin voltage during FB pin voltage is under 0.3 V.

Therefore an GD signal does not appears in this case.

#### 3.6.3 Dynamic Over Voltage Function (D-OVP)

Dynamic Over Voltage Protection Function starts to decrease the On time of the MOSFET when FB pin voltage reaches  $1.04 \times V_{FB}$  (2.51 V typ).

The Power MOSFET ON time is decreased gradually, so that, the audio noise, that occurs when the current of inductor stops suddenly, can be avoided.

#### 3.6.4 Dynamic Under Voltage Function (D-UVP)

When the voltage of the FB-pin is less than  $0.92 \times V_{FB}$ , R2A20113A starts to increase the On time of the MOSFET regardless of the COMP voltage. The maximum On time while D-UVP is working is twice as long as the On time at steady state.

This function is active when once the voltage of the FB-pin is more than  $0.96 \times V_{FB}$  after the IC starts.

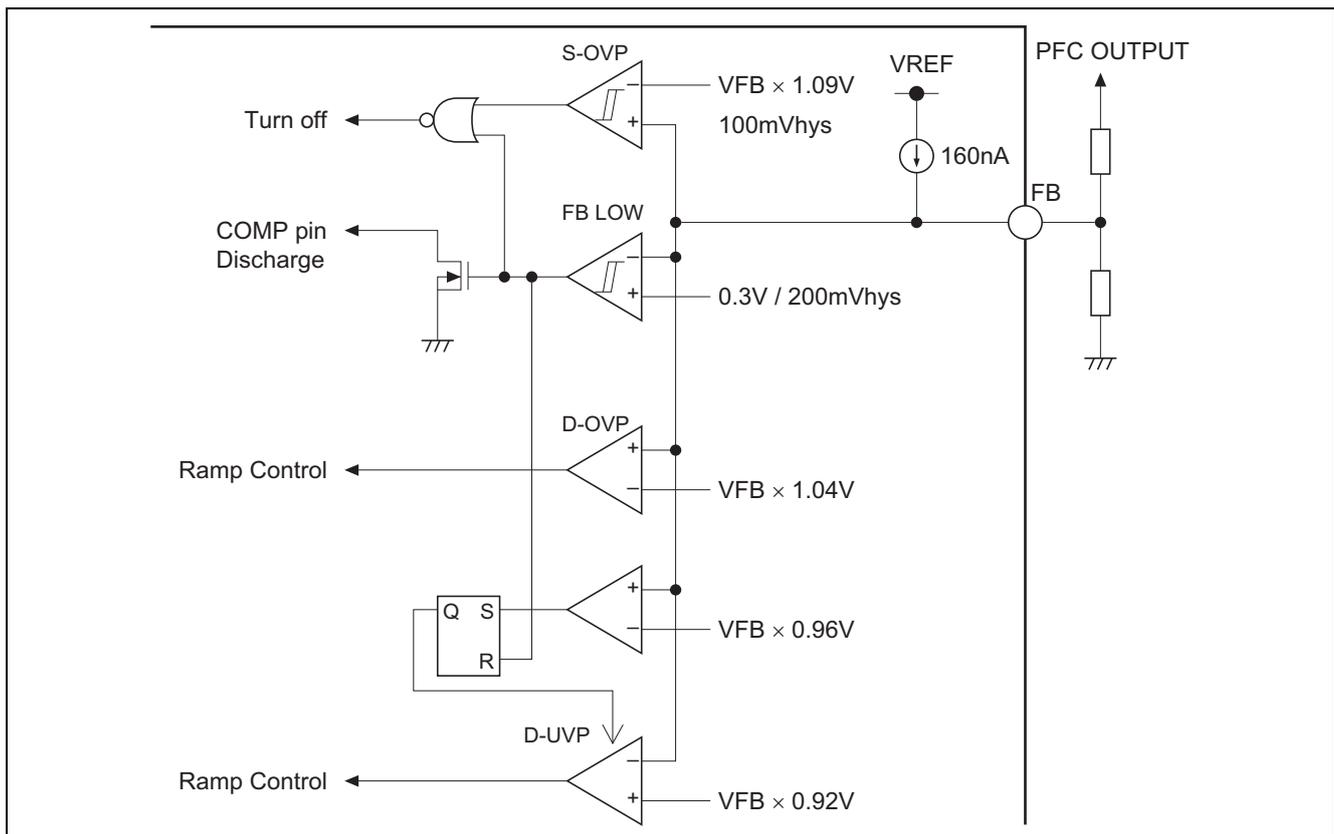


Figure 4

### 3.6.5 Over Current Protection (OCP)

This function defend Power MOSFET, boost inductor and boost Diode from over current. OCP pin senses the each Power MOSFET source current by using an external sense resistor. When OCP pin reaches  $-0.6V$ , an output is stopped with pulse-by-pulse.

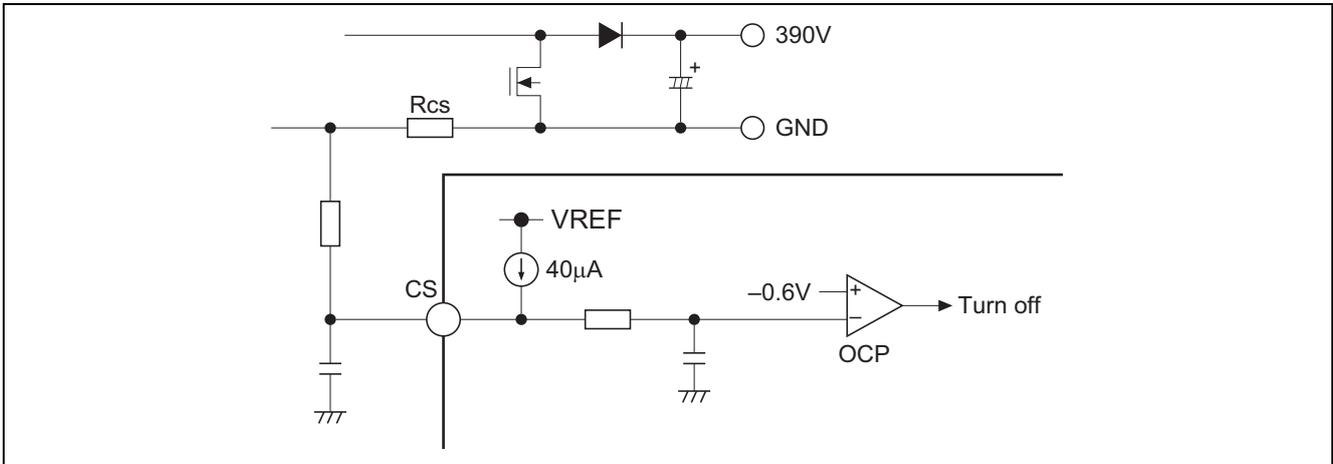


Figure 5

### 3.6.6 Off Time Control (Frequency Limit Function)

By masking ZCD signals for a certain period after the MOSFET shifts from On to Off, the frequency of the MOSFET switching is limited. So the decrease of the efficiency due to the MOSFET heating during the light load would be avoided.

The masking period is  $1.4\ \mu s$  (typ.).

ZCD signals are ignored during the masking period after the MOSFET shifts from On to Off. At the first signal of ZCD just after the masking period, the MOSFET is turned on.

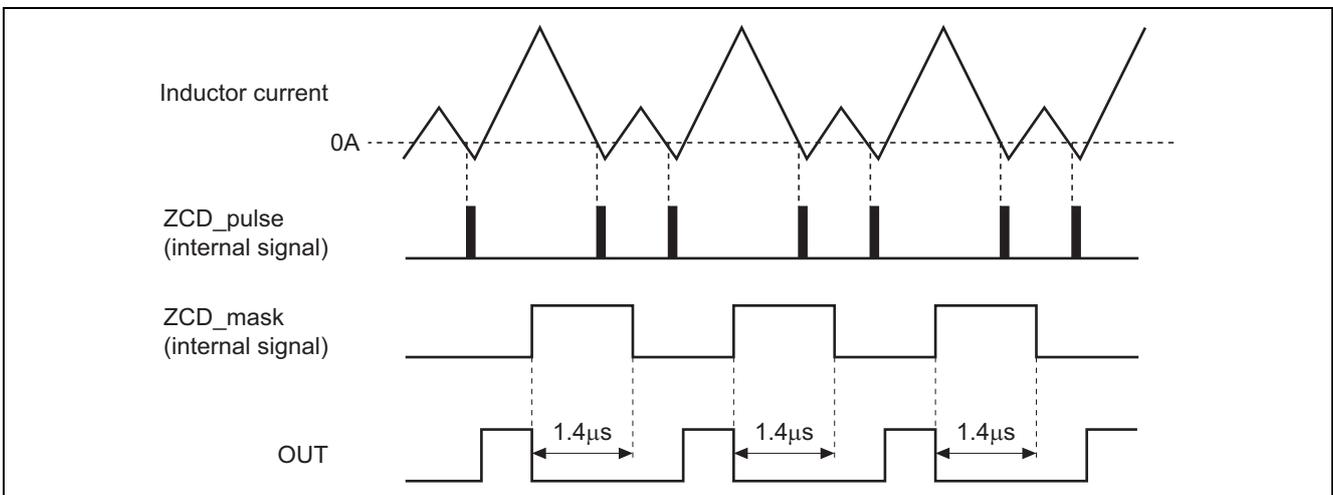



Figure 6 Example of Off Time Control

### 3.6.7 Restriction Function on Restart Mode

Although R2A20113A contains the function which turns on the MOSFET forcedly when there is no ZCD signal in a certain period, 150  $\mu$ s (typ.), the IC stops the Restart mode in order to prevent the high current from flowing into the MOSFET under the situations as follows:

- (Example 1) The case when the inrush current flows into the output capacitor through the boost inductor at the instance of turning on the AC input voltage.
- (Example 2) The case when the peaks of the AC input voltage rectified by the diode bridge are larger than the total voltage of the PFC output voltage and the forward voltage of the boost diode.

In both examples, because the currents continue to flow into the boost inductors, the voltage of the CS-pin is negative. Under these situations like two examples above, R2A20113A stops the Restart mode.

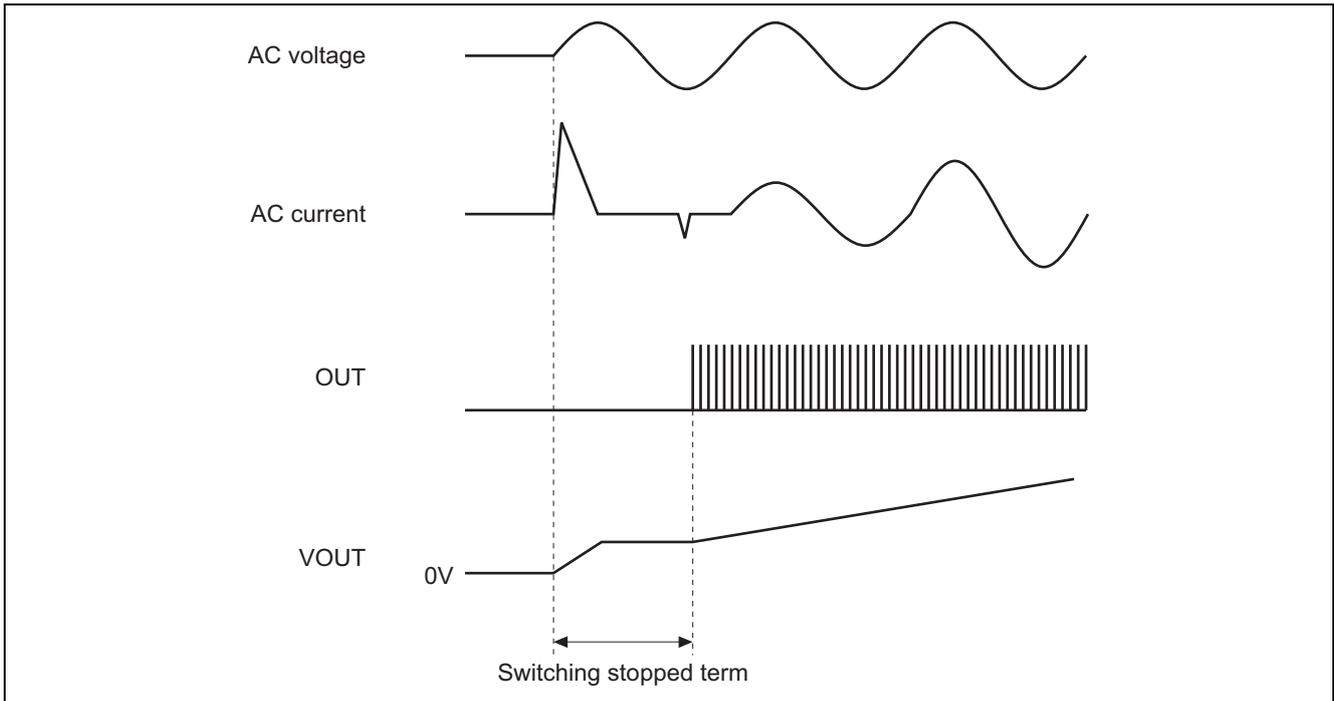

**Figure 7 Example(1) Stop of the Switching Operation**

## 4. Design Guide

### 4.1 Boost Inductor

The inductance of the boost inductor is determined by the output power and a minimum switching frequency. A minimum switching frequency must be higher than 20 kHz which is audio frequency to avoid audio noise of the inductor or the input capacitor. The frequency is generally set to the frequency higher than 50 kHz. The inductance of boost inductor is obtained by Equation 1.

Use the value around 0.9 as the conduction loss  $\eta$ .

$$L[H] = \frac{V_{ACLow}^2 \times [V_o - \sqrt{2} \times V_{ACLow}] \times \eta}{2 \times f_{SWLow} \times V_o^2 \times I_{omax}} \quad \dots (1)$$

$V_o$  [V]: PFC output voltage

$V_{ACLow}$  [V]: Effective value of minimum input voltage

$I_{omax}$  [A]: Maximum output current

$f_{SWLow}$  [Hz]: Minimum switching frequency

### 4.2 Output Capacitance

The capacitance of the output capacitor for arbitrary hold-up time is expressed in the next equation.

$$C_o[F] \geq \frac{2 \times P_o \times t_{hold}}{V_o^2 - V_{omin}^2} \quad \dots (2)$$

$t_{hold}$  [s]: Hold-up time

$V_{omin}$  [V]: Minimum output voltage

### 4.3 Power MOS FET and Boost Diode

A peak current flowing on the Power MOSFET or the boost diode is expressed in the next equation. Use the value around 0.9 as the conduction loss  $\eta$ .

$$I_{Lpk}[A] = \frac{2 \sqrt{2} \times P_o}{V_{ACLow} \times \eta} \quad \dots (3)$$

### 4.4 Overcurrent-Detecting Resistor (Rcs)


RCS is obtained by Equation 4. Use the value around 0.9 as the conduction loss  $\eta$ .

RCS might be very small, so that care should be taken in the PCB pattern impedance.

And it is suggested that a CR filter of around 1MHz is put on the OCP pin to avoid a switching noise.

Also, use the value of 1.2 as the current-limiting factor  $\beta$  to allow a margin of 20% in the normal value of  $I_{Lpk}$ .
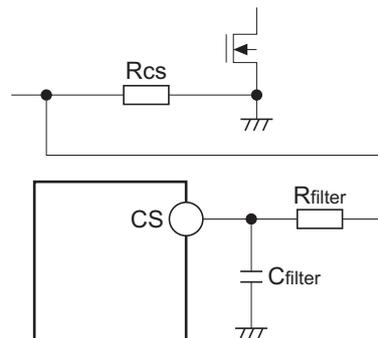
$$R_{cs}[\Omega] = \frac{0.6 \times V_{ACLow} \times \eta}{2 \sqrt{2} \times P_o \times \beta} \quad \dots (4)$$



Note: When Rcs becomes smaller, the voltage that is impressed to the terminal of CS becomes smaller. And then, it becomes easy for the restart operation to start at a high input voltage, and it causes the "sound bark", the audio noise of the inductor. This should be noted, when small value of Rcs is utilized to improve efficiency.

If you change the cutoff frequency of the filter, please set the resistance of Rfilter as a fixed value and adjust the capacitance of Cfilter. When the resistance of Rfilter is enlarged, it becomes easy for the restart operation to start.

### 4.5 The Resistance of RT

The maximum ON time (tonmax) is obtained from the following formula.  
 Use the value of around 0.9 as the conversion efficiency (the conduction loss) η.

$$T_{on\ max}[s] = \frac{2 \times L \times P_o}{V_{ACLow}^2 \times \eta} \dots (5)$$

Shown as figure 8, R2A20113A controls tonmax according to the resistance connected to the RT pin (RRT). By referring to figure 8, the resistance connected to the RT pin can be decided to achieve the tonmax calculated by the formula (5).

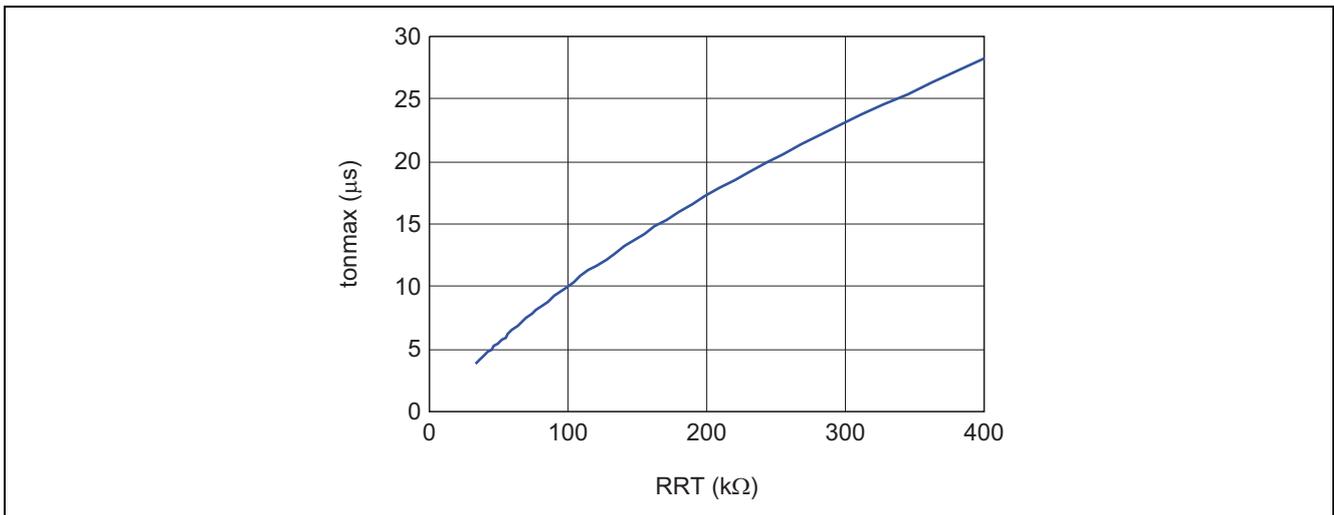


Figure 8 RRT-tonmax Characteristics

### 4.6 Soft Start Circuit and PFC OFF

If an over shoot of the PFC output or an audio noise of the inductor in start-up duration occurs and might be problems, an external soft start circuit should be added on the COMP pin.  
 Please refer to the figure 9(A) when you use the Q1 such that the tolerance of E-B reverse voltage is larger than the Vref voltage. Please refer to the figure 9(B) when you can not use the Q1 described above.  
 The soft start time is defined by CR time constant in figure 9(A) case. It is defined with charging time of COMP pin source current in figure 9(B). Though the soft start time should be decided and adjusted by the degrees of an over shoot and an audio noise level.  
 The operation of the PFC is stopped when the switch Q2 turns on and the COMP pin voltage becomes smaller than 1 V (typ).

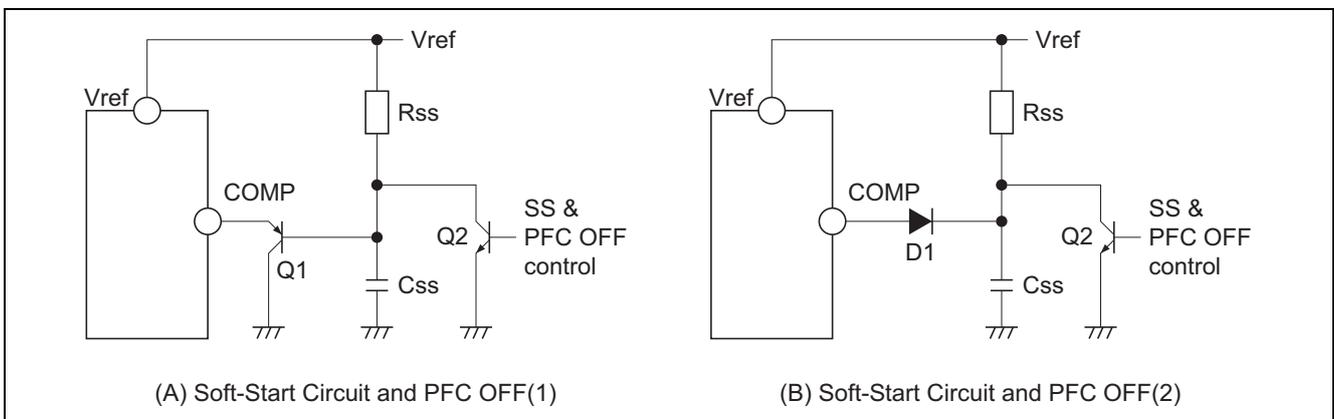


Figure 9

### 4.7 Frequency Characteristics of the Error Amplifier (gm Amplifier)

The error amplifier is a transconductance amplifier (gm amplifier). It does not need a feedback on input side. Therefore, it is possible to minimize influence on input circuit by a feedback circuit.

Gain of gm amplifier is calculated by product of transconductance and output impedance.

It is obtained by Equation 6, where  $G_{m-v}$  is transconductance of the gm amplifier and  $R_{vo}$  is an output resistor of the gm amplifier itself.

The overview of Gain-Frequency characteristics is shown in figure 10, in which the tendencies of the characteristics variation are illustrated when each parameter changes. Frequency characteristics of the amplifier is also shown in figure 11.

$$G_V = G_{m-v} \times \frac{1}{\frac{1}{R_{vo}} + \frac{1}{R_{eo1}} + j\omega C_{eo1} + \frac{1}{R_{eo2} + \frac{1}{j\omega C_{eo2}}}} \dots (6)$$

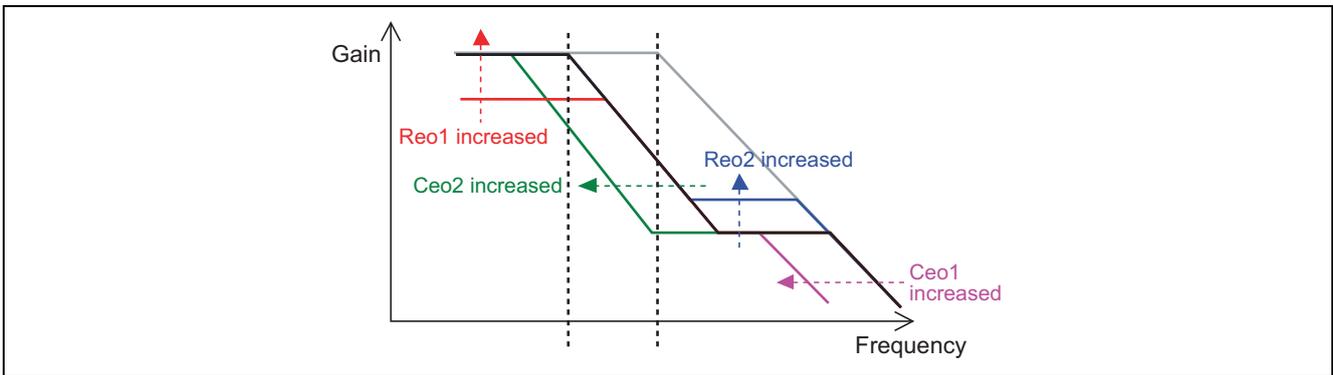
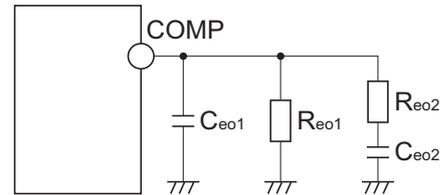


Figure 10 Overview of Gain-Frequency Characteristics

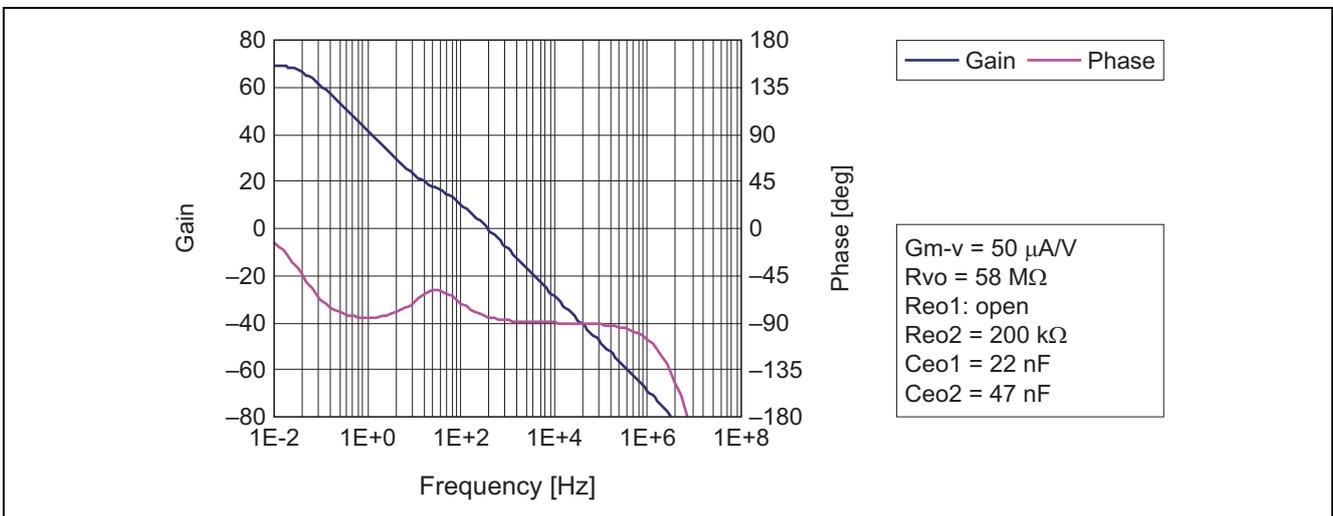


Figure 11 Frequency Characteristics of the Error Amplifier

#### 4.8 About Abnormal Examination (1pin(FB) – 2pin(COMP) short)

Outline of operation:

It becomes voltage follower connection when 1pin (FB) and 2pin (COMP) are shorted, and the COMP operates to output 2.51 V. So, when 1pin and 2pin are shorted, the operation of the chip differs according to the state of the COMP voltage of normal operation: a) the COMP voltage is controlled by 2.51 V or more, b) the COMP voltage is controlled by 2.51 V or less.

- When the COMP voltage is controlled to keep 2.51 V or more (Low input voltage and heavy load)  
The output voltage of COMP decreases when the pins are shorted. And then ON time duration enough to keep the load power can not be obtained.
- When the COMP voltage is controlled to keep 2.51 V or less (High input voltage and light load)  
When the pins are shorted, the output voltage of the COMP is raised. And then ON time duration becomes longer than needed. The final voltage of PFC\_OUT is obtained from the following formula.

$$PFC\_OUT_{short}[V] = (PFC\_OUT_{normal} \times 1.09) + (I_{comp} \times R_{fb}) \quad \dots (7)$$

PFC\_OUT(short): The output voltage when the short-circuit between FB pin and COMP pin happens.

PFC\_OUT(normal): The voltage of PFC\_OUT at normal operation

I<sub>comp</sub>: Sink current of the Error Amplifier (max 10 μA)

R<sub>fb</sub>: The resistance of the feedback resistor

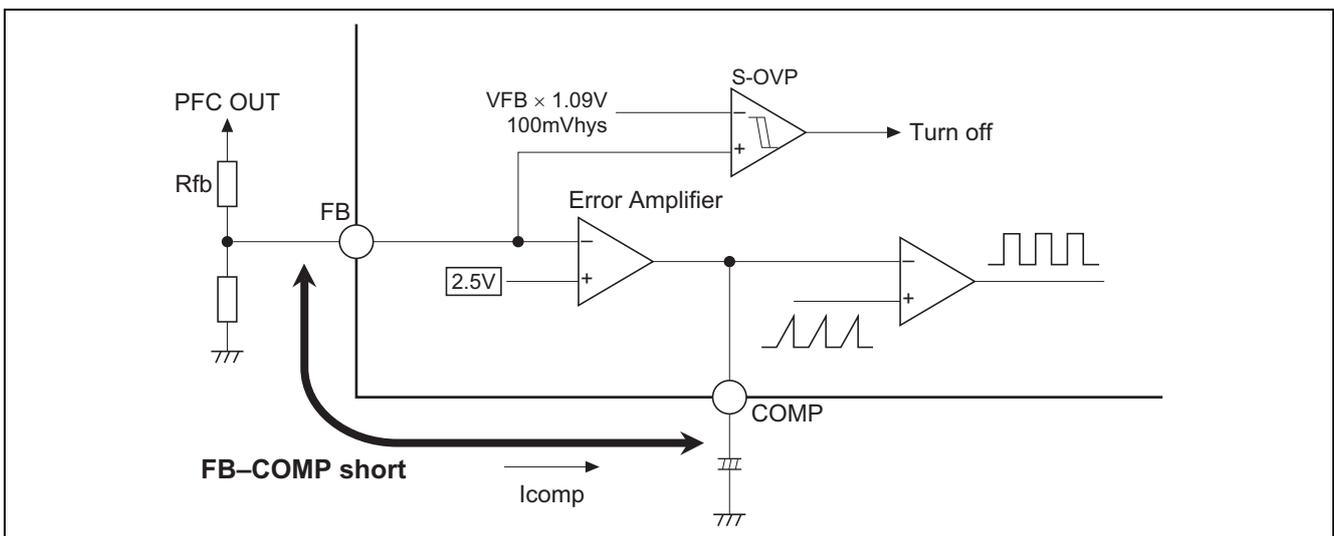


Figure 12

Countermeasure:

In case in which the feed-back resistor of the large resistance value is used between the output voltage and the FB-pin, or in case in which the output voltage is restricted at the lower voltage obtained by (7), the external circuit for the Over Voltage Protection (OVP) shown below should be prepared.

The PFC-OUT voltage rising can be prevented by this circuit depicted below when 1pin and 2pin are shorted.

When PFC output voltage (Vout) rises and exceeds 443 V (the OVP setting voltage), Vref becomes 2.5 V or more. And then, Ik increases rapidly by the characteristic of Shunt Regulator (IC1). So that, PNP transistor (Q1) is turned on, and Vref raises up near Vcc. As a result, zener diode (ZD1) is turned on and this makes the Q2 turn on and keep on hereafter, and then, the voltage of FB lowers to 0.5 V or less. So that, the PFC operation is stopped because of low voltage level of the FB.

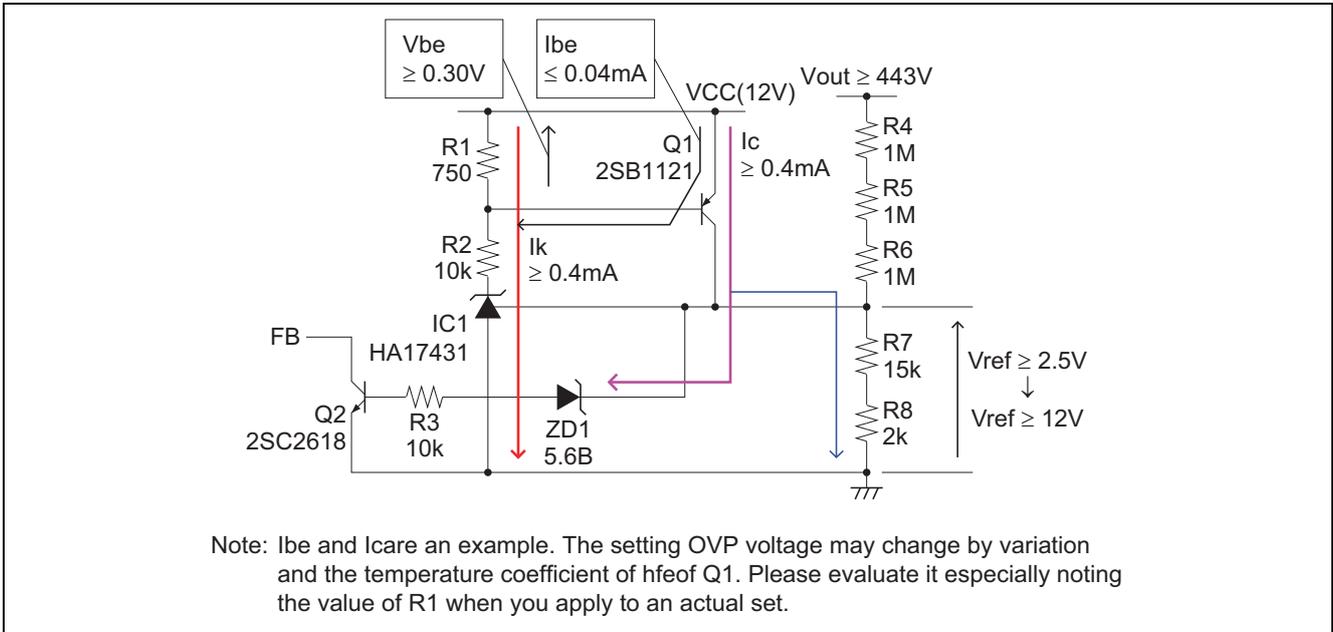


Figure 13



**Website and Support**

Renesas Electronics Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

All trademarks and registered trademarks are the property of their respective owners.



## Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.  
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.  
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.  
"Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.  
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.  
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



### SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

**Renesas Electronics America Inc.**  
2880 Scott Boulevard Santa Clara, CA 95050-2554, U.S.A.  
Tel: +1-408-588-6000, Fax: +1-408-588-6130

**Renesas Electronics Canada Limited**  
1101 Nicholson Road, Newmarket, Ontario L3Y 9C3, Canada  
Tel: +1-905-898-5441, Fax: +1-905-898-3220

**Renesas Electronics Europe Limited**  
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K  
Tel: +44-1628-585-100, Fax: +44-1628-585-900

**Renesas Electronics Europe GmbH**  
Arcadiastrasse 10, 40472 Düsseldorf, Germany  
Tel: +49-211-65030, Fax: +49-211-6503-1327

**Renesas Electronics (China) Co., Ltd.**  
7th Floor, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100083, P.R.China  
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

**Renesas Electronics (Shanghai) Co., Ltd.**  
Unit 204, 205, AZIA Center, No.1233 Lujiazui Ring Rd., Pudong District, Shanghai 200120, China  
Tel: +86-21-5877-1818, Fax: +86-21-6887-7858 / -7898

**Renesas Electronics Hong Kong Limited**  
Unit 1601-1613, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong  
Tel: +852-2886-9318, Fax: +852 2886-9022/9044

**Renesas Electronics Taiwan Co., Ltd.**  
13F, No. 363, Fu Shing North Road, Taipei, Taiwan  
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

**Renesas Electronics Singapore Pte. Ltd.**  
1 harbourFront Avenue, #06-10, keppel Bay Tower, Singapore 098632  
Tel: +65-6213-0200, Fax: +65-6278-8001

**Renesas Electronics Malaysia Sdn.Bhd.**  
Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia  
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

**Renesas Electronics Korea Co., Ltd.**  
11F., Samik Lavi'd or Bldg., 720-2 Yeoksam-Dong, Kangnam-Ku, Seoul 135-080, Korea  
Tel: +82-2-558-3737, Fax: +82-2-558-5141