

BCPX3 Evaluation Kit

R30AN0326EJ0100

Rev.1.00

Nov 1, 2017

PLC Evaluation Board Design Guideline

Introduction

This document is a design guide that is described about attentions to parts placement, PCB layout and wiring of PLC evaluation board with PLC modem LSI (CPX3), Power Amp (ISL15110) and power supply IC for a direct current power line communication (DC PLC) and in reference to BCPX3 Evaluation kit. PLC evaluation board has two kinds of a drive method, CPX3 direct drive (after, CPX drive) type or CPX3+Power Amp drive (after, PA drive) type. As for the PA drive, an output level has a bigger 20dB than CPX drive, PA drive is used in a case with long transmission distance or many connection number. This document explains it when you use each drive type.

[Note]

The attention to describe with this document made the PLC board of BCPX3 evaluation kit J80D1 and J80D2 an example. Depending on board size, parts, layout of a customer's evaluation board, there is the case that is not necessarily effective.

Contents

1.	The circuit constitution by the drive type	3
1.1	CPX drive (CPX3 direct drive).....	3
1.2	PA (CPX3+Power Amp) drive	4
2.	Instructions about parts placement	6
2.1	Placement of the decoupling capacitors	6
2.1.1	U1 (CPX3) neighborhood parts (CPX drive/PA drive common)	6
2.1.2	U3 (ISL15110) neighborhood parts (PA drive)	8
2.2	Placement of crystal oscillation's neighboring circuit (CPX drive/PA drive common).....	9
2.3	Direct current power supply circuit (CPX drive/PA drive common).....	10
2.4	Input and Output protective circuit (CPX drive/PA drive common)	11
3.	Instructions about the PCB layout.....	12
3.1	About PCB Layers (CPX drive/PA drive common)	12
3.2	About GND layer (CPX drive/PA drive common).....	13
3.3	About power supply layer (CPX drive/PA drive common)	15
3.4	About thermal dissipation and back side GND (CPX drive/PA drive common)	16
3.5	About U1 (CPX3) & U3 (ISL15110) wiring	17
3.5.1	About signal wiring of U1 (CPX3) (CPX drive/PA drive common)	17
3.5.2	About input/output signal, Power supply and GND of U3 (ISL15110) (PA drive)	18
3.6	About layout of direct current power supply line (CPX drive/PA drive common)	20
3.7	About isolation of signal wiring.....	21
3.7.1	Isolation of RXPGAIN signal (CPX drive/PA drive common).....	21
3.7.2	Power supply circuit and RXPGAIN (CPX drive/PA drive common)	23
3.8	Others (CPX drive/PA drive common)	25
4.	Instructions about the wiring pattern.....	27

4.1 Length 27

4.2 Width 27

4.3 Clearance and Creepage distance 27

1. The circuit constitution by the drive type

This chapter shows circuit constitution of CPX drive and PA drive to Figure 1-1, Figure 1-2.

1.1 CPX drive (CPX3 direct drive)

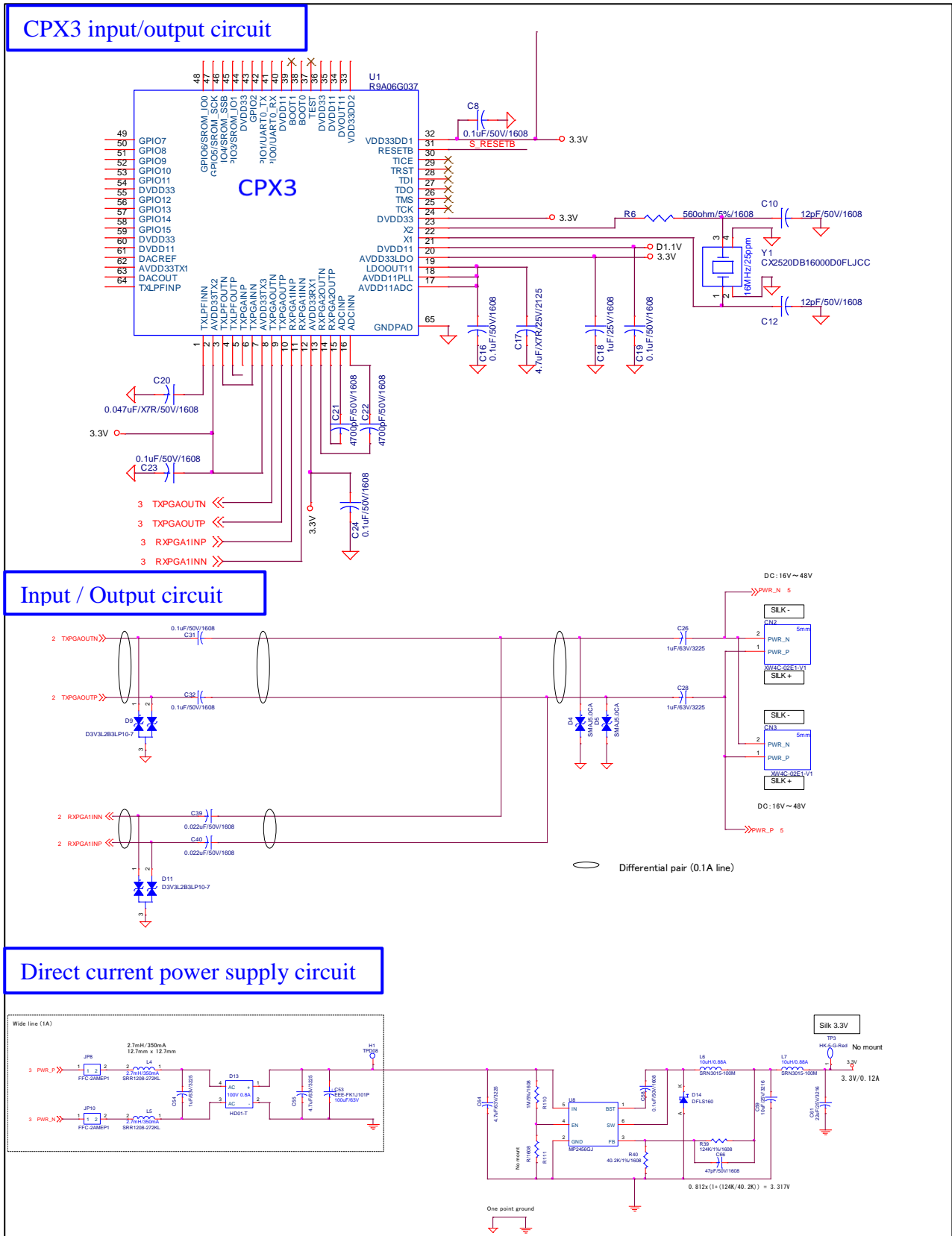


Figure 1-1 Constitution of the main part (CPX drive)

2. Instructions about parts placement

2.1 Placement of the decoupling capacitors

2.1.1 U1 (CPX3) neighborhood parts (CPX drive/PA drive common)

About the decoupling capacitors C2 ~ C9, C11, C14, C16, C17, C23, C24 of U1 (CPX3), please place it in the neighborhood of each terminal to Figure 2-1 and shorten a wiring pattern. Please refer to chapter 3.7 too, about product placement.

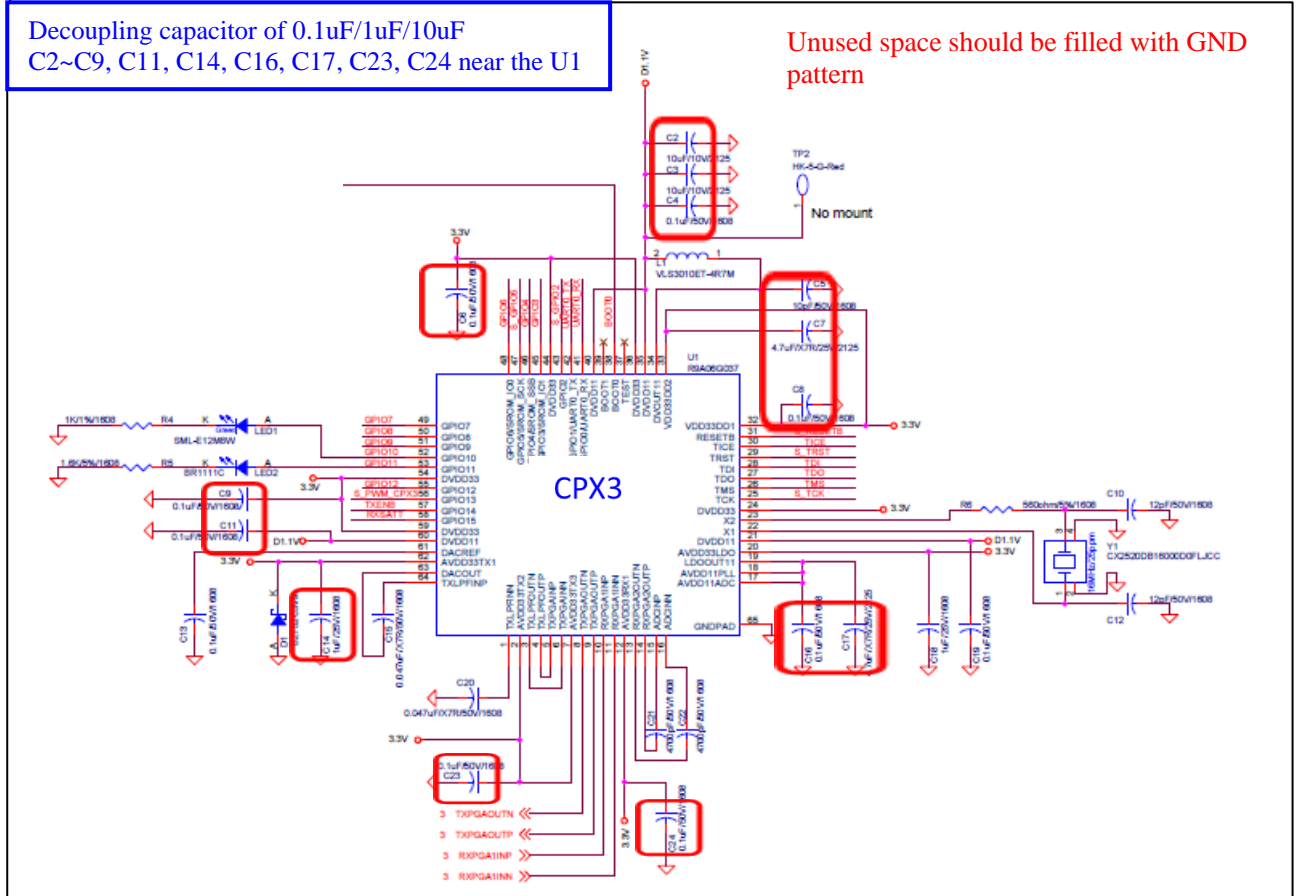


Figure 2-1 Decoupling capacitors to place in the U1 (CPX3) neighborhood

Example:

Figure 2-2 shows placement example of the decoupling capacitor with L-1/L-4 of the U1 (CPX3) neighborhood.

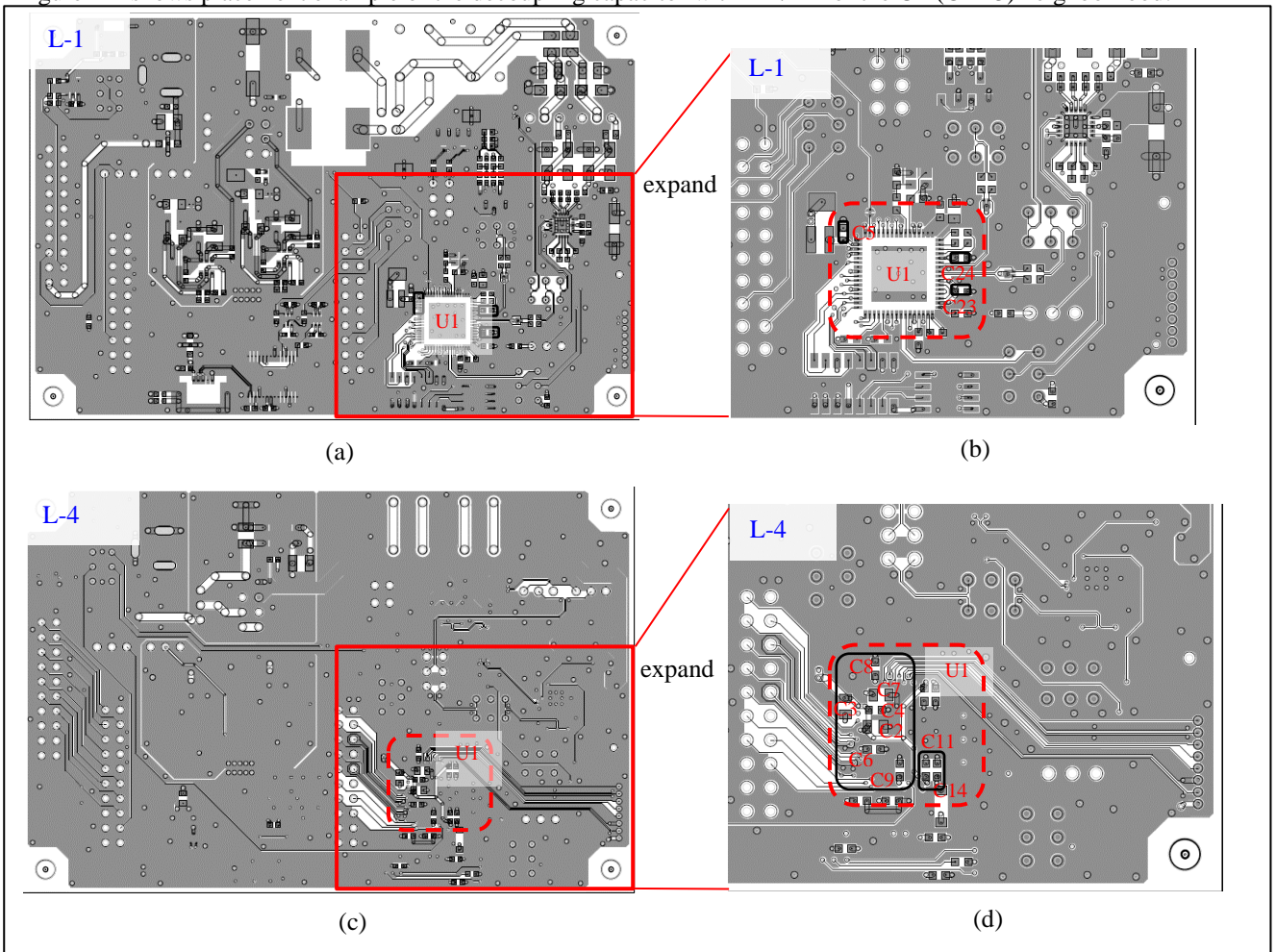


Figure 2-2 Example of the decoupling capacitor with L-1/L-4 of the U1 (CPX3) neighborhood.

2.1.2 U3 (ISL15110) neighborhood parts (PA drive)

About the decoupling capacitors C33 ~ C35 of U3 (ISL15110), please place it in the neighborhood of each terminal to Figure 2-3 and shorten a wiring pattern. Please refer to chapter 3.8 too, about product placement.

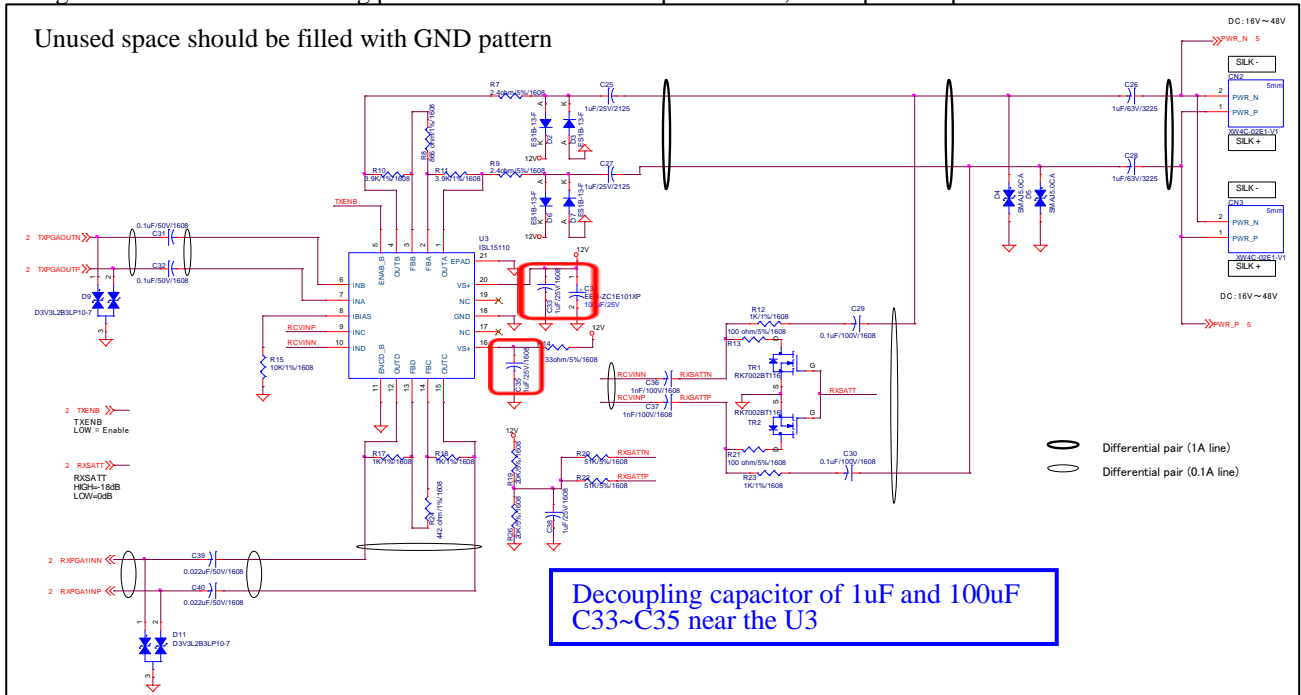


Figure 2-3 Decoupling capacitors to place in the U3 (ISL15110) neighborhood

Example:

Figure 2-4 shows placement example of the decoupling capacitor with L-1/L-4 of the U3 (ISL15110) neighborhood.

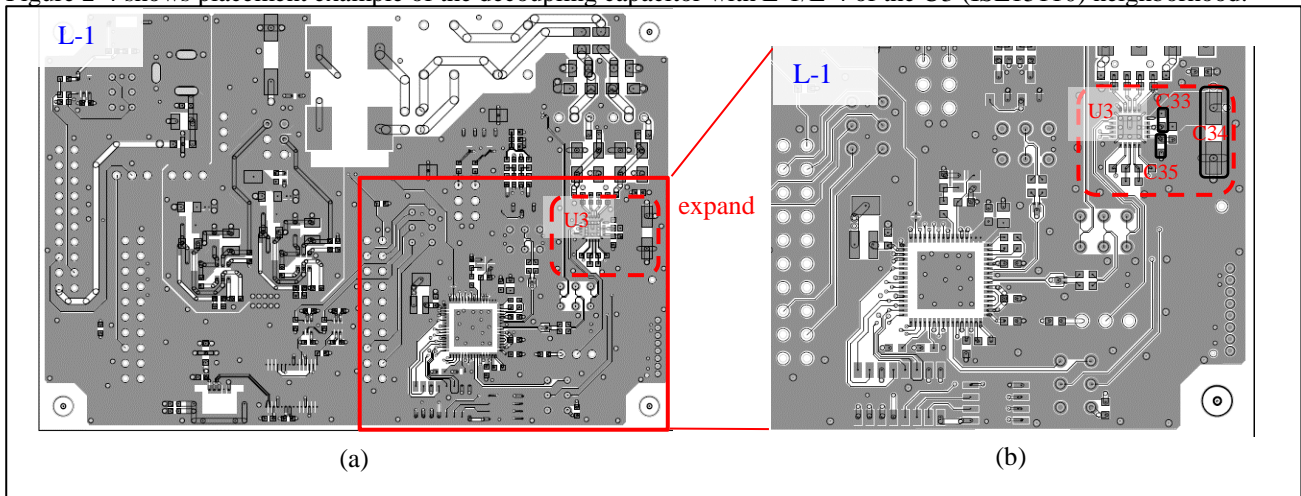


Figure 2-4 Example of decoupling capacitor placement of U3 (ISL15110)

2.2 Placement of crystal oscillation's neighboring circuit (CPX drive/PA drive common)

Crystal oscillation (Y1), R6, C10, C12 place the near U1 (CPX3) as much as possible to Figure 2-5 and shorten a wiring pattern. Moreover, under of crystal oscillation and neighboring place GND stereotypical pattern.

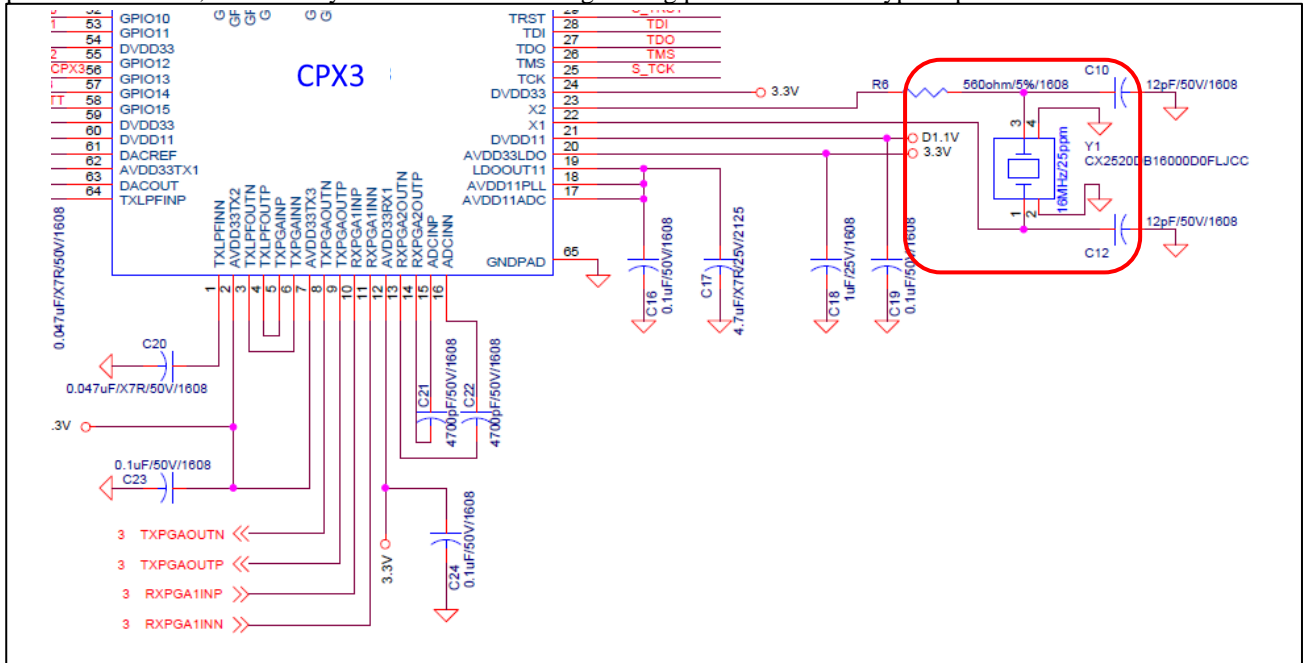


Figure 2-5 Neighboring circuit of crystal oscillation

Example: Figure 2-6 shows placement example of Crystal(Y1) , R6, C10 and C12.

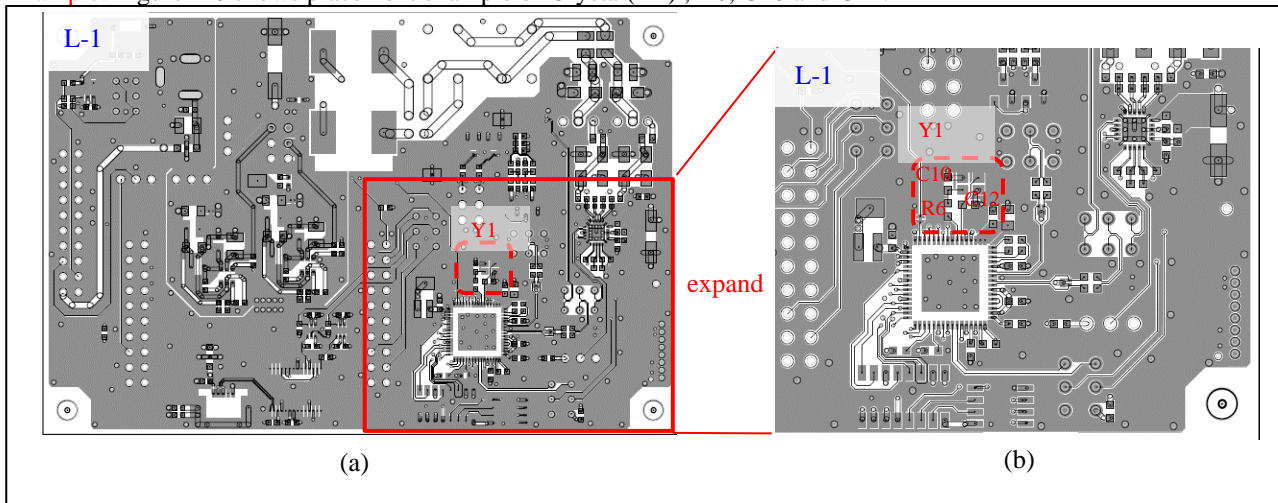


Figure 2-6 Example of crystal oscillation and neighboring circuit placement

2.3 Direct current power supply circuit (CPX drive/PA drive common)

About inductance (L4, L5) and capacity (C54), we recommend that you insert it as impedance upper so that didn't affect by the impedance of the power supply circuit for the DC PLC communication to Figure 2-7. About the choice of the inductance (L4, L5), because the input impedance of the DC PLC reception department is 1-2kΩ, the impedance of the power supply circuit side sets more than double the impedance of using frequency band so that it doesn't affect the DC PLC reception department input impedance. the evaluation board is L=2.7mH, for example, impedance Z_L in 150kHz becomes the following expressions;

$$Z_L = 2\pi fL = 2 \times 3.14 \times 150kHz \times 2.7mH = 2.54k\Omega$$

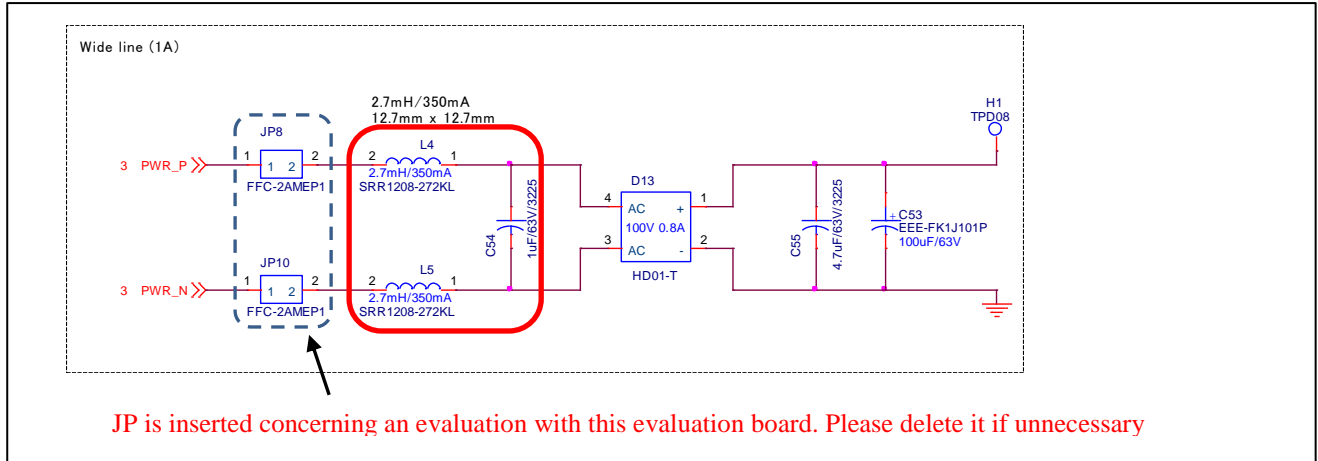


Figure 2-7 Direct current power supply circuit

2.4 Input and Output protective circuit (CPX drive/PA drive common)

We recommend that input and output circuit for CPX drive or PA drive of PLC evaluation board insert a protective circuit to Figure 2-8.

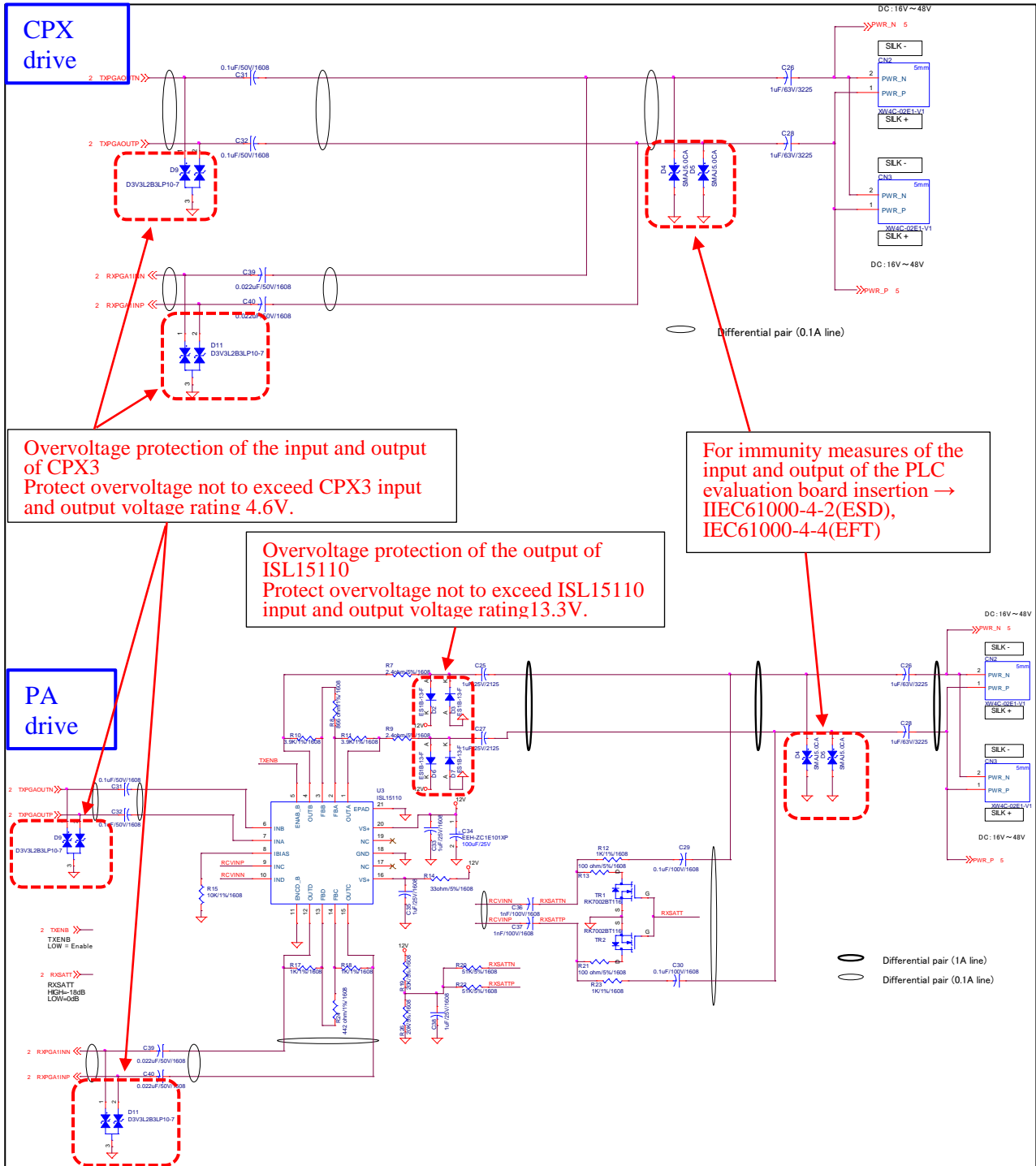


Figure 2-8 Input and Output protective circuit

3. Instructions about the PCB layout

This chapter explains the PCB layout of PLC evaluation board.

3.1 About PCB Layers (CPX drive/PA drive common)

We recommend that you adopt 4 layers PCB, and each layer's usage is shown below. Figure 3-1 shows example of the layer constitution of each layers. In order to keep signal isolation, for noise shielding and for thermal dissipation, the formation of the ground layer in L-2 or L-3 becomes important. For this reason, unused area of L-1 that are the signal layer and L-2 should be used as ground pattern, and L-1 GND & L-2 GND & L-4 GND should be connected with sufficient number of via holes (as many as possible) to strengthen. In addition, U3 (PA: ISL15110) should be fully considered with the thermal design.

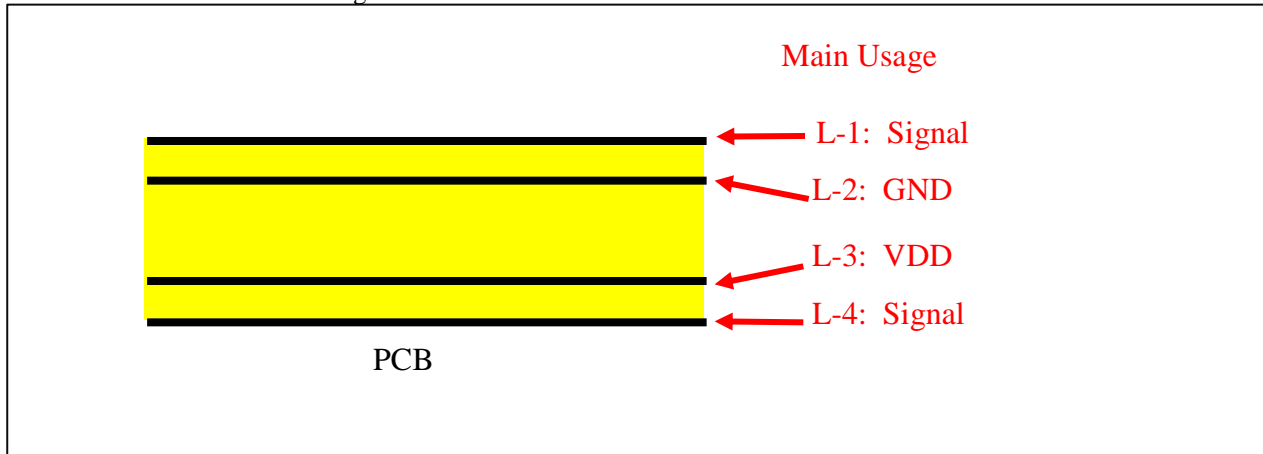


Figure 3-1 Example of the layer constitution of 4 layers board

3.2 About GND layer (CPX drive/PA drive common)

We recommend the GND pattern (L-2 or L-3) constitute in the single layer. the GND pattern is the GND stereotypical pattern without separating analog GND and digital GND. But, if you avoid the influence of the noise from power supply circuit, then it becomes the effective means to isolate between other circuit's analog GND/digital GND and GND stereotypical pattern of power supply circuit. Figure 3-2 shows PCB layout exmple to connect only L-1's one point that it isolates by L-1, L-2, and L-4 between other circuit's analog GND/digital GND and GND stereotypical pattern of power supply circuit.

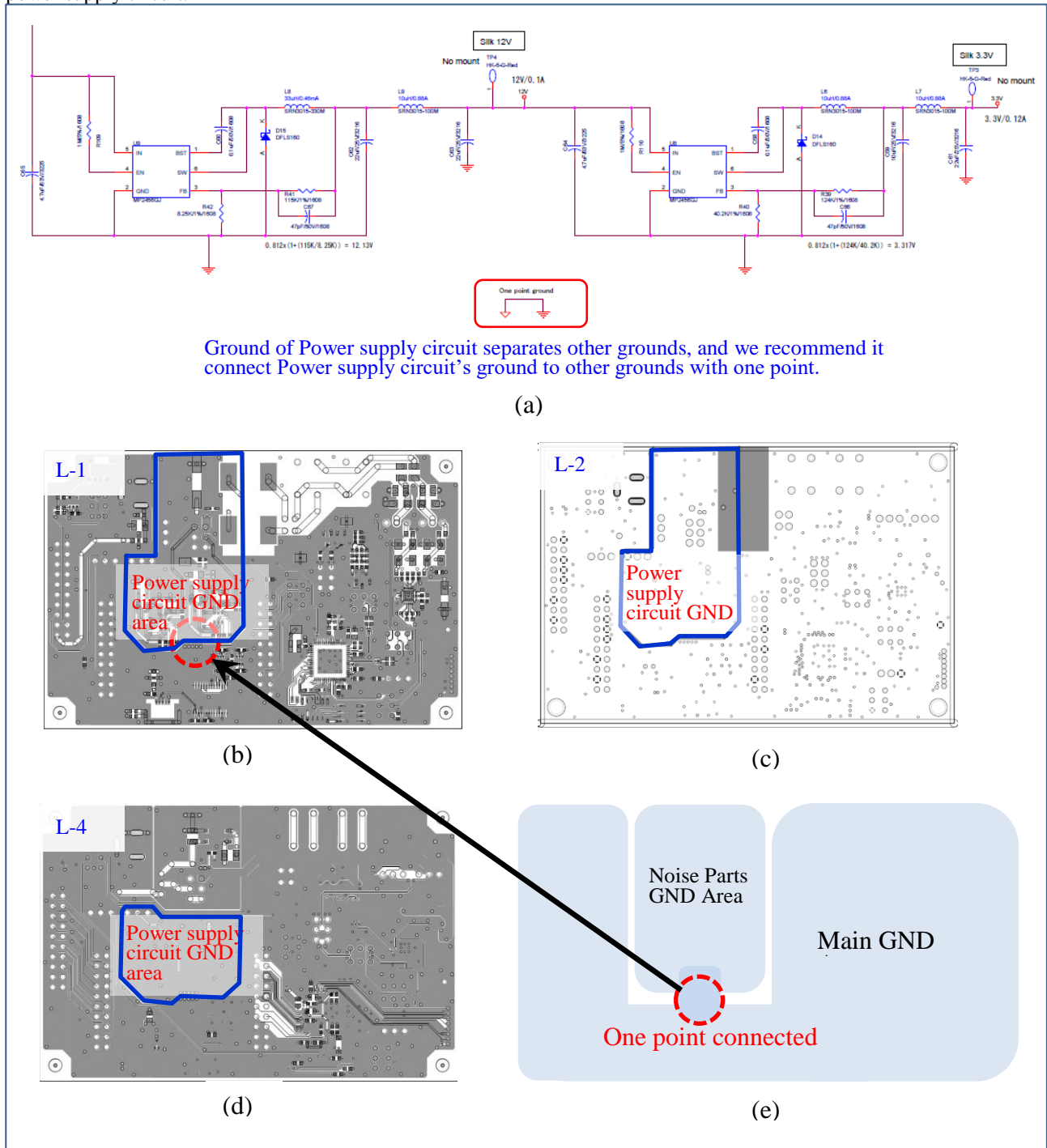


Figure 3-2 Example of GND pattern

In addition, Figure 3-3 shows the instruction about the GND pattern. Unused area of signal layer fill with GND pattern as much as possible and add a lot of via hall. It's not necessary to bury for GND pattern in the cases that it becomes a floating pattern of GND in the small area or becomes the antenna of the noise by the parallel wiring with signal. Particularly, please don't fill with GND pattern for inductor.

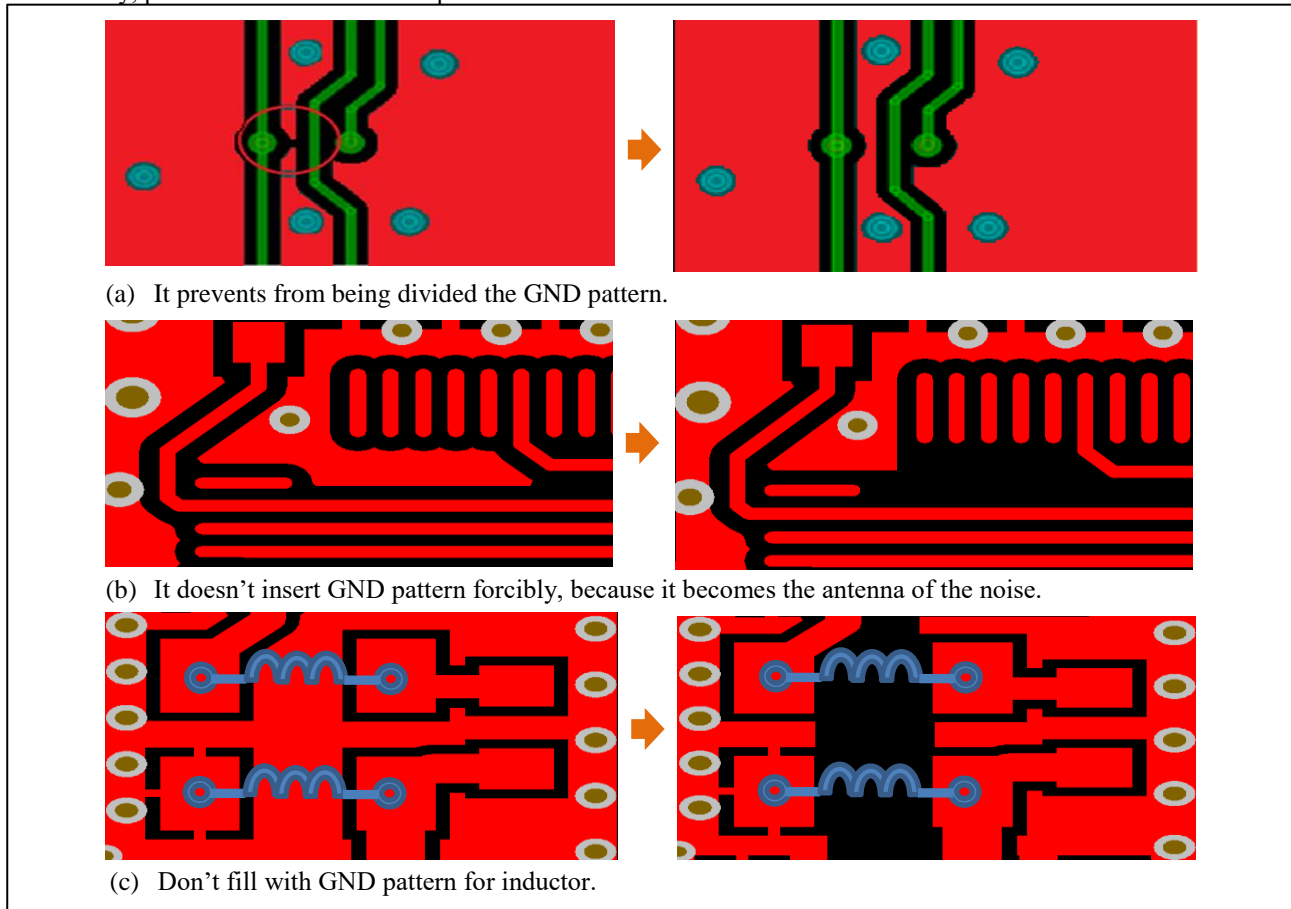


Figure 3-3 Instructions of GND pattern

3.3 About power supply layer (CPX drive/PA drive common)

We recommend that the power supply layer place a 3.3V power supply area and a 12V power supply area using with PLC evaluation board, and the part except the power supply area place a GND pattern. Figure 3-4 shows layout patterns example of the power supply layer which constituted to L-3.

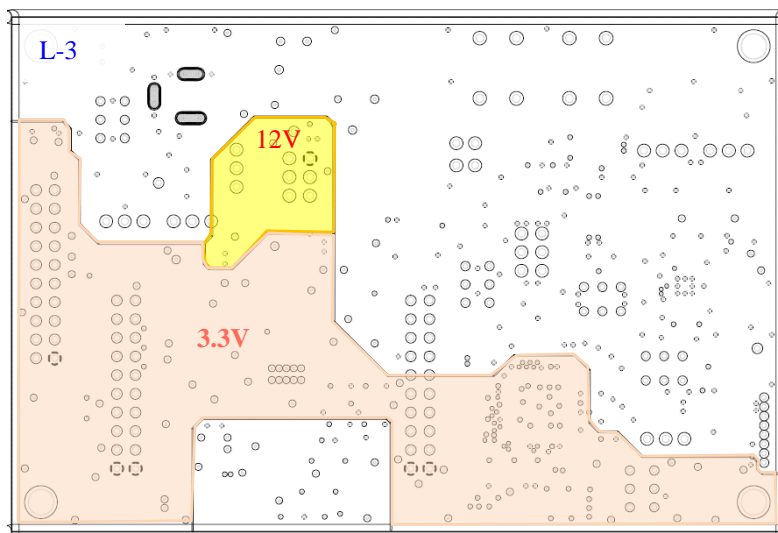


Figure 3-4 Example of the power supply area

In addition, when a power supply noise is big, and there is concern of the interference between power supply area, we recommend that insert GND wiring (secure the space where it can place a via hole for GND) between power supply wiring that minimize the influence of the noise to Figure 3-5.

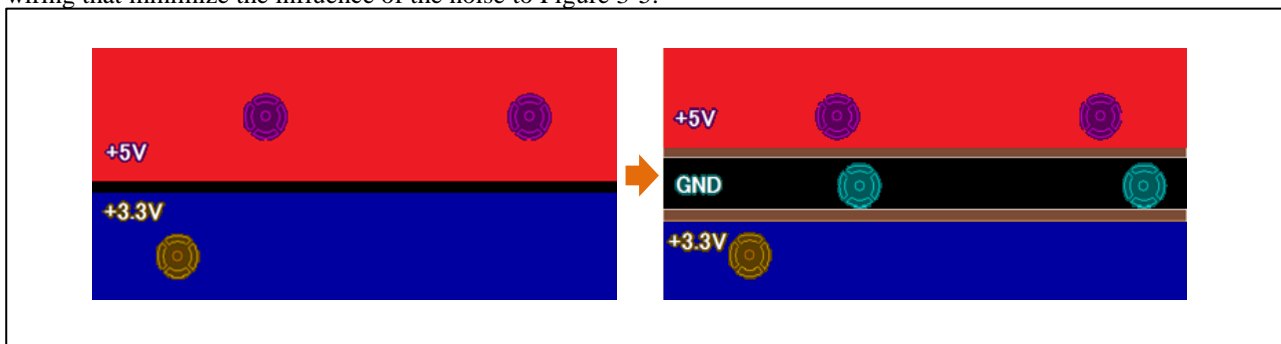


Figure 3-5 Instructions of power supply wiring

3.4 About thermal dissipation and back side GND (CPX drive/PA drive common)

U1(CPX3) and U3(ISL15110) need to consider GND reinforcement and thermal dissipation, it connects back side GND. Figure 3-6 shows GND pattern constitute to each substrate layer for connecting back side PAD, please connect each layer in via holes. GND pattern place via holes (recommendation: ϕ 0.3mm, CPX3: 9 or more, ISL15110: 8 or more). In addition, the GND pattern connecting back side GND connects big wiring (aim: 3mm or more) with GND pattern stereotypical in L-1 or L-4.

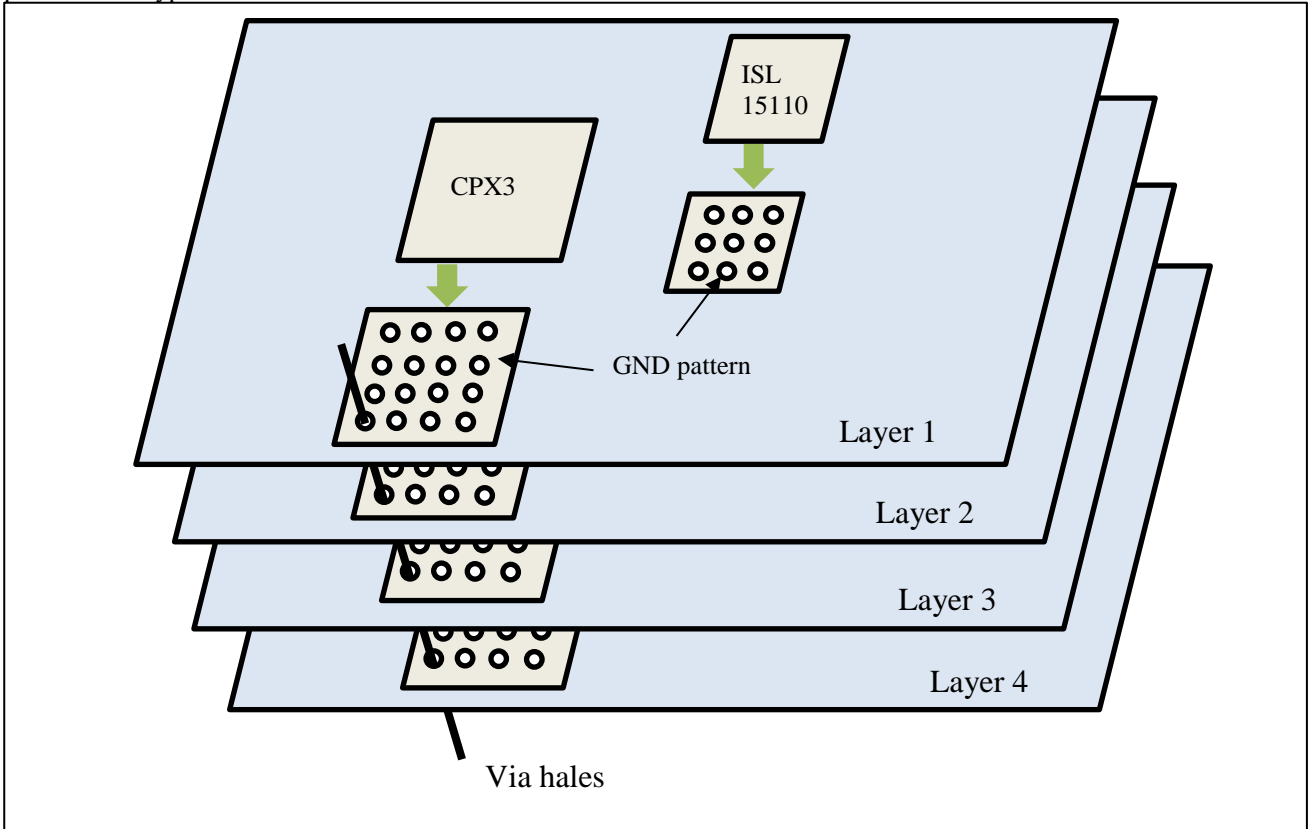


Figure 3-6 Example of thermal dissipation

Example: Figure 3-7 shows the example of back side GND of U1, U3 and the thermal dissipation

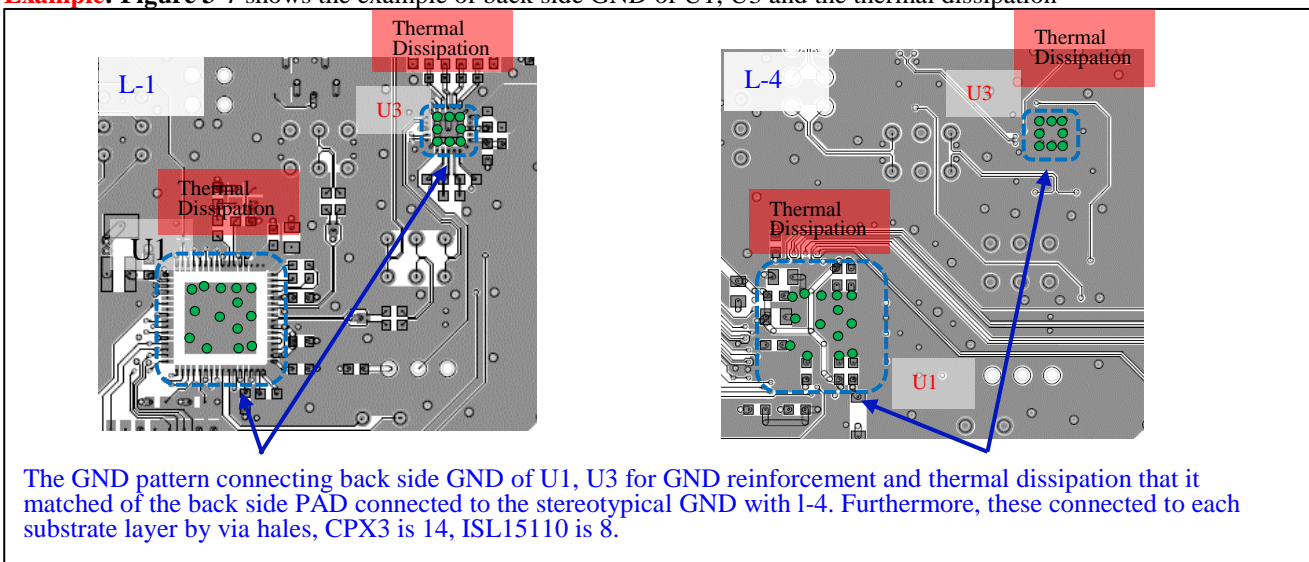


Figure 3-7 Example of back side GND of U1, U3 and the thermal dissipation

3.5 About U1 (CPX3) & U3 (ISL15110) wiring

3.5.1 About signal wiring of U1 (CPX3) (CPX drive/PA drive common)

TXPGAOUT/RXPAIN signal of U1 (CPX3) is a differential signal. Please wires in isometry, and shields it in GND. **Figure 3-8** shows instructions of the signal wiring of U1 (CPX3).

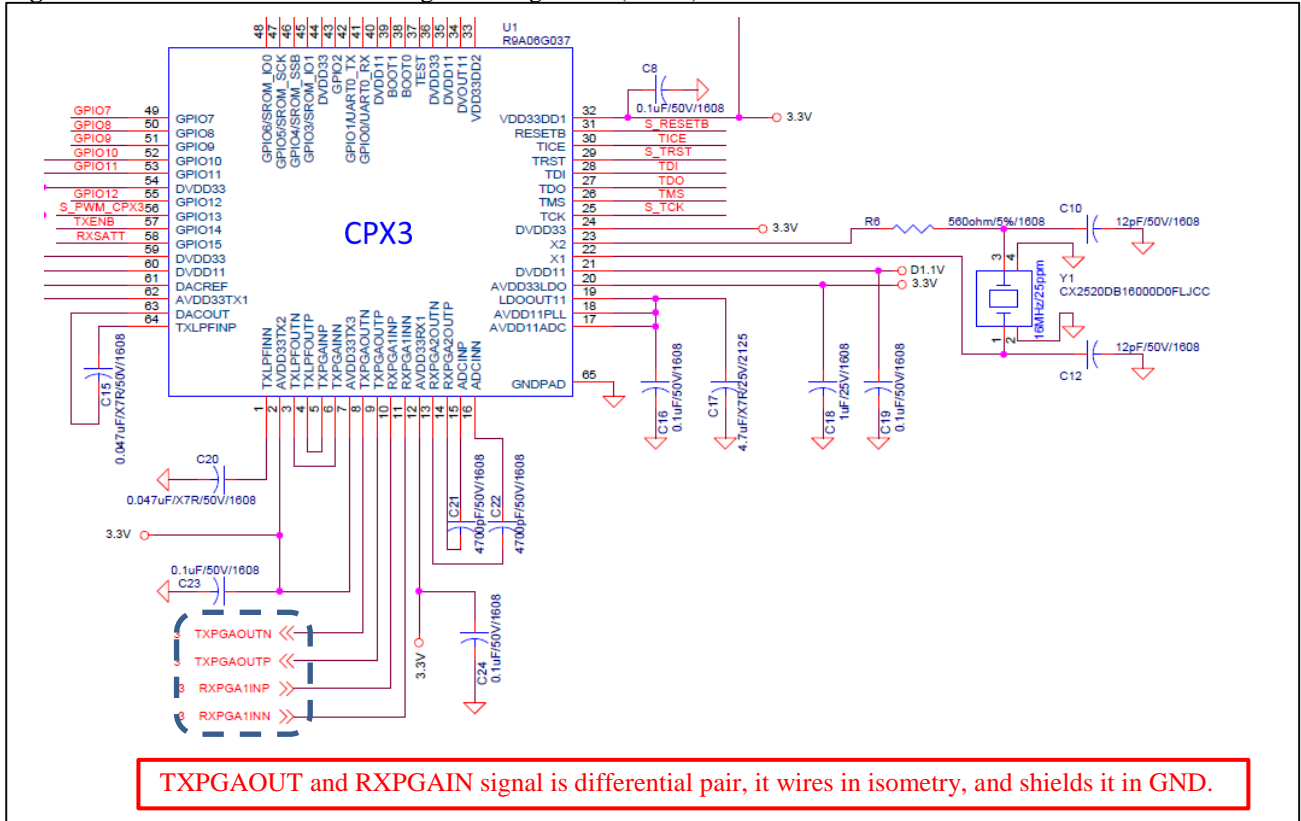


Figure 3-8 Instructions of U1 (CPX3) wiring

Example:

Figure 3-9 shows example of TXPGAOUT/RXPAIN signals of U1(CPX3). A red broken line is TXPGAOUTP/TXPGAOUTN signals, and a green broken line is RXPAINN/RXPAINP signals. It is wiring in isometry between U1 and U3.

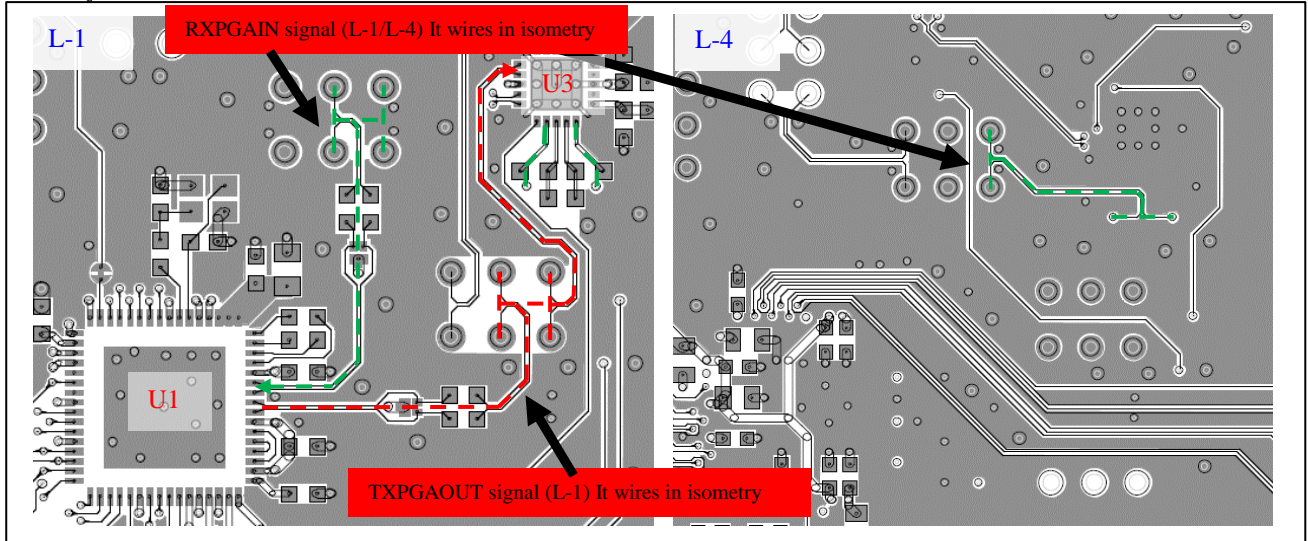


Figure 3-9 Example of TXPGAOUT/RXPAIN signals of U1(CPX3)

Example:

Figure 3-11 shows the example of the PCB layout around U3 (ISL15110). A red and a green line of ① are output signals, and this signal uses patterns more than 1mm because current of up to 1A flows. A red and a green line surrounded in a broken red line of ② are input signals, and are wiring in isometry. A blue broken arrow line of ③ is 12V wiring pattern, and this signal uses patterns more than 1mm because current of up to 1A flows. GND of U3 of ④ is connected 8 via holes in L-2 (the GND layer) and GND of L-4.

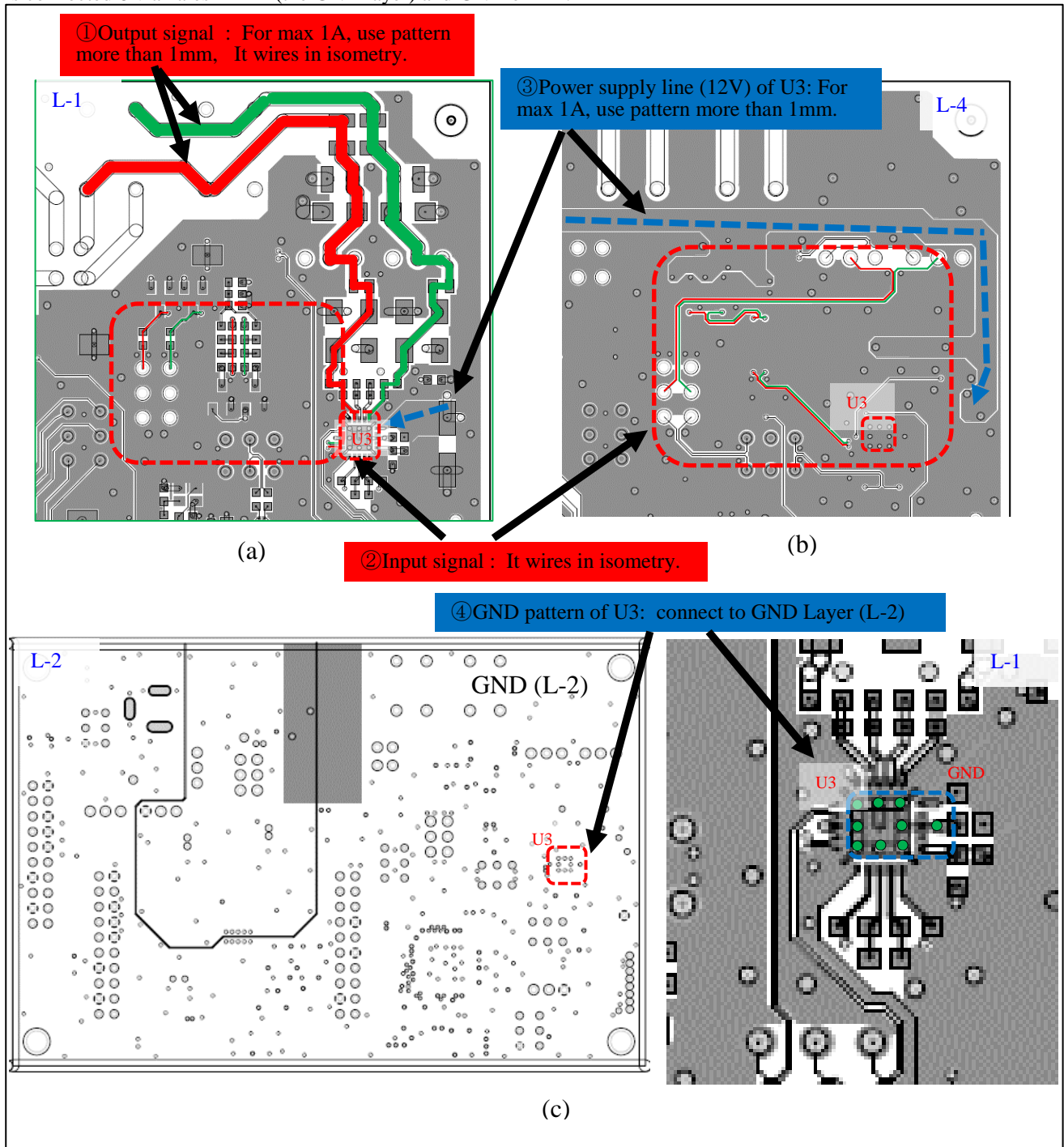


Figure 3-11 Example of the PCB layout around U3 (ISL15110)

3.6 About layout of direct current power supply line (CPX drive/PA drive common)

The power supply line from a direct current power line sets in the most suitable wiring width that accepted the voltage and current of the application to use. This document is that the power supply from a direct current power line designs the wiring that assumed up to 1A. **Figure 3-12** shows instructions of direct current power supply line.

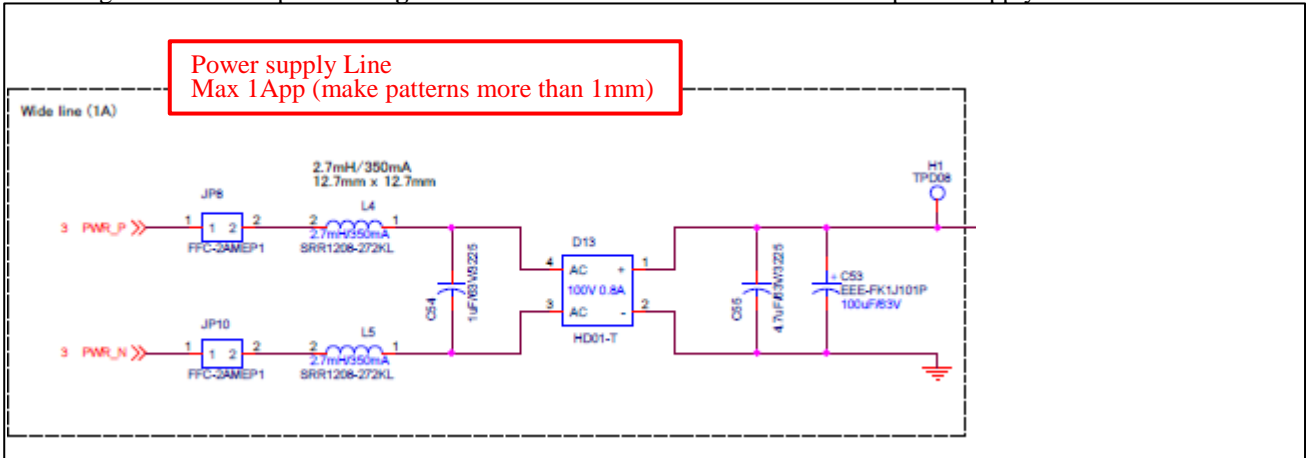


Figure 3-12 Instructions of direct current power supply line

Example: **Figure 3-13** shows the example of the PCB layout for direct current power supply line

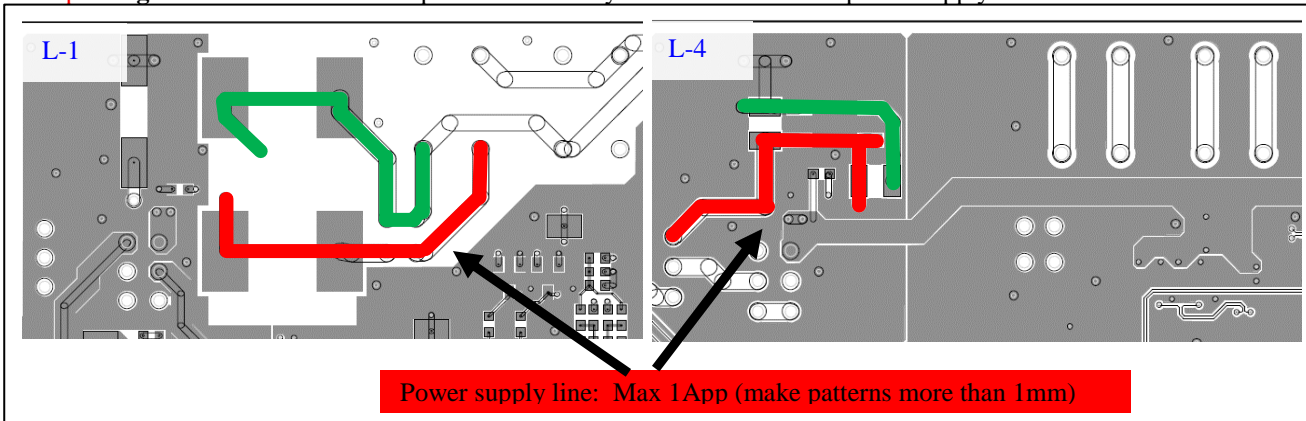


Figure 3-13 Example of direct current power supply line

3.7 About isolation of signal wiring

3.7.1 Isolation of RXPGAIN signal (CPX drive/PA drive common)

When other signals and noises interfere the RXPGAIN signal, reception properties deteriorate. Thus, as for the RXPGAIN signal, please be careful enough not to interfere other signals and noises. In particular, about between the RXPGAIN signal and crystal oscillation (Y1), X1/X2 signal, between the RXPGAIN signal and RXPGAOUT signal, between the RXPGAIN signal and TXPGAOUT signal, please these signals isolate by keeping distance, by placing shielding GND, by using different layers in consideration of interference. **Figure 3-14** shows instructions of the interference with the RXPGAIN signal.

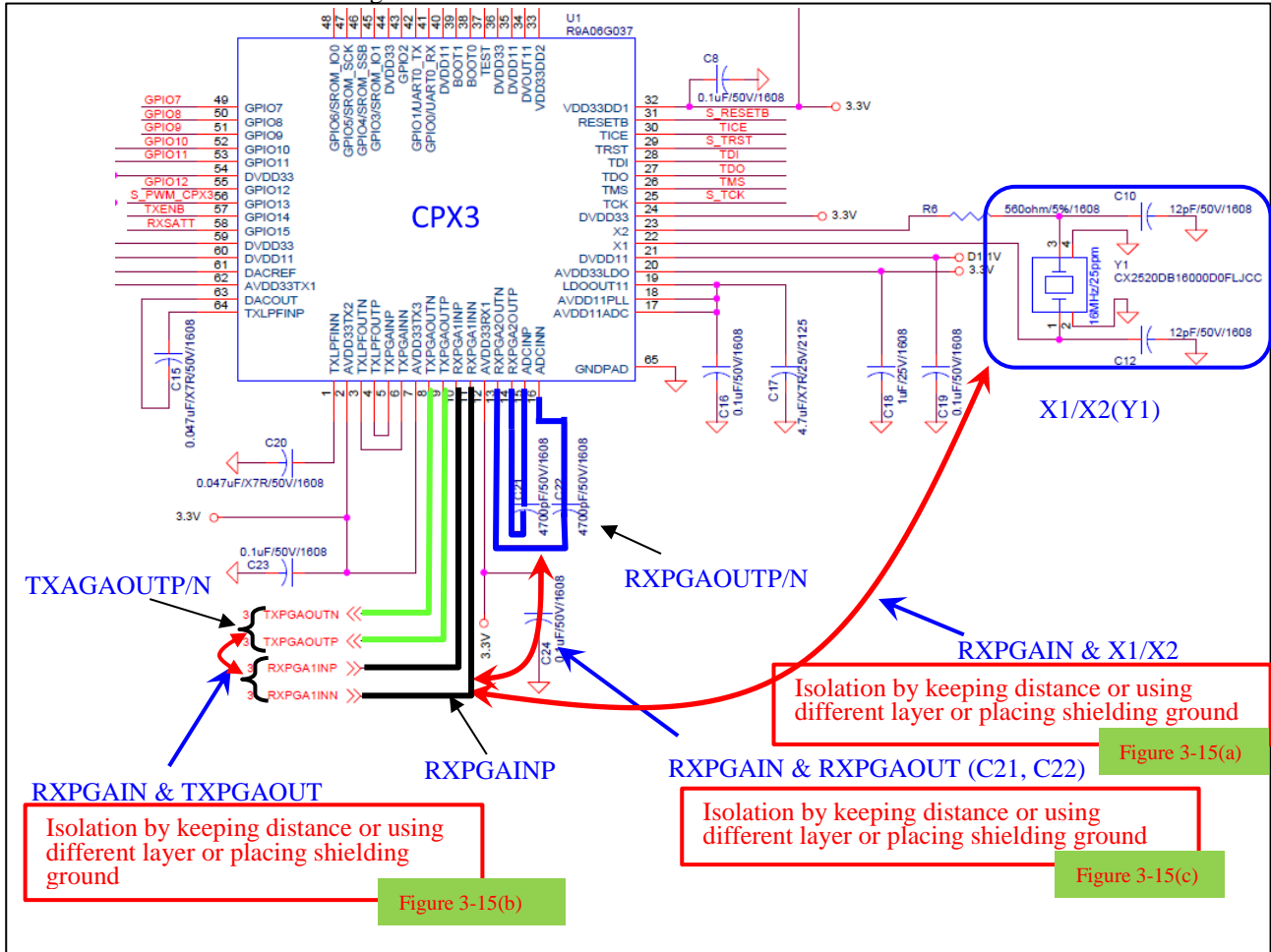


Figure 3-14 Instructions of the interference with the RXPGAIN signal.

Example:

Figure 3-15 shows PCB layout example between the RXPAGIN signal and crystal oscillation (Y1), X1/X2 signal, between the RXPAGIN signal and RXPAGOUT signal, between the RXPAGIN signal and TXPGAOUT signal, in consideration of interference.

(a) RXPAGIN signal is a red line and X1/X2(Y1) is a blue line. These are place same layer on the evaluation board, but isolate by keeping distance.

(b) RXPAGIN signal is a red line and RXPAGOUT signal is a blue line. These are place same layer on the evaluation board, but isolate by placing shielding GND.

(c) RXPAGIN signal is a red line and TXPGAOUT signal is a blue line. These are place same layer on the evaluation board, but isolate by placing shielding GND, these signal don't wire parallel, also these signals don't let intersect.

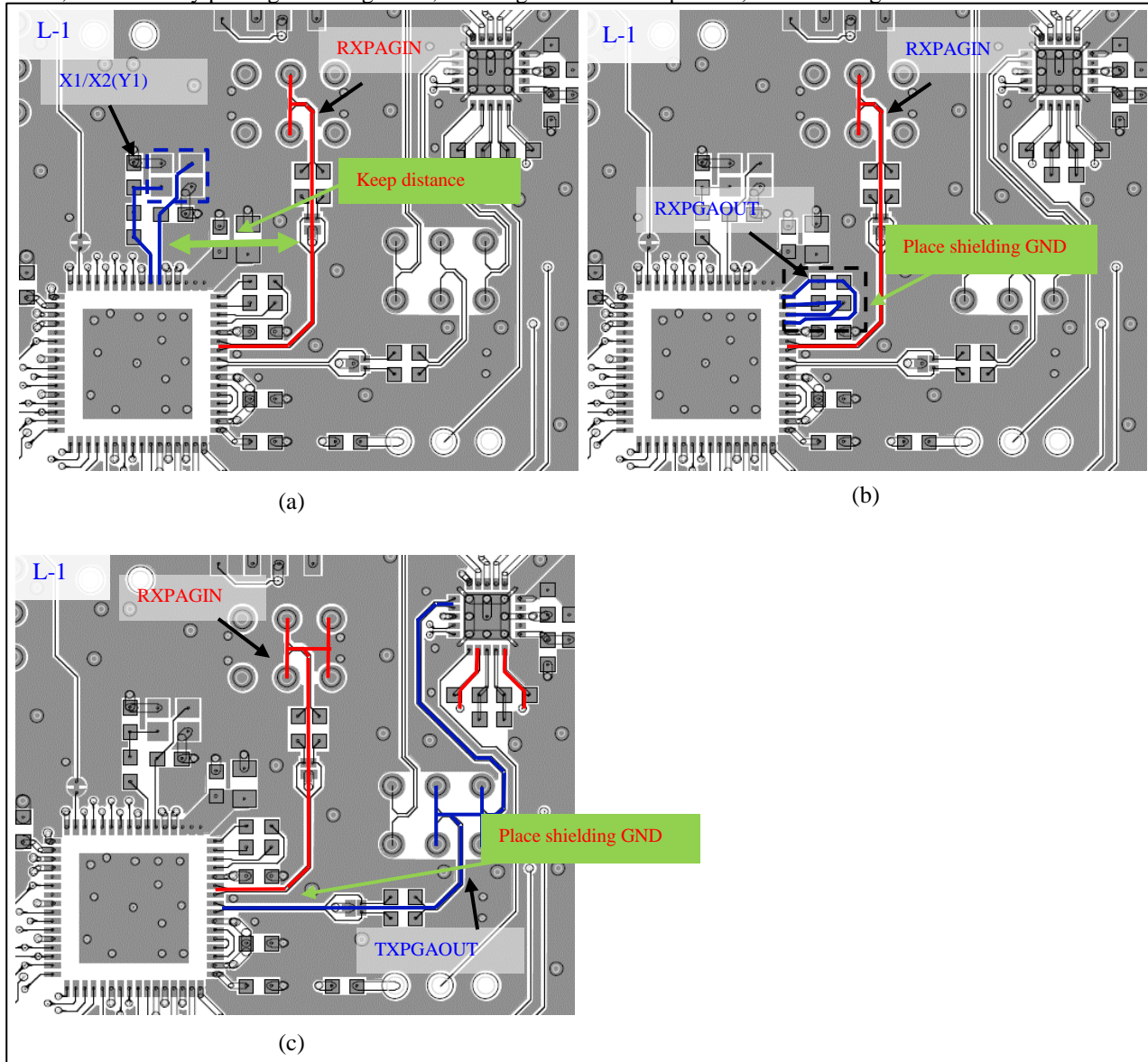


Figure 3-15 PCB layout example of RXPAGIN signal for each signal line

3.7.2 Power supply circuit and RXPGAIN (CPX drive/PA drive common)

Because the RXPGAIN signal is easy to be affected by the noise, please isolate (recommendation: 40mm or more) by keeping distance, by placing shielding GND, by using different layers between the RXPGAIN signal and power supply circuit so that the noise of the power supply circuit does not interfere it. **Figure 3-16** shows instructions of RXPGAIN signal and power supply circuit.

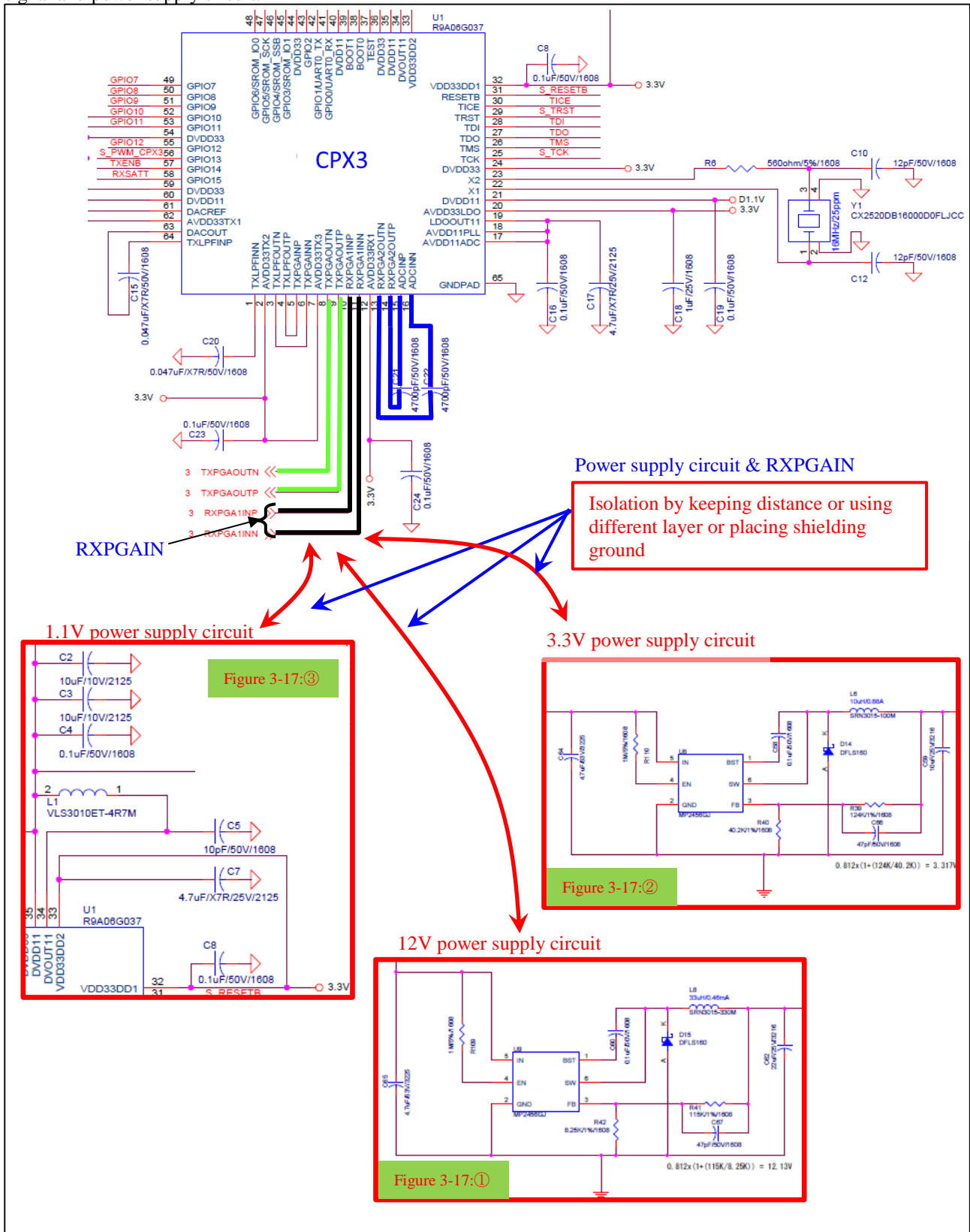


Figure 3-16 Instructions of RXPGAIN signal and Power supply circuit

Example:

Figure 3-17 shows PCB layout example of RXPGAIN signal and the power supply circuit. RXPGAIN signal and the power supply circuit isolated by keeping distance more than 40mm, by placing shielding GND patterns between RXPGAIN signal and the power supply circuit so that the noise of the power supply circuit does not interfere it.


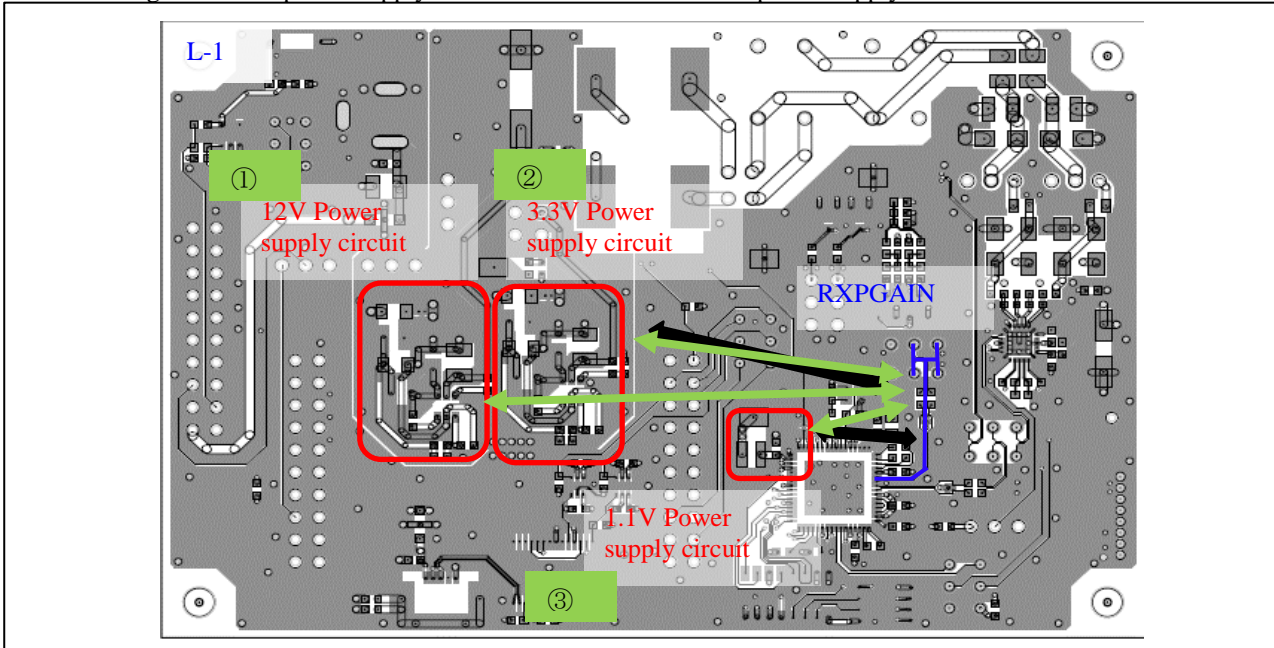



Figure 3-17 PCB layout example of RXPGAIN signal and the power supply circuit

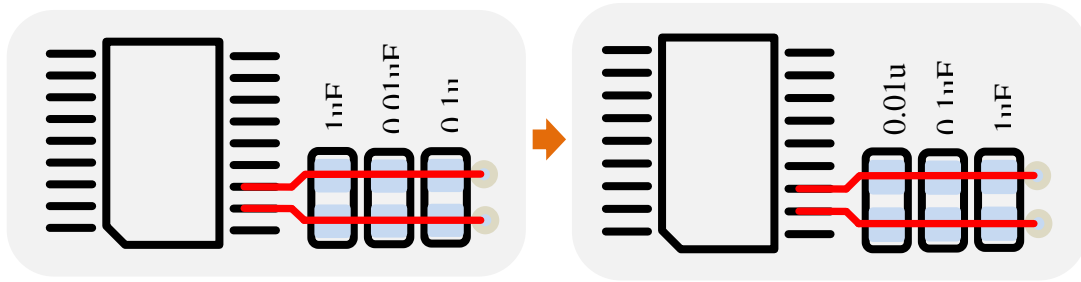3.8 Others (CPX drive/PA drive common)


This chapter explains the general instructions for the PCB layout to **Figure 3-18**. When you design the PCB, please refer.



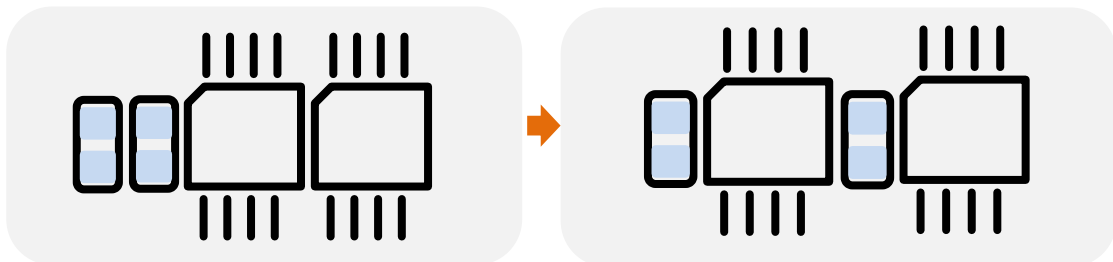
(a) The bypass capacitor connects to the small order.



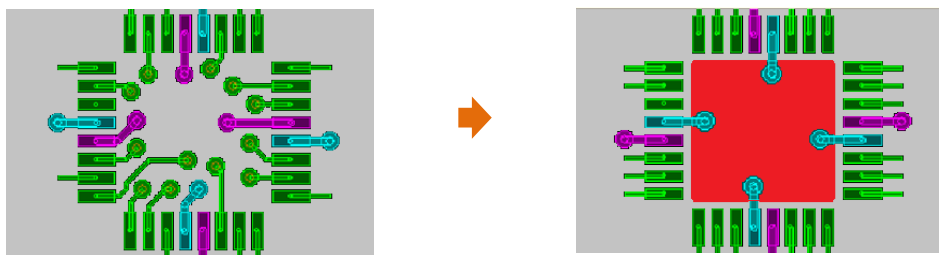
(b) The bypass capacitor locates in the neighborhood of the IC.



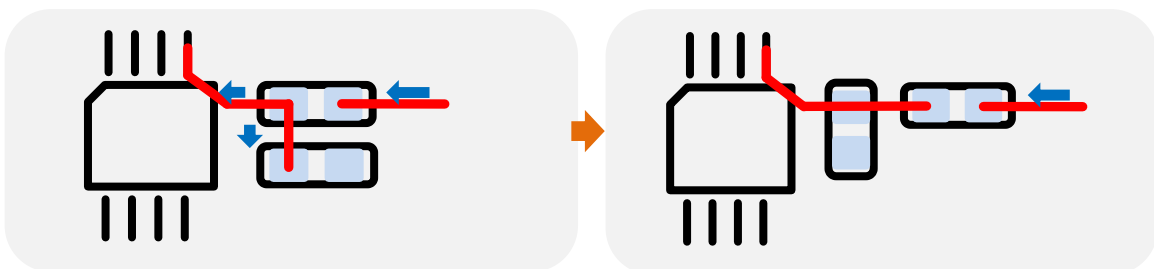(c) Under of IC pattern inserts a GND pattern.



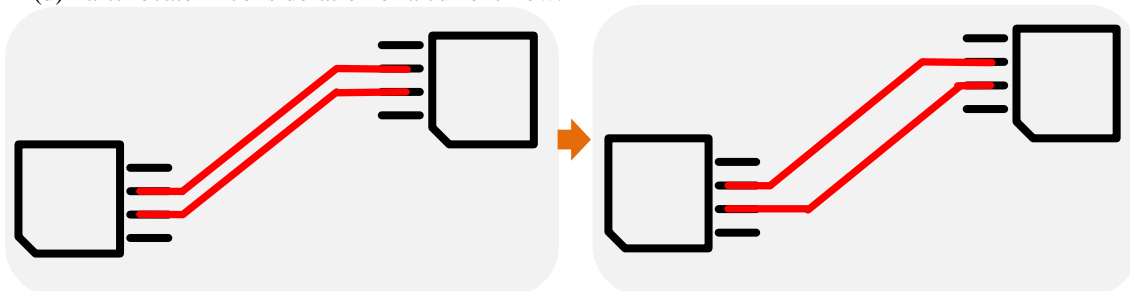(d) Parts locate in consideration of a current flow.



(e) the distance of the parallel wiring shortens it as much as possible.

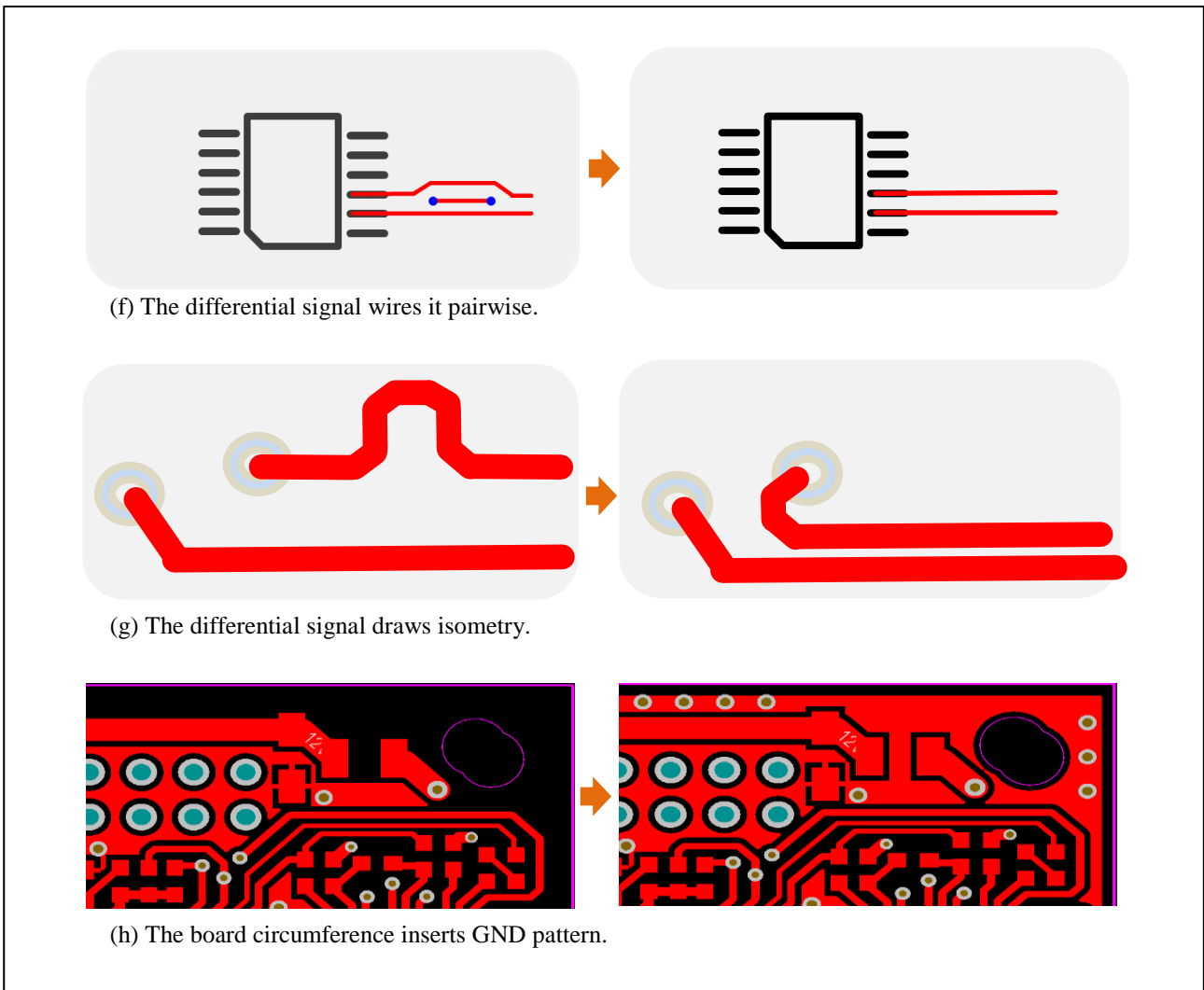


Figure 3-18 General instructions

4. Instructions about the wiring pattern

This chapter shows the general instructions in the wiring pattern. When you design the PCB, please refer.

4.1 Length

Please the signal pattern doesn't bend as much as possible, and wire at the shortest distance.

Please the signal pattern doesn't diverge as much as possible, and wire in a single stroke of the brush.

4.2 Width

Please make the wiring width of a GND pattern and the power supply pattern wide as much as possible to lower impedance. In the case of wiring with current specifications, please secure necessary wiring width. With the PLC evaluation board, the signal wiring that a characteristic doesn't have the current designation does 0.1-0.15mm, the wiring of 1A specifications does wiring width more than 1mm.

4.3 Clearance and Creepage distance

Depending on a system and the use area of the developed PLC modem by customer, there is the case that the clearance and creepage distance are regulated by laws and ordinances. Please confirm them.

Website and Support

Renesas Electronics Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/contact/>

All trademarks and registered trademarks are the property of their respective owners.

Revision History

Rev	Date	Description	
		Page	Summary
1.00	Nov 01, 2017		First Edition issued

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
 3. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from such alteration, modification, copy or otherwise misappropriation of Renesas Electronics product.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; and safety equipment etc.
Renesas Electronics products are neither intended nor authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems, surgical implantations etc.), or may cause serious property damages (nuclear reactor control systems, military equipment etc.). You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application for which it is not intended. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for which the product is not intended by Renesas Electronics.
 6. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You should not use Renesas Electronics products or technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. When exporting the Renesas Electronics products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, who distributes, disposes of, or otherwise places the product with a third party, to notify such third party in advance of the contents and conditions set forth in this document, Renesas Electronics assumes no responsibility for any losses incurred by you or third parties as a result of unauthorized use of Renesas Electronics products.
 11. This document may not be reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com>" for the latest and detailed information.

Renesas Electronics America Inc.

2801 Scott Boulevard Santa Clara, CA 95050-2549, U.S.A.
Tel: +1-408-588-6000, Fax: +1-408-588-6130

Renesas Electronics Canada Limited

9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited

Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: +44-1628-585-100, Fax: +44-1628-585-900

Renesas Electronics Europe GmbH

Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.

Room 1709, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100191, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.

Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, P. R. China 200333
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited

Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852 2886-9022

Renesas Electronics Taiwan Co., Ltd.

13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

Renesas Electronics Singapore Pte. Ltd.

80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.

Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.

No.777C, 100 Feet Road, HAL II Stage, Indiranagar, Bangalore, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.

12F., 234 Teheran-ro, Gangnam-Gu, Seoul 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141