

Notes

By Rakesh Bhatia

Introduction

The RC32336 device is a member of the IDT™ Enterprise™ family of integrated communications processors. It provides an effective solution for small office/home office (SOHO) applications including gateways and both single-band or dual-band wireless access points. Featuring a MIPS compatible CPU core, the device also includes a memory controller supporting SDRAM memory, a PCI interface featuring an on-chip arbiter to support up to three external devices, a PCMCIA interface that supports a single I/O device, and two integrated on-chip 10/100 Ethernet MACs to enable WAN and LAN connectivity.

This application note provides information on board architecture, signal routing requirements, and system loading requirements that should be followed when designing an SDRAM-based memory subsystem capable of operating at the maximum system bus frequency/s of the processor.

Architectural Design

The SDRAM controller provides a glueless interface to industry standard SDRAMs and SDRAM SODIMMs. The SDRAM controller provides two chip selects (SDCSN[1:0]) with each chip select supporting two or four internal SDRAM banks. Two internal banks are supported when 16 Mb SDRAMs are used and four internal banks when 64 Mb, 128 Mb, 256 Mb, 512 Mb SDRAMs are used. Each SDRAM chip select (that is, external SDRAM bank) supports a 32-bit data path.

For maximum SDRAM speed, it is recommended that all SDRAM control and data signals be directly connected to the RC32336. All other memory devices should be placed behind the data and address buffers. The SDCLKOUT pin should be used to drive only the clocks on the SDRAM chips. It should not be used to drive any other device on the board.

The SDCLKINP clock is used to clock in the data from the SDRAM. The SDCLKINP signal should be tapped off from the SDCLKOUT at the SDRAM. The length of the resulting SDCLKINP trace should match the SDRAM data trace length as much as possible. In no case should the length of the SDCLKINP trace exceed the length of the SDRAM data traces. The SDRAM data flow architecture for normally loaded systems is shown in Figure 1 below.

 


Figure 1 SDRAM Data Flow Architecture for Normally Loaded Systems

Notes

The SDRAM data flow architecture for heavily loaded systems is shown in Figure 2 below. The timing of the data path through data transceivers must be considered when designing such systems.

 


Figure 2 SDRAM Data Flow Architecture for Heavily Loaded Systems

Signal Routing

To provide the most margin for SDRAM hold times:

- *Keep all signals going to the SDRAM, address, data, and control signals as short as possible*
- *Match trace lengths as close as possible*
- *Minimize as much as possible the trace length for SDCLKOUT (this is very important)*
- *Make the SDCLKOUT trace the shortest SDRAM trace on the board*
- *Match the length of the SDCLKINP to the SDRAM data lines.*

Although this optimum configuration may not be achievable, the further that the layout deviates from it, the less margin there will be for SDRAM hold times.

System Loading

To support maximum speeds, reasonable SDRAM loading constraints must be followed. For high-speed operation, it is recommended that no more than 6 loads (total) be used. For example, a system with four discrete SDRAM chips, a PROM and possibly one other peripheral can be connected directly to the processor. It is acceptable to use a SODIMM or DIMM, provided it does not contain more than four chips. In addition, any unused clock lines should be left unconnected; otherwise, the loading on SDCLKOUT could exceed the drive capability of the RC32336 SDCLKOUT pin.

It is possible to use more than four SDRAM chips or very large DIMMs at lower speeds. However, if the loading exceeds the above recommendation, users should buffer all of the control, address, and data lines accordingly. Because of the extra delay associated with this, higher system speeds are not achievable. Also, timing analysis should be done when designing such systems. To calculate maximum possible system speeds for specific designs, users should review the RC32336 Data Sheet on IDT's RC32336 web page and the data sheets for the buffers and other devices being used.

Notes**Connecting SDRAM Clocks**

SDRAM accesses are expected to operate at the full bandwidth of the system clock (CLK). In order to accomplish this, the RC32336 provides an output clock (SDCLKOUT) and accepts an input clock (SDCLKINP). Both clocks run at the same frequency as CLK. The output clock, SDCLKOUT, should be connected to the SDRAM chips and returned to the RC32336 through SDCLKINP. Figure 3 below shows the connection of SDRAM clocks.

 


Figure 3 Connection of SDRAM Clocks

When accessing SDRAMs, the RC32336 outputs all SDRAM control signals (such as RASN, MADDR, BWEN, SDWEN, etc.) relative to SDCLKOUT. SDCLKINP is used to register SDRAM read data. This implies that all signals going to the SDRAM chips from the RC32336 must meet setup and hold times relative to SDCLKOUT, while signals going to the RC32336 from the SDRAM chips (i.e. the SDRAM read data) must meet setup and hold times relative to SDCLKINP. Finally, as shown in Figure 3, the circuit board routing and load delay of the SDRAM clock must be within the limits specified in the data sheet.

SODIMM Support

The SDRAM controller can be configured to control SODIMMs. In this mode, the RC32336 drives eight data masks (four on BWEN [3:0] and four on MADDR [20:17]). Because the RC32336 data bus is 32-bits wide and an SODIMM supports a 64-bit data path, either BWEN [3:0] or MADDR [20:17] will control the accessing of the correct word to the SODIMM, depending on the state of an internally decoded upper address bit. To connect an SODIMM to the RC32336, connect the 32-bit data bus (MDATA [31:0]) to the 64-bit data bus of the SODIMM. MDATA [0] connects to SODIMM DATA [0] and SODIMM DATA [32]; MDATA [1] connects to SODIMM DATA [1] and SODIMM DATA [33], and so on. Connect MADDR [20:17] to the upper data masks of the SODIMM (DQM [7:4]) and BWEN [3:0] to the lower data masks (DQM [3:0]).

All remaining SDRAM control signals are connected as usual. SODIMM mode is enabled by setting the SODIMM Mode Enable (SOD) bit in the SDRAMC register. The SDRAMC register DTTYPE field is configured with the type of SDRAMs on the SODIMM. For SODIMMs that require two chip selects (SDCSN [0:1]), both SDRAM memory regions must be configured so that the two regions are equal, contiguous, and together total the amount of memory on the SODIMM. For an example, see Figure 4.

Notes

 


Figure 4 SODIMM Connection Example

SDRAM System Example

The purpose of this example is to show how to program the SDRAM controller with the RC32336 and 128MB of SDRAM (SODIMM). Refer to Figure 4. Because the system uses two 64MB SODIMMs, one of the SODIMMs must be connected to SDCSN [0] and the other to SDCSN [1]. Finally, because each of the two SODIMMs provides 64MB and is connected to one of the RC32336's SDRAM chip-selects, the SDRAM Base and Mask registers could be programmed to the following:

- *SDRAMC.DTYPE = 2Mb x 8 x 4 (the SODIMM is composed of eight 2Mb x 8 x 4 SDRAM chips).*
- *SDRAMC.SOD = 1 (enable SODIMM mode).*

SDRAM0BASE = 0x0000_0000	64MB
SDRAM0MASK = 0xFC00_0000	
SDRAM1BASE = 0x0400_0000	64MB
SDRAM1MASK = 0xFC00_0000	

Note: The above Base and Mask register programming will allocate 128MB of continuous SDRAM space starting at physical address 0x0000_0000. If each SODIMM is composed of eight 2Mb x 8 x 4 SDRAM chips, the SDRAMC register must be programmed as follows:

Other SDRAM fields, such as CL, RCD, RP, and RC should be programmed to values consistent with those in the SODIMM's specification. Note that if DIMMs are used, they should contain a maximum of 8 chips. For example, if two DIMMs are used, each DIMM should contain no more than four chips.

Design Resources

Detailed information on the 79EB336 evaluation board, which is designed to support the maximum system bus frequencies, is available at:

(TO BE ADDED WHEN PRODUCT IS ANNOUNCED AND WEB PAGE CREATED)

The SDRAM board architecture is depicted in Figure 5.

Notes

 


Figure 5 Block Diagram of the 79EB336 Evaluation Board

Acknowledgements

The following persons contributed to this document by providing technical content.

Harold Gomard, IDT Inc.

Paul Snell, IDT Inc.

References

79RC32336 Data Sheet — IDT Inc.

79RC32336 User Reference Manual — IDT Inc.

79EB336 Evaluation Board Manual — IDT Inc.

SDRAM Architecture, Signals and Routing, AN 260 — Paul Snell, IDT Inc.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.