

Transient Protection for the Standard RS-485 Transceiver: ISL3152E

Standard compliant RS-485 transceivers, such as the ISL3152E, have asymmetric stand-off voltages of -9V and +14V. This requires a bidirectional TVS with asymmetric breakdown voltages. The only device satisfying this requirement is the 400W TVS, SM712 from Semtech. This application note provides the schematic, bill of materials, and layout guidelines for a transient protection circuit for the ISL3152E transceiver.

Contents

| | |
|--------------------------------------------------------|---|
| 1. Asymmetric Transient Voltage Suppressor SM712 | 2 |
| 2. TVS Design Cautions | 3 |
| 3. Layout Suggestions | 4 |
| 4. Revision History | 4 |

List of Figures

| | |
|--------------------------------------------------------------------------------------------------|---|
| Figure 1. SM712 | 2 |
| Figure 2. Transceiver Damage Due to Zener Sharing High Transient Current with External TVS | 3 |
| Figure 3. IEC61000-4-5 Level 2 (1kV) Surge Protection and Associated Bill of Materials | 3 |
| Figure 4. Suggested PCB Layout with Ground and VCC Layers | 4 |

Related Literature

For more detailed information on transient protection for RS-485 transceivers, refer to the following application notes on our website [ISL3152E](#).

- AN1976: Important Transient Immunity Tests for RS-485 Networks
- AN1977: Transient Voltage Suppressors: Operation and Features
- AN1978: Surge Protection for Renesas' Standard RS-485 Transceivers
- AN1979: Surge Protection simplified with Renesas' Overvoltage Protected (OVP) Transceivers

1. Asymmetric Transient Voltage Suppressor SM712

The SM712 transient voltage suppressor (TVS) is designed for asymmetrical (+12 to -7V) protection in standard RS-485 applications. The device is used to protect transceivers against transient voltages resulting from Electrostatic Discharge (ESD), Electrical Fast Transients (EFT), and lightning. The SM712 integrates two 12V and two 7V TVS diodes in a single SOT23 package. It is rated for 400W peak-pulse power ($t_p = 8/20\mu s$) and protects to:

- IEC61000-4-2 (ESD) +15kV (air), +8kV (contact)
- IEC61000-4-4 (EFT) 40A (%/50ns)
- IEC61000-4-5 (Lightning) 12A (8/20 μs)

Figure 1 shows the SM712 inner structure and Table 1 lists its key parameters.

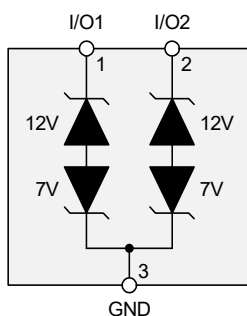


Figure 1. SM712

Table 1. Key Parameters of SM712

| Parameter | Symbol | 12 TVS | 7V TVS | Unit |
|-------------------------------|-----------|---------|--------|------|
| Stand-Off Voltage | V_{WM} | 12 | 7 | V |
| Breakdown Voltage | V_{BR} | 13.3 | 7.5 | V |
| Clamping Voltage at $I_{P,P}$ | V_C | 26 | 12 | V |
| Peak-Pulse Current | $I_{P,P}$ | 17 | | A |
| Derating Factor at +85°C | DF | average | 0.5 | - |
| | | pulse | 0.8 | |
| Junction Capacitance | C_J | 45 | | pF |

2. TVS Design Cautions

Many application examples of transient protected RS-485 nodes have the TVS diodes directly connected to the transceiver bus terminals. Because standard RS-485 transceivers have internal ESD structures whose trigger levels are close to the external SM712 breakdown voltage (V_{BR}), the transceiver ESD cells might interact with the external TVS.

The ESD structures within the ISL3152E have a Zener switching characteristic, similar to the one of the SM712, and therefore will share the high transient current with the external TVS. Because a surge transient has about eight million times the energy of an ESD transient of the same peak-pulse voltage, the transceiver ESD cells are at risk of damage by high surge currents.

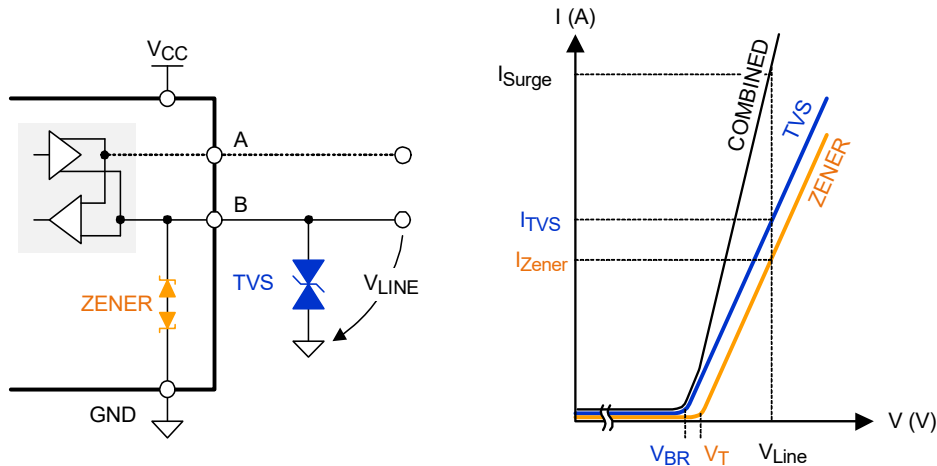


Figure 2. Transceiver Damage Due to Zener Sharing High Transient Current with External TVS

To limit the bus currents into the transceiver during a surge event, carbon composite or pulse-proof thick-film resistors should be inserted between the TVSs and the transceiver. Due to their voltage divider action with the bus termination resistors, their value should be less than 20Ω to minimize bus voltage attenuation during normal operation. Figure 3 shows the schematic of a Level 2 surge protection example for the ISL3152E and its bill of materials.

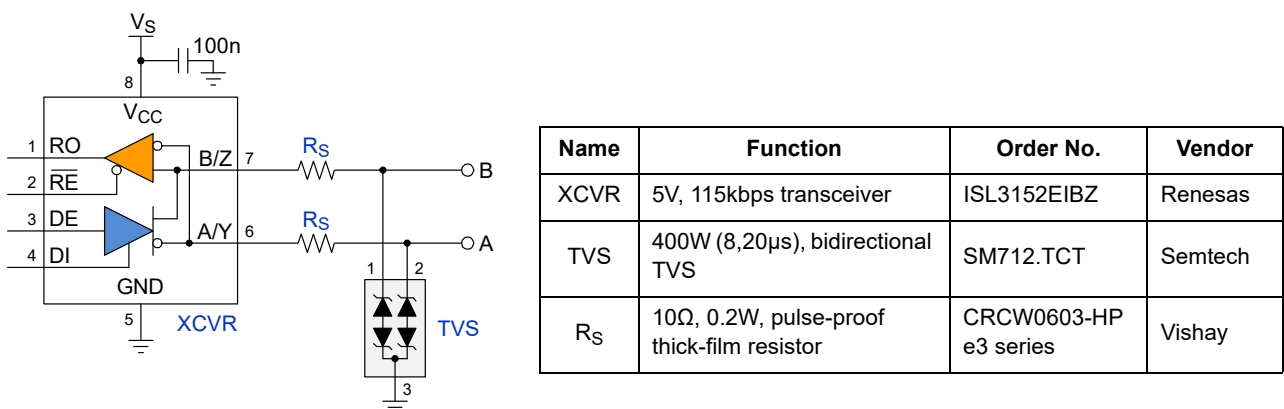


Figure 3. IEC61000-4-5 Level 2 (1kV) Surge Protection and Associated Bill of Materials

Note: The design does not use a TVS for differential transients, as these mainly occur when TVS switching does not happen simultaneously (as with some older, high-capacitance TVS diodes), or when non-twisted pair cables, such as lamp wires or flat band cables are used. When using twisted pair cable in combination with modern TVS devices, the possibility for differential voltage transients is eliminated.

3. Layout Suggestions

While it is possible to use smaller size 0402 resistors for R_S , manufacturer Vishay does not recommend them for wave soldering but reflow soldering only. To enable the application of either technique, 0603 resistors are recommended.

Figure 4 shows a recommended PCB layout for the TVS section. Because electrical transients span a wide frequency range, the application of low-inductance reference planes for V_{CC} and ground layers is strongly advised. This will typically require a minimum 4-layer board.

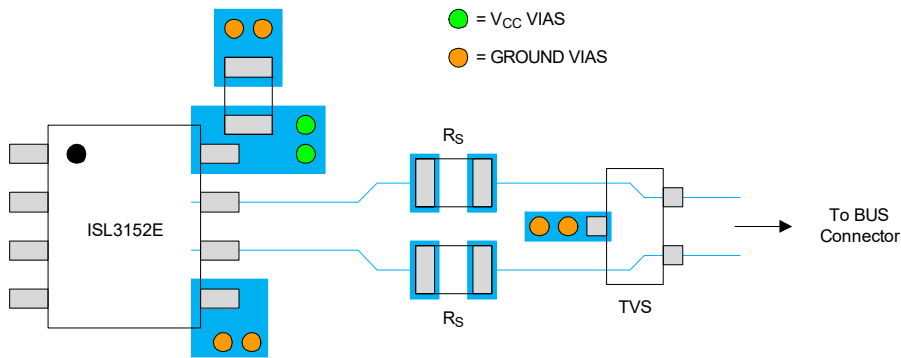


Figure 4. Suggested PCB Layout with Ground and V_{CC} Layers

- Place the components in the direction of the current flow.
- Use 45° bends for PCB traces.
- Place decoupling capacitors close to all active components, such as transceiver, voltage regulator, and MCU.
- Use at least two vias for each connection to the VCC or ground planes to reduce via inductance.

4. Revision History

| Revision | Date | Description |
|----------|--------------|---------------------------------------------------------------------------------------------------------------|
| 1.00 | Aug 19, 2022 | Applied new template. Updated titles in the related literature section. Added Revision History section. |
| 0.00 | Jul 17, 2017 | Initial release |

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Rev.1.0 Mar 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.