

HA5020 Operational Amplifier Feedback Resistor Selection

AN9305
Rev 0.00
January 1995

Optimum AC performance of current feedback amplifiers in general and of the HA-5020 in particular depends upon careful selection of the feedback resistor, R_F . The benefit of higher usable bandwidth (compared with conventional voltage feedback amplifiers) and the ability to control the frequency response (by choosing the value of R_F) carries an expense in that the design process becomes more complicated. This is particularly true if an intuitive knowledge of how the device will behave in the end application is lacking. The purpose of this App Note is to provide a conceptual foundation on which this intuitive knowledge can be built.

The choice of the optimum resistor value depends upon design goals for the application subject to conditions of closed loop gain, source impedance, and load. As a point of reference, typical curves are provided in the data sheet that show how the frequency response is affected by closed loop gain, feedback resistor value, and load resistance. Source impedance, if it is large, becomes a factor only in conjunction with capacitance at the inputs. The data sheet curves are all generated with a 50Ω source impedance.

To illustrate how one might approach the problem of selecting a feedback resistor based on closed loop gain, consider the simple model of Figure 1. Between the inputs is a unity gain voltage buffer with non-zero output impedance indicated by R_I . The transimpedance gain, R_Z , is a function of frequency having a high DC value that forces I_ϵ to zero. The model's behavior is influenced by external elements consisting of a feedback network (R_F and R_G), source and load impedances (R_S and R_L), and stray capacitance at the amplifier's inputs (C_S).

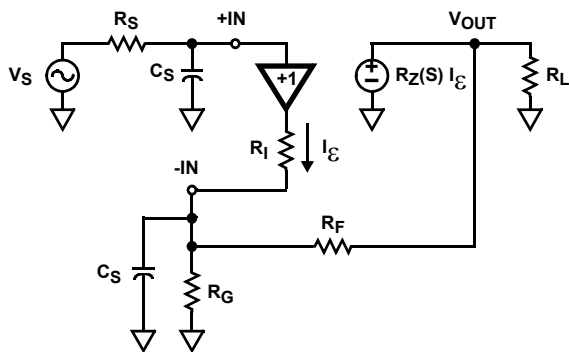


FIGURE 1. SIMPLE CURRENT FEEDBACK AMPLIFIER MODEL

Derivation of the transfer function will confirm that the non-zero inverting input impedance, R_I , causes the circuit's bandwidth to degrade as the closed loop gain increases, while stray capacitance at the negative input gives rise to gain peaking particularly at low gains (intuitively, C_S is in parallel with R_G causing the gain as determined by the feedback network to increase with frequency).

Gain peaking due to capacitance at the inverting input is most easily dealt with by placing a resistor in series with the positive input. If we assume that the stray capacitance at the

positive input equals the stray at the negative input, we can choose R_S equal to the parallel combination of R_F and R_G . This introduces a pole at the positive input which cancels the zero at the negative input, thereby eliminating the gain peak. Note that any remaining gain peaking is a result of excessive phase shift around the loop. Excess phase shift around the loop can be reduced by increasing R_F .

Bandwidth degradation due to non-zero inverting input resistance is also easy to deal with as long as the product of the closed loop gain and the inverting input resistance does not exceed the optimum value for R_F in unity gain. By solving the transfer function for constant bandwidth, we arrive at the following equations for R_F and R_G :

$$R_F = R_{FO} - A_{CL} * R_I \quad (\text{EQ. 1})$$

$$R_I = R_F / (A_{CL} - 1) \quad (\text{EQ. 2})$$

Where,

R_{FO} is the optimum value for unity gain (1000Ω),

R_I is the inverting input impedance (75Ω), and

A_{CL} is the desired closed loop gain.

A comparison between actual measured results in Figures 2 and 3 provides graphic reinforcement for the utility of these equations. Figure 2 illustrates the failure to consider stray input capacitance and inverting input resistance, while Figure 3 incorporates the lessons learned from analyzing our simple model.

In Figure 2, a family of closed loop gain curves was obtained on a representative unit using $R_S = 50\Omega$ and constant R_F ($R_F = R_{FO} = 1000\Omega$). The measured stray capacitance at either input was 2pF . The results in Figure 3 were obtained from the same unit, except that (within the constraints of available standard resistor values) R_F and R_G were chosen according to the equations above and R_S was chosen to be equal to the parallel combination of R_F and R_G .

One limitation of the above model is that it does not include the effects of the load. In general if R_L is 400Ω or above, the response is independent of the load. If R_L is less than 400Ω , the response becomes more damped and the bandwidth degrades. Here again the bandwidth degradation can be compensated for by lowering the value of R_F .

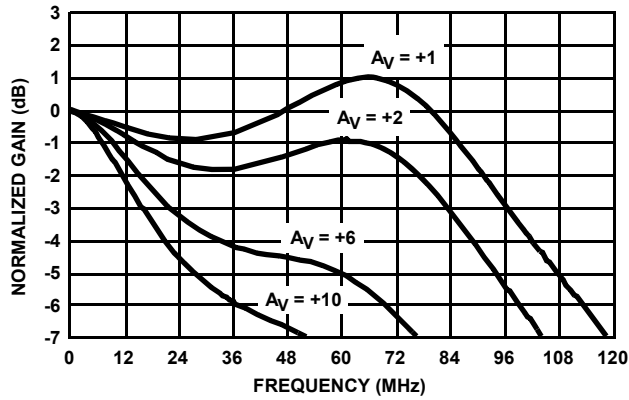


FIGURE 2. FREQUENCY RESPONSE vs CLOSED LOOP GAIN
USING FIXED $R_F = 1k\Omega$, $R_S = 50\Omega$, $R_L = 402\Omega$

TABLE 1. RESISTOR VALUES FOR FIGURE 2

A_V	$R_F (\Omega)$	$R_G (\Omega)$	$R_S (\Omega)$	BW (MHz)	PEAKING (dB)
+1	1K	-	50	97	1
+2	1K	1K	50	84	<0
+6	1K	200	50	22	<0
+10	1K	110	50	16	<0

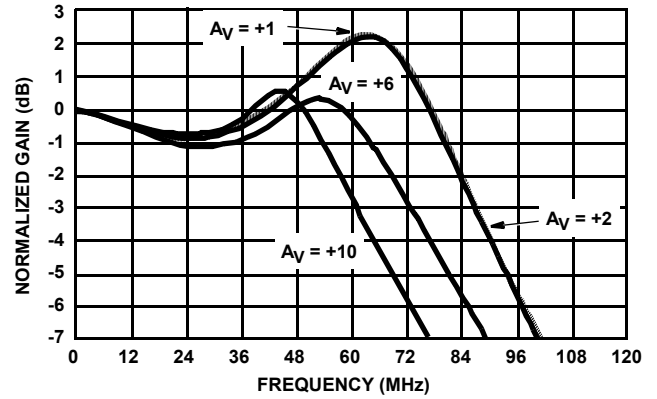


FIGURE 3. FREQUENCY RESPONSE vs CLOSED LOOP GAIN
 $R_F = 1000 - A_V(75\Omega)$, $R_S = R_F \parallel R_G$, $R_L = 402\Omega$

TABLE 2. RESISTOR VALUES FOR FIGURE 3

A_V	$R_F (\Omega)$	$R_G (\Omega)$	$R_S (\Omega)$	BW (MHz)	PEAKING (dB)
+1	909	-	909	87	2
+2	825	825	422	87	2
+6	562	110	90.9	74	0.5
+10	237	26.1	23.7	62	0.5

NOTE: $R_F = 1000 - A_V(75\Omega)$, $R_S = R_F \parallel R_G$, $R_L = 402\Omega$

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338