

Selecting Among HIP6004/5, HIP6004A/5A, HIP6004B/5B, and HIP6014/15

TB356
Rev.0.00
July 1998

Introduction

All eight part numbers listed above belong to voltage-mode PWM controllers targeted at desktop computer and/or microprocessor applications. These components were designed with emphasis on various Intel and industry requirements, specifically regarding the Pentium II processor and its derivatives.

Background Details

The evolution of these different, yet very similar ICs, was dictated by changes in Intel requirements as well as customer feedback. To ease the system migration to subsequent parts, all the ICs are compatible within their class type. Specifically, all even part numbers (HIP6004/4A/4B/14) represent pin-for-pin compatible synchronous buck controllers, while the odd numbers (HIP6005/5A/5B/15) are pin-for-pin compatible standard buck controllers [1-8]. Among the four pairs (4/5, 4A/5A, 4B/5B, and 14/15), however, there are functional subtleties that differentiate them.

Functional Differences

Reference Voltage DAC

All these converters have a 5-bit DAC-controlled internal voltage reference.

HIP6004 and HIP6005 have an analog DAC, where the VID inputs connect directly to a resistive internal network. Shorting various VID (voltage identification) inputs to ground changes the reference voltage and the converter's output voltage as a result. The drawback of such architecture is that the VID inputs have to be either open or shorted to ground. Pull-up or pull-down resistors on the VID input lines result in erroneous output voltage settings.

HIP6004A/4B/5A/5B/14/15, on the other hand, have fully buffered TTL-compatible VID inputs. Pull-ups to 5V do not affect the output voltage settings (open circuit still regarded as logic 'high'). Table 1 summarizes this difference.

TABLE 1. REFERENCE VOLTAGE DAC TYPE / PULL-UP COMPATIBILITY

5-BIT DAC	6004/5	6004A/5A	6004B/05B	6014/15
TTL-Compatible	No	Yes	Yes	Yes
Pull-up Resistors	Not Allowed	Allowed	Allowed	Allowed

Output Voltage Program

Among the eight part types, there are small differences in the operation of the DAC, as shown in Table 2. While the DAC is, in all cases, programmed to provide the same output voltage for a given VID combination, some controllers have certain voltage settings disabled.

TABLE 2. OUTPUT VOLTAGE PROGRAM AND PGOOD RESPONSE

VID PINS LOGIC STATE	OUTPUT VOLTAGE (HIP60xx)				PGOOD LOGIC STATE (HIP60xx)			
	VID 4 3 2 1 0	04 05	04A 05A	04B 05B	14 15	04 05	04A 05A	04B 05B
0 1 1 1 1	1.30	0	1.30	0	X	0	X	1
0 1 1 1 0	1.35	0	1.35	0	X	0	X	1
0 1 1 0 1	1.40	0	1.40	0	X	0	X	1
0 1 1 0 0	1.45	0	1.45	0	X	0	X	1
0 1 0 1 1	1.50	0	1.50	0	X	0	X	1
0 1 0 1 0	1.55	0	1.55	0	X	0	X	1
0 1 0 0 1	1.60	0	1.60	0	X	0	X	1
0 1 0 0 0	1.65	0	1.65	0	X	0	X	1
0 0 1 1 1	1.70	0	1.70	0	X	0	X	1
0 0 1 1 0	1.75	0	1.75	0	X	0	X	1
0 0 1 0 1	1.80	1.80	1.80	1.80	X	X	X	X
0 0 1 0 0	1.85	1.85	1.85	1.85	X	X	X	X
0 0 0 1 1	1.90	1.90	1.90	1.90	X	X	X	X
0 0 0 1 0	1.95	1.95	1.95	1.95	X	X	X	X
0 0 0 0 1	2.00	2.00	2.00	2.00	X	X	X	X
0 0 0 0 0	2.05	2.05	2.05	2.05	X	X	X	X
1 1 1 1 1	2.00	0	0	0	X	0	1	1
1 1 1 1 0	2.10	2.10	2.10	2.10	X	X	X	X
1 1 1 0 1	2.20	2.20	2.20	2.20	X	X	X	X
1 1 1 0 0	2.30	2.30	2.30	2.30	X	X	X	X
1 1 0 1 1	2.40	2.40	2.40	2.40	X	X	X	X
1 1 0 1 0	2.50	2.50	2.50	2.50	X	X	X	X
1 1 0 0 1	2.60	2.60	2.60	2.60	X	X	X	X
1 1 0 0 0	2.70	2.70	2.70	2.70	X	X	X	X
1 0 1 1 1	2.80	2.80	2.80	2.80	X	X	X	X
1 0 1 1 0	2.90	2.90	2.90	2.90	X	X	X	X
1 0 1 0 1	3.00	3.00	3.00	3.00	X	X	X	X
1 0 1 0 0	3.10	3.10	3.10	3.10	X	X	X	X
1 0 0 1 1	3.20	3.20	3.20	3.20	X	X	X	X
1 0 0 1 0	3.30	3.30	3.30	3.30	X	X	X	X
1 0 0 0 1	3.40	3.40	3.40	3.40	X	X	X	X
1 0 0 0 0	3.50	3.50	3.50	3.50	X	X	X	X

NOTE: 'X' = '0' or '1', depending whether the output voltage is within PGOOD limits

PGOOD Response

During normal converter operation (with the VID combination resulting in an output voltage other than 0V), PGOOD asserts a logic 'high' ('1') if the output voltage is within 10% (typical) of the DAC setting (reference).

In the case of HIP6004A/5A, for VID settings resulting in converter shutdown (0V output voltage), PGOOD will assert a logic 'low' ('0'), thus indicating the absence of output voltage.

A case that requires special consideration is the dual-processor system. For these systems, designers use one converter for each processor, "wire AND-ing" the open-drain PGOOD signals from both power converters in order to generate a 'System Power Good' signal. However, if these systems ship with only one processor populated (second processor offered as an upgrade), the empty processor slot would generate a '11111' VID code, which in turn would disable the corresponding converter. If this converter were to employ a HIP6004A or HIP6005A, the 0V output voltage setting would generate a PGOOD 'low', and consequently cause the System Power Good to go 'low', disabling the entire computer system. HIP6004B/5B/14/15 handle this situation by generating a PGOOD 'high' for all VID settings that result in a 0V converter output.

References

For Intersil documents available on the internet, see web site <http://www.intersil.com/>

- [1] *HIP6004 Data Sheet*, Intersil Corporation, FN4275
- [2] *HIP6005 Data Sheet*, Intersil Corporation, FN276
- [3] *HIP6004A Data Sheet*, Intersil Corporation, FN4417
- [4] *HIP6005A Data Sheet*, Intersil Corporation, FN4418
- [5] *HIP6004B Data Sheet*, Intersil Corporation, FN4567
- [6] *HIP6005B Data Sheet*, Intersil Corporation, FN4568
- [7] *HIP6014 Data Sheet*, Intersil Corporation, FN4420
- [8] *HIP6015 Data Sheet*, Intersil Corporation, FN4421

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338