

Flammable Gas Monitor SLG46537

The application note gives step-by-step guidelines for creating a flammable gas monitor.

The application note comes complete with design files which can be found in the Reference section.

Contents

1. Terms and Definitions	2
2. References.....	2
3. Introduction.....	2
4. MQ-2 Sensor background	2
5. Testing the sensors	4
6. Implementation of an Alarm using the MQ-2 for LPG gas.....	6
7. Possible modifications of this design	7
8. Conclusion	8
9. Revision History	9

Figures

Figure 1. MQ-2 module.....	2
Figure 2. Sensor application schematic.....	3
Figure 3. Response curves for various gases	3
Figure 4. Sensor response vs. Temperature	4
Figure 5. MQ-2 output with no flammable gas.....	4
Figure 6. MQ-2 output with flammable gas.....	5
Figure 7. LM35D output at 25C	5
Figure 8. Schematic in GreenPAK Designer	6
Figure 9. Complete detector design in clean air	7
Figure 10. CCS801 resistor setting	7
Figure 11. CCS801 resistor calculation	8
Figure 12. CCS801 response chart	8

Tables

Table 1. Pin function	3
-----------------------------	---

1. Terms and Definitions

LED	Light Emitting Diode
RL	Load Resistance

2. References

For related documents and software, please visit:

[GreenPAK Programmable Mixed-Signal Products | Renesas](#)

Download our free Go Configure Software Hub [1] to open the .gp files [2] and view the proposed circuit design. Use the GreenPAK development tools [3] to freeze the design into your own customized IC in a matter of minutes. Renesas provides a complete library of application notes [4] featuring design examples as well as explanations of features and blocks within the Renesas IC.

[1] [Go Configure Software Hub](#), Software Download and User Guide, Renesas Electronics

[2] [AN-1133 Flammable Gas Monitor.gp](#), GreenPAK Design File, Renesas Electronics

[3] [GreenPAK Development Tools](#), GreenPAK Development Tools Webpage, Renesas Electronics

[4] [Application Notes](#), GreenPAK Application Notes Webpage, Renesas Electronics

[5] [SLG46537 Datasheet](#), Renesas Electronics

3. Introduction

Described here is a flammable gas detector using a GreenPAK5. It monitors continuously, which makes it suitable for industrial use. The detector includes a temperature failsafe to alert when readings are compromised because of ambient temperature deviation.

4. MQ-2 Sensor background

The MQ-2 sensor can detect a wide range of gases such as LPG, Propane, Methane, Alcohol, Hydrogen and Smoke etc. A module with MQ-2 ([Figure 1](#)) is available having a built-in potentiometer for the load resistance. This allows adjustment of the resolution.



Figure 1. MQ-2 module

The MQ-2 datasheet shows the sensing circuit implementation with a Load Resistance (RL), as shown in [Figure 2](#).

The graph in [Figure 3](#) shows the expected sensor response to various gases (in controlled Humidity and temperature).

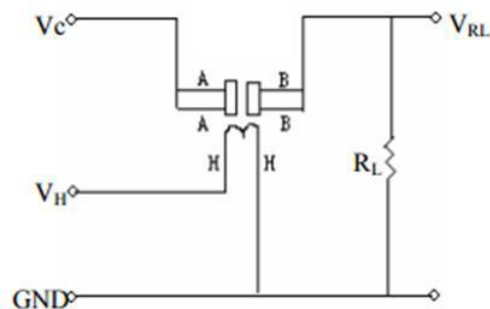


Figure 2. Sensor application schematic

Table 1 shows the PIN functions. D0 (Digital output) will not be used this time since its function is to only detect the presence of a gas, but not its quantity. We will be using A0 (Analog out) so that we can set a threshold corresponding to a permissible concentration.

Table 1. Pin function

PIN	Function
VCC	5V supply
GND	Ground
A0	Analog Output
D0	Digital Output

Ambient temperature does affect the MQ-2 behavior, so we will use the LM35D to let us know when the room temperature exceeds 30° C. This will be a way to alert us that the readings have moved past the calibration setting.

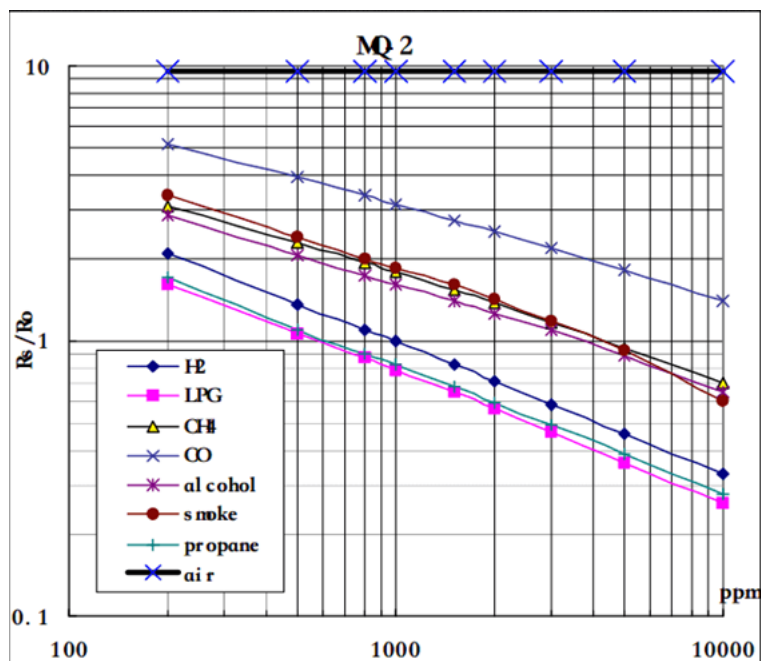


Figure 3. Response curves for various gases

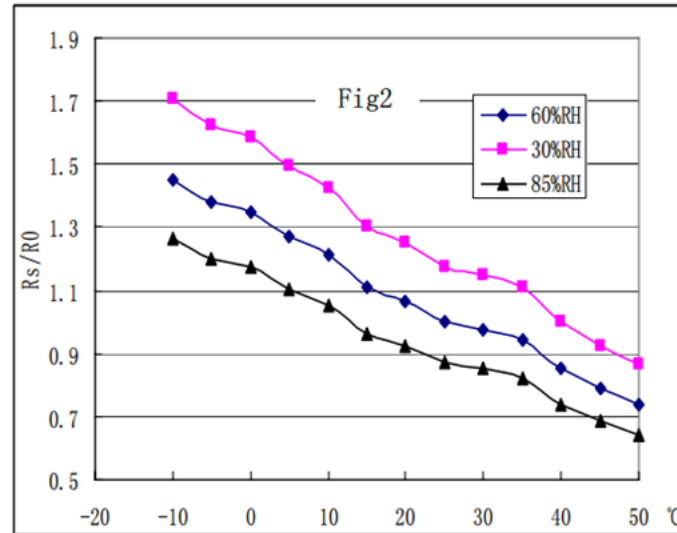


Figure 4. Sensor response vs. Temperature

5. Testing the sensors

After powerup and several minutes warmup time, the MQ-2 sensor output stabilized at approx. 0.250 V with no flammable gas present, (see [Figure 5](#)).

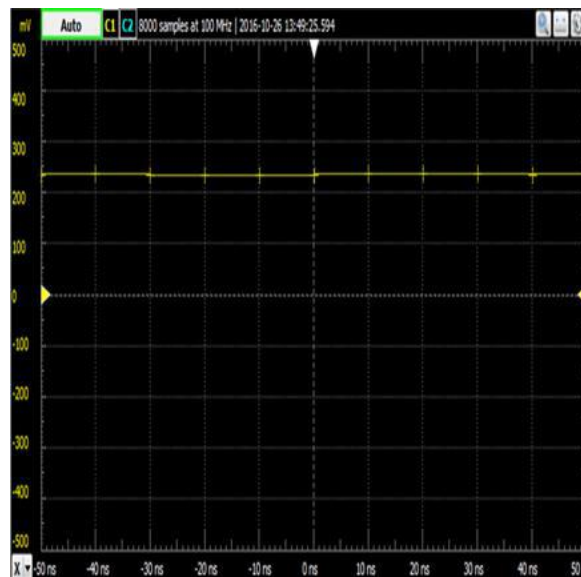


Figure 5. MQ-2 output with no flammable gas

The first test is done using the LPG fumes from inside a cigarette lighter. The lighter was nearly empty, but with the last fumes of the LPG gas, we were able to see a noticeable change in the stabilized output value of the sensor. We measured a delta of almost 0.75V (see [Figure 6](#)).

From MQ-2 datasheet information, we can extract the following equations:

$$RS_{Neutral} = \frac{V_{input} - V_{output}}{V_{output}} \quad (1)$$

V Input is always going to be 5V and our stabilized voltage/output voltage will be 0.25V. This Yields an RsNeutral of 19.

Going back to [Figure 3](#), we can see that the Rs/Ro ratio of clean air is 9.8. That allows us to obtain the Ro using the formula:

$$R_0 = RS_{Neutral}/9.8 \quad (2)$$

In our case R_0 yields a value of 1.93.

Note that these values don't have units, and are only referencing to the Chart described in [Figure 3](#). To confirm this, we will be using the 1V value sensed from the LPG fumes.

Applying the Formula again (1)

$$R_{SLPG} = \frac{5V - 1V}{1V}$$

$R_{SLPG} = 4$ and now when we look for the $\frac{R_S}{R_0}$ ratio again, we get a ratio of 2.07.

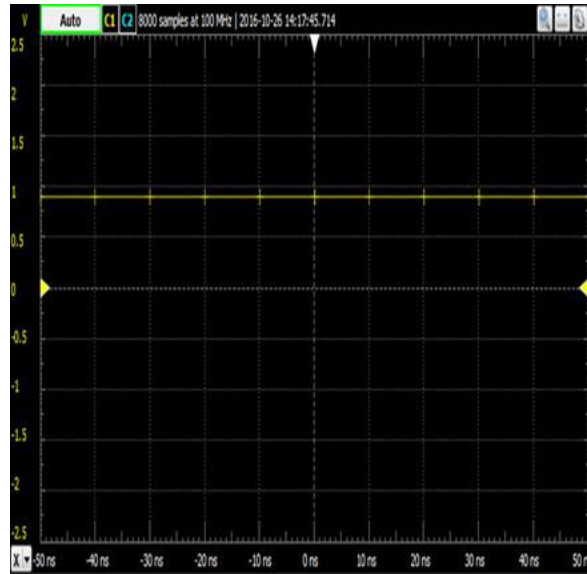


Figure 6. MQ-2 output with flammable gas

Going back to the datasheet and [Figure 3](#), we can see that the LPG curve has its first point at 200 ppm. Also, the R_S/R_0 ratio closely aligns with the ratio described by the graph.

Implementing the LM35D is straightforward since its output follows a very linear change of 10mV/C°. [Figure 7](#) shows the reading for a typical room temperature measurement (at almost 25° C).

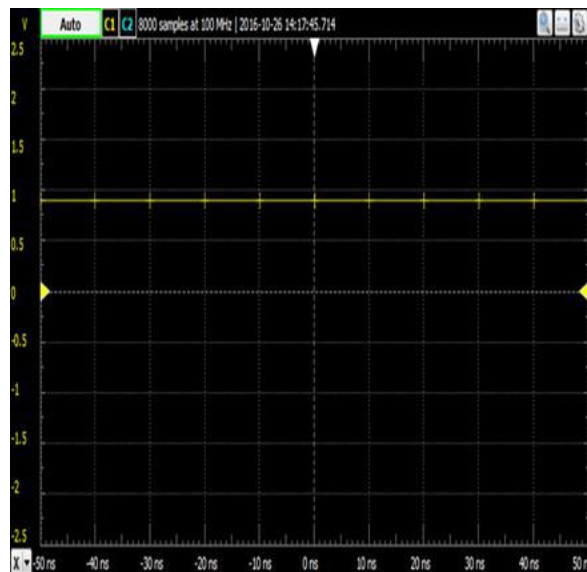


Figure 7. LM35D output at 25C

6. Implementation of an Alarm using the MQ-2 for LPG gas

We select a ppm value for the LPG curve and correlate it with the chart shown in [Figure 3](#). For this application, let us select a value of 700 ppm.

The R_s/R_o for it will be almost 0.9. Using the previously mentioned values, we can see that $R_s = R_o \cdot 0.9 = 1.737$. Now, when we substitute this value in equation (1), we get a Voltage threshold of 1.82V.

Also, (as part of the temperature alert), when the LM35D gives us 300mV, the GreenPAK will show a different color on the RGB LED.

Along with this Appnote, a .gp5 file is available which contains the configuration shown in [Figure 8](#).

The signal LM35D_Threshold and MQ-2_Threshold were faster than the Inverted ones coming from the blocks 2-L0 and 2-L1. Thus, first ones were delayed using two inverters and it led to LM35D_delayed and MQ-2_delayed. Both now have enough delay time between them for the latches to work reliably.

This design uses an RGB LED where the color represents the status. GREEN means that there is no LPG gas present; BLUE means that the room temperature is higher than the normal sensing conditions (causing a change on the readings, as shown in [Figure 5](#)); and RED shows that the LPG threshold has been reached.

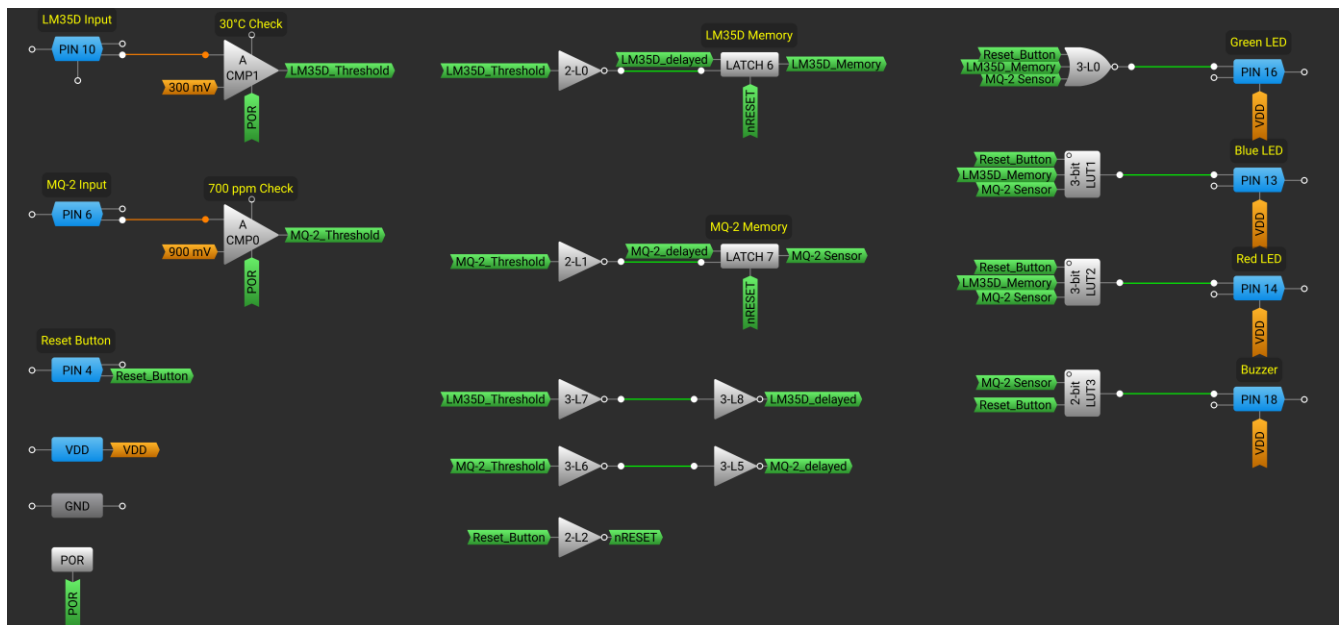


Figure 8. Schematic in GreenPAK Designer

Along with the red color, an Alarm will also start sounding.

The latches get reset when nReset is LOW. When the Reset button is not pressed, its value is LOW, so we invert its signal to get nReset which will be HIGH. This will ensure normal behavior of the latches until the Reset Button is Pressed.

[Figure 9](#) shows the complete detector design operating in clean air.

The CCS801 works like the MQ-2; it changes its resistance according to the concentration of the desired gas present. However, unlike the MQ-2, its warmup/stabilization period is shorter, and that allows us using a PWM to power the resistance heater. This also makes more practical the use of WAKE/SLEEP cycles for the ACMP power savings.

The CCS801 load resistors chosen are shown in [Figure 10](#).



Figure 9. Complete detector design in clean air

7. Possible modifications of this design

The current design proposes the use of the MQ-2 Gas sensor as a broader solution to detect several kinds of gases. The downside of the MQ-2 is that it consumes 150mA at 5V. As a result, the MQ-2 is better suited for continuous monitoring using a wall adapter.

An alternative sensor is the CCS801 from CMOS SENSORS. In contrast to the MQ-2 5V oven, the CCS801 oven works with a peak voltage of only 1.8V. During normal and datasheet specified characteristics, the CCS801 has an average power consumption of 0.9mW.

PIN 1 along with PIN 3 of the CCS801 represent the sensing resistor. A simple voltage divider can be used to obtain the R_s Neutral of this sensor. The formula is shown in [Figure 11](#).

The value of R_s Neutral can now be used along with the chart in [Figure 12](#) to obtain a ratio proportional to the desired concentration of gas.

While the CCS801 can't detect a wide range of gases, it can still detect CO; the main component of smoke.

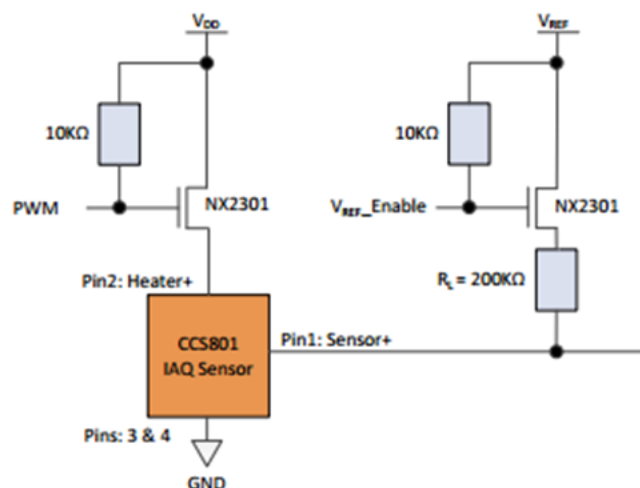


Figure 10. CCS801 resistor setting

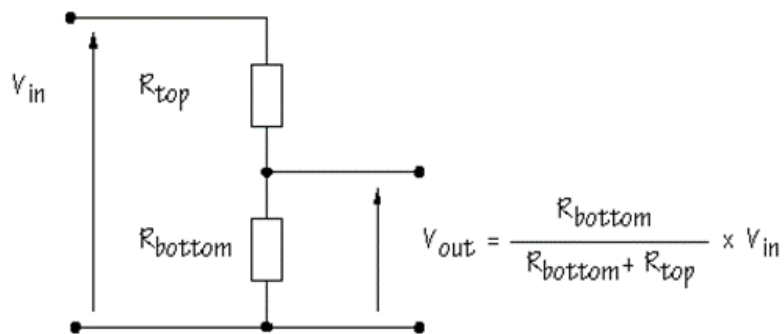


Figure 11. CCS801 resistor calculation

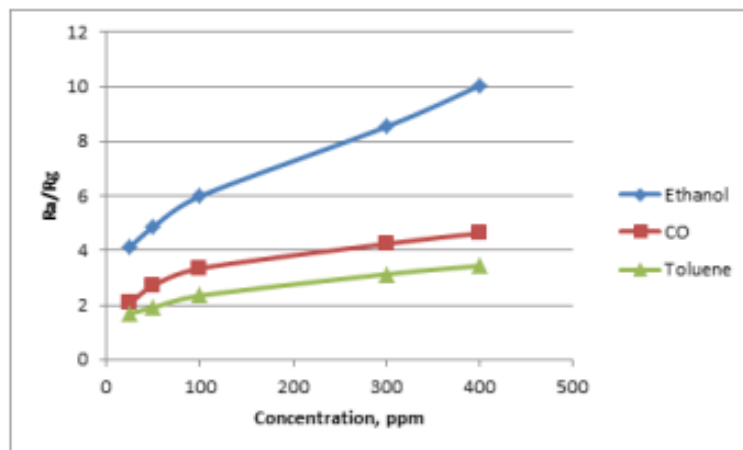


Figure 12. CCS801 response chart

8. Conclusion

It was demonstrated that the GreenPAK versatility allows the designer to customize an analog front end for interface to the MQ-2 and similar sensors. Designing industrial detectors of many types are within reach because of the flexibility of the circuit resources available within the GreenPAK family of products.

9. Revision History

Revision	Date	Description
1.00	November 15, 2016	Initial release.
2.00	April 28, 2026	The part number has been changed from SLG46531V to SLG46537V.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.