

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

38K0/38K2 Group

Application Circuit Reference

Renesas Single-Chip Microcomputers

All information contained in these materials, including products and product specifications, represents information on the product at the time of publication and is subject to change by Renesas Electronics Corp. without notice. Please review the latest information published by Renesas Electronics Corp. through various means, including the Renesas Electronics Corp. website (<http://www.renesas.com>).

Keep safety first in your circuit designs!

* RENESAS TECHNOLOGY CORPORATION puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of non-flammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

- These materials are intended as a reference to assist our customers in the selection of the RENESAS semiconductor product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to RENESAS TECHNOLOGY CORPORATION or a third party.
- RENESAS TECHNOLOGY CORPORATION assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
- All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by RENESAS TECHNOLOGY CORPORATION without notice due to product improvements or other reasons. It is therefore recommended that customers contact RENESAS TECHNOLOGY CORPORATION or an authorized RENESAS Semiconductor product distributor for the latest product information before purchasing a product listed herein. The information described here may contain technical inaccuracies or typographical errors. RENESAS TECHNOLOGY CORPORATION assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors. Please also pay attention to information published by RENESAS TECHNOLOGY CORPORATION by various means, including the RENESAS Semiconductor home page (<http://www.renesas.com/eng/>).
- When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. RENESAS TECHNOLOGY CORPORATION assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
- RENESAS TECHNOLOGY CORPORATION semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact RENESAS TECHNOLOGY CORPORATION or an authorized RENESAS Semiconductor product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical aerospace, nuclear, or undersea repeater use.
- The prior written approval of RENESAS TECHNOLOGY CORPORATION is necessary to reprint or reproduce in whole or in part these materials.
- If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination. Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
- Please contact RENESAS TECHNOLOGY CORPORATION or an authorized RENESAS Semiconductor product distributor for further details on these materials or the products contained therein.

Revision History	38K0/38K2 Group Application Circuit Reference
------------------	---

Rev. No.	Date	Contents
0.0	2001/11/7	Draft version
1.0	2001/11/26	First Edition of PDF Version
1.1	2002/1/30	Page 9, Figure 1.4.3 (1) Circuit example: connection between programmer connector and 38K0/38K2 for standard serial interface of boot ROM area and F0USB interface.
1.2	2002/10/20	P4 Figure 1.2.1(4) D0+/D0- Pin Connection, 68pF condenser of addition to D0+/D0-
		P5 Figure1.3.1 D1+/D1- (D2+/D2-) Pin Connection, 68pF condenser of addition to D1+/D1- (D2+/D2-)
		P5 Figure1.3.1 D1+/D1- (D2+/D2-) Pin Connection, 68pF condenser of addition to D1+/D1- (D2+/D2-)
1.4	2003/2/17	P5 Additional Notes for Down-port Settings P9 Corrections for "Table 1.4.3 Application Program Selections according to Port"

* Related Materials

RENESAS Microcomputers: 38K0 (38K2) Group Data Sheet

Instructions for MFW-1 Multi-Flash Programmer (Sunny Giken Inc.)

* Home page of **RENESAS** Semiconductors.

<http://www.renesas.com/en/usb>

- Table of Contents -

1.1	Introduction	1
1.2.1	USB-related Pins	2
1.3.1	HUB-related Pins	7
1.3.2	Over-Current Detection/Protection	9
1.4.1	Vcc Pin and USBVref Pin Voltage	10
1.4.2	Vref and VccE Voltage Pins	11
1.4.3	On-Board Flash Programming	12

1.1 Introduction

This reference note describes implementing RENESAS 38K0/38K2 Group MCUs for USB application systems through various example circuits. The reference value of each component used in these example circuits needs to be adjusted when applying to your system. Therefore, RENESAS recommends calibrating each value to fit the target application,

1.2 38K0/38K2 Group Standard USB Circuits

This section describes the standard USB circuits for the 38K0/38K2 Group. For more details concerning other peripheral functions, refer to the 38K0/38K2 Group data sheet.

1.2.1 USB-related Pins

Table 1.2.1 shows USB-related pin functions of 38K0/38K2 Group MCUs.

Table 1.2.1 38K0/38K2 Group USB –related Pins

Pin No.	Symbol	Name	Function
23	USBV _{REF}	USB reference power source	Power source pin for USB port circuit (3.00~3.60V). <u>*Power supply source can be selected in register setting.</u>
24	TrON	USB reference voltage output	Output pin to pull-up D0+ by 1.5k-ohm external resistor. Outputs USBVref voltage when register is enabled.
25	D0+	USB upstream	USB upstream I/O port. USB input level. USB output level output structure.
26	D0-	I/O	

(1) USB Reference Power Supply Pin (USBVref)

The USB ports of the 38K0/38K2 MCU operate at 3.00~3.60V. The supply voltage is provided from the USBVref pin (USB reference power source pin). Normally, the built-in USB reference voltage circuit generates 3.30V. But the 38K0/38K2 Group allows the user to enable/disable this circuit through VREFE (USB reference voltage enable bit), bit 4 of USBCON (USB control register). When the circuit is disabled, supply 3.00~3.60V from this pin.

When the reference circuit is enabled, this pin must be pulled down to ground with a 0.1uF by-pass capacitor and a 2.2uF capacitor (electrolytic type), as shown in Fig. 1.2.1(1)-a. The capacitors must be placed as close to the pin as possible. When the reference circuit is disabled, the pin must be supplied with 3.00~3.60V externally and connected to ground with a 0.1uF capacitor, as shown in the figure.

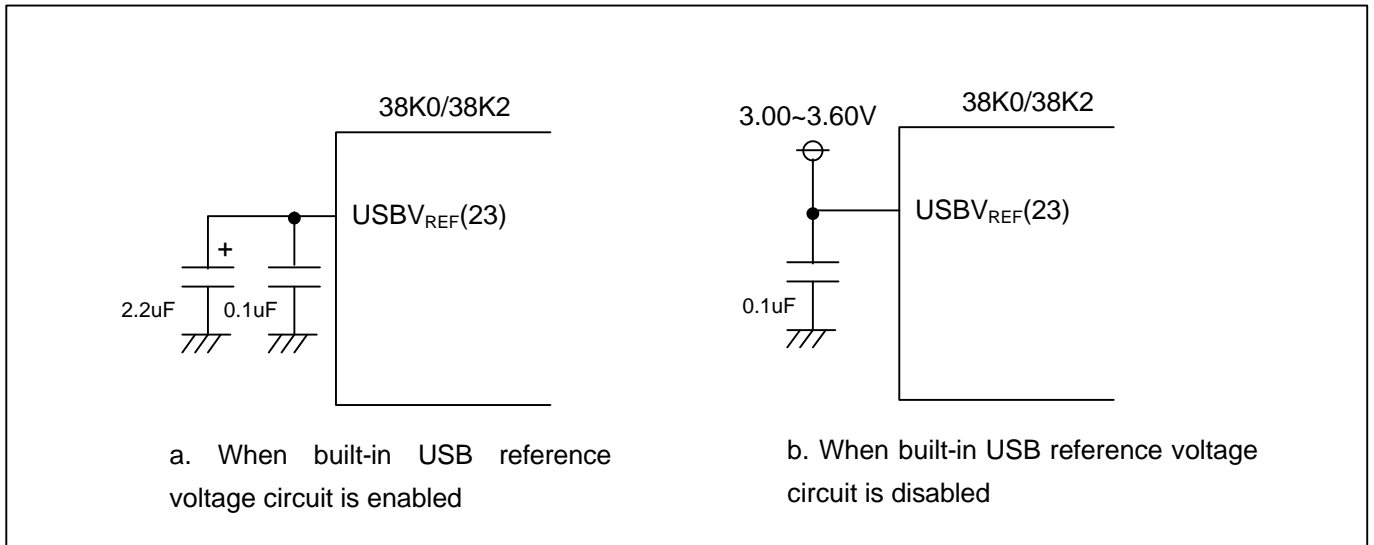


Figure 1.2.1(1) USBV_{REF} Pin Connection

(1) USB Reference Voltage Output Pin (TrON)

This is the pull-up voltage output pin for the up-port. The $USBV_{REF}$ voltage supplied either internally or externally is output from this pin. Connect the D0+ pin to the TrON pin through a 1.5k-ohm resistor.

The output of the TrON pin can be turned ON/OFF by bit TRONCON (TrON output control bit: bit 1 of USBCON). Normally, the TrON pin must be turned ON after detection of the $USBV_{BUS}$ voltage (supply voltage from USB up-port bus). However, the 38K0/38K2 MCU does not perform this control through hardware. Therefore, the user must add external hardware to detect the $USBV_{BUS}$ voltage and supply the TrON voltage, as shown in Figure 1.2.1 (2)-a. Or the user must utilize an interrupt pin for the $USBV_{BUS}$ voltage detection as shown in Figure 1.2.1 (2)-b and turn on the TrON pin by software.

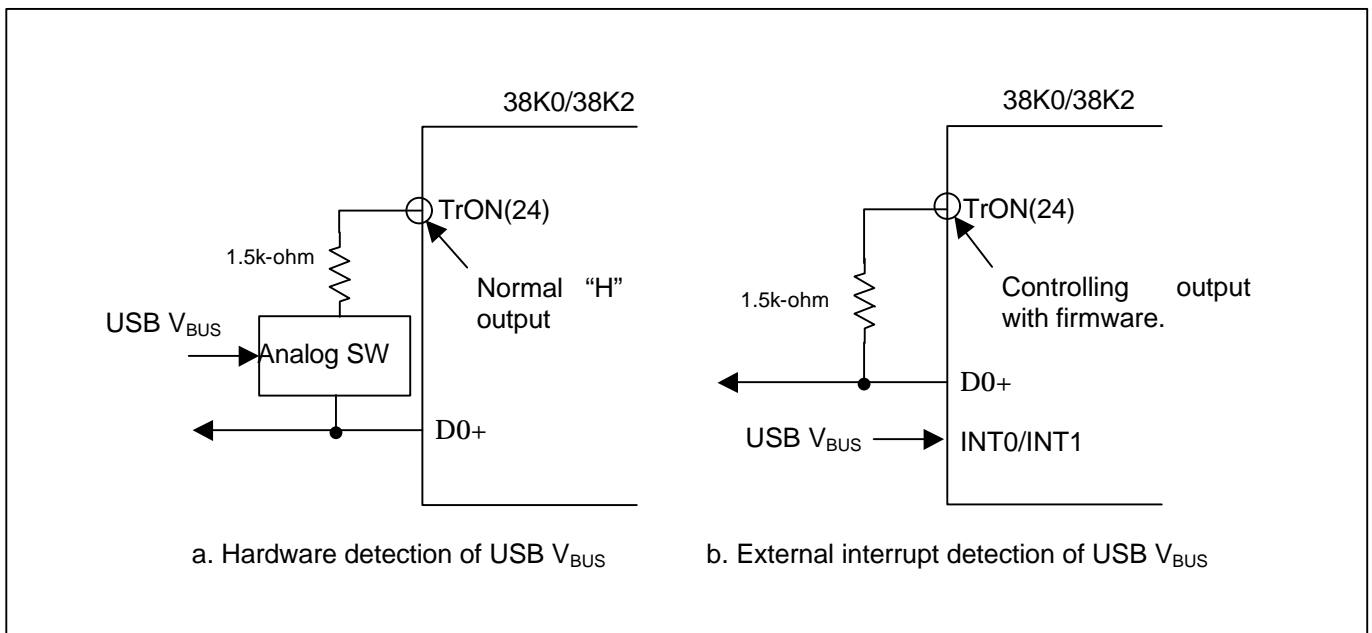


Figure 1.2.1(2) TrON Pin Connection

-- Note --

Figure 1.2.1(3) shows the relation between the $USBV_{BUS}$ power source and the TrON signal when the USB reference voltage circuit is enabled for operation.

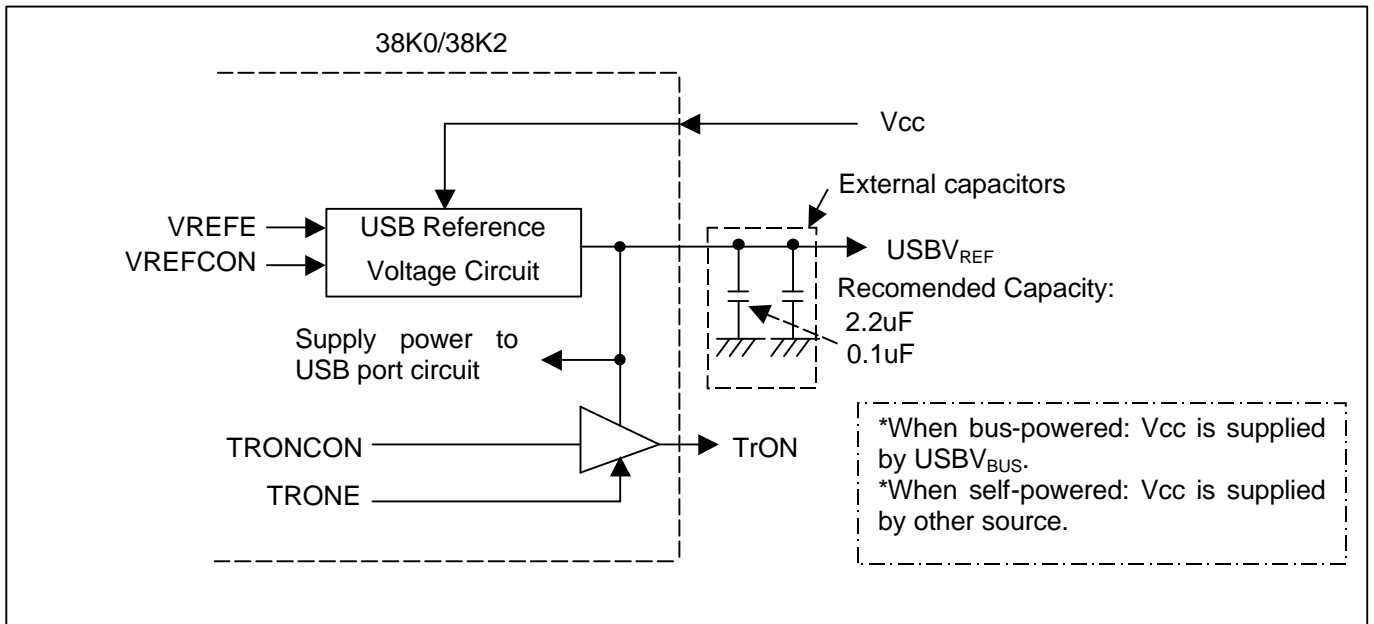


Figure 1.2.1(3) Relation between USBV_{BUS} and TrON Signals

(2) USB Up-Stream I/O Pins (D0+/D0-)

Pins D0+/D0- represent the USB up-stream signal pair D+ and D-. To enable proper impedance matching, serially insert 27-ohm (recommended value) resistors between the MCU pins and signal lines and 68pF (recommended value) capacitors between the pins and resistors, as shown in Figure 1.2.1. Because these values vary according to the board impedance, select optimal values by measuring the signal skew in actual evaluation. In addition, insert a 15-ohm pull-down resistor for each signal line and, if necessary, common-mode ferrite beads as an EMI countermeasure (reference: signal line is equal to or greater than 120 ohms/100mA, supply line is equal to or greater than 120 ohms/2A at 100MHz).

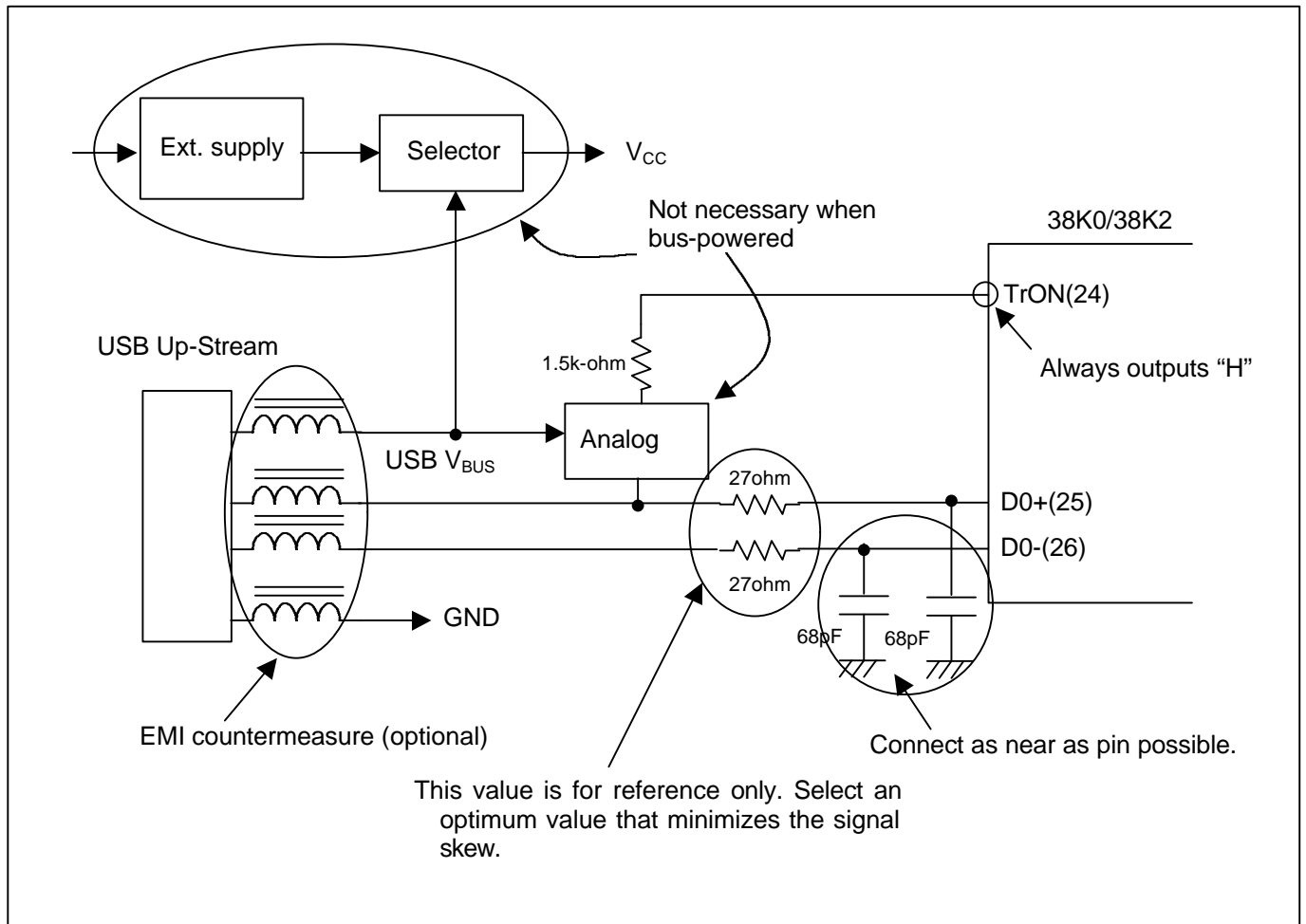


Figure 1.2.1 (4) D0+/D0- Pin Connection

For details concerning the V_{CC} pin, refer to Section 1.4.1 "V_{CC} and USBV_{ref} Voltages".

1.3 38K2 Down-Port Pin Reference Circuit

This section describes the HUB down-port circuit of the 38K2 Group. For details concerning the USB standard circuit, refer to Section 1.2 “38K0/38K2 Group USB Standard Circuit”. For more details concerning other peripheral functions, refer to the 38K0/38K2 Group data sheet.

1.3.1 HUB-related Pins

Table 1.3.1 shows HUB-related pin functions.

Table 1.3.1 HUB-related Pin Functions

Pin No.	Symbol	Name	Function
27	D1-	USB down-stream 1 I/O	Down-stream 1 signal pair D+ and D-
28	D1+		
29	D2-	USB down-stream 2 I/O	Down-stream 2 signal pair D+ and D-
30	D2+		

(1) USB Downstream 1/2 Input/Output (D1-/D1+/D2- D2+)

These are the D+ and D- signal lines for USB hub downstreaming. To enable proper impedance matching, serially insert 27-ohm (recommended value) resistors between the MCU pins and signal lines and 68pF (recommended value) capacitors between the pins and resistors, as shown in Figure 1.3.1. Because these values vary according to the board impedance, select optimal values by measuring the signal skew in actual evaluation. In addition, insert a 15-ohm pull-down resistor for each signal line and, if necessary, common-mode ferrite beads as an EMI countermeasure (reference: signal line is equal to or greater than 120 ohms/100mA, supply line is equal to or greater than 120 ohms/2A at 100MHz). (Note 1)

Note 1: For 382K Group - when setting the downports (P020-P23), use the input (default) settings for Port 2 direction register (bit 0 – bit 3).

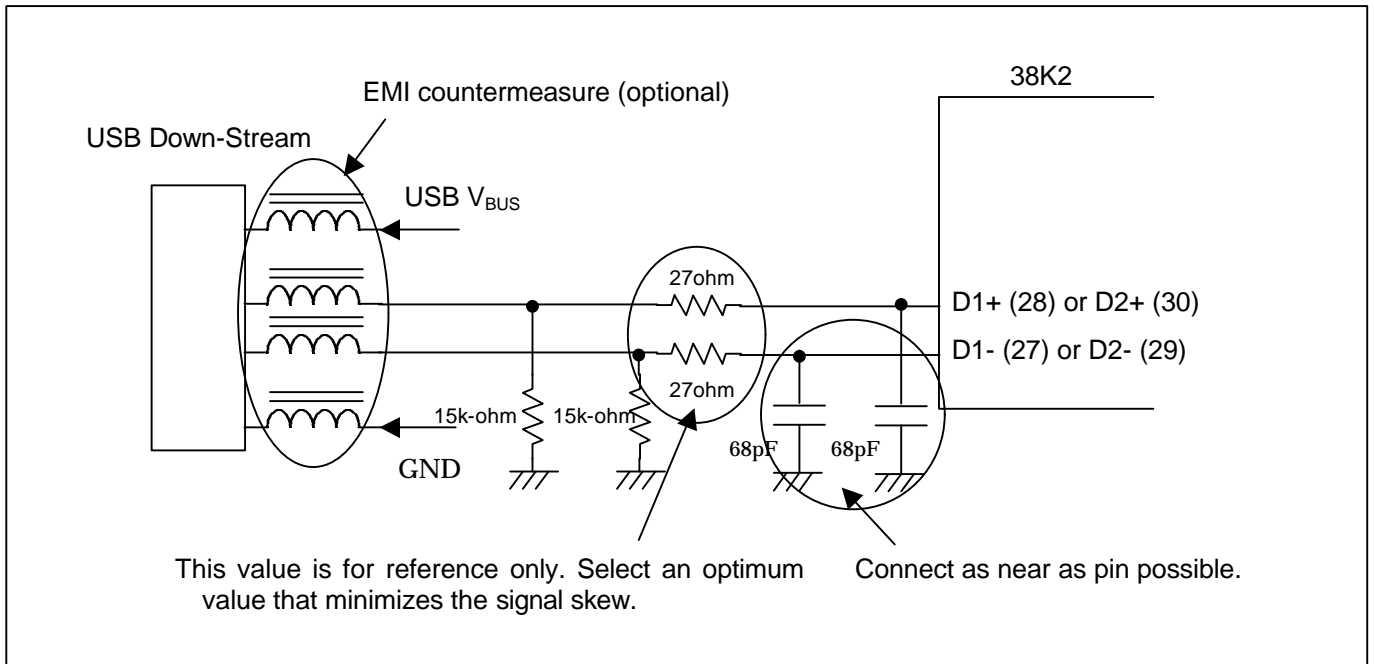


Figure1.3.1 D1+/D1- (D2+/D2-) Pin Connection

1.3.2 Over-Current Detection/Protection

USB Version 1.1 (or later) Specification requires an ON/OFF switch for each bus-powered HUB down-port. Figure 1.3.2 shows an example of this requirement (down-port power ON/OFF, over-current detection/protection) with a standard current control IC.

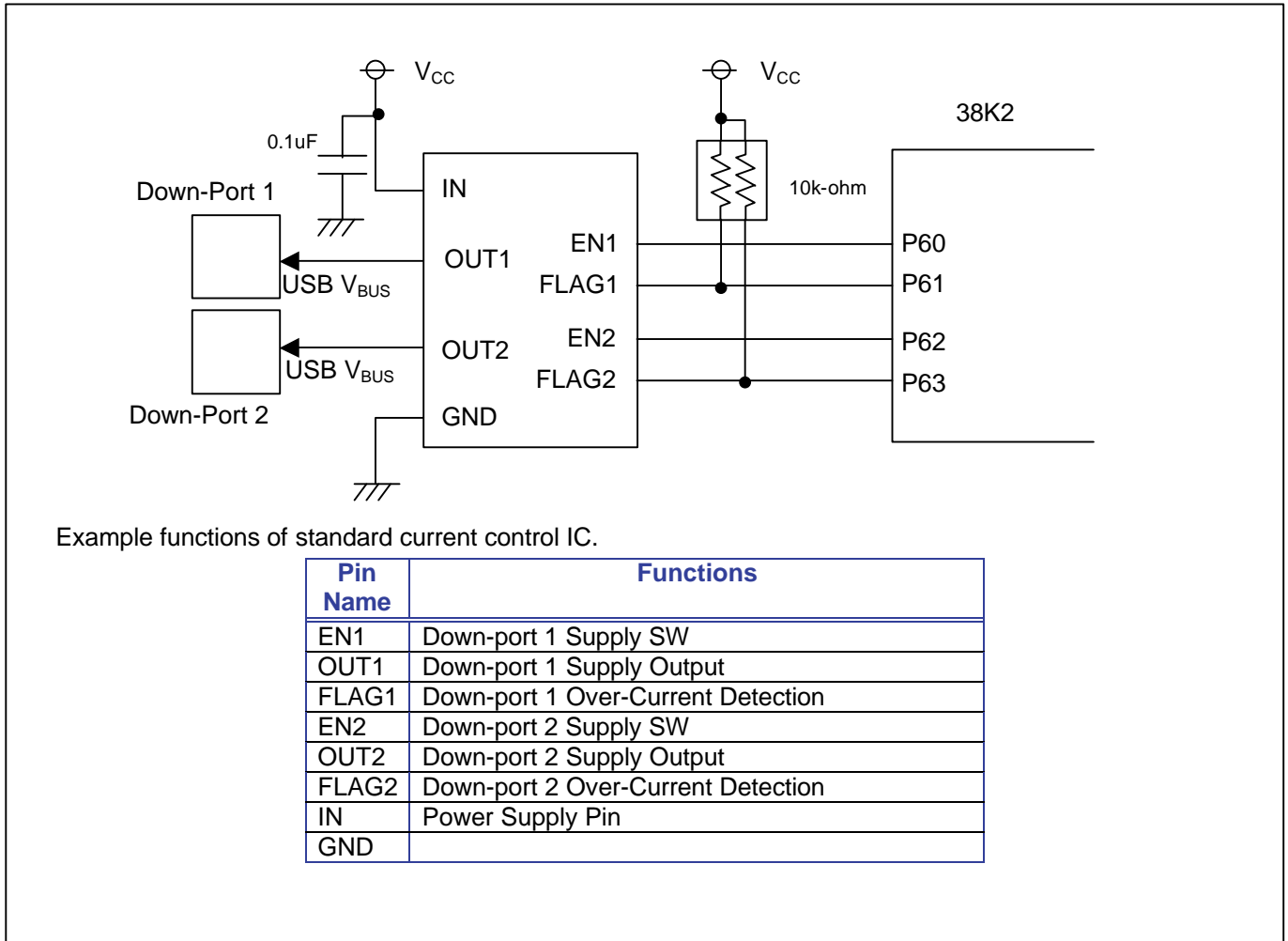


Figure 1.3.2 Standard Current Control IC Connection Example

1.4 Cautions

This section describes various cautionary items to be aware of when designing a board with 38K0/38K2 MCUs.

1.4.1 Vcc Pin and USBVref Pin Voltage

The guaranteed range of the MCU supply voltage (V_{CC}) will change depending on the MCU operation speed (defined by the system clock and main clock-phi), as shown in Table 1.4.1. When $V_{CC} = 3.00\sim 4.00V$, the USB reference voltage circuit must be turned off and USB power ($3.00\sim 3.60V$) must be supplied from the USBVref pin. Please note that the voltage level of the USBVref pin cannot exceed the level of the V_{CC} pin.

Figure 1.4.1 shows two examples of the connection between USBVref and V_{CC} pins (when $V_{CC} = 3.00\sim 4.00V$).

Table 1.4.1 Relation between Clock, Supply Voltage V_{CC} , and USB Ref. Power Supply USBVREF

System Clock	Main Clock-phi	Supply Voltage V_{CC} (Dev. Status)	USB Ref. Power Supply USBV _{REF}
12MHz	12MHz	4.50~5.25V (Planning)	Internal USB Reference Voltage Circuit enabled
	6MHz (divide-by-2)	4.00~5.25 (Under development)	
8MHz	8MHz	4.00~5.25	
6MHz	6MHz	4.00~5.25	
		3.00~4.00 (Under development)	3.00~3.60V supplied from USBV _{REF} pin.

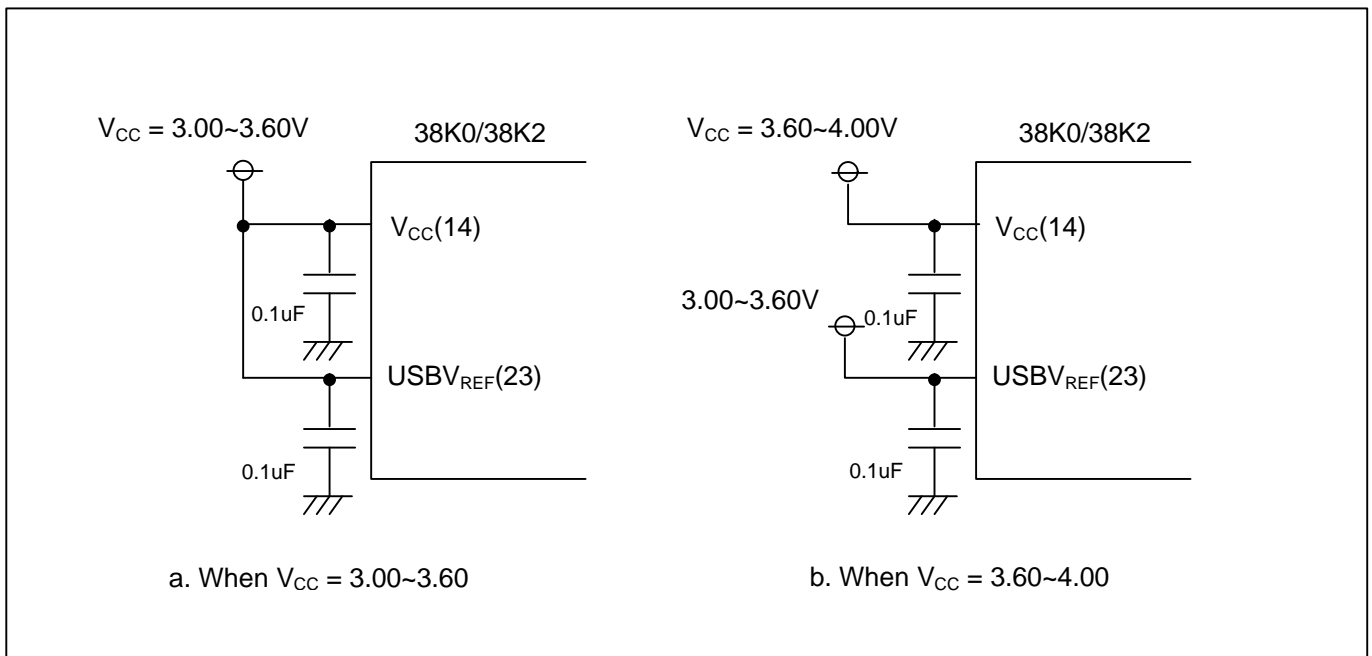


Figure 1.4.1 Vcc (3.00~4.00V) Connection

1.4.2 Vref and VccE Voltage Pins

The Vref pin is an input pin that provides the reference voltage to the AD converter circuit. The VccE pin is an input pin that supplies power to the AD converter circuit and Ports 1, 3, and 4. (These ports supply the bus voltage when using the EXB function. Because the VccE pin is used for supplying power to the AD converter circuit, the Vref pin must be left open or the voltage of the pin must be equal to or lower than the voltage of the VccE pin, as shown in Figure 1.4.2. The VccE pin, which is a power supply pin, should be connected to Vcc when the corresponding circuits above are not in use.

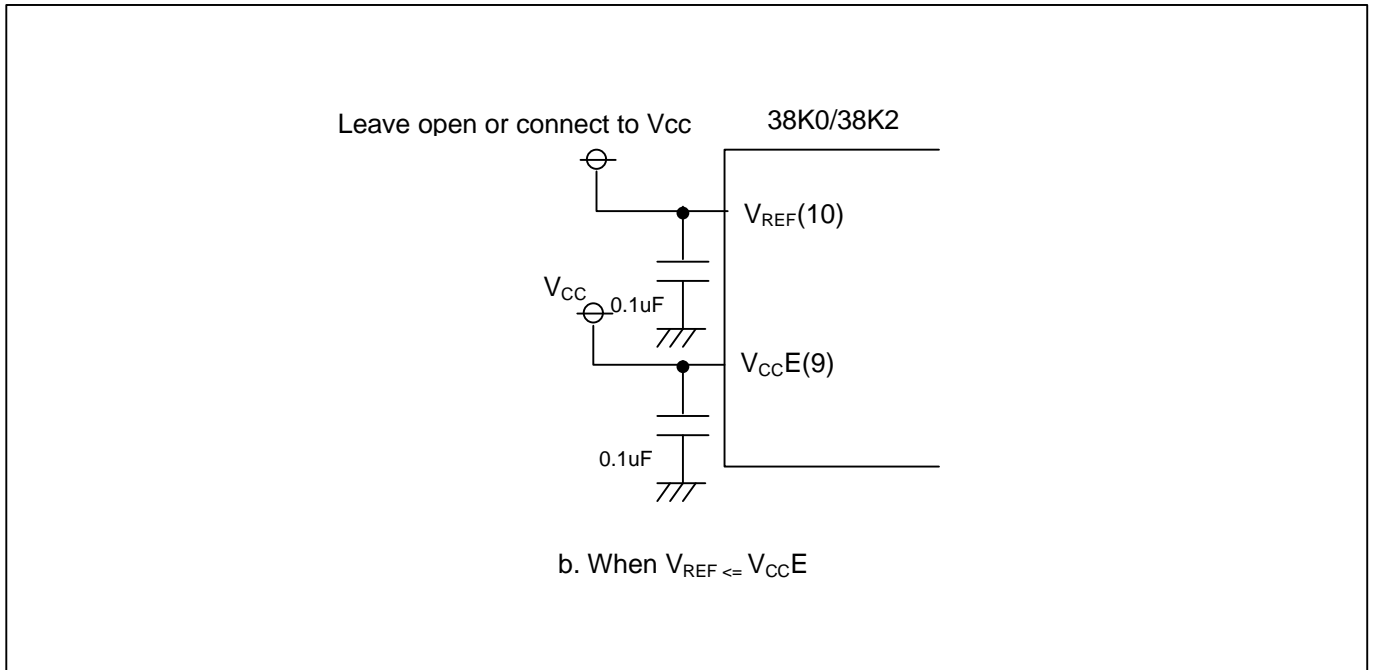


Figure 1.4.2 Connection Example of Vref and VccE Pins

1.4.3 On-Board Flash Programming

38K0/38K2 Group Flash memory version allows you to reprogram application F/W on-board by pre-programming the rewriting control program to the Flash memory boot ROM area (or user ROM area) in advance. Note 1

This rewriting control program, as shown in Table 1.4.3, can be programmed with either a serial writer (MFW-1) or the FOUSB method Note 2 (3V/5V, 6MHz/12MHz), by setting the port status at MCU reset. Note 3

Table 1.4.3 Selection of rewriting control program through port settings

P26	P27	P42	P16	Mode
*	*	H	H	Serial Mode (note 4)
*	H	L	H	FOUSB 3V/6MHz (Notes 5 & 6)
H	L	L	H	FOUSB 5V/12MHz
L	L	L	H	FOUSB 5V/6MHz

*: Don't care

Note 1. The boot program in the Flash memory boot ROM area can be reprogrammed with either a program-writer or in the parallel mode.

Note 2. "FLASH OVER USBTM" (abbreviation: "FOUSB") is a registered trademark of Renesas Technology Corporation.

Note 3. Renesas Technology software programs are in HEX code. The FOUSB function can be used during the trial period for evaluation purposes only. Please contact us directly concerning purchase of source code and modify functions.

Note 4. The serial mode is not affected by power supply voltage or external oscillation frequency.

Note 5. When using FOUSB at 3V, peripheral circuits must be converted to 3V operations as well. For more details, please refer to Page 7. Note that even at 3V operations, programming voltage CNV_{SS} must be at 4.50 – 5.25V.

Note 6. FOUSB will not run on settings other than those listed above.

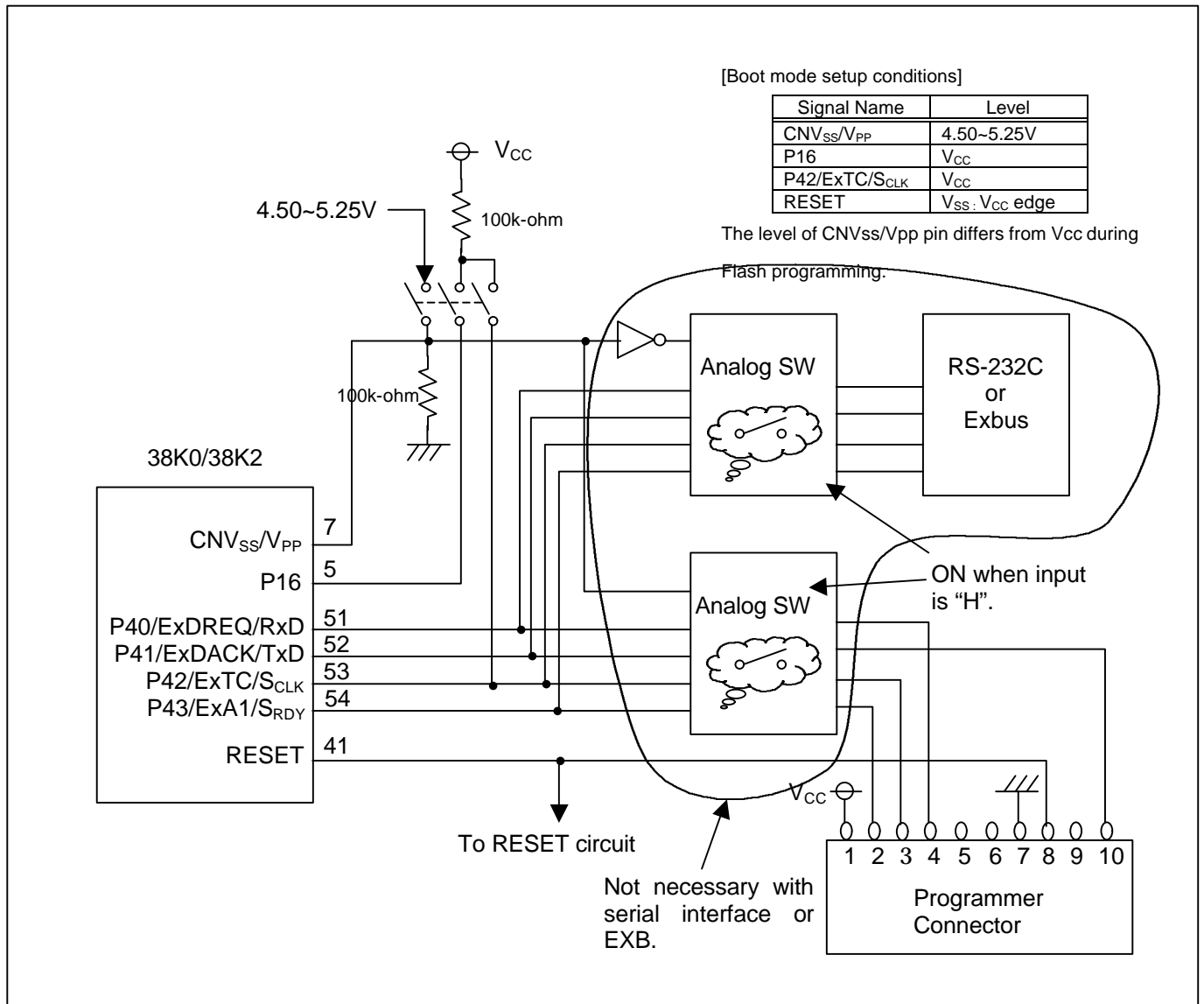


Figure 1.4.3 (1) Example Circuit showing Boot ROM Area Standard Serial Interface and FOUSB Interface.

Figure 1.4.3 (2) shows a configuration specific for the FOUSB interface operation. The specified switch must be set in the same manner as shown in Fig. 1.4.3 (1) and then a reset must be applied to invoke the firmware.

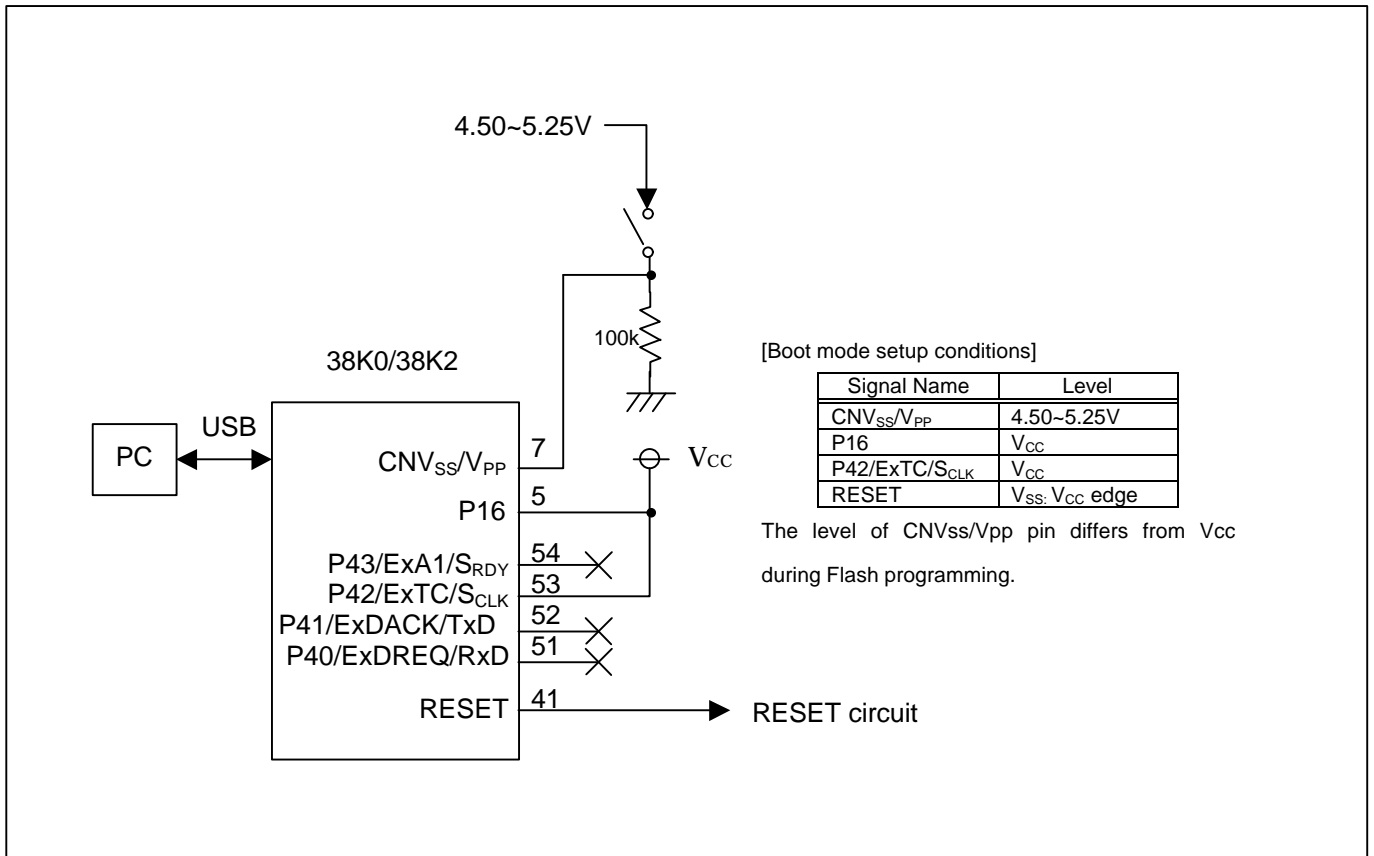


Figure 1.4.3 (2) Circuit Example specific for FOUSB interface.



RENESAS Single-Chip Microcomputer
38K0/38K2 Group
USB Application Circuit Reference VER.1.4
RENESAS TECHNOLOGY CORPORATION.
RENESAS SOLUTIONS CORPORATION.

No unauthorized copy, please.
Any contents (including charts) are not allowed for reprinting without contact to RTC.
Copyright(C) 2003 RENESAS TECHNOLOGY CORPORATION and
RENESAS SOLUTIONS CORPORATION.