

Third Generation E²POT Devices From Intersil-Part 1

The X9315 and X9316

The introduction of the X9315 and the X9316 from Intersil marks the beginning of the third generation of E²Pots. Characterized by low power, low noise and small size, this generation of devices finds application in a number of new products. These range from portable, battery powered systems to audio control to sensor circuits sensitive to noise levels. This Application note presents some application ideas, the benefits of using E²POTs and illustrates E²Pot industry trends.

Intersil introduced the first E²Pots in 1987 as NMOS devices. These revolutionary products found many applications where standard mechanical potentiometers were hard to adjust, made the system hard to design and were sensitive to unexpected resistance changes. But, these early E²Pots were limited in their application by high power consumption. In 1992, the introduction of second generation CMOS E²Pots brought a new standard to the industry. These devices offered lower power to systems designers. By 1995 3-V operation allowed designers to consider E²Pots for portable applications.

The X9315 and X9316 third generation E²Pots continues the trend to low power and add low noise and small packages to make true portable solutions possible. In addition to power and noise considerations, there are a number of reasons designers now choose digital potentiometers over mechanical types. The major areas are form factor, automated calibration, and reliability.

Often one of the first advantages of a digital pot (over a mechanical counterpart) is the ability to place the device in

the most convenient location in the system. This lets the designer make the best use of the physical space to achieve small size or lower the cost of manufacturing. At the same time, the package designer places the pot controls at the most convenient location for the user. The result is a system that better meets the needs of both the designer and the user. New innovations in semiconductor packaging further increases the value of digital pots in system design, since single E²Pots now fit in packages as small as 15 mm². In the future, quad potentiometers will fit in packages as small as the 24-lead TSSOP (only 50 mm²). As more functions reside together with the digital pots on the same silicon, new small packages provide additional pins, without a significant loss of board space.

Automating system design is a key factor in the use of digital potentiometers. Today we have a global manufacturing model. It is no longer possible to design and build systems in the same plant. Often, a system designed in one country is manufactured in several others. This creates problems in communicating calibration procedures for optimum performance. Digital Pots become key in these situations. The designer can now build testability and automated calibration into the design while specifying the calibration procedure. This built-in procedure is repeatable at all manufacturing locations and is easily upgraded at any time in all sites by a simple software change. Now, with the addition of the new low power X9315, building in this automation need not add loading to the power supply or compromise circuit design performance.

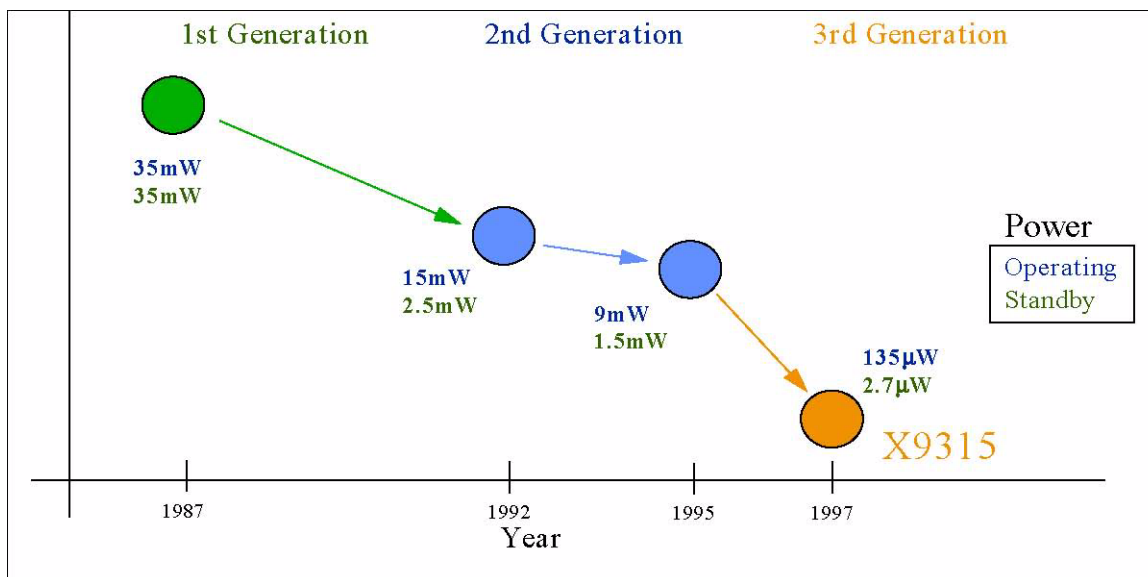


FIGURE 1. DIGITAL POT POWER TRENDS

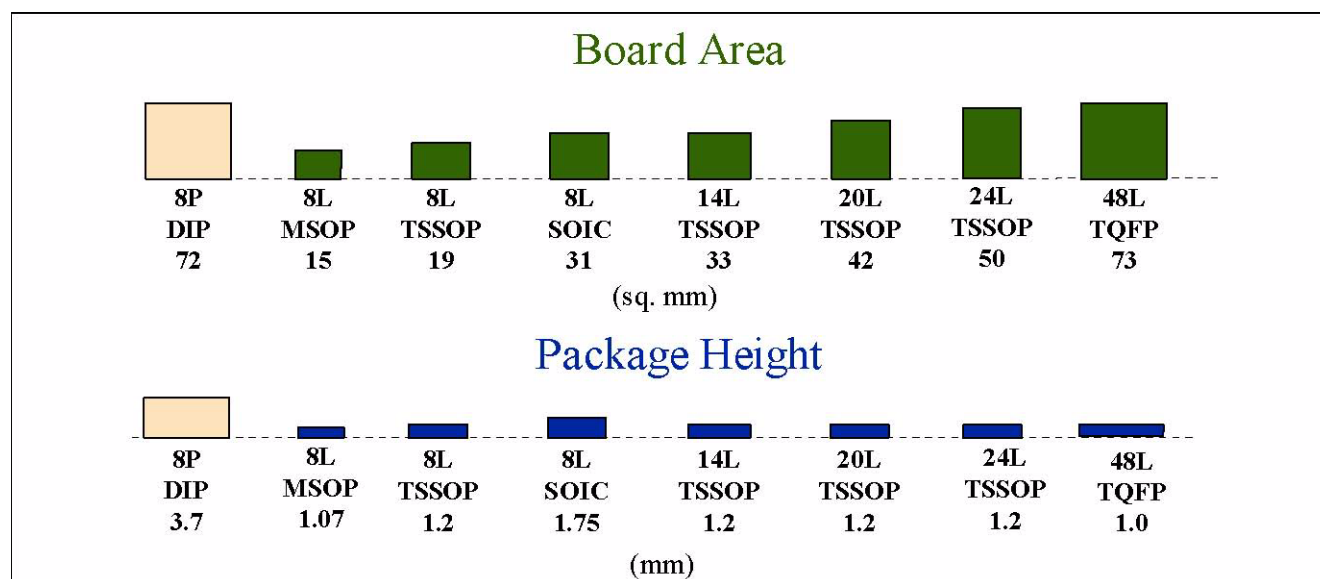


FIGURE 2. SMALL SIZE PACKAGES FIT ANYWHERE

Automatic calibration adds two additional features to a system design - for free! The first of these is remote calibration. What this means is that equipment in the field can now be recalibrated without sending a technician. A phone call is sufficient to make a change to a digital pot. This can save a tremendous amount of money on service calls and it can maintain equipment at the highest level for a very low cost.

The ability to adjust a potentiometer in-circuit adds another capability. In a system, components are always being stressed, by use or by the environment. With digital pots, the circuit itself can automatically and continuously recalibrate itself. The circuit then becomes adaptive, reacting to the environment and maintaining optimal performance.

The digital potentiometer increases system reliability. This improvement results from reducing the impact of environmental effects and by removing the temptation by individuals to recalibrate or optimize the system. Because there are no moving parts and because the wiper controls are separated from the active element, digital potentiometers can be sealed in a rugged weather-proof container. This virtually eliminates unwanted changes to the potentiometer setting.

Reliability of a system increases also because of the combination of non-volatility and digital control. A product calibrated in the factory and programmed one time only by special pot adjustment hardware maintains its calibration and cannot be tampered with in the field, since there may be no control circuitry shipped with the device. This can dramatically reduce the number of returned units that the user thought to make better by "tuning" the circuit.

Third generation E²Pots from Intersil implement a number of improvements to the circuit design to enhance operation. The first of these is the use of CMOS switches to lower overall operating current (when the wiper is moving) and standby current (when the device is powered, but not the wiper is not moving.) The X9315 operates with V_{CC} as low as 2.7V @ 50 μ A and takes only 1 μ A of current in standby. Future third generation E²Pots from Intersil will be even more miserly.

The second improvement in the new E²Pots from Intersil is the reduction of noise. One source of noise in earlier devices resulted from on-chip "charge-pumps". The charge pump provided higher voltages for biasing the wiper FETs. In the new devices, this bias voltage is supplied elsewhere. In the X9315, the biasing comes from the same digital supply that powers the device. This required FETs that do not need a high voltage bias. Another new device, the X9316 provides isolation between the digital and analog supplies. In these devices, the separate V+ and V- resistor bias voltage provides both low noise operation and power supply isolation. These changes result in 25dB less noise for the X9315 over the X9313. Future products will continue the use of these circuits for noise reduction.

The E²Pot finds application in a wide variety of systems. To show the range of these applications, some examples appear in Figures 3 and 4.

LCD Contrast Control

LCD panels often require a backlight to improve display readability. The output level of the backlight must be adjusted to suit the ambient light levels. So this setting is often adjusted by the user to suit individual preferences. A potentiometer is a good choice for making these adjustments. A digital potentiometer is a better choice. With a digital potentiometer, software in the system can now control the contrast. This means that the system can use a "virtual knob" for adjustment that only exists as an image on the screen or as part of an existing keyboard. Since the LCD control typically requires a high voltage, the E²Pot is typically coupled with an Op Amp that can supply the needed voltage. This combination works for controlling other high voltage applications as well.

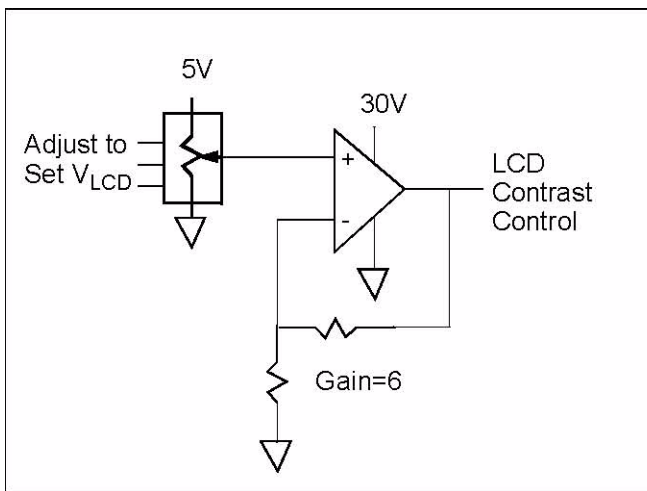


FIGURE 3. LCD CONTRAST CONTROL

Power Supply Adjustment

In this application, the E²Pot controls the setting on a power supply. This adjustment is made as a final step in the manufacturing to calibrate the power supply output. This is a set and forget application, with the wiper position maintained in a nonvolatile register. This register maintains the wiper position even in the absence of power. Using the pot in this application prevents tampering with the output voltage. Because there is no unauthorized field adjustment, there are fewer "out of spec" returned units.

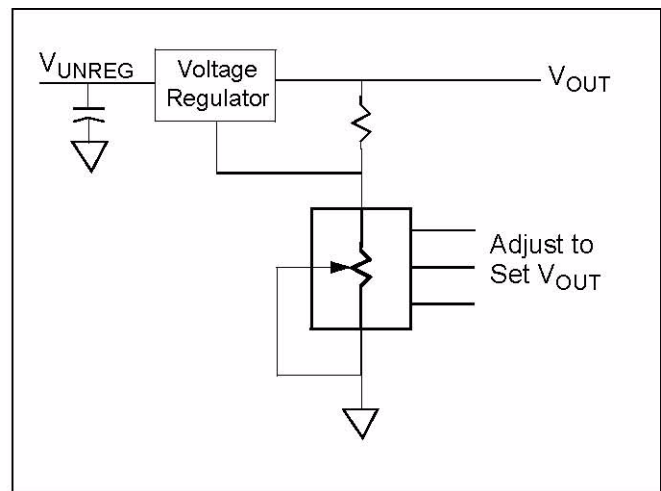


FIGURE 4. POWER SUPPLY ADJUSTMENT

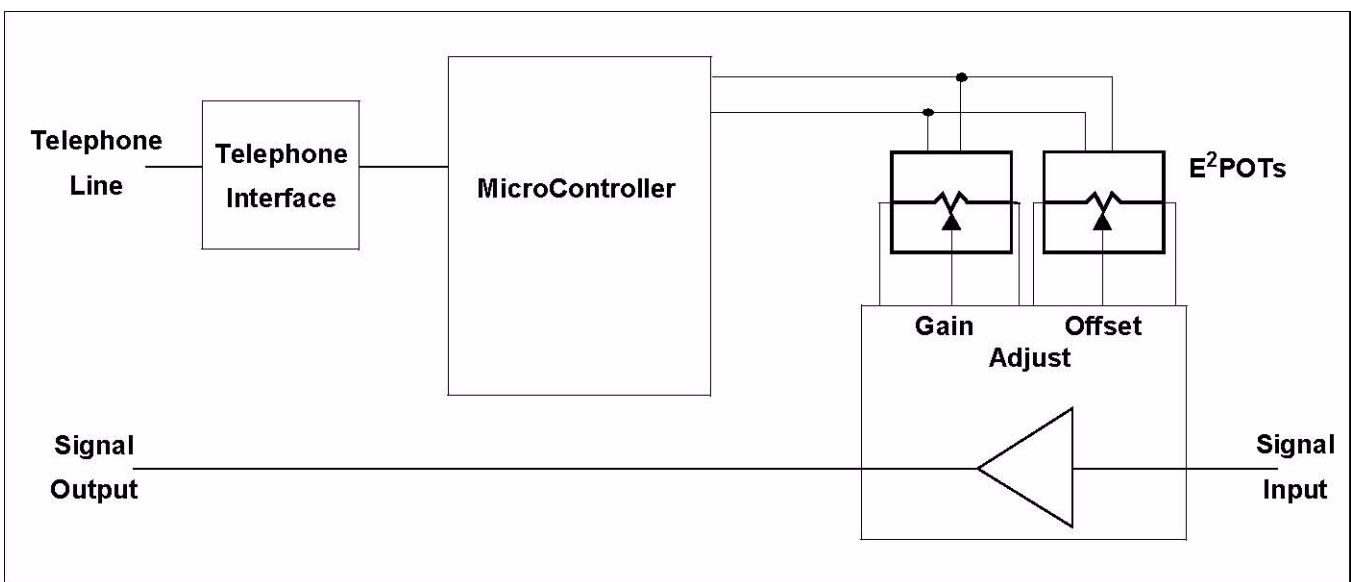


FIGURE 5. REMOTE CALIBRATION

Remote calibration

In this application, the E²Pot resides in a piece of equipment located at a remote site. Because of the lack of access, it is very difficult to send a service person to make adjustments to this device. However, it is important to periodically calibrate the equipment to maintain offset and gain parameters to guarantee optimum signal levels. In this application, a telephone line communicates to the remote system. By sending signals to the remote system via the phone line and monitoring the output voltage levels on a separate cable, the signal conditioning circuits are maintained from hundreds of miles away.

The applications presented here are simplifications of actual system solutions. They are meant to convey the range of possible applications of digital potentiometers and the importance of Intersil's third generation advances. This technology will find it's way into new and innovative mixed signal devices from Intersil in the future as digital control of analog signals continues to gain in importance.

Part 2 of this Application note will accompany a new family of Third Generation devices from Intersil. In this Application Note the focus will be digital control of analog circuits and the benefits and application of increased integration.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338