

Processor Power Controller with Intel VR9, VR10, and AMD Hammer VID Support (ISL6563EVAL1)

Introduction

The progress of the advanced computing cores coming from microprocessor manufacturers such as Intel and AMD have necessitated a change in the topology of the switching regulators traditionally used to power them. Multiphase buck regulators have proven to be the topology of choice for such high-current applications. The ISL6563 is a cost-effective alternative to a core power solution for a typical VRM9 or VRM10 Pentium, or Hammer-class processor system. Utilizing a proven $r_{DS(ON)}$ sensing 2-phase buck approach, the ISL6563 consists of a multiphase core controller with a selectable VID input and two half-bridge, high current drivers, along with all the necessary protection and coordination features required by a typical VR9, VR10, or AMD Hammer design.

The ISL6563EVAL1 evaluation board embodies a 55-60A regulator solution targeted at supplying power to the core of either of the three types of processors mentioned above. The physical board ships out configured for VR10 VID coding, but can be easily modified to support any of the other two VID tables.

Quick Start Evaluation

To facilitate the evaluation of the ISL6563 in a typical setting, the ISL6563EVAL1 is designed to be powered primarily from an ATX supply. However, the board does have terminals that allow it to be powered from standard laboratory power supplies. Figure 1 details the available input and output connections.

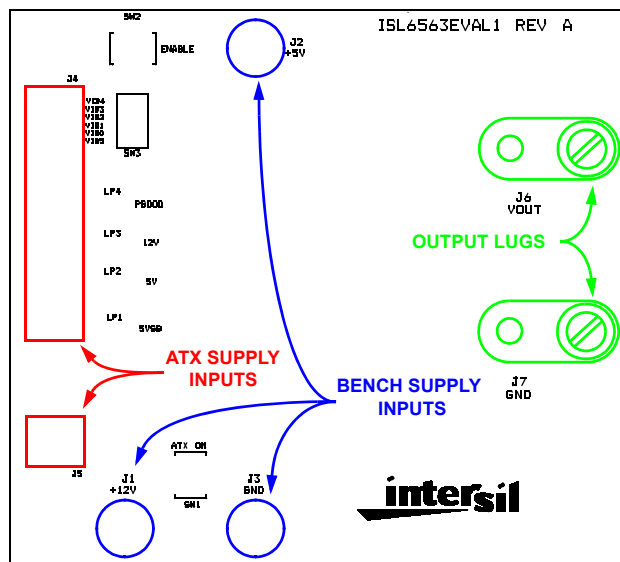


FIGURE 1. ISL6563EVAL1 INPUT AND OUTPUT CONNECTIONS

Circuit Setup

Before connecting an input supply to the board, consult and familiarize yourself with the circuit schematic and the connection options offered by the ISL6563EVAL1.

• Set Switches

Ensure the 'ATX ON' (SW1) and 'ENABLE' (SW2) switches are in the off position (away from 'ATX ON' and 'ENABLE' markings, respectively).

SW3 selects the output voltage setting and DAC compatibility (Intel VRM9.0, or AMD Hammer; when not in VRM10 setting). Please consult the ISL6563 datasheet and the circuit schematic for a thorough understanding of the available options for setting the output voltage. Figure 2 details the typical default configuration for SW3 when the board is received. In this default setting, the evaluation board is set for VRM10 support; all sections of SW3 representing inputs into the 6-bit VID DAC.

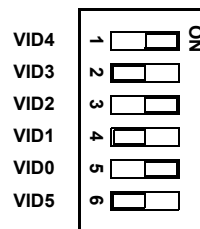


FIGURE 2. TYPICAL SW3 DEFAULT SETTING (1.600V; VRM10)

• Set DAC Compatibility (optional)

Should the default VRM10.0 DAC compatibility not be the desired version, VRM9.0 or AMD Hammer DAC compatibility can be programmed by removing R22 (see evaluation board schematic). Once the VRM10 pin is open, the VID5 section of the SW3 switch selects the new DAC compatibility: set to the ON position for AMD Hammer or leave in the OFF position for VRM9.0 compatibility. Consult the ISL6563 datasheet for more information.

• Hookup Guide Using a Standard ATX12V Supply

Connect the 20-pin main and the 4-pin 12V ATX connectors to the J4 and J5 mating on-board connectors. Connect an output load to the evaluation board's output (VOUT and GND; J6 and J7); an electronic load is generally recommended for its ease of use.

• Hookup Guide Using Standard Bench Supplies

Connect a 5V, 1A supply to the +5V input (J2) and a 12V, 12A, supply to the +12V input (J1); connect both ground leads to the GND (J3) input. Connect an output load to the evaluation board's output (VOUT and GND; J6 and J7); an electronic load is generally recommended for its ease of use.

Operation

• Provide Power to the Board

If using an ATX supply, plug it into the mains, and, if the supply has an AC switch, turn it on. The '5VSB' LED should light up, indicating the presence of 5V standby. Flip on the 'ATX ON' switch; immediately thereafter, the '5V' and '12V' LEDs should light up indicating the presence of main ATX 5V and 12V on the evaluation board.

Should bench supplies be used, simply turn them on; any turn-on sequence is fine. The '5V' and '12V' LEDs should light up, but in this case, the '5VSB' LED should stay off (there is no 5V standby voltage provided by bench supplies).

To enable the circuit for operation, flip on the 'ENABLE' switch (SW2); the circuit should immediately bring up the output voltage corresponding to the DAC setting.

• Examine Start-Up Waveforms/Output Quality Under Varying Loads

Start-up is immediate following application of bias voltage. Using an oscilloscope or other laboratory equipment, you may study the ramp-up and/or regulation of the output voltage. Loading of the output can be most easily done via an electronic load; however, most any other method will work as well.

• Examine VID-Directed Output Voltage Transitions (VRM9.0 or AMD Hammer DAC Settings Only)

Although the evaluation board ships populated for VRM10 DAC compatibility, depopulating R22 changes the DAC compatibility to either VRM9.0 or AMD Hammer (check circuit schematic and ISL6563 datasheet).

In either of these DAC compatibility modes, the VID setting can be changed while the board is enabled and operational, resulting in an immediate and controlled change in the output voltage setting as per the new VID code selected. Exercise this function and observe the resulting changes under desired loading conditions.

Fault Handling

The ISL6563 protects the output against over-current (OC) and over-voltage (OV) events.

In case of an over-current event, the circuit turns off and attempts an output soft-start (SS) after waiting for a time period equaling two SS cycles. In the unlikely case of an over-voltage event, the controller turns on the lower MOSFETs as needed in order to lower the output voltage below the falling OV threshold. However, the OV behavior is masked by the normal feedback loop behavior; as soon as the output starts to exceed the internal reference the lower MOSFETs' duty cycle is increased as necessary to maintain the output regulation.

The behavior of the circuit, in either situation (OC or OV), repeats until the fault condition is removed or the circuit is disabled. Review the appropriate datasheet sections for more details.

Reference Design

General

The evaluation board is built on 2-ounce, 4-layer, printed circuit board (see last three pages of this application note for layout plots). The board is designed to support a continuous output current level of up to 55-60A, while operating at room temperature, under natural convection cooling; consult the 'Modifications' section for information on modifying the evaluation board to meet your special needs.

Performance

Figures 3 through 11 depict the evaluation board's performance during typical operational situations.

Soft-Start Start-Up

Figure 3 details a typical ISL6563EVAL1 start-up. For this scope capture, the ATX supply powering the board is turned on via SW1 prior to time T0. At time T0, SW2 is enabling the circuit for operation and EN pin starts to rise. As the EN pin is surpassing its threshold at time T1, a soft-start sequence is initiated and the output voltage is increased, under a constant rate of rise, to its set value. Once the output voltage rises up to

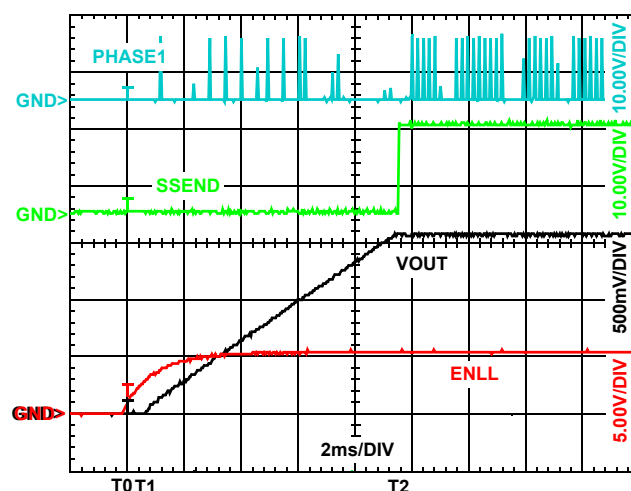


FIGURE 3. ISL6563EVAL1 NORMAL START-UP
($V_{DAC} = 1.600V$)

its set point, SSEND (Soft-Start END) pin is released (T2), signaling the conclusion of the start-up sequence.

Special consideration is given to start-up into a pre-charged output (where the output is not 0V at the time the SS cycle is initiated). Under such circumstances, the ISL6563 keeps off both sets of output MOSFETs until the internal ramp starts to exceed the output voltage sensed at the FB pin. This special scenario is detailed in Figure 4. The circuit is enabled, similar to Figure 3, at time T0. As the internal ramp exceeds the magnitude of the output voltage at time T1, the MOSFETs drivers are enabled and the output voltage ramps up in a

The pre-POR OV protection cleverly attempts to limit the rise of the output voltage in such a scenario to the lowest level possible in the given application circuit: the $V_{GS(TH)}$ of the lower MOSFETs. This feat is achieved via a special circuitry acting upon the lower MOSFETs' gates while the ISL6563's VCC level is below POR threshold, by effectively shorting the gates to the drains of the respective MOSFETs via finite impedances (LGATE to PHASE; typically 5k Ω).

Figure 7 details the typical circuit behavior when this feature is activated. A very small impedance was placed across Q1 in order to simulate a manufacturing short-circuit, then the ATX supply was enabled, at time T0. At time T1, the 5V and 12V outputs of the ATX supply begin to ramp up, and, with the 12V, so does the output of the circuit. Since the output inductors do not carry any significant current, the PHASE node follows the output voltage closely and so does LGATE1 (LGATE2, not shown, exhibits identical behavior). The moment LGATE pins reach the $V_{GS(TH)}$ of the lower MOSFETs, at time T2, the rise of the output voltage is quickly curbed.

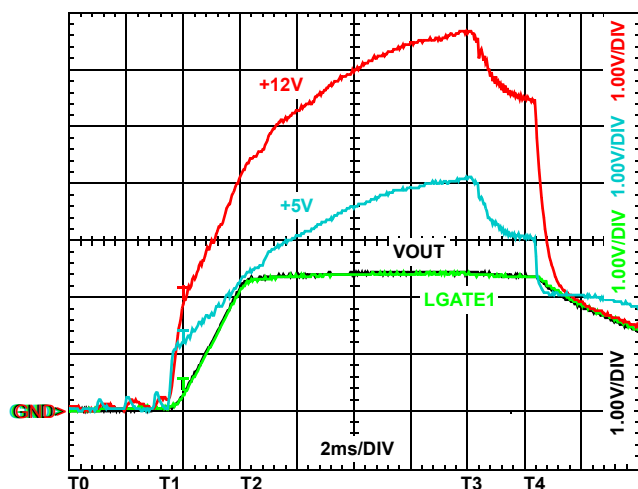


FIGURE 7. ISL6563EVAL1 PRE-POR OUTPUT OVER-VOLTAGE PROTECTION (START-UP WITH SHORTED Q5)

Even though the output voltage no longer increases, the current sunk from the ATX input supply is increasing from T2 to T3, causing the supply to reach its OC threshold and trip. At time T4, the current sunk from the input supply diminishes and the 12V input collapses to the V_{OUT} level (a small constant-current output load discharges the output from that point on).

Normal Over-Voltage Protection

While biased and operational, the ISL6563 benefits from a secondary over-voltage protection. Normally, the feedback loop takes control and prevents the OV condition before the real OVP mechanism can begin operation; both activating the lower MOSFETs, it is hard to distinguish between the two.

Figure 8 details the operation of the OVP mechanism while the ISL6563 is fully biased and the circuit is operational. At time T0

Q1 is shorted, and as a result, the increase in the output voltage makes the controller decrease the duty cycle. Turning on the lower MOSFET, while the upper is shorted, results in a very large current being drawn from the input supply, further leading to the effective collapse of the +12V input. Following, at time T1, the ATX supply's OC protection kicks in; the lack of current being delivered from the input is causing the output to ramp down below the regulation setpoint, from T1 to T2. At time T2, the +5V input drops below the falling POR threshold of the ISL6563, and the controller stops operating. Due to the short still present across Q1, the output voltage drifts slightly higher to the potential still held in the input supply's output capacitors.

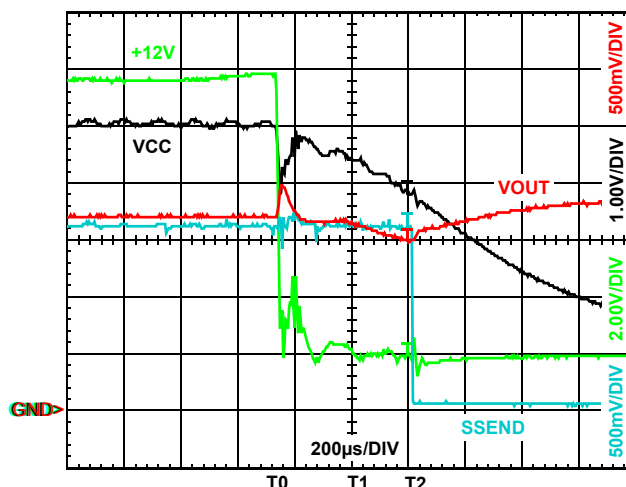


FIGURE 8. ISL6563EVAL1 OUTPUT OVER-VOLTAGE PROTECTION

Should strict OVP thresholds need be monitored at all times, it is recommended the ISL6563 bias is provided from a source which is always present (independent of the power conversion input); in a computer system, the source that could be used is the +5VSB. On the evaluation board, this can be achieved by depopulating R7 and using the same resistor to populate R9.

Output Transient Response

The ISL6563EVAL1 circuit is designed to exhibit output voltage droop, at a slope of roughly 1m Ω . Figure 9 details the circuit's response to a load step transient. During the T0-T1 transient duration, the output voltage droops, corresponding to the load slope programmed. Although the droop cannot be eliminated completely, it can be easily reduced to relatively small magnitudes. However, in most instances, the presence of some

amount of output droop helps minimize the total peak-to-peak output excursion when responding to fast transient loading.

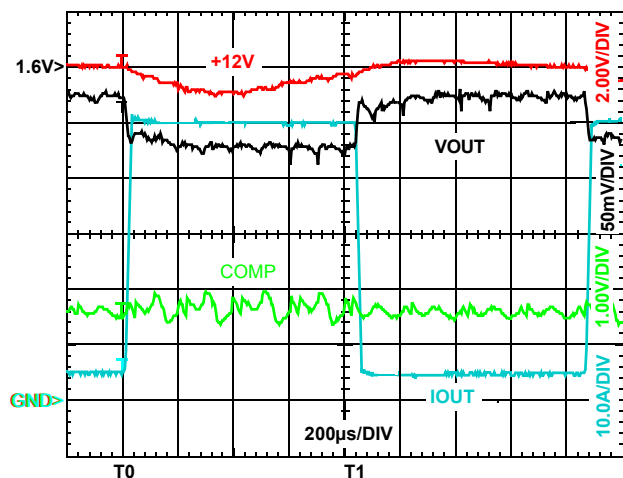


FIGURE 9. ISL6563EVAL1 LOAD TRANSIENT RESPONSE

Channel-to-Channel Current Sharing

Channel-to-channel current sharing is an important feature of a multi-phase controller, helping ensure uniform thermal performance across the individual power trains. Figure 10 details the current sharing during transient response, offering a glimpse into the tight channel-to-channel current balancing during both steady-state, as well as during dynamic response operation.

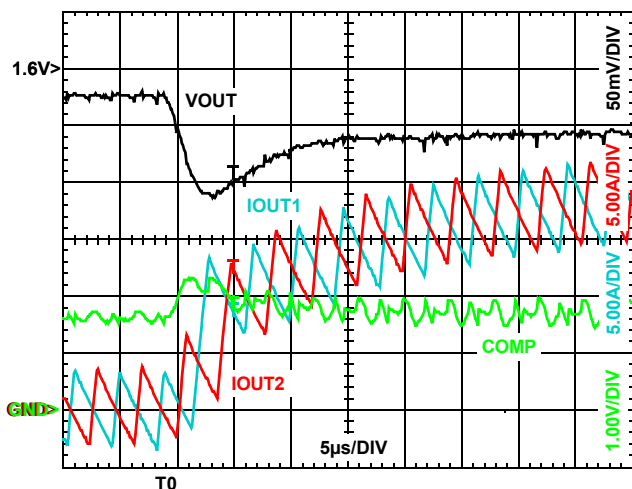


FIGURE 10. ISL6563EVAL1 PHASE-TO-PHASE CURRENT SHARING

Channel-to-channel current sharing/balancing is influenced primarily by the lower MOSFETs' $r_{DS(ON)}$ matching and the layout parasitics. As the ISL6563 does not provide any means of adjusting the channel-to-channel current sharing, close attention should be paid to these design parameters.

Switching Efficiency

Figure 11 highlights the evaluation board's conversion efficiency, including all bias power. The measurements were performed with all board components at (or very close to) room temperature.

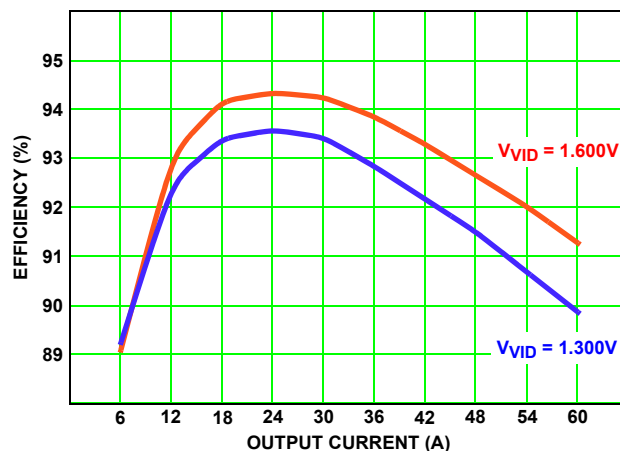


FIGURE 11. ISL6563EVAL1 MEASURED EFFICIENCY

Modifications

Adjusting the Output Voltage

The output voltage can be adjusted via the DAC-set internal reference. Please consult the datasheet for the available voltage ranges and the required settings.

The offset pin (OFS) allows for small-range (less than 100mV), positive or negative, offsetting of the output voltage. Should an output voltage setting outside the normal range provided via the internal DAC be required, a separate resistor from FB to GND or to VCC will be required in order to increase or decrease, respectively, the output voltage. Figure 12 details

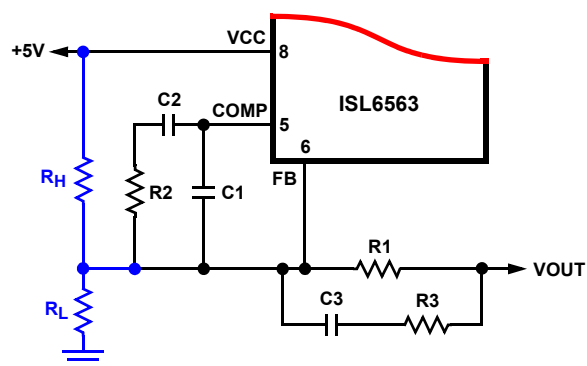


FIGURE 12. ADJUSTING V_{OUT} OUTSIDE THE DAC RANGE

the connection of such a resistor in the ISL6563-based circuit. R_H would be used should a lower output voltage be desired, while R_L would be used in case of a higher voltage. Assuming

the OFS pin is left floating in such a situation (no offset programmed), use the following relationships to compute the value of either resistor based on the known parameters.

$$R_H = \frac{R_1 \cdot (V_{VCC} - V_{DAC})}{V_{DAC} - V_{OUT}}$$

$$R_L = \frac{R_1}{\frac{V_{OUT}}{V_{FB}} - 1}$$

Down-Converting From a Different Input Voltage

The ISL6563EVAL1 is primarily set up to use an ATX computer supply as a bias and down-conversion source. However, when powered from bench supplies, the down-conversion input labeled '+12V' can be adjusted down as desired. If experimenting with a lower voltage, be mindful of a few aspects:

- The duty cycle of the controller is limited to 66%; the circuit will not be capable of properly regulating the output voltage should the input be reduced to a level low enough to induce duty cycle saturation
- The input-RMS current will likely increase as the input voltage is decreased; maximum will be achieved at duty cycles around 25% to 35%
- As the evaluation board (as shipped) was not optimized for high duty cycle operation, closely monitor the board temperatures and increase the output current only as allowed by the board thermal situation
- The reduced input voltage will decrease the amount of loop gain the modulator provides in the feedback loop, as a result, expect a more sluggish transient response when operating the board at reduced down-conversion voltage


Conclusion

The ISL6563EVAL1 evaluation board showcases a highly integrated approach to providing control in a variety of applications, with emphasis on computer systems. The sophisticated feature set and high-current MOSFET drivers of the ISL6563 yield a highly efficient power conversion solution with a reduced number of external components in a compact footprint.

References

Visit us on the internet, at: <http://www.intersil.com>

ISL6563EVAL1 Schematic

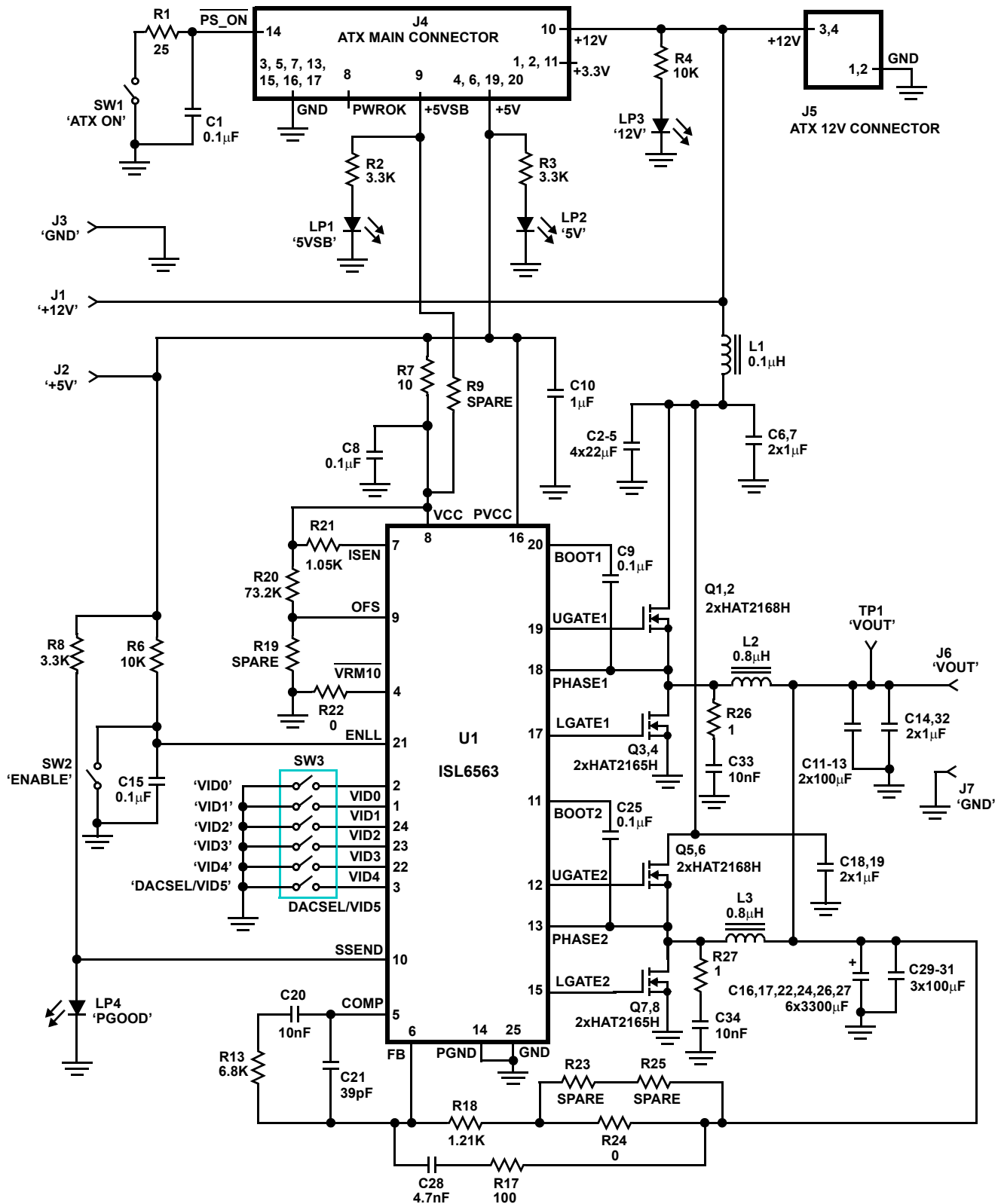


Bill of Materials for ISL6563EVAL1


REFERENCE DESIGNATOR	PART NUMBER	DESCRIPTION	CASE/ FOOTPRINT	MANUF. OR VENDOR	QTY
C1, 8, 9, 15, 25	0.1μF Ceramic	Ceramic Capacitor, X7R, 25V	0603	Any	5
C2-5	C3225Y5V1C226Z	Ceramic Capacitor, Y5V, 16V	1210	TDK	4
C6, 7, 10, 14, 18, 19, 32	1μF Ceramic	Ceramic Capacitor, X7R, 16V	0805	Any	7
C11, 13, 29-31	C3225X5R0J107M	Ceramic Capacitor, X5R, 6.3V	1210	TDK	5
C16, 17, 22, 24, 26, 27	6.3MBZ3300M	Al. Electrolytic Capacitor, 6.3V, 3300μF	10 x 23	Rubycon	6
C20, 33, 34	10nF Ceramic	Ceramic Capacitor, X7R, 25V	0603	Any	3
C21	39pF Ceramic	Ceramic Capacitor, X7R, 50V	0603	Any	1
C28	4.7nF Ceramic	Ceramic Capacitor, X7R, 25V	0805	Any	1
C12	spare				
J1,2	111-0702-001	Banana Jack/Binding Post, Red		Digikey	2
J3	111-0703-001	Banana Jack/Binding Post, Black		Digikey	1
J4	39-29-9203	20-pin Mini-Fit, Jr.™ Header Connector		Molex	1
J5	39-29-9022	4-pin Mini-Fit, Jr.™ Header Connector		Molex	1
J6, 7	KPA8CTP	Tin-Plated Lug Terminal		Burndy	2
L1	P1681	0.1μH inductor, SM Inductor	8 x 15	Pulse	1
L2, 3	PG0077.801	0.8μH inductor, SM Inductor	10 x 17	Pulse	2
LP1-4	L63111CT-ND	Miniature LED, through-board indicator		Digikey	4
Q1, 2, 5, 6	HAT2168H	MOSFET, 30V, 8.8mΩ	LFPAK	Renesas	4
Q3, 4, 7, 8	HAT2165H	MOSFET, 30V, 3.4mΩ	LFPAK	Renesas	4
R1	24Ω	Resistor, 5%, 0.1W	0603	Any	1
R2, 3, 8	3.3kΩ	Resistor, 5%, 0.1W	0603	Any	3
R4, 6	10kΩ	Resistor, 5%, 0.1W	0603	Any	2
R7	10Ω	Resistor, 5%, 0.1W	0603	Any	1
R22, 24	0Ω	Shorting resistor	0603	Any	2
R26, 27	1Ω	Resistor, 5%, 0.16W	0805	Any	2
R20	73.2kΩ	Resistor, 1%, 0.1W	0603	Any	1
R21	1.05kΩ	Resistor, 1%, 0.1W	0603	Any	1
R18	1.21kΩ	Resistor, 1%, 0.1W	0603	Any	1
R17	100Ω	Resistor, 5%, 0.1W	0603	Any	1
R13	6.8kΩ	Resistor, 5%, 0.1W	0603	Any	1
R9, 19, 23, 25	spare				
SW1, 2	GT11MSCKE	Miniature Switch, Single Pole, Double Throw		C&K	2
SW3	TDA06H0SK1R	Miniature Switch, SPST, 6 positions		C&K	1
TP1	131-5031-00	Board Test Point (bag of 25)		Tektronix	1/25
	0293-0-15-01-16-01-10-0	Socket		Mill-Max	1
U1	ISL6563CR	Two-Phase Multiphase PWM Buck Controller with Integrated MOSFET Drivers	QFN-24	Intersil	1
	SJ5003-0-ND	3M rubber bumper		Digikey	6

ISL6563EVAL1 Layout

TOP SILK SCREEN

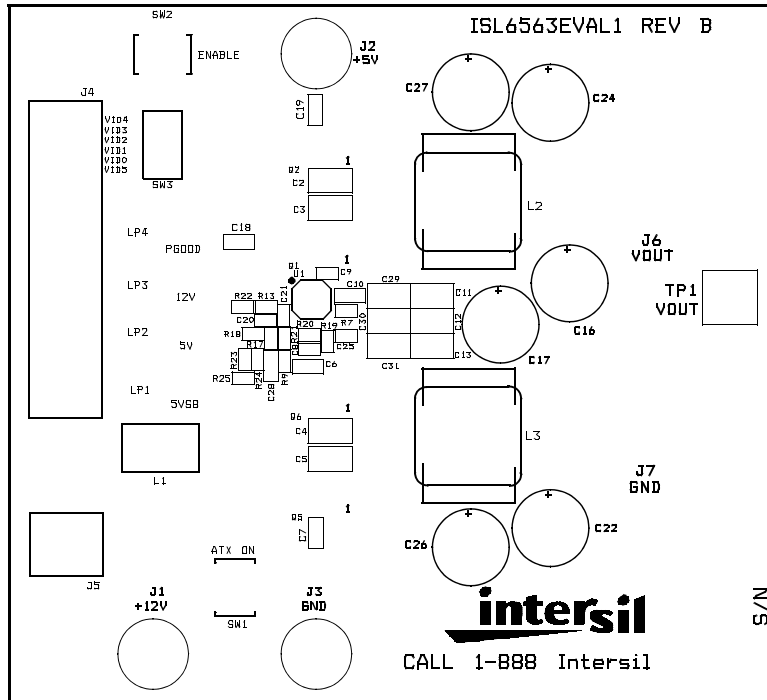


TOP LAYER (1st)

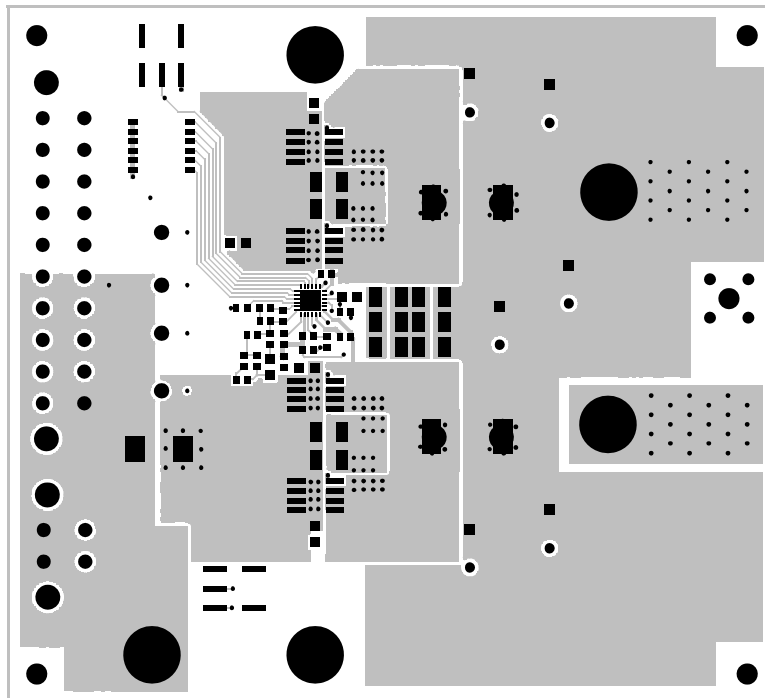


ISL6563EVAL1 Layout (Continued)

GROUND LAYER (2nd)

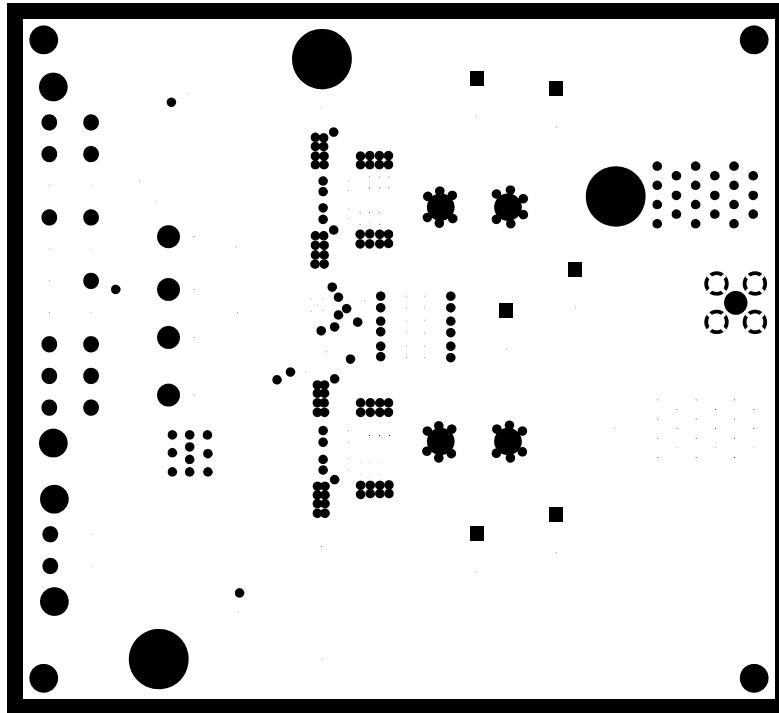

POWER LAYER (3rd)

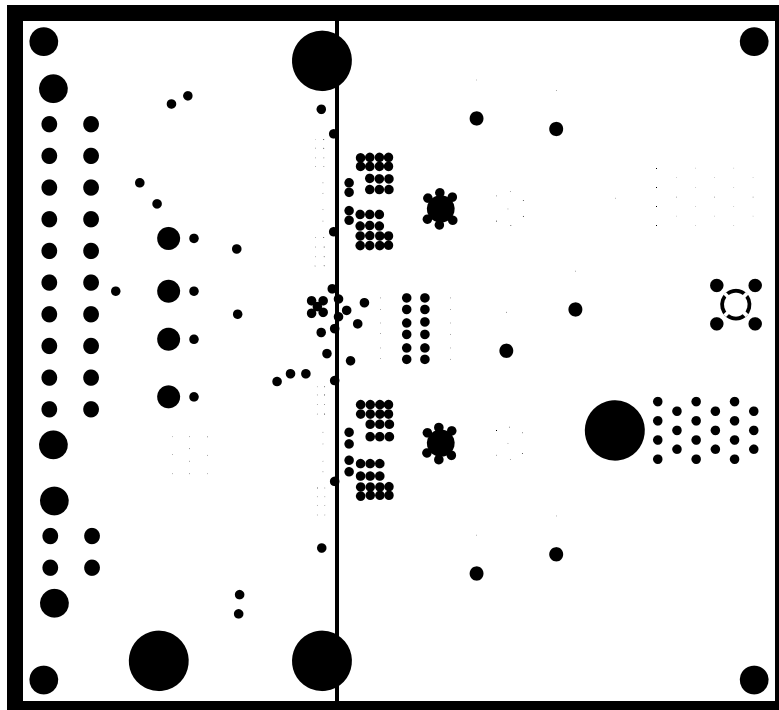

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338