

Designing with Xicor's X5000 Series CPU Supervisors

In recent years, product designs have changed rapidly. There is an increasing need for small, programmable, high performance products. Designers face greater demands for system reliability from consumers. Three of the more common circuits used to improve system reliability are Watchdog Timer, Low Voltage Reset and Power-On management. By combining these features, Intersil offers a small, powerful, cost effective solution for system designers. In addition, Intersil's X5000 series devices offer flexibility never before possible with resettable watchdog timeout periods, reprogrammable low voltage thresholds and various combinations of on-chip serial EEPROM.

Power On Reset Operation

The first, perhaps most critical safeguard that can be added to a system is a reliable power on reset. This circuit is designed to ensure that the microcontroller powers up correctly every time. The combination of power supply design and microcontroller sensitivity to power on conditions can make this difficult. Often, a noisy or slow power supply will cause the microcontroller to improperly initialize, resulting in system failure. One of the best ways to prevent this is to "hold" the microcontroller until the power supply stabilizes. This Power-On Reset feature is standard on all of Intersil's X5000 Series CPU Supervisors.

The Power-On Reset Circuit holds the RESET pin active (preventing the microcontroller from operating) until the Power supply voltage is above a fixed threshold for a nominal 250ms. The X51638 is a special family member. Its 800ms nominal power on reset period is ideal for devices with power supplies that have longer settling times on power up, for oscillators that take longer to stabilize or for systems that use FPGAs that must download code before they start their operation.

Low Voltage Reset Operation

The second most critical area to consider in preventing system failures is low voltage protection. In most systems, there are differing operating voltages for different components. As the power goes down, one or more devices may stop operating correctly. This is particularly bad if the failing device is the microcontroller. On the edge of operation, the microcontroller may execute incorrectly and send out incorrect data or turn on the wrong signal. Since other devices are likely still operating correctly, the system can fail. Sometimes the result is unexpected data changes in the memory. When activated, RESET remains active until the V_{CC} supply again exceeds the trip voltage for (a nominal) 250ms. This delay in releasing RESET helps to avoid frequent system reset conditions.

The Low Voltage Reset controller provided on Intersil's CPU supervisors protects systems from low voltage conditions by activating the RESET output when V_{CC} drops below a V_{CC} trip point. RESET is asserted until V_{CC} returns and stabilizes above the V_{CC} trip point. The V_{CC} trip points are factory set at one of several standard voltage levels. See Table 1

TABLE 1. FACTORY SET V_{trip} POINTS

POWER SUPPLY (V)	SUFFIX	MIN (V)	MAX (V)
4.5-5.5	-4.5A	4.5	4.75
4.5-5.5	Blank	4.25	4.50
2.7-5.5	-2.7A	2.85	3.0
2.7-5.5	-2.7	2.55	2.70
1.8-3.6	-1.8	1.7	1.8

Other V_{CC} trip points or tighter V_{CC} tolerances are possible by re-programming the low voltage trip point. This is a relatively simple process that is documented in each devices' data sheet. Intersil uniquely implements an "analog EEPROM" cell for setting the low voltage threshold. This requires very little current, can be reprogrammed thousands of times and remains stable over both time and temperature. Programming the threshold requires the application of a 15V signal, so it is not something that will happen inadvertently.

To facilitate programming of the low voltage threshold, Intersil has a kit for programming small quantities of devices (XK5000). For high volume needs, standard component test/inspection equipment can be used. In the future, programming will be supported by standard EEPROM programmers. Look for future application notes that provide more detailed support documentation. For other information on reprogrammability or special options, please contact the factory.

Programmable Watchdog Timer

The low voltage and power-on reset circuits helps to keep a system operational. However, there are conditions that are impossible to predict. Many of these involve software or the hardware/software interface. For example:

- A software subroutine waiting for a peripheral to respond may never exit if the peripheral has failed.
- In a complicated design, many different programmers develop different pieces of code. Data passing is defined well, but not completely. When the unit is in the field, a condition arises that was not tested and unexpected data is passed, causing the software to "crash".
- Noise on an input causes the processor to enter an unexpected mode of operation.

To deal with these, and other potential system failures, more systems today incorporate a watchdog timer. A watchdog timer ensures system reliability by providing a RESET signal to the microcontroller, microprocessor, ASIC or DSP. This RESET signal returns the system to a known state, while the watchdog timer continues to monitor system operations, providing improved reliability.

Intersil's programmable watchdog timer provides several advantages over its competitors:

1. The designer can choose from three programmable time-out intervals. There is no need to decide on a factory preset time-out interval before prototypes begin.
2. The programmable watchdog timer can be disabled easily, via software, during debug or during field recalibration or upgrade. This eliminates the endless resets that normally occur during debug of a system with a fixed watchdog timer and it eliminates the need to remove hardware from the board to disable the watchdog.
3. Since software revisions may require a tighter or looser time-out interval, software programming of the time-out period results in easy system upgrades. This eliminates the need to make changes to the PC board, as is the case with hard-wired devices.

A watchdog timer is a simple countdown timer which activates a RESET signal when it reaches zero. This RESET signal provides the system reset for the microcontroller, microprocessor, ASIC or DSP. During normal operation, the system software sends a signal to reset the countdown timer to its maximum value before it reaches zero. If the system locks up or enters some unwanted state, or if the software operates unexpectedly or gets stuck in an infinite loop, the watchdog timer will time-out and assert the reset signal. By asserting the RESET, the system returns to a known state and continues to operate. After deasserting the RESET signal, the watchdog timer automatically begins another countdown, thus providing the system continuous reliability.

The system software provides the watchdog timer restart signal by toggling the Supervisory EEPROM $\overline{CS}$ pin HIGH to LOW. The watchdog timer begins to countdown from its maximum value once the $\overline{CS}$ is pulled low. If the $\overline{CS}$ remains low longer than the programmable time interval, the watchdog timer will 'time-out' and assert the reset signal. This edge triggered restart prevents the watchdog timer from being kept in a continuous restart mode without toggling $\overline{CS}$. This feature provides protection to the system even when restarting the watchdog timer.

Programming the Watchdog Timer

Two non-volatile bits (WD1, WD0) in the status register control the programmable watchdog timer intervals (See Table 2) These bits are accessed via a read/write status register command (as described in the data sheet.) As with any nonvolatile write operation, a write enable command precedes the status register write operation. This write enable command, which sets the WEL bit, helps prevent inadvertent changes to

the watchdog timer intervals. In applications where the Watchdog timer setting is very critical, setting the WPEN bit to a '1' and soldering the WP pin active LOW creates a psuedo-OTP function that requires a both a hardware change and a series of software commands to change the watchdog time-out interval.

TABLE 2. STATUS RESGISTER EXAMPLE

7	6	5	4	3	2	1	0
WPEN	0	WD1	WD0	BP1	BP0	WEL	WIP

NOTE: Only available in devices with 16K, 32K, or 64K of EEPROM

The watchdog timer is programmable to four preset values: 200ms, 600ms, 1.4s and disabled, see Table 3 Disabling the watchdog timer provides for easy software debugging during prototyping without the nuisance of frequent resets. Once the watchdog timer is enabled (initially disabled from the factory) the watchdog timer will power-up and begin to count down once the power reset circuit (POR) has de-asserted the reset signal. Once enabled, Intersil's watchdog timer requires no initialization after power-up.

TABLE 3. WATCHDOG TIMER INTERVALS

WD1	WD0	MIN.	TYP	MAX	UNITS
1	0	100	200	300	ms
0	1	450	600	800	ms
0	0	1	1.4	2	sec
1	1	OFF			

Summary

Intersil's new family of supervisory EEPROMs combines Power-On Reset, Low Voltage Reset and Watchdog Timer features with standard SPI BlockLock™ EEPROM. Combined, these five features provide a small, powerful, cost efficient way to improve system reliability. Since it is not always necessary to use all three supervisory features or EEPROM, Intersil provides choices to give the designer the greatest possible flexibility. For a summary of the available devices, see Table 4.

TABLE 4. INTERSIL SUPERVISORY EEPROMS

INTERSIL DEVICE	LOW VOLTAGE RESET OPTIONS (V)	POWER ON RESET (ms)	WATCHDOG TIMER TIMEOUT PERIOD (s)	WATCHDOG TIMER RESET PERIOD (ms)	RESET ACTIVE LEVEL	EEPROM DENSITY	
X5001	4.62 4.38 2.92 2.62 1.75	200	Off, .2, .6, 1.4	200	Low	0K	
X5043/X5045		250		250	Low/High	4K	
X5163/X5165						16K	
X5323/X5325						32K	
X5643/X5645		800	Off, .4, .6, 1.4	400	Low/High	64K	
X51638						16K	
X5168/X5169						16K	
X5328/X5329		250	N/A	N/A		32K	
X5648/X5649						64K	

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338