RENESAS

APPLICATION NOTE

ISL95311 VCOM Applications

The ISL95311 device contains a 3-terminal digital potentiometer and control section. All three terminals are utilitized when the device is used in voltage divider mode. If the wiper (Vw terminal) is connected to either the Vh or VL terminals, then the device is used in rheostat mode and is effective for current control. These two configurations can be used with opamps and comparators to implement a variety of control and signal processing circuits.



FIGURE 1A. VOLTAGE DIVIDER MODES

FIGURE1B. RHEOSTAT MODES

VCOM Circuits

LCD TFT panels need to have a common voltage supplied to their backplane. This signal is generally referred to as the VCOM voltage and is typically set to half the main bias voltage, with some offset compensation required. The ISL95311 provides 128-step resolution for VCOM voltage adjustment as just a simple voltage divider. Note that the maximum potentiometer pin voltage of the device is determined by the bias on the V+ pin, and is specified to be a maximum of +13.5V. The ISL95311 can handle higher LCD bias voltages by using series resistors on the Vh and VL pins.

The loading of a VCOM input is very capacitive, with dynamic changes in loading as pixels change, and therefore requires buffering of the potentiometer wiper voltage. An opamp is configured as a unity gain buffer and placed between the wiper output and the VCOM input. The resulting control circuit is shown in Figure 2. AN183 Rev 0.00 May 10, 2005



FIGURE 2. BASIC VCOM CONTROL

The EL5111 amplifier is chosen for this application as it is designed for VCOM load driving with high slew rate, fast settling, and high output drive. It has rail-rail outputs and handles a maximum supply voltage of 16.5V. The ISL95311 uses Vcc = 5V and V+ = 12V. R1, R2 and Rtotal (the potentiometer resistance) control the range and resolution of adjustment for VCOM. The ISL95311 has 128 total settings (n), yielding 127 steps of adjustment (n–1), so the equation for resolution will be:

Resolution = [V(RH) - V(RL)] / (n-1)

and

V(RH) – V(RL) = AVDD • [Rtotal / (R1+R2+Rtotal)]

Therefore,

Resolution = AVDD • Rtotal / [(n-1) • (R1+R2+Rtotal)]



Since VCOM is normally targeted at 1/2 the AVDD voltage, we usually center the adjustment range by setting R1 = R2. The values for R1 and R2 can be calculated using the equations and design targets, but the most expeditious method is to pick initial values which would yield approximately the range desired.

Example:

AVDD = +15V

Rtotal = $10k\Omega$ ($50k\Omega$ can also be used, and R1, R2 increased in value).

We would like an adjustment range of about 10% of the AVDD value, so R1 = R2 = $50k\Omega$. The resulting resolution will be:

Resolution= 15V • 10 / [(127 • (50+50+10)]

= 10.7mV per step

If higher resolution (smaller step sizes) are desired, then R1 and R2 can be increased appropriately. Also, since the maximum recommended value for V(VH) = +12V, we need to check to make sure we have not exceeded this value.

V(RH)= AVDD • [(R2+Rtotal) / R1+R2+Rtotal)]

= +15V • (50 +10) / [(50+50+10)]

= +8.18V

Filtering

If significant noise or switching transients are expected on the AVDD line, it is especially easy to add filtering to the circuit of Figure 2. A capacitor should be added from the noninverting input of the EL5111 to ground. Note the 3dB frequency for the filter will vary with the tap position of the potentiometer, but an equation for the maximum f3dB (given R1 = R2) is:

 $F3dB(max) = 1 / (2\pi \cdot R1 \cdot C)$

For C = 0.1μ F in our example above, this yields a 3dB frequency of about 64Hz, and response will be down 24dB at 1kHz.

Design Considerations

The ISL95311 uses 2-wire serial interface control to adjust the wiper position and store the desired value in nonvolatile memory. No programming voltage is required to perform the nonvolatile storage. See the ISL95311 data sheet for details on correct serial interface operation. Note that Vcc for the ISL95311 can be as low as 2.7V, as long as the logic and interface pins use that voltage. The V+ bias for the ISL95311 should be chosen so that it will be greater than or equal to the potentiometer pin voltages under all conditions. There is very little current drawn by the V+ input (<2 μ A), so it is possible to use a resistor divider to supply current to this input if care is taken in choosing resistor values (10k Ω minimum resistance recommended).

The EL5111 is a high speed device, so proper supply decoupling and layout are required, as well as proper consideration of the capacitive load in the application. See that device data sheet for more details.



Notice

- 1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information
- 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples
- 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
- 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
- Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard" Computers: office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment: industrial robots: etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc. Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.

- 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics oroducts outside of such specified ranges
- 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
- 8. Plea e contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions
- 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
- 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

RENESAS

SALES OFFICES

Renesas Electronics Corporation

http://www.renesas.com

Refer to "http://www.renesas.com/" for the latest and detailed information

Renesas Electronics America Inc. 1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A. Tel: +1-408-432-8888, Fax: +1-408-434-5351 Renesas Electronics Canada Limited 9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3 Tel: +1-905-237-2004 Renesas Electronics Europe Limited Dukes Meadow, Miliboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K Tei: +44-1628-651-700, Fax: +44-1628-651-804 Renesas Electronics Europe GmbH Arcadiastrasse 10, 40472 Düsseldorf, Germar Tel: +49-211-6503-0, Fax: +49-211-6503-1327 Renesas Electronics (China) Co., Ltd. Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China Tel: +86-10-8235-1155, Fax: +86-10-8235-7679 Renesas Electronics (Shanghai) Co., Ltd. Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China Tel: +86-21-2226-0888, Fax: +86-21-2226-0999 Renesas Electronics Hong Kong Limited Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong Tel: +852-2265-6688, Fax: +852 2886-9022 Renesas Electronics Taiwan Co., Ltd. 13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan Tel: +886-2-8175-9600, Fax: +886 2-8175-9670 Renesas Electronics Singapore Pte. Ltd. 80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949 Tel: +65-6213-0200, Fax: +65-6213-0300 Renesas Electronics Malaysia Sdn.Bhd. Unit 1207, Block B, Menara Amcorp, Amco Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia Unit 1207, Block B, Menara Amcorp, Amcorp Tel: +60-3-7955-9390, Fax: +60-3-7955-9510 Renesas Electronics India Pvt. Ltd. No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India Tel: +91-80-67208700, Fax: +91-80-67208777 Renesas Electronics Korea Co., Ltd. 17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea Tei: +822-558-3737, Fax: +822-558-5338