

Introduction

When working with op amp circuits an engineer is frequently required to predict the total RMS output noise in a given bandwidth for a certain feedback configuration. While op amp noise can be expressed in a number of ways, "spot noise" (RMS input voltage noise or current noise which would pass through 1Hz wide bandpass filters centered at various discrete frequencies), affords a universal method of predicting output noise in any op amp configuration.

The Noise Model

Figure 1 is a typical noise model depicting the noise voltage and noise current sources that are added together in the form of root mean square to give the total equivalent input voltage noise (RMS), therefore:

$$E_{ni} = \sqrt{e_{ni}^2 + i_{ni}^2 R_G^2 + 4KTR_G} \text{ where,}$$

E_{ni} is the total equivalent input voltage noise of the circuit,

e_{ni} is the equivalent input voltage noise of the amplifier, and

$i_{ni}^2 R_G^2$ is the voltage noise generated by the current noise.

$4KTR_G$ expresses the thermal noise generated by the external resistors in the circuit where $K = 1.38 \times 10^{-23}$ joules/°K; $T = 300^\circ\text{K}$ (27°C) and:

$$R_G = \left(\frac{R_1 R_3}{R_1 + R_3} \right) + R_2$$

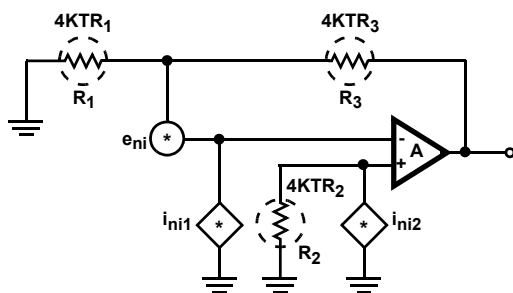


FIGURE 1.

The total RMS output noise (E_{no}) of an amplifier stage with gain = G in the bandwidth between f_1 and f_2 is:

$$E_{no} = G \left(\int_{f_1}^{f_2} (E_{ni})^2 df \right)^{1/2}$$

Note that in the amplifier stage shown, G is the non-inverting gain:

$$\left(G = 1 + \frac{R_3}{R_1} \right),$$

regardless of which input is normally driven.

Procedure for Computing Total Output Noise

1. Refer to the voltage noise curves for the amplifier to be used.
2. Enter values of e_{ni}^2 line (a) of the table below from the curve labeled "Noise spectral density" (the values must be squared).
3. From the current noise curves for the amplifier, obtain the values of i_{ni}^2 for each of the frequencies in the table, and multiply each by R_G^2 , entering the products in line (b) of the table.
4. Obtain the value of $4KTR_G$ from Figure 8, and enter it on line (c) of the table. This is constant for all frequencies. The $4KTR_G$ value must be adjusted for temperatures other than normal room temperature.
5. Total each column in the table on line (d). This total is E_{ni}^2 .

	10Hz	100Hz	1kHz	10kHz	100kHz
(a) e_{ni}^2					
(b) $i_{ni}^2 R_G^2$					
(c) $4KTR_G$					
(d) E_{ni}^2					


6. On linear scale graph paper enter each of the values for E_{ni}^2 versus frequency. In most cases, sufficient accuracy can be obtained simply by joining the points on the graph with straight line segments.

For the bandwidth of interest, calculate the area under the curve by adding the areas of trapezoidal segments. This procedure assumes a perfectly square bandpass condition; to allow for the more normal -6dB/octave bandpass skirts, multiply the upper (-3dB) frequency by 1.57 to obtain the effective bandwidth of the circuit, before computing the area. The total area obtained is equivalent to the square of the total input noise over the given bandwidth.

7. Take the square root of the area found above and multiply by the gain (G) of the circuit to find the total Output RMS noise.
8. Take the square root of the area found above and multiply by the gain (G) of the circuit to find the total Output RMS noise.

A Typical Example

It is necessary to find the output noise of the circuit shown below between 1kHz and 24kHz.

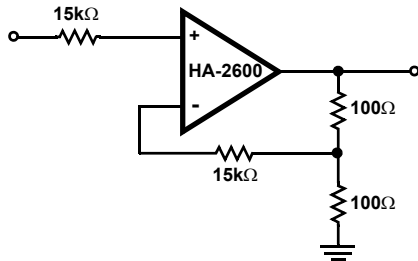FIGURE 2. THE HA-2600 IN A TYPICAL $G = 1000$ CIRCUIT

Values are selected from the data sheet and Figure 8 to fill in the table as shown below. An R_G of $30k\Omega$ was selected.

	10Hz	100Hz	1kHz	10kHz	100kHz
(a) e_{ni}^2	3.6×10^{-15}	1.156×10^{-15}	7.84×10^{-16}	7.29×10^{-16}	7.29×10^{-16}
(b) $I_{ni}^2 R_G^2$	9.9×10^{-16}	1.89×10^{-16}	3.15×10^{-17}	7.2×10^{-18}	72×10^{-18}
(c) $4KTR_G$	4.968×10^{-16}	4.968×10^{-16}	4.968×10^{-16}	4.968×10^{-16}	4.968×10^{-16}
(d) E_{ni}^2	5.09×10^{-15}	1.86×10^{-15}	1.31×10^{-15}	1.23×10^{-15}	1.23×10^{-15}

The totals of the selected values for each frequency is in the form of E_{ni}^2 . This should be plotted on linear graph paper as shown below:

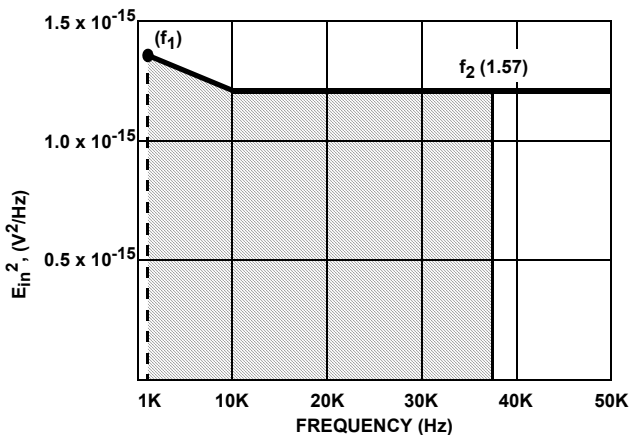


FIGURE 3. HA-2600 TOTAL EQUIVALENT INPUT NOISE

Since a noise figure is needed for the frequency of 1kHz to 24kHz, it is necessary to calculate the effective bandwidth of the circuit. With $A_V = 60\text{dB}$ the upper 3dB point is approximately 24kHz. The product of 1.57 (24kHz) is 37.7kHz and is the effective bandwidth of the circuit.

The shaded area under the curve is approximately $45 \times 10^{-12} \text{V}^2$; the total equivalent input noise is $\sqrt{E_{in}^2}$ or $6.7 \mu\text{V}$, and the total output noise for the selected bandwidth is $\sqrt{E_{in}^2} \times$ (closed loop gain) or $6.7 \text{mV}_{\text{RMS}}$.

Actual Measurements for Comparison

The circuit shown below was used to actually measure the broadband noise of the HA-2600 for the selected bandwidth:

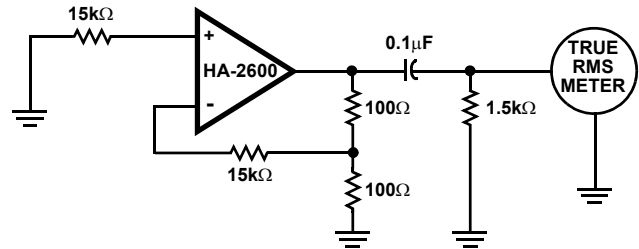


FIGURE 4. A TYPICAL TEST CIRCUIT FOR BROADBAND NOISE MEASUREMENTS

The frequencies below the f_1 point of the bandwidth selected are filtered out by the RC network on the output of HA-2600. The measurement of the broadband noise is observed on the true RMS voltmeter. The measured output noise of the circuit is $4.7 \text{mV}_{\text{RMS}}$ as compared to the calculated value of $6.7 \text{mV}_{\text{RMS}}$.

Acquiring the Data for Calculations

Spot noise values must be generated in order to make the output noise prediction. The effects of "Popcorn" noise have been excluded due to the type of measurement system.

The Quan-Tech Control Unit, Model No. 2283 and Filter Unit, Model No. 2181 were used to acquire spot noise voltage values expressed in $(\text{V}/\sqrt{\text{Hz}})$. The test system performs measurements from 10Hz by orders of magnitude to 100kHz with an effective bandwidth of 1Hz at each tested frequency.

Several source resistance (R_G) values were used in the measuring system to reveal the effects of R_G on each type of Intersil's op amps and to obtain proper voltage noise values essential for current noise calculations.

A Discussion On "Popcorn" Noise

"Popcorn" noise was first discovered in early 709 type op amps. Essentially it is an abrupt step-like shift in offset voltage (or current) lasting for several milliseconds and having amplitude from less than one microvolt to several hundred microvolts. Occurrence of the "pops" is quite random - an amplifier may exhibit several pops per second during one observation period and then remain "popless" for several minutes. Worst case conditions are usually at low temperatures with high values of R_G . Some amplifier designs and some manufacturer's products are notoriously bad in this respect. Although theories of the popcorn mechanism differ, it is known that devices with surface contamination of the semiconductor chip will be particularly bad "poppers". Advertising claims notwithstanding, the author has never seen any manufacturer's op amp that was completely free of "popcorn." Some peak detector circuits have been developed to screen devices for low amplitude "pops", but 100% assurance is impossible because an infinite test time would be required. Some studies have shown that spot noise measurements at 10Hz and 100Hz, discarding units that are much higher than typical, is an effective screen for potentially high "popcorn" units.

The vast majority of Intersil op amps will exhibit less than

$3\mu V_{P-P}$ "popcorn". Screening can be performed, but it should be noted that the confidence level of the screen could be as low as 60%.

References

- [1] Fitchen, F.C. and Motchenbacher, C.D. Low Noise Electronic Design. New York: John Wiley and Sons, 1973. Instruction Manual, Model 2173C Transistor Noise Analyzer Control Unit. Quan-Tech, Division of KMS Industries. Whippany, New Jersey.

Typical Spot Noise Curves Unless Otherwise Noted: $V_S = \pm 15V, T_A = 25^\circ C$

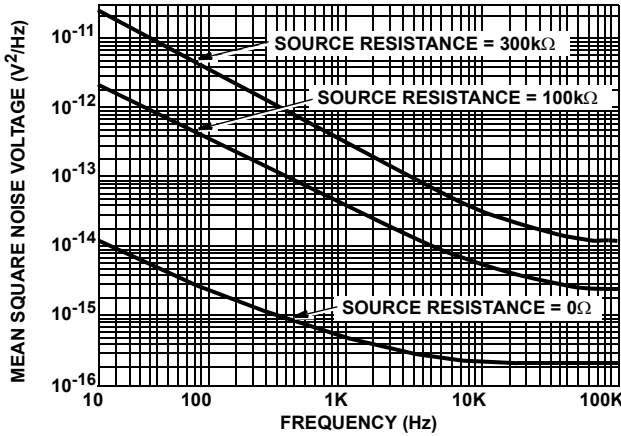


FIGURE 5. HA-2500/2510/2520 INPUT NOISE VOLTAGE

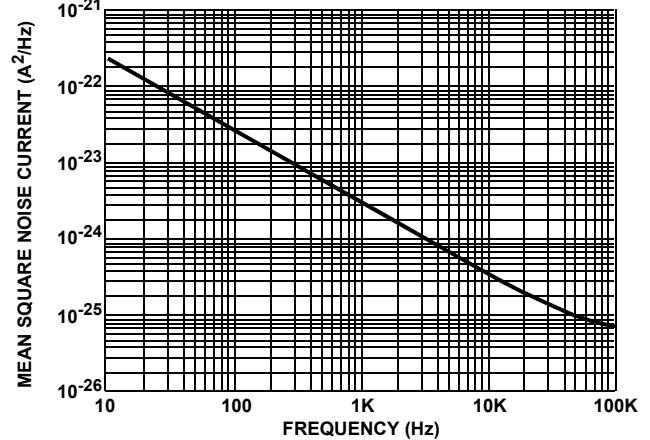


FIGURE 6. HA-2500/2510/2520 INPUT NOISE CURRENT

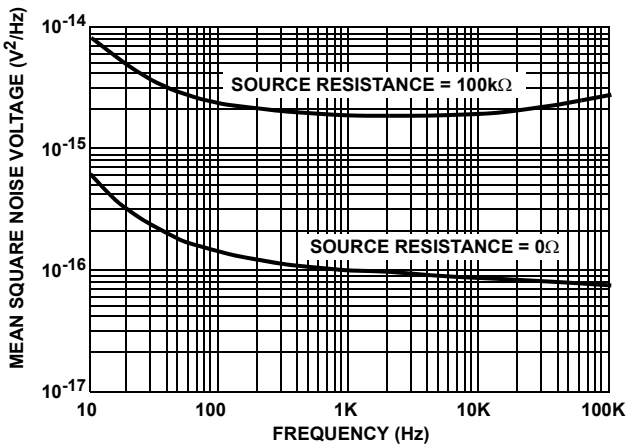


FIGURE 7. HA-4741 INPUT NOISE VOLTAGE

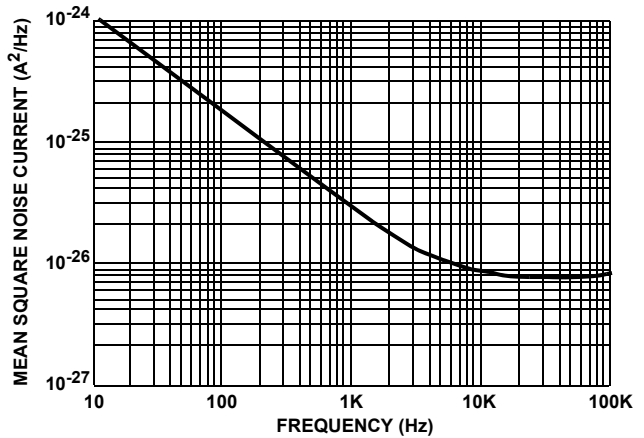


FIGURE 8. HA-4741 INPUT NOISE CURRENT

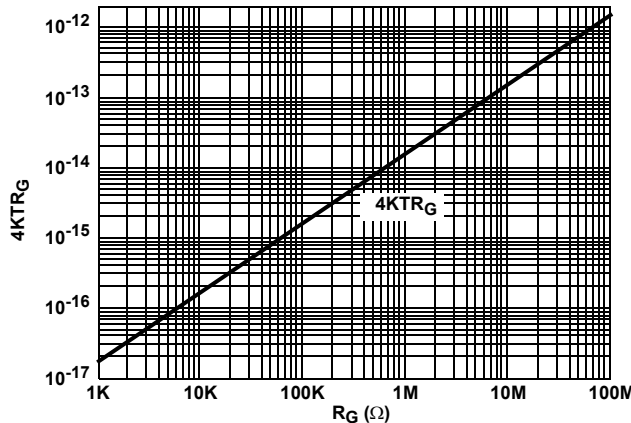


FIGURE 9. NOISE vs RESISTOR VALUE

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338