

Basic Analog for Digital Designers

Introduction

This application note starts with an overview of the basic laws of physics, progresses through circuits 1 and 2, and explains op amp operation through the use of feedback principles. Math is the foundation of circuit design, but it is in the simplest level possible for this application note^[1].

Contents

1. Basic Physics Laws, Circuit Theorems, and Analysis	2
2. Ohm's and Kirchoff's Laws	2
3. Voltage and Current Dividers	3
4. Thevenin's and Norton's Theorems	4
5. Superposition	6
6. Analysis Tools - Why Do We Need More Than One?	6
7. Feedback Principles	7
8. The Op Amp Symbol	7
9. The Inverting Op Amp	8
10. The Non-Inverting Op Amp	9
11. The Differential Amplifier	9
12. T Networks in the Feedback Path	10
13. Video Amplifiers	11
14. AC Theory	12
15. Op Amp Circuits Containing Capacitors	12
16. Conclusion	13
17. Revision History	13

1. For more advanced op amp topics, refer to the following documents: *Feedback, Op Amps and Compensation Application Note* and *Current Feedback Amplifier Theory and Applications Application Note*.

1. Basic Physics Laws, Circuit Theorems, and Analysis

The following provides basic analog information for designers that allow for analyzing circuits and writing op amp circuit equations.

2. Ohm's and Kirchoff's Laws

Ohm's law states that there is a relationship between the current in a circuit and the voltage potential across a circuit. This relationship is a function of a constant called the resistance.

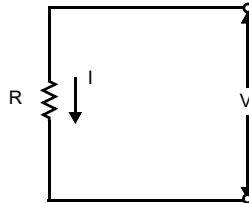


Figure 1. Illustration of Ohm's Law

(EQ. 1) $V = IR$

Kirchoff's voltage law states that the algebraic sum of the voltages around any closed loop equals zero. The sum includes independent voltage sources, dependent voltage sources and voltage drops across resistors (called IR drops).

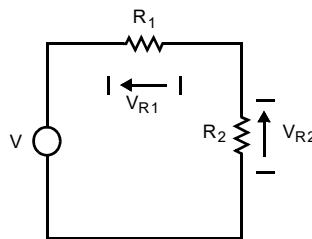


Figure 2. Illustration of Kirchoff's Voltage Law

(EQ. 2) $V - V_{R1} - V_{R2} = 0$ or $V = V_{R1} + V_{R2}$

(EQ. 3) $\Sigma \text{ voltage sources} = \Sigma \text{ voltage drops}$

Kirchoff's current law states that the algebraic sum of all the currents leaving a node equals zero. The sum includes independent current sources, dependent current sources, and component currents.

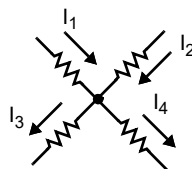


Figure 3. Illustration of Kirchoff's Current Law

(EQ. 4) $I_1 + I_2 = I_3 + I_4$

(EQ. 5) $I_1 + I_2 - I_3 - I_4 = 0$

(EQ. 6) Σ currents into a junction = 0

3. Voltage and Current Dividers

Voltage dividers are seen often in circuit design because they are useful for generating a reference voltage, for biasing active devices, and acting as feedback elements. Current dividers are seen less often, but they are still important so equations are developed for them. The voltage divider equations, which assume that the load does not draw any current, are developed in [Figure 4](#).

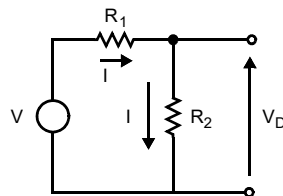


Figure 4. Derivation of the Voltage Divider Rule

(EQ. 7) $V = IR_1 + IR_2 = I(R_1 + R_2)$

(EQ. 8) $I = \frac{V}{(R_1 + R_2)}$

(EQ. 9) $V_D = IR_2 = \frac{V}{(R_1 + R_2)}(R_2) = V \frac{R_2}{R_1 + R_2}$

The current divider equations, assuming that the only load is R_2 , is given in [Figure 5](#).

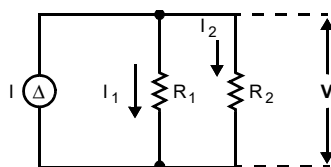


Figure 5. Derivation of the Current Divider Rule

(EQ. 10) $I = I_1 + I_2$

(EQ. 11) $V = I_1 R_1 = I_2 R_2$

(EQ. 12) $I_1 = I_2 \frac{R_2}{R_1}$

(EQ. 13) $I = I_1 + I_2 = I_2 \frac{R_2}{R_1} + I_2 = I_2 \left(1 + \frac{R_2}{R_1} \right) = I_2 \left(\frac{R_1 + R_2}{R_1} \right)$

(EQ. 14) Then: $I_2 = I \frac{R_1}{R_1 + R_2}$

4. Thevenin's and Norton's Theorems

There are situations where it is simpler to concentrate on one component rather than write equations for the complete circuit. When the input source is a voltage source, Thevenin's theorem is used to isolate the component of interest, but if the input source is a current source, Norton's theorem is used to isolate the component of interest.

To apply Thevenin's theorem look back into the terminals of the component being replaced. Next, calculate the open circuit voltage seen at these terminals, and during this calculation, consider that there is no load current so that the voltage divider rule can be used. Short the independent voltage sources and open the independent current sources, and calculate the impedance seen looking into the terminals. The final step is to replace the original circuit with the Thevenin equivalent voltage, V_{th} , and Thevenin equivalent impedance, Z_{th} .

Thevenin's theorem is illustrated in [Figure 6](#).

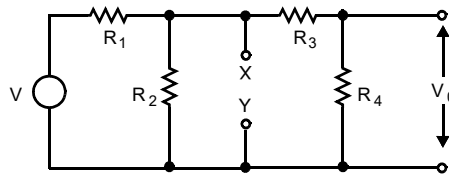


Figure 6. The Original Circuit

The open circuit voltage is calculated by first looking into the terminals X - Y, and calculating the open circuit voltage with the voltage divider rule.

(EQ. 15) $V_{th} = V \frac{R_2}{R_1 + R_2}$

The impedance looking back into the terminals X - Y with the independent source, V, shorted is provided in [Equation 16](#).

(EQ. 16) $Z_{th} = Z_{x-y} = \frac{R_1 R_2}{R_1 + R_2} \equiv R_1 \parallel R_2$

The circuit to the left of X - Y is replaced by the Thevenin equivalents.

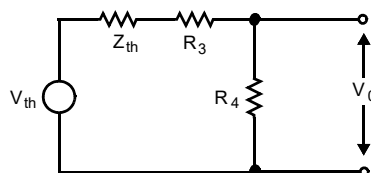


Figure 7. The Thevenin Equivalent Circuit

$$\begin{aligned}
 (EQ. 17) \quad V_0 &= V_{th} \frac{R_4}{Z_{th} + R_3 + R_4} \\
 &= V \frac{R_2}{R_1 + R_2} \frac{R_4}{\frac{R_1 R_2}{R_1 + R_2} + R_3 + R_4}
 \end{aligned}$$

The loop equations are shown in the following figure equations. Not only is the derivation of the equations more laborious, but the process complicates with the addition of another loop. This is why Thevenin's theorem is preferred over loop equations.

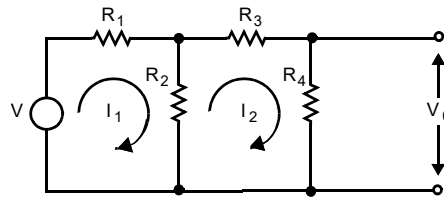


Figure 8. Loop Equation Analysis of the Same Circuit

$$(EQ. 18) \quad V = I_1(R_1 + R_2) - I_2 R_2$$

$$(EQ. 19) \quad I_2(R_2 + R_3 + R_4) = I_1 R_2$$

$$(EQ. 20) \quad I_1 = \frac{R_2 + R_3 + R_4}{R_2} I_2$$

$$(EQ. 21) \quad V = I_2 \frac{(R_2 + R_3 + R_4)}{R_2} (R_1 + R_2) - I_2 R_2$$

$$(EQ. 22) \quad I_2 = \frac{V}{\frac{R_2 + R_3 + R_4}{R_2} (R_1 + R_2) - R_2}$$

$$(EQ. 23) \quad V_0 = I_2 R_4$$

$$(EQ. 24) \quad V_0 = V \frac{R_4}{\frac{(R_2 + R_3 + R_4)(R_1 + R_2)}{R_2} - R_2}$$

The Norton equivalent circuit is seldom used in circuit design. (See additional references for details on the derivation^[2].)

2. Van Valkenberg, N.E., *Network Analysis*, Prentice-Hall, 1964.

5. Superposition

The principle of superposition states that the equation for each independent source can be calculated separately, and the equations (or results) can be added to give the total result. When implementing superposition, the equation for each source is calculated with (1) the other independent voltage sources short circuited and (2) the independent current sources open circuited. The equations for all the sources are added together to obtain the final answer.

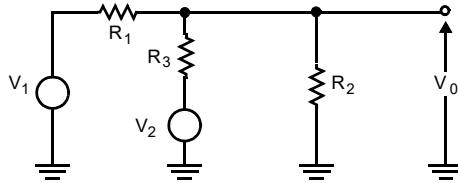


Figure 9. Superposition Example

$$(EQ. 25) \quad V_{01}|_{V_2=0} = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} V_1 \quad V_{02}|_{V_1=0} = \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} V_2$$

$$(EQ. 26) \quad V_0 = V_{01} + V_{02} = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + V_2 \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$

6. Analysis Tools - Why Do We Need More Than One?

Each one of the analysis tools shown has a place where it is optimal. When the op amp analysis occurs, the tools are employed to relieve the burden of detailed calculation. Figure 10 and Figure 11 illustrate an example of the extra calculations caused by using the less optimal tool to perform the analysis.

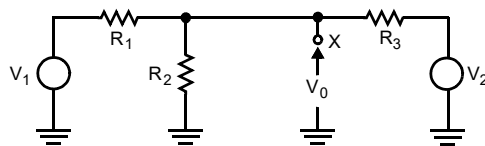


Figure 10. Superposition Example Redraw

$$(EQ. 27) \quad V_{th} = \frac{R_2}{R_1 + R_2} V_1 \quad R_{th} = R_1 \parallel R_2$$

$$(EQ. 28) \quad I = \frac{V_2 - V_{th}}{R_{th} + R_3} \quad V_0 = V_2 - IR_3$$

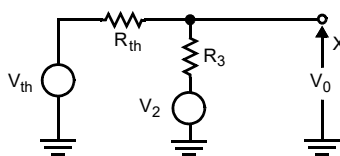


Figure 11. Thevenin Equivalent Circuit Model

$$(EQ. 29) \quad V_0 = V_2 - \frac{V_2 - V_{th}}{R_{th} + R_3} R_3 = V_2 - \frac{V_2 - \frac{R_2 V_1}{R_1 + R_2}}{R_1 \parallel R_2 + R_3} R_3$$

The Thevenin method used twice as many equations to describe the circuit as were required to arrive at the same result with superposition. Also, the form of the final equation arrived at by superposition is easier to analyze.

7. Feedback Principles

This discussion of feedback principles is simple because they are easy to understand. The application of the principles can be complicated for the design engineer, but the principles can be grasped without understanding all of the nuances.

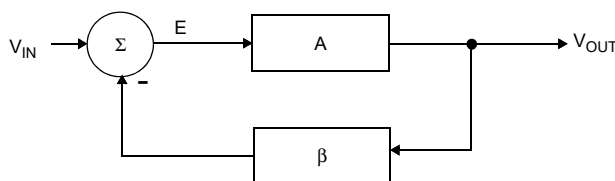


Figure 12. Feedback Block Diagram

$$(EQ. 30) \quad V_{OUT} = EA$$

$$(EQ. 31) \quad E = V_{IN} - \beta V_{OUT}$$

$$(EQ. 32) \quad \frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + A\beta}$$

Equation 30 and Equation 31 are written on the block diagram, and Equation 32 is obtained by combining them to eliminate the error, E. If $\beta = 1$ in Equation 32 $V_{OUT} = V_{IN}$, or the feedback circuit has turned into a unity gain buffer. If $\beta = 0$ in Equation 32 $V_{OUT} = AV_{IN}$, or there is no feedback. Notice that the direct gain, A, does not control the feedback circuit closed loop gain; rather, the feedback factor, β , controls the closed loop gain in a feedback circuit. This is the essence of a feedback circuit; next, the closed loop gain is a function of the feedback factor which is comprised of passive components. The closed loop gain error, stability, and drift are now dependent on stable, accurate, and inexpensive passive components. The closed loop gain assumption is valid as long as $A\beta \gg 1$, also $E \Rightarrow 0$ if this assumption is valid.

If $A\beta = -1$ then Equation 32 becomes $V_{OUT}/V_{IN} = 1/0$, or it is indeterminate. The energy in the circuit is limited, so the circuit oscillates from positive to negative saturation. This is an oscillator, therefore, the definition of an oscillator is that the gain be ≥ 1 while the phase shift equals -180 degrees. In conclusion, the feedback factor controls the closed loop gain, and the direct gain/feedback factor combination determines if the circuit is stable or is an oscillator.

8. The Op Amp Symbol

It is important to understand the op amp symbol shown in Figure 13. The -input, V_- , is the inverting input, and the +input, V_+ , is the non-inverting input. The point of the triangle is the op amp output, and the op amp multiplies the differential voltage, $(V_+ - V_-)$, by a large gain, a.

9. The Inverting Op Amp

Three assumptions are made in the calculation of the inverting op amp circuit equations. First, the current into the op amp inputs, I_B in Figure 13, is assumed to be zero; this is a valid assumption because the bias currents are usually much lower than signal currents. The second assumption is that the op amp gain, a , is extremely high, and this is a valid assumption in most situations where the op amp's bandwidth is much greater than the signal bandwidth. The third assumption, which is that the error voltage, V_E , equals zero, is a result of assuming an extremely high op amp gain. When a has a large V_{OUT} , it can assume any value required to drive the inverting input voltage to the non-inverting input voltage, so V_E is always forced to zero.

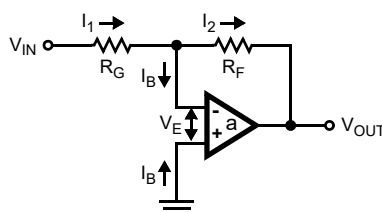


Figure 13. Inverting Op Amp Circuit

Assume $I_B = 0$, $V_E = 0$, $a = \infty$

Then:

$$(EQ. 33) \quad I_1 = \frac{V_{IN}}{R_G} = I_2 = -\frac{V_{OUT}}{R_F}$$

$$(EQ. 34) \quad V_{IN} R_F = -V_{OUT} R_G$$

$$(EQ. 35) \quad \frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_G}$$

Equation 33 is written by applying Kirchhoff's current law to the inverting node. Equation 35 is obtained through algebraic manipulation of Equation 33 and Equation 34. The ideal closed loop gain, Equation 35, does not contain the op amp gain, so it is independent of the op amp gain while the assumptions are valid.

The inverting op amp can be configured as an inverting adder as shown in Figure 14. The analysis is similar to that shown for the inverting amplifier, but it is easier to understand if the concept of a virtual ground is understood. Virtual is defined as "existing or resulting in effect though not in actual fact". The inverting node acts as a real ground because no voltage is developed across it, but the current path is restricted to the PC traces attached to the node. The non-inverting input of the op amp is connected to ground, therefore, if the error voltage is to be zero as was assumed, the inverting input functions as though it were tied to ground. Considering the virtual ground, the three currents flowing through R_{G1} , R_{G2} , and R_{G3} can be calculated separately. As a result, superposition can be applied to the circuit; Equation 36 calculates the gain for each independent source, and Equation 37 recombines the separate gains.

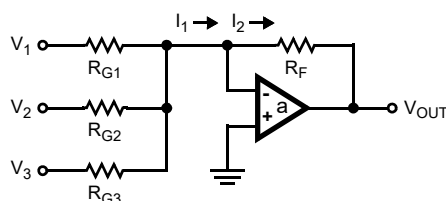


Figure 14. The Inverting Adder

$$(EQ. 36) \quad V_{01} = -V_1 \frac{R_F}{R_{G1}}, V_{02} = -V_2 \frac{R_F}{R_{G2}}, V_{03} = -V_3 \frac{R_F}{R_{G3}}$$

$$(EQ. 37) \quad V_{OUT} = V_{01} + V_{02} + V_{03} = -V_1 \frac{R_F}{R_{G1}} - V_2 \frac{R_F}{R_{G2}} - V_3 \frac{R_F}{R_{G3}}$$

$$(EQ. 38) \quad \text{If } R_F / R_{GX} = 1 \quad \text{Then;} \\ V_{OUT} = -(V_1 + V_2 + V_3)$$

10. The Non-Inverting Op Amp

Referring to [Figure 15](#), because V_E is equal to zero the voltage at point X is equal to V_{IN} . There is voltage divider formed by the feedback resistor, R_F , and the gain setting resistor, R_G , and the voltage divider input voltage is the output voltage of the op amp. [Equation 39](#) is written using the voltage divider rule, and [Equation 40](#) is obtained through algebraic manipulation. The ideal closed loop gain is again independent of the op amp gain.

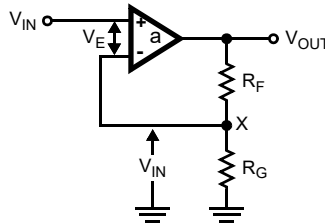


Figure 15. Non-Inverting Op Amp

$$(EQ. 39) \quad V_{IN} = \frac{V_{OUT} R_G}{R_F + R_G}$$

$$(EQ. 40) \quad \frac{V_{OUT}}{V_{IN}} = \frac{R_F + R_G}{R_G}$$

11. The Differential Amplifier

The differential amplifier schematic is given in [Figure 16](#), and the analysis is done in two parts because of the use of superposition. Two output voltages, one corresponding to each input voltage source, is calculated separately and added together. The output from V_1 is calculated in [Equation 42](#); V_+ is first calculated with the voltage divider rule, and it is substituted into the non-inverting gain equation yielding [Equation 43](#). The output from V_2 is calculated from the inverting gain equation in [Equation 44](#). The results of [Equation 43](#) and [Equation 44](#) are added in [Equation 45](#) to obtain the complete circuit equation. The output is a function of the difference between the two input voltages, this accounts for the name differential amplifier.

If a small signal is riding on a large signal, say 10mV, 0.001Hz riding on 5V_{DC}, the DC can be stripped off by putting the combined signal into the non-inverting input, and putting 5V_{DC} into the inverting input. The 5V_{DC} becomes a common mode signal (a signal which is common to both inputs), so it is rejected by the differential amplifier if $R_1 = R_3$, and $R_2 = R_4$.

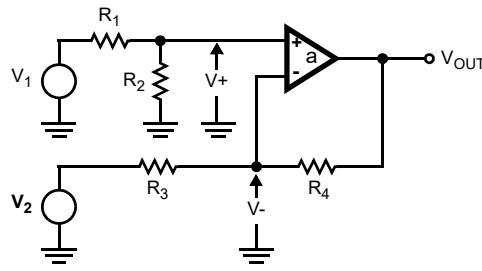


Figure 16. The Differential Amplifier

$$(EQ. 41) \quad V_{OUT} = V_{OUT_1} + V_{OUT_2}$$

$$(EQ. 42) \quad V_{OUT_1} = V_+ \left(1 + \frac{R_4}{R_3} \right) \quad V_+ = V_1 \frac{R_2}{R_1 + R_2}$$

$$(EQ. 43) \quad V_{OUT_1} = V_1 \frac{R_2}{R_1 + R_2} \left(\frac{R_3 + R_4}{R_3} \right)$$

$$(EQ. 44) \quad V_{OUT_2} = V_2 \left(-\frac{R_4}{R_3} \right)$$

$$(EQ. 45) \quad V_{OUT} = V_1 \frac{R_2}{R_1 + R_2} \left(\frac{R_3 + R_4}{R_3} \right) - V_2 \frac{R_4}{R_3}$$

If $R_1 = R_3$, and $R_2 = R_4$

$$(EQ. 46) \quad V_{OUT} = (V_1 - V_2) \frac{R_4}{R_3}$$

This effect could be accomplished through the use of a coupling capacitor, but because the frequency of the signal is so low the capacitor value and size would be too big. The differential amplifier also rejects AC common mode signals. Data transmission schemes often use twisted pairs for the interconnections so that any noise coupled on the lines will be common mode. Differential amplifiers are used as receivers in this data transmission scheme because they reject the common mode noise while amplifying the signal.

12. T Networks in the Feedback Path

Putting a T network in the feedback path as shown in [Figure](#) complicates the analysis, but offers the advantage of high closed loop gain coupled with low value feedback resistors. This configuration is also useful for some filter configurations. Thevenin's theorem is applied as shown in [Figure 18](#). Look into R_4 from X, Y and calculate the Thevenin equivalent voltage and resistance, and redraw the circuit as shown in [Figure 18](#). The inverting gain can now be calculated in the normal manner using the algebraic simplification shown in [Equation 48](#).

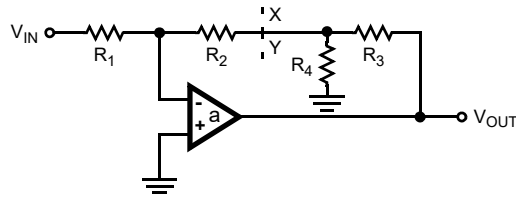


Figure 17. T Network in The Feedback Path

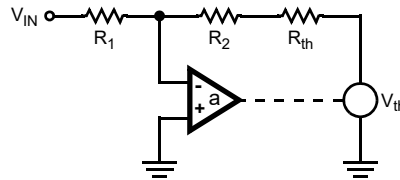


Figure 18. Thevenin Analysis of T Networks in the Feedback Path

$$(EQ. 47) \quad V_{th} = \frac{V_{OUT} R_4}{R_3 + R_4} \quad R_{th} = R_3 \parallel R_4 \quad -\frac{V_{th}}{V_{IN}} = \frac{R_2 + R_{th}}{R_1}$$

$$(EQ. 48) \quad -\frac{V_{OUT}}{V_{IN}} = \frac{R_2 + R_{th}}{R_1} \frac{R_3 + R_4}{R_4} = \frac{R_2 + \frac{R_3 R_4}{R_3 + R_4}}{R_1} \frac{R_3 + R_4}{R_4}$$

$$= \frac{R_2 + R_3 + \frac{R_2 R_3}{R_4}}{R_1}$$

13. Video Amplifiers

All op amps are the same because the ideal closed loop equations are identical. The two big classifications of op amps are voltage feedback and current feedback. The type of feedback is not the only difference between these op amps. The internal circuit configurations are dramatically different so that recommended reference #1 dwells on voltage feedback while reference #2 dwells on current feedback. Whenever an op amp is used in a high frequency circuit such as a video amp there is a strong likelihood that it will be a current feedback op amp. Again, the closed loop ideal gain equations are identical for voltage and current feedback op amps.

In [Figure 19](#), R_{IN} is usually the terminating resistance for the input cable, and it is usually 50Ω or 75Ω. R_M is the matching resistance for the cable being driven, and R_T is the terminating resistance for the driven cable. R_T is often shown here for gain calculations while it is physically placed at the cable end. Using [Equation 49](#), we see that when $R_G = R_F$ and $R_M = R_T$, the overall circuit gain is one.

$$(EQ. 49) \quad \frac{V_{OUT}}{V_{IN}} = \frac{R_F + R_G}{R_G} \frac{R_T}{R_M + R_T}$$

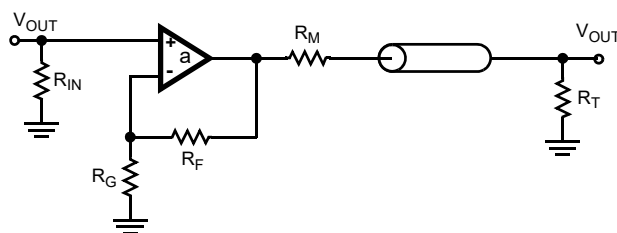


Figure 19. A Typical Video Amplifier

14. AC Theory

The emphasis here is on capacitors because they are responsible for the vast majority of AC effects. The capacitor has an impedance and a phase shift both of which are a function of frequency. Although it is paramount in stability calculations, the phase shift is neglected because you can obtain a reasonable understanding of circuit performance by considering the impedance. Referring to [Equation 50](#) it is apparent that when the frequency is very high, $s = j\omega$ is very high, so the capacitor impedance, X_C , is very low. The converse happens when the frequency is very low.

The key to this section of AC theory is that high frequency means low capacitive impedance, and low frequency means high capacitive impedance. At $F = \infty$, $X_C = 0$, and at $F = 0$, $X_C = \infty$. At intermediate values of frequency the capacitive impedance must be calculated with the assistance of [Equation 50](#).

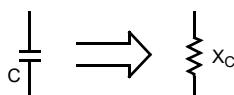


Figure 20. Capacitor Impedance

(EQ. 50) $X_C = \frac{1}{sC} = \frac{1}{j\omega C}$ where $s = j\omega$ and $j = \sqrt{-1}$

15. Op Amp Circuits Containing Capacitors

Referring to [Figure 21](#), when $F = 0$, $X_C = \infty$ so the gain, $G = -R_F/R_G$. When $F = \infty$, $X_C = 0$ then $G = 0$. The gain starts off high and decreases to zero at very high frequencies. Often C_F is an unwanted stray capacitor that yields an undesirable effect; namely, the circuit loses high frequency performance.

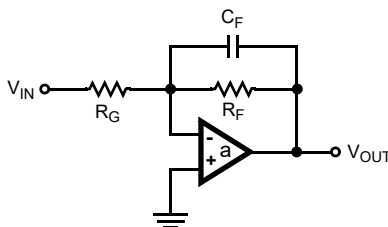
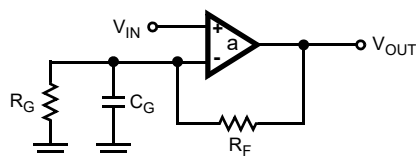


Figure 21. Low Pass Filter

A high pass filter is shown in [Figure 22](#). At $F = 0$ the gain is $(R_F + R_G)/R_F$, and at high frequencies the gain tries to approach the op amp gain, a . Sometimes the stray input capacitance forms this circuit, and the result is unwanted peaking or overshoot because the capacitor phase shift tends to make the circuit unstable.

**Figure 22. High Pass Filter**

This general method is useful for analyzing the performance of op amp circuits which have capacitors. Depending on where they are connected the capacitors can stabilize or destabilize the op amp, but they always shape the transfer function in the frequency domain.

16. Conclusion

With algebra, the basic laws of physics, and the basic circuit laws are adequate to gain an understanding of op amp circuits. By applying these tools to various circuit configurations it is possible to predict performance. Also, further in-depth knowledge is required to do op amp design, and there are many sources where this knowledge can be obtained.

17. Revision History

Revision	Date	Description
4.00	Aug 25, 2026	Applied latest template. Added Revision History section.
1.00	May 2002	Initial release

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.