

Application Note Atmel SAMA5D3 Power Management with DA9061/2 AN-PM-067

Abstract

The Dialog DA9061 and DA9062 provide cost-effective power management for the Atmel® SMART SAMADx series of microprocessors. This application note describes the SAMA5D3 and DA9061 interface based on the Atmel SAMA5D3 Xplained Evaluation Kit.



Contents

Αb	bstract	1
Сс	ontents	2
Fiç	gures	2
Та	ables	2
1	Terms and Definitions	3
2	References	3
3	Introduction	4
4	Atmel SAMA5D3 Power Requirements	4
5	Interconnections Between DA9061/2 and SAMA5D3	4
6	Evaluation	6
	6.1 Optimised Low Power Operation	7
7	Ordering Information	7
8	Conclusions	7
Re	evision History	7
Fi	igures	
	gure 1: DA9061 and SAMA5D3 Interconnectsgure 2: DA9061 Start-Up Power Sequence	
Ta	ables	
Ta Ta	able 1: Power requirements of the SAMA5D3 and Xplained Evaluation Kit	5 5



1 Terms and Definitions

DVC Dynamic Voltage Control MPU Microprocessor Unit

OTP One-Time Programmable (memory)

PFM Pulse Frequency Modulation

PMIC Power Management Integrated Circuit

SAM SMART Atmel Microcontroller

2 References

- [1] DA9062, Datasheet, Dialog Semiconductor
- [2] DA9061, Datasheet, Dialog Semiconductor
- [3] 'SAMA5D3 Series', Atmel-11121E-ATARM-SAMA5D3-Series-Datasheet_02-Feb-15, Atmel
- [4] SAMA5D3 Xplained User Guide, Atmel-11269C-ATARM-SAMA5D3-Xplained-XPLD-User Guide 03-Oct-14, Atmel



3 Introduction

The Dialog DA9061 and DA9062 provide cost-effective power management of the Atmel SMART SAMA5D3 series of MPUs. Benefits of the Dialog PMIC solutions include:

- Provides the lowest power consumption in all system operation modes
- Improved regulator efficiencies
- Integrated internal and external safety features such as die temperature supervision, voltage supervision and watchdog
- High buck switching frequency enables low profile (mostly ≤1 mm), ultra-small external components
- Flexible power rail sequencing adaptable to any application

This document describes the interconnections required and the power supply sequence. The PMIC configuration was evaluated using an Atmel SAMA5D3 Xplained Evaluation Kit.

4 Atmel SAMA5D3 Power Requirements

For reliable operation, the SAMA5D3 processors require precise power management of the system supplies as listed in Table 1.

Table 1: Power requirements of the SAMA5D3 and Xplained Evaluation Kit
--

System Rail	Range /V	Nominal /V	Current /A
VDDCORE	1.10-1.32	1.2	0.35
VDDIODDR (DDR2)	1.70–1.90	1.8	0.05
VDDIODDR (LPDDR2)	1.14–1.32	1.2	0.03
VDDIOM	1.65–1.95	1.8	0.03
VDDIOM	3.00-3.60	3.3	0.03
VDDIOP	1.65–3.60	3.3	0.03
VDDANA	3.00–3.60	3.3	-
VDDFUSE	2.25–2.75	2.5	0.05

5 Interconnections Between DA9061/2 and SAMA5D3

The DA9061 has sufficient regulators for powering the SAMA5D3 Xplained Evaluation Kit. A recommended mapping is shown in Table 2. The evaluation kit is configured with several system rails driven from a single PMIC regulator. For example, VDDCORE, VDDPLLA, and VDDUTMIC are tied together. The DA9062 can be used instead of the DA9061 where a system requires additional power rails. Compared with the DA9061, the DA9062 has an extra buck converter, dual-phase buck capability, DDR VTT supply capability, real-time clock and coin cell charger.

The sequence shown in Table 2 retains the default used by the Xplained Evaluation Kit and meets the requirements of the MPU in that VDDCORE, VDDUTMIC and VDDPLLA must power up ≥1 ms after other rails. To meet the requirements of the SAMA5D3 datasheet, the DA9061/2 nRESET line is released ≥1 ms after all rails have reached their target voltage. The completed sequence is shown in Figure 2, with nRESET being released on the edge coincident with POWER_END. The GPIO0(WKUP) RISE and FALL generates an MPU wake-up pulse.



Table 2: Mapping of DA9061/2 to SAMA5D3 Xplained Evaluation Kit Supplies

System Rail	Nominal voltage /V	Power-up sequence	DA9062 regulator	DA9061 regulator
VDDCORE, VDDPLLA, VDDUTMIC	1.2	3	Buck 1	Buck 1
VDDIODDR (DDR2) (Note 1)	1.8	2	Buck 4	Buck 3
VDDIOM (Note 2)	3.3	1	Buck 3	Buck 2
VDDIOP0, VDDIOP1, VDDUTMII	3.3	1	Buck 3	Buck 2
VDDANA	3.3	not sequenced (software controlled)	LDO2	LDO2
VDDFUSE	2.5	not sequenced (software controlled)	LDO3	LDO3

Note 1 VDDIODDR = 1.2 V for LPDDR2

Note 2 VDDIOM can optionally be 1.8 V when driven from a separate DA9061/2 regulator.

The SAMA5D3 Xplained Evaluation Kit was used as a reference design for signal mapping between MPU and PMIC. Suggested interconnects are provided in Table 3 and illustrated in Figure 1.

Table 3: Xplained Evaluation Kit Signal Mapping to DA9061/2

Evaluation Kit System Line	DA9061/2 line
5V_MAIN	VSYS
NRST	nRESET (O/P - open drain)
PC31	nIRQ (O/P - open drain)
SHDN	nRESETREQ (level triggered)
WKUP (nPBSTAT)	GPIO0 (GPO; push-pull; sequenced low-high when powering-up to ACTIVE state)
SDA	SDA
SCL	SCL
nPBPIN	nONKEY (configured with short debounce to ensure the wakeup FET input works): Requires addition of pull-up to VSYS.
-	VDDIO (Note 3)

Note 3 VDDIO can be supplied from DA9061 Buck 2 at 3.3 V (DA9062 Buck 3).



 


Figure 1: DA9061 and SAMA5D3 Interconnects

 


Figure 2: DA9061 Start-Up Power Sequence

6 Evaluation

A SAMA5D3 Xplained Evaluation Kit was successfully powered using a DA9061. The system was verified with its default boot configuration (with the processor mainly idle) and with a stress script to force the processor duty up to 100%. The tests were performed with the DA9061 bucks set in Auto mode. (In this test the bucks were running in PFM mode because of the low supply currents. The Dialog bucks are configured in Auto mode to ensure efficiency is optimised under all system load

Application Note Revision 1.1 17-Feb-2022



conditions.) The total board current, I_{VBUS}, was measured at the USB input. This is the current supplying 5V_MAIN and is also the PMIC supply, VSYS.

Table 4: SAMA5D3 Xplained with DA9061 Evaluation Results

Parameter Measured DA9061 current /mA		DA9061 current /mA
	Standard Boot	Boot with MPU Stress Script
Ivbus	150	177
Івискз	31	60
Івиск1	57	109
I _{BUCK2}	124	124

6.1 Optimised Low Power Operation

The above evaluation results were achieved without optimising buck auto-thresholds, inductors, PCB layout and so forth. Dialog's PMIC architecture allows the optimised configuration to be programmed into the OTP so that the system automatically operates from startup with optimal efficiency. This avoids the need for software writes that are otherwise needed to place a PMIC into a power-saving mode.

Dialog PMICs also include dynamic voltage control (DVC) for the buck regulators. This feature allows setting of the regulator output voltage to a minimum value depending on the corresponding processor conditions (such as Active, Idle, Ultra Low-power and Backup). The DVC feature allows optimising of the power dissipation based on the actual processor speed and enables optimised low power operation. Such a scheme is implemented with minimal software overhead.

The DA9061/2 LDOs support switching between two pre-configured output voltages, VLDOx_A and VLDOx_B, either via software control or GPIO control. This allows lowering of the peripheral supply voltage when in suspend mode. Additionally, an LDO SLEEP mode can be linked to either the A or B settings. These features allow further reductions in system power dissipation.

7 Ordering Information

Devices with OTP configured for SAMA5D3 systems are orderable as standard variants:

DA9061-50

DA9062-50

Refer to the product datasheets for general ordering information. Please contact your Dialog Sales representative for further details on OTP variants.

8 Conclusions

The Dialog DA9061 and DA9062 support power management of the SAMA5D3 series of MPUs. Standard OTP variants are available from Dialog which have been verified in an Atmel SAMA5D3 Xplained Evaluation Kit.

Revision History

Revision	Date	Description
1.1	17-Feb-2022	File was rebranded with new logo, copyright and disclaimer
1.0	11-Feb-2016	Initial version.



Status Definitions

Status	Definition
DRAFT	The content of this document is under review and subject to formal approval, which may result in modifications or additions.
APPROVED or unmarked	The content of this document has been approved for publication.

RoHS Compliance

Dialog Semiconductor's suppliers certify that its products are in compliance with the requirements of Directive 2011/65/EU of the European Parliament on the restriction of the use of certain hazardous substances in electrical and electronic equipment. RoHS certificates from our suppliers are available on request.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu, Koto-ku, Tokyo 135-0061, Japan www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.