

RBK04U04GN

BMS Shunt-less Short-circuit

About this document

This document will discuss the importance of the Renesas BMS Shunt-Less short circuit test for battery management systems (BMS). This will demonstrate some functionality tests with the internal BMS evaluation board.

Target Device

MOSFET: RBK04U04GN

Contents

1.	Introduction.....	2
1.1	Overview.....	2
2.	Short Circuit Test & Detection.....	3
2.1	Battery pack short circuit durability test.....	3
2.2	Over-current Detection	4
2.3	Short-circuit Current Detection	4
3.	MOSFET Introduction	5
3.1	Product Outline.....	5
3.2	Introduction for RBK04U04GNS.....	6
3.2.1	Dual MOSFET Topology	6
3.2.2	Benefits.....	6
4.	Conclusion.....	6
	Revision History.....	7

1. Introduction

1.1 Overview

Short-circuit current detection refers to the ability of a circuit or system to identify and respond to the occurrence of a short circuit promptly and effectively. Detecting short circuits is crucial in preventing damage to components, ensuring safety, and maintaining reliable operation of electrical and electronic devices.

In this application note, we will discuss the short-circuit test using the Sense MOS with the Renesas BMS shunt-less evaluation board. For a detailed overview of the evaluation board and its specifications, please refer to the related application note available on the Renesas website (R07AN0021EJ0100).

Below is the diagram of the EVB that will be used for the short-circuit test measurements.

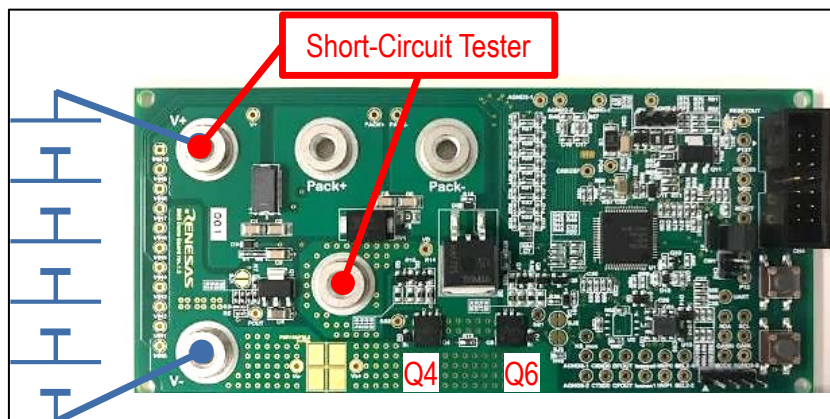


Figure 1-1 Renesas BMS Eva. board “WS (0)”

2. Short Circuit Test & Detection

This section highlights the features of the evaluation board that are part of the Renesas solution. It is important to ensure that these features function correctly to protect both the user and the battery pack from potential hazards. The key features include short circuit testing of the evaluation board and battery pack, over-current detection, and short-circuit current detection. These functions are crucial for preventing damage and ensuring safety.

2.1 Battery pack short circuit durability test

The figure below shows the short circuit test performed with the evaluation board connected to a battery pack. This test monitors the board's safety protection during a short circuit. The waveform indicates that when a short-circuit current is applied for 160 milliseconds, the battery pack voltage turns off. The voltage remains off until the short-circuit current is removed, at which point the voltage turns back on.

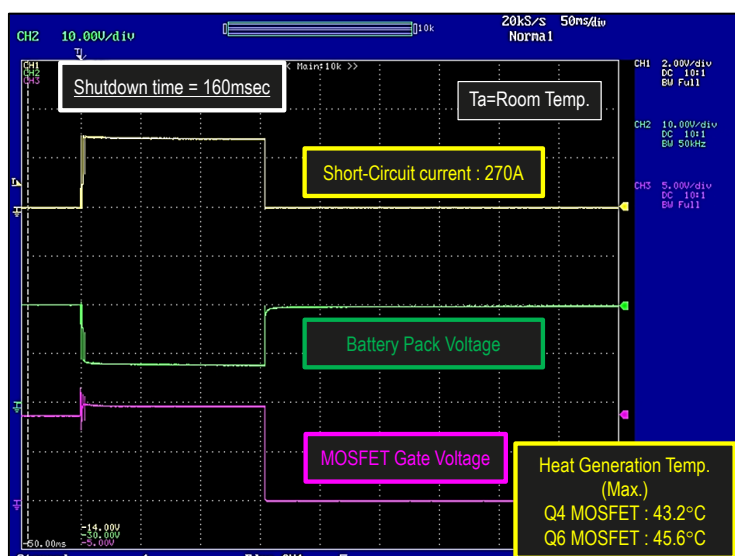


Figure 2-1 Waveform of Board Short-Circuit test

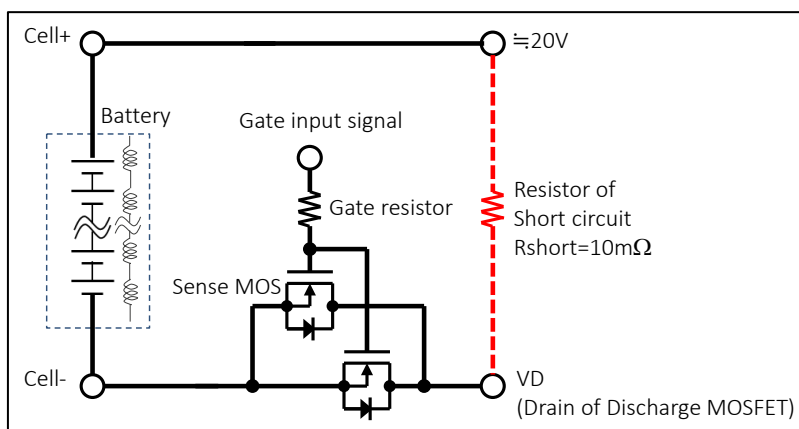


Figure 2-2 Circuits diagram of Short-Circuit test

2.2 Over-current Detection

The waveform below shows how the over-current detection works. The MOSFET responds by shutting down the operation within 0.6ms when the current exceeds the overcurrent detection point. The Load Current shuts down in 0.9ms.

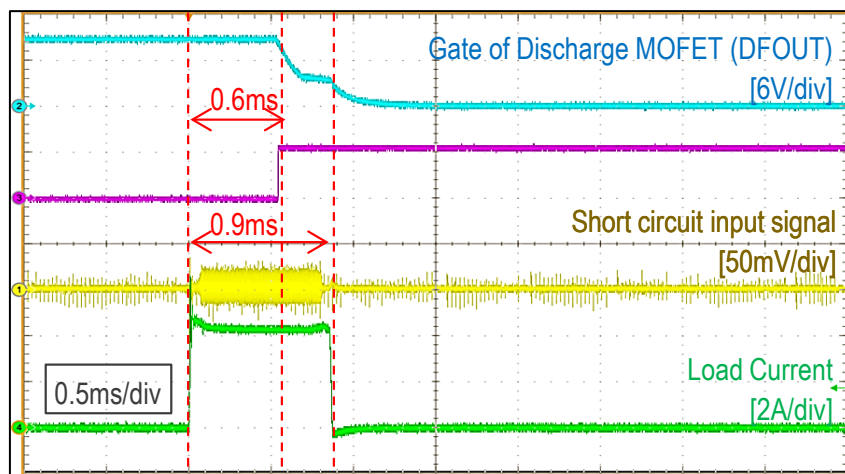


Figure 2-3 Waveform of Over-current Detection

2.3 Short-circuit Current Detection

The waveform below shows how the short-circuit current detection works. When a short-circuit signal is applied, the Sense MOS detects the current and quickly shuts down the circuit by turning off the discharge MOSFET. This happens within the short-circuit withstand time to protect the system. The system detected the short-circuit input signal by 0.1ms, the MOSFET has responded by shutting down the operation.

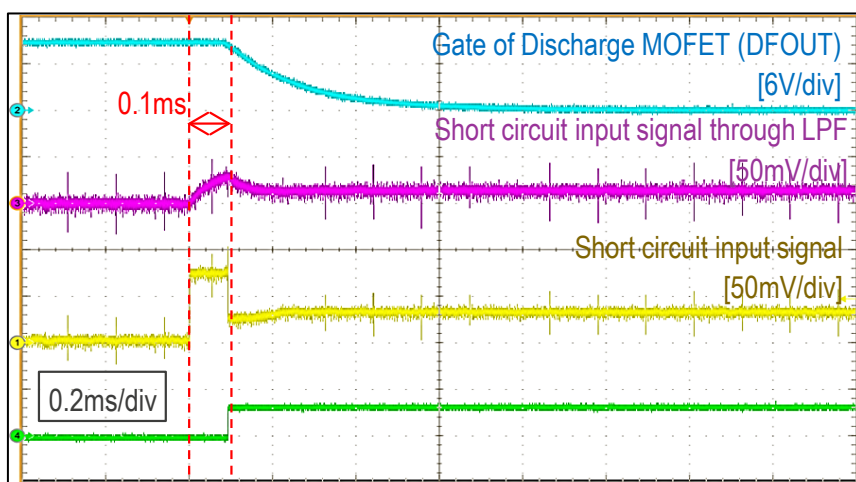


Figure 2-4 Waveform of Short-circuit current Detection

3. MOSFET Introduction

The MOSFET (RBK04U04GNS) selected for this solution is suitable for use in Li-ion battery management systems. This MOSFET has a capability of 40V with 35A N-Channel Power MOSFET.

The main reasons for selecting this MOSFET are its features:

- Low on-state resistance $R_{DS(on)}$ of 1.2m Ω typ. (at $V_{GS} = 10V$, $I_D = 18A$)
- Built-in current sensing feature, useful for:
 - Over Current Detection
 - Static current monitoring
- HSON-8 pin, surface mount package (5 x 6 mm)

This MOSFET targets mid-voltage products such as power tools, cleaners, e-bikes, drones, and other industrial products. It is suitable for use as a low-side protection switch for BMS, BLDC inverters, and DC-DC inverters.

3.1 Product Outline

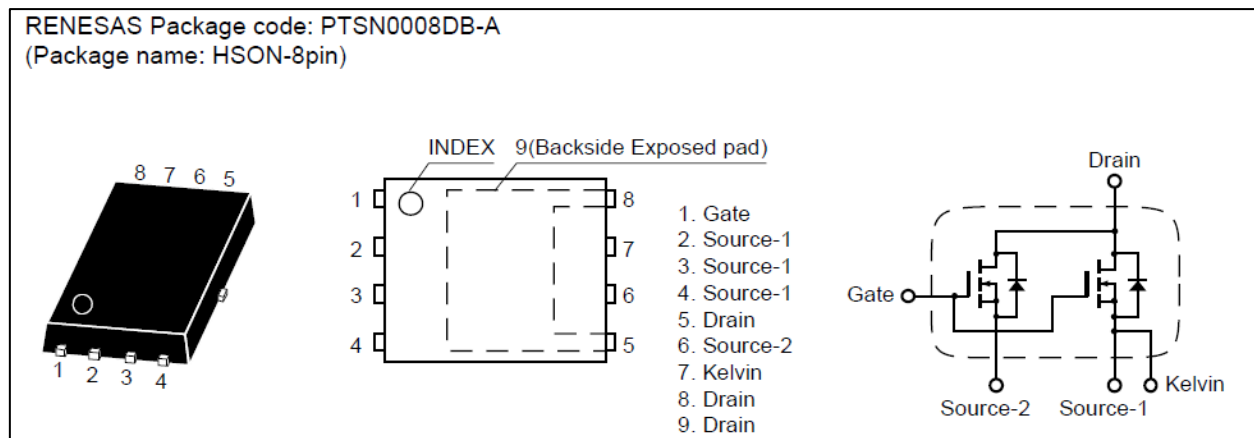


Figure 3-1 RBK04U04GNS MOSFET outline

3.2 Introduction for RBK04U04GNS

MOSFETs are commonly used in power systems to control switching and current flow. They can also function as current sensors by detecting the voltage drop across the drain-source terminals (V_{DS}), which is directly related to the current flowing through the MOSFET, based on its internal resistance, $R_{DS(on)}$.

In current-sensing applications, MOSFETs play two key roles:

- **Switching Role:** MOSFETs control current flow to the load, acting as a switch between the power supply and the load.
- **Sensing Role:** MOSFETs can provide a voltage signal that reflects the current flowing through them by leveraging the voltage drop across the drain and source terminals.

3.2.1 Dual MOSFET Topology

The RBK04U04GNS MOSFET incorporates a dual MOSFET topology with Kelvin sensing pins to improve current-sensing accuracy. This design integrates two MOSFETs within a single package, which helps reduce conduction losses and enhance current measurement precision.

The Kelvin pin is connected to the source and ground, it is used to provide a low-resistance, isolated path for sensing the voltage drop across the MOSFET. This setup allows for precise current measurement, which is important for managing short-circuit conditions and power control.

This dual MOSFET setup makes the RBK04U04GNS ideal for applications requiring high accuracy, such as motor control system and automotive power application.

3.2.2 Benefits

- **Reduced Component Count:** By integrating the switching and sensing functions into a single package, the overall system design is simplifying and reducing the need for additional components.
- **Improved Accuracy:** The integration of dual MOSFETs allows for better control over device characteristics and improving efficiency in current-sensing applications by eliminating parasitic resistances.

By integrating a dual-source configuration with Kelvin pins, the RBK04U04GNS offers a highly efficient and accurate solution for power-sensitive applications where precision is critical.

4. Conclusion

The short-circuit and overcurrent detection in the battery management system (BMS) proved to be highly effective during testing. The results demonstrated that the system can reliably detect short circuits and overcurrent conditions, triggering the shutdown of the MOSFET (RBK04U04GNS) to prevent potential damage to the battery pack and ensure user safety.

The built-in sensing feature of the MOSFET simplified the design and contributed to the overall performance, showing that the integration of these features helps reduce the design complexity and cost while maintaining a high level of protection.

Revision History

Rev.	Date	Description	
		Page	Summary
1.00	10.10.2024	-	First edition

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.

7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:

www.renesas.com/contact/.