

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

CHARACTERISTICS AND USAGE OF μ PC1228HA

1. OUTLINE OF μ PC1228HA

μ PC1228HA is a silicon monolithic integrated circuit including preamplifiers for two channels which is specifically designed for a car stereo set.

This IC has a high open loop voltage gain coupled with low noise and low distortion characteristics. A design allowing a resistor with high resistance to be used in the NAB feedback circuit achieves more excellent characteristics than conventional ones even when a capacitor with low capacitance is employed in the feedback circuit. This results in reduction of the area for mounting components and cost. 8-lead SIP construction employed assures high workability.

Characteristics and usage of this IC are described below.

2. FEATURES OF μ PC1228HA

- 1) Preamplifiers for two channels accommodated in an 8-lead SIP, which ensures compact size of a set and labor saving.
- 2) A high open loop voltage gain of 100 dB(TYP.) together with a design allowing a resistor with high resistance value to be used in the NAB feedback circuit which achieves excellent characteristics compared with conventional ICs even when a capacitor of low capacitance is used.
- 3) Equivalent Input Noise Voltage is as low as $1.1 \mu\text{V}$ (TYP.)($R_G=2.2 \text{ k}\Omega$, NAB)
- 4) Distortion level is as low as 0.05 % (TYP.). ($V_O=0.3 \text{ V}$)
- 5) Wide dynamic range: $V_{OM}=2.0 \text{ V}$ (TYP.)(T.H.D.=1 %).
- 6) Because of DC current output available, switching circuit from a tape player to a car radio or vice versa is made simplified. $I_{ODC}=1.0 \text{ mA}$ (MAX.)
- 7) The IC can drive a load with low impedance: $R_L=1 \text{ k}\Omega$ (MIN.)

3. EQUIVALENT CIRCUIT OF μ PC1228HA

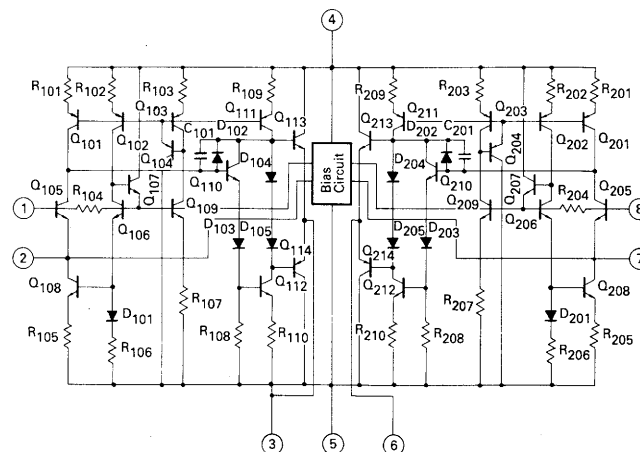


Fig.1 Equivalent Circuit

4. RATINGS OF μ PC1228HA

4.1 ABOLUTE MAXIMUM RATINGS ($T_a = 25\text{ }^\circ\text{C}$)

Supply Voltage	V_{CC}	18	V
Package Dissipation	P_D	270*	mW
Operating Temperature	T_{opt}	-30 to +75	$^\circ\text{C}$
Storage Temperature	T_{stg}	-40 to +125	$^\circ\text{C}$

* $T_a = 75\text{ }^\circ\text{C}$

4.2 RECOMMENDED CONDITIONS ($T_a = 25\text{ }^\circ\text{C}$)

Operating supply Voltage	V_{CC}	13.2	V
Supply Voltage Range	V_{CC}	6 to 16	V
Operating Ambient Temperature	T_a	-30 to +75	$^\circ\text{C}$
Load Impedance	R_L	10 k Ω TYP.	

4.3 ELECTRICAL CHARACTERISTICS ($T_a = 25\text{ }^\circ\text{C}$, $V_{CC} = 10\text{ V}$, $f = 1\text{ kHz}$, $R_L = 10\text{ k}\Omega$)

CHARACTERISTIC	SYMBOL	MIN.	TYP.	MAX.	UNIT	TEST CIRCUIT	TEST CONDITIONS
Quiescent Current	I_{CC}	2.5	3.3	4.8	mA	(1)	$V_{in} = 0$
Open Loop Voltage Gain	A_{VO}	90	100		dB	(1)	$V_O = 0.3\text{ V}$, $f = 100\text{ Hz}$
Voltage Gain	A_V		40		dB	(2)	$V_O = 0.3\text{ V}$, NAB
Maximum Output Voltage	V_{OM}	1.0	2.0		V	(2)	T.H.D. = 1 %, ANB
Total Harmonic Distortion	THD		0.05	0.3	%	(2)	$V_O = 0.3\text{ V}$, NAB
Input impedance	R_{in}	50	100		k Ω	(2)	
Equivalent Input Noise Voltage	V_{nin}		1.1	1.7	μV	(3)	$R_G = 2.2\text{ k}\Omega$, NAB
Cross Talk	CT	-50	-65		dB	(4)	$V_O = 1\text{ V}$, (The other channel $V_{in} = 0$, $R_G = 2.2\text{ k}\Omega$)
Channel Balance	Ch.B	-0.3	0	+0.3	dB	(4)	$V_O = 0.3\text{ V}$

5. PACKAGE DIMENSIONS

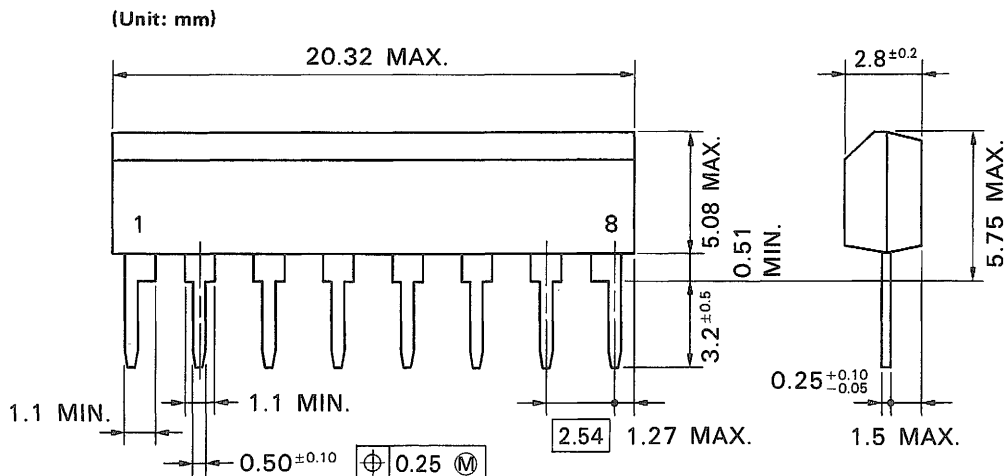


Fig.2 Package Dimensions

P8HA-254B

6. TEST CIRCUITS

6.1 I_{CC}, A_{VO} TEST CIRCUIT (for Ch.1)

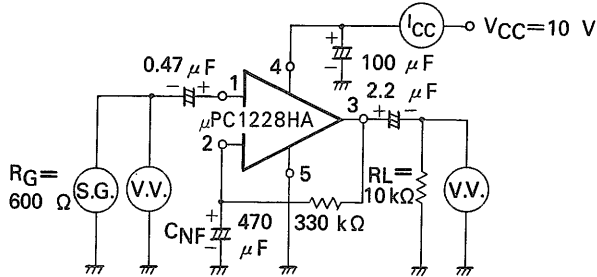


Fig.3 Test Circuit 1

6.2 A_V, V_{OM}, THD, R_{in} TEST CIRCUIT (for Ch. 1)

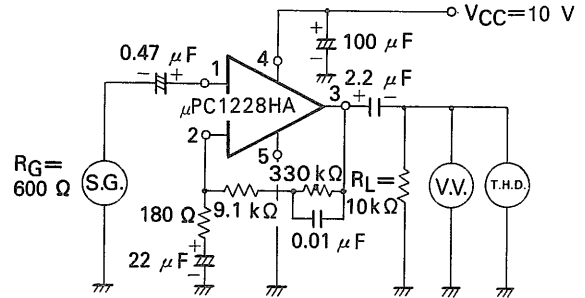


Fig.4 Test Circuit 2

6.3 V_{nin} TEST CIRCUIT (for Ch. 1)

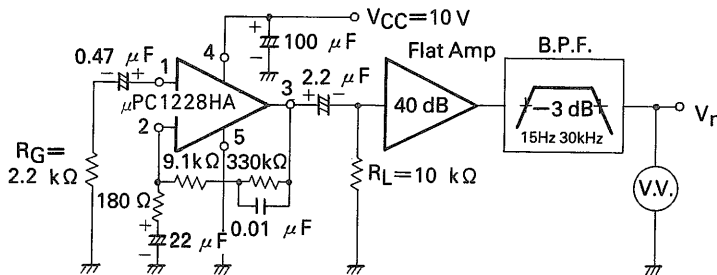


Fig.5 Test Circuit 3

NOTE: V_{nin} is calculated by V_n and amp. gain ($A_V + 40$ dB).

6.4 CROSS TALK, CHANNEL BALANCE

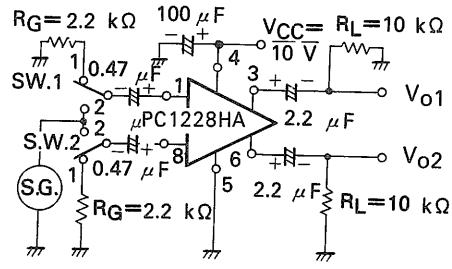


Fig.6 Test Circuit 4

NOTE 1: External components of the IC are the same as the test circuit (2).

2: Cross talk procedure

Switch position SW.1 → 2, SW.2 → 1, $20 \log V_{O2}/V_{O1}$

Switch position SW.1 → 1, SW.2 → 2, $20 \log V_{O1}/V_{O2}$

3: Channel balance

Switch position SW.1 → 2, SW.2 → 2, $20 \log V_{O1}/V_{O2}$

7. CONNECTION DIAGRAM OF μ PC1228HA

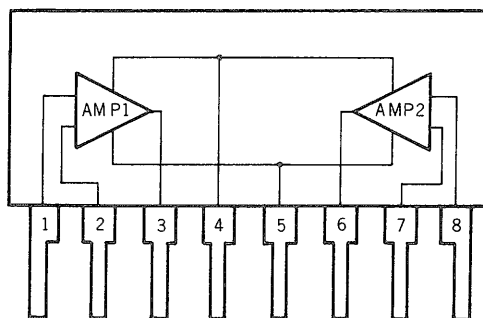


Fig.7 Block Diagram

Table 1. Pin Connection

Pin No.	Electrical connection
1	Input 1
2	Negative feed back 1
3	Output 1
4	Power supply: +V _{CC}
5	Ground
6	Output
7	Negative feed back 2
8	Input 2

8. EXPLANATION OF EXTERNAL COMPONENTS

8.1 TYPICAL APPLICATION CIRCUIT

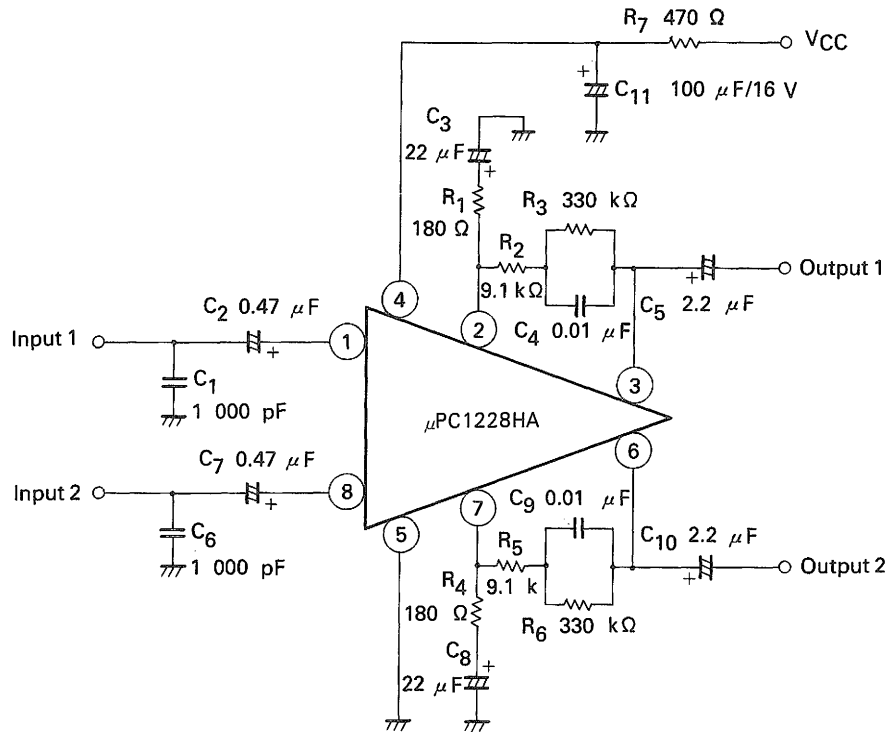


Fig.8 Typical Application Circuit

8.2 PURPOSE AND RECOMMENDED VALUES

C₁ and C₆ are used for preventing interference by external noises and self-oscillation occurring when a circuit has a signal source of high resistance and should be preferably around 1 000 pF.

C₂ and C₇ are coupling capacitors for input signals.

A preamplifier with NAB characteristics has high voltage gain for low frequency signals, and thus 1/f noises of the IC itself are emphasized as output noises: high impedance of the capacitance in low frequency results in increased output noise voltages because of the dependence of 1/f noises on signal source resistance. Therefore, impedance of the capacitance should be sufficiently lower than that of the signal source. On the other hand, C₂ and C₇ over 2.2 μF extends operation starting time. Accordingly, around 0.47 μF is desirable.

C₃ and C₈ for negative feedback circuit affect the lower cut off frequency. (See Fig.22.) As C₃ and C₈ with large capacitance also extends operation starting time, 22 μF is preferable.

The frequency response and gain of the preamplifier depends on C₄, R₁, R₂, and R₃ (or C₉, R₄, R₅, and R₆). Time constants for obtaining a standard NAB characteristics are as follows.

Table 5 Time Constans for a Standard NAB Characteristics

Time constant	Tape Speed	
	9.5 cm/s	4.75 cm/s
C ₄ (R ₂ + R ₃)	3 180 μs	1 590 μs
C ₄ R ₂	90 μs	120 μs

C_{11} is a bypass capacitor on the power supply line. It reduces ripple component by the ratio of the impedance of to R_7 . A 100 μF capacitor should be attached as close to the power supply terminal(Pin④) and GND terminal(Pin⑤) as possible. R_7 with a too high resistance value degrades the supply voltage characteristic while that with a too low resistance degrades the filtering effect, and therefore the value of around 470 Ω is recommended. C_5 and C_{10} are coupling capacitors for output signals, and should preferably be of 2.2 μF .

8.3 ELEMENTS FOR NEGATIVE FEEDBACK CIRCUIT AND DETERMINATION OF GAIN

A DC feedback current flows through negative feedback elements R_2 and R_3 (or R_5 and R_6) to provide an output voltage at the terminal ③ (⑥) which is given as follows:

$$V_{ODC} \cong (R_2 + R_3) \times 9 \times 10^{-6} + 0.7 \text{ (V)} \dots(1)$$

Consequently, the maximum output level is obtained under the supply voltage of V_{CC} by determining values of R_2 and R_3 so that the voltage V_{ODC} is $1/2 V_{CC}$. (See Fig. 20.)

$$V_{ODC} \cong 1/2 V_{CC}$$

$$\therefore R_2 + R_3 \cong (1/2 V_{CC} - 0.7) / (9 \times 10^{-6}) \text{ (\Omega)} \dots(2)$$

In addition to the above relation, however, degradation in supply voltage characteristics at low temperature should be taken into account for determining R_2 and R_3 . Usually, around 300 $\text{k}\Omega$ is suitable as the resistance value of R_3 , or around 200 $\text{k}\Omega$ when the voltage at the pin ④ is approximately 6 V. (See Fig.21.) Determination of the gain is accomplished by adjusting R_1 (or R_4) while keeping C_4 , R_2 , and R_3 (C_9 , R_5 and R_6) constant in their values. (See Fig.23.)

As for an amplifier with negative feedback applied, the gain generally follows an equation $A_V = A_{V0} / (1 + A_{V0} \beta)$.

Taking the impedance of a feedback circuit as Z ,
 $A_V = Z/R_1$ when $1 \ll A_V \ll A_{V0}$. (where $\beta = R_1 / (R_1 + Z)$)
 Therefore, R_1 is determined by $R_1 = Z/A_V$. (Where A_V and Z respectively the gain and impedance of the feedback element employed when $f = 1 \text{ kHz}$.)

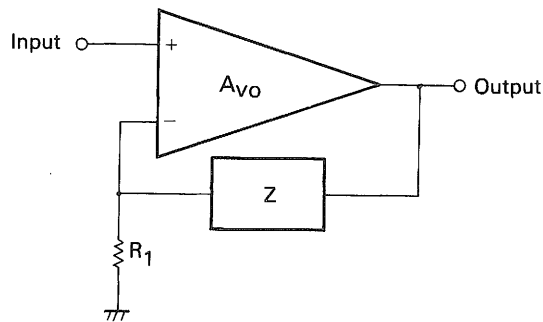


Fig.9 An Amplifier with Negative Feedback

8.4 EXAMPLES OF NEGATIVE FEEDBACK CIRCUIT

Table 3 Time Constants for NAB

Time constant	Tape Speed	9.5 cm/s	4.75 cm/s
$C_4(R_2+R_3)$		3 180 μs	1 590 μs
C_4R_2		90 μs	120 μs

(1) When the tape speed is 9.5 cm/s

Taking C_4 as $0.01 \mu\text{F}$ gives $R_2 = 9 \text{ k}\Omega$. Therefore, $R_3 = 309 \text{ k}\Omega$, $R_2 = 9.1 \text{ k}\Omega$ and $R_3 = 330 \text{ k}\Omega$ should be employed. This causes $Z = R_2 = R_3 \parallel (1/j \omega C_4) = 18.7 \text{ k}\Omega$.

(2) When the tape speed is 4.75 cm/s

Taking C_4 as $0.0047 \mu\text{F}$ gives $R_2 = 25.5 \text{ k}\Omega$ and $R_3 = 313 \text{ k}\Omega$. Therefore, $R_2 = 27 \text{ k}\Omega$ and $R_3 = 330 \text{ k}\Omega$ should be employed, which give the impedance $Z = 34.3 \text{ k}\Omega$.

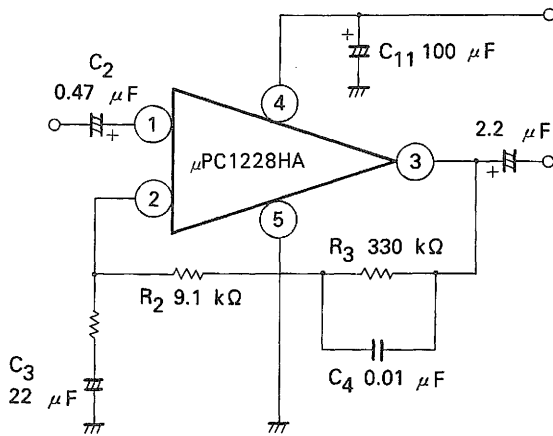


Fig.10 Example in the Case of the Tape Speed of 9.5 cm/s

A_v	35	40	45	dB
R_1	330	180	100	Ω

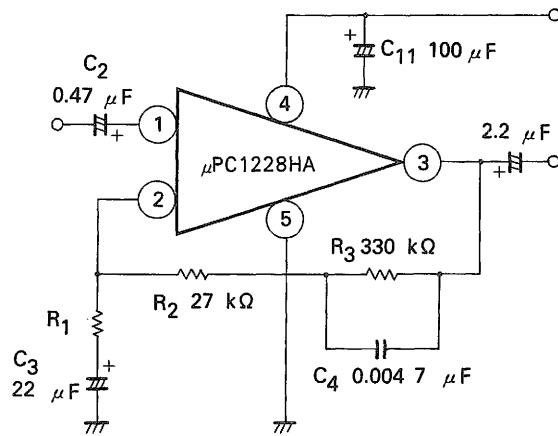


Fig.11 Example in the case of the Tape Speed of 4.75 cm/s

A_v	35	40	45	dB
R_1	620	330	180	Ω

8.5 SUMMARY

Table 4 Summary of Usage of External Components

External Components	Purpose of use	Recommended value	When smaller than recommended value	When larger than recommended value
C ₁ (C ₆)	• Protection from ignition noises, radio interference and self oscillation	1 000 pF	• Liable to be influenced by noises	• Degradation in high frequency response
C ₂ (C ₇)	• Coupling of input signals	0.47 μF	• Degradation in low frequency response • Increase in output noises	• Later start of operation
C ₃ (C ₈)	• Elimination of DC component in a feedback circuit	22 μF	• Degradation in low frequency response • Sooner start of operation	• Improvement in low frequency response • Later start of operation
R ₁ (R ₄)	• Determination of the gain of an equalizer	180 Ω	• Higher gain	• Lower gain
R ₂ (R ₅) R ₃ *(R ₆) C ₄ (C ₉)	• Determination of frequency response characteristic of an equalizer	9.1 kΩ 330 kΩ* 0.01 μF	• Higher turnover frequency * V _{OM} lowers * Supply voltage characteristic is improved	• Lower turn over frequency * V _{OM} is raised. * Supply voltage characteristic is degraded.
C ₅ (C ₁₀)	• Coupling of output signals	2.2 μF	• Degradation in low frequency response	• Improvement in low frequency response
R ₇	• Elimination of ripple components in supply voltage R ₇ should be 220 Ω or larger to secure stability when the device is connected to a power amplifier When R ₇ is lower than 100 Ω, C ₁₁ should be 220 μF or larger.	470 Ω	• Decrease in SVR Improvement in supply voltage characteristic	• Improvement in SVR • Degradation in supply voltage characteristic
C ₁₁	• Elimination of ripple component in supply voltage	100 μF	• Decrease in SVR	• Improvement in SVR

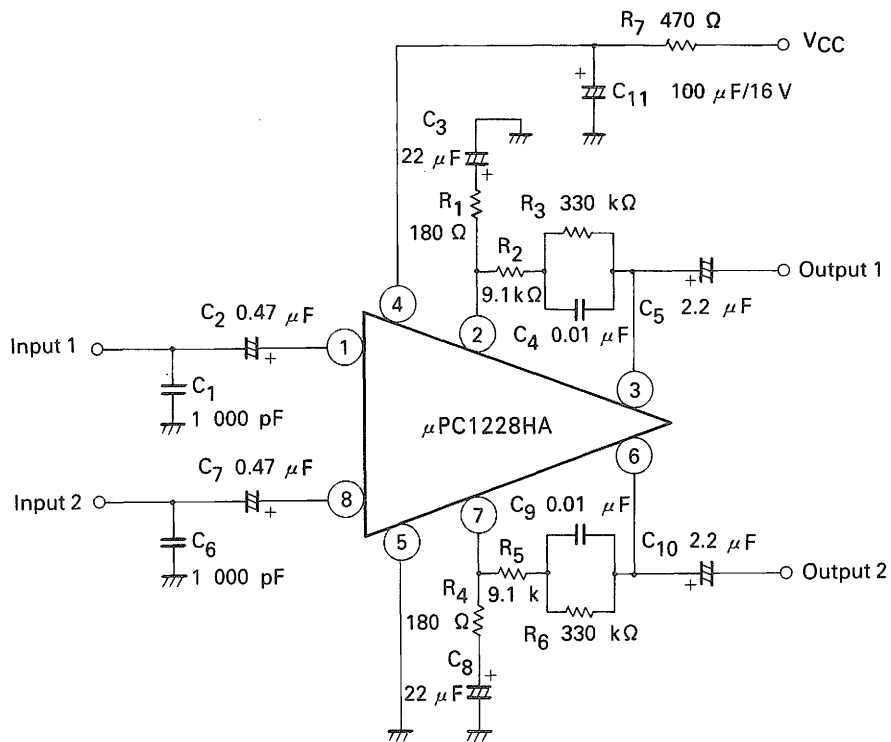


Fig. 12 External Components

9. Application to Signal Switching Circuits

The output stage of the μ PC1228HA is an SEPP circuit capable of driving a load with low impedance as well as delivering output DC current, simplifying a signal switching circuit to be connected by constituting the circuit as shown on Fig.13.

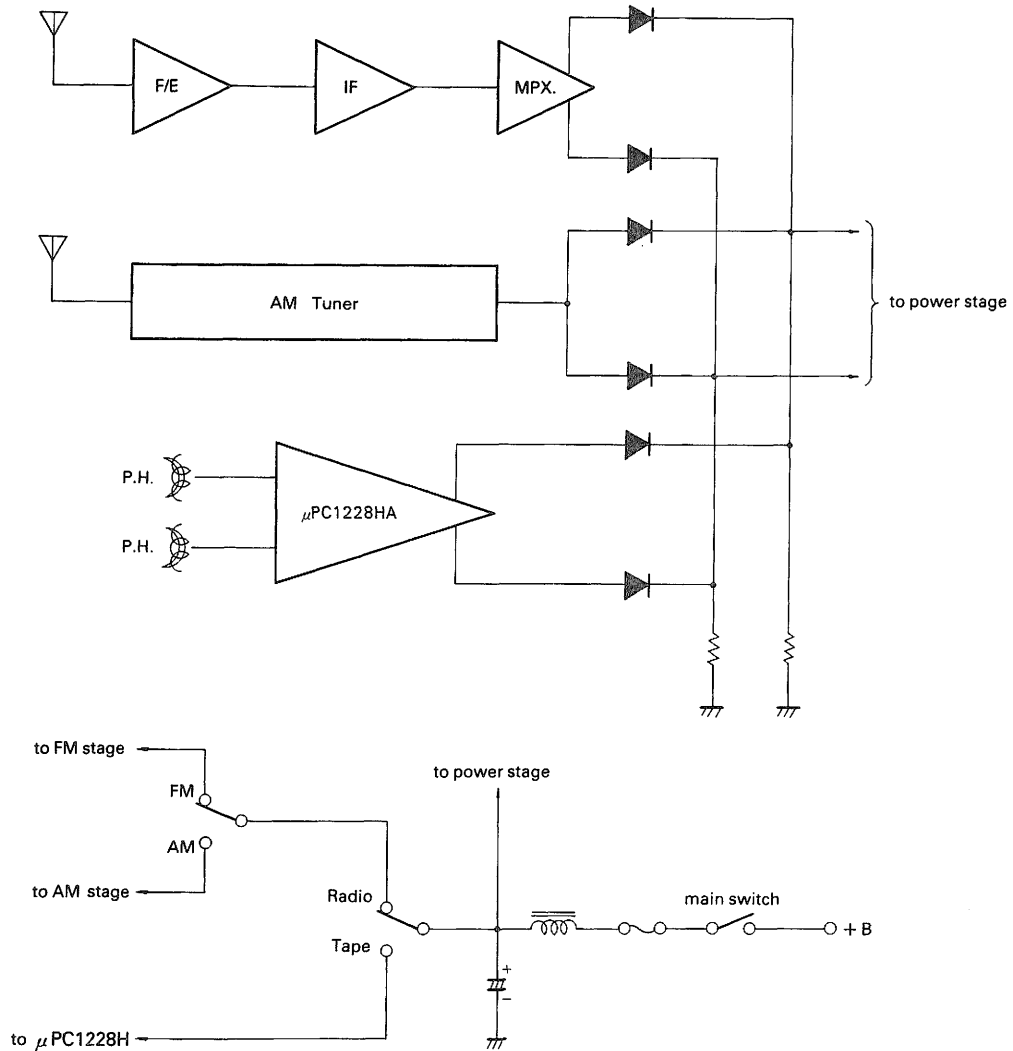


Fig.13 Signal Switching Circuit

10. TYPICAL CHARACTERISTICS

Fig.14 OUT PUT VOLTAGE vs. INPUT VOLTAGE

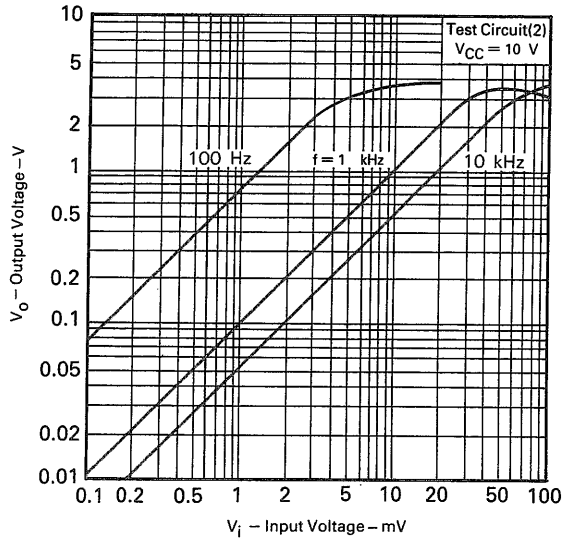


Fig.15 TOTAL HARMONIC DISTORTION vs. OUTPUT VOLTAGE

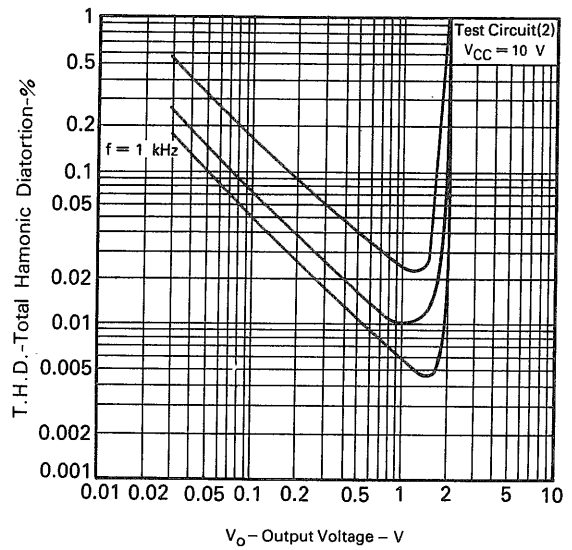


Fig.16 TOTAL HARMONIC DISTORTION vs. OUTPUT VOLTAGE

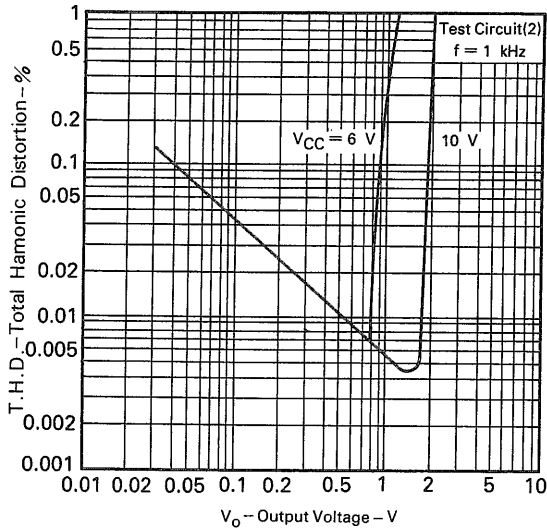


Fig.17 VOLTAGE GAIN vs. FREQUENCY

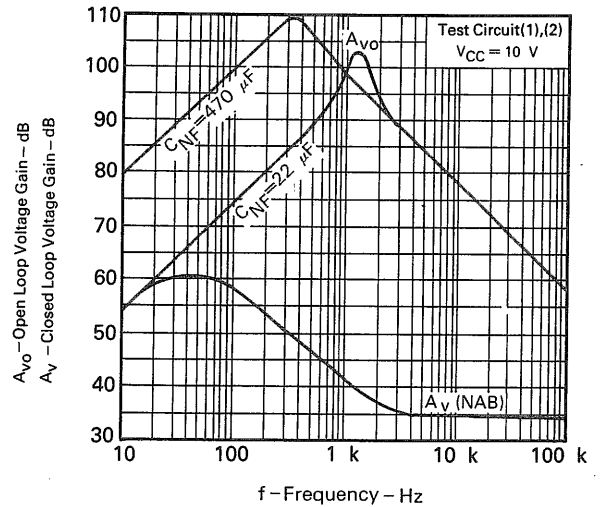


Fig.18 MAXIMUM OUTPUT VOLTAGE vs. LOAD RESISTANCE

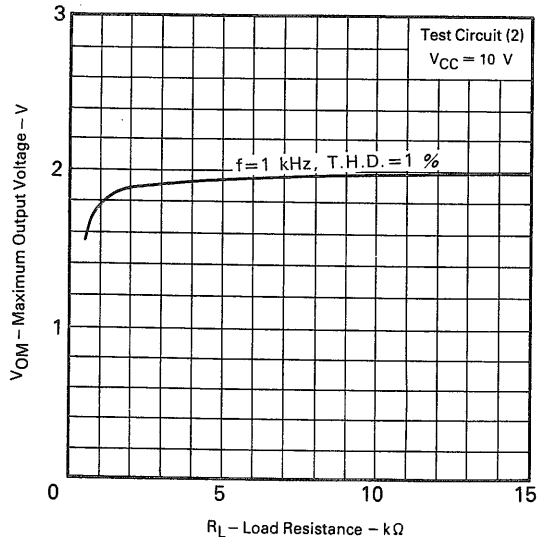


Fig.19 CIRCUIT CURRENT, MAXIMUM OUTPUT VOLTAGE, VOLTAGE vs. SUPPLY VOLTAGE

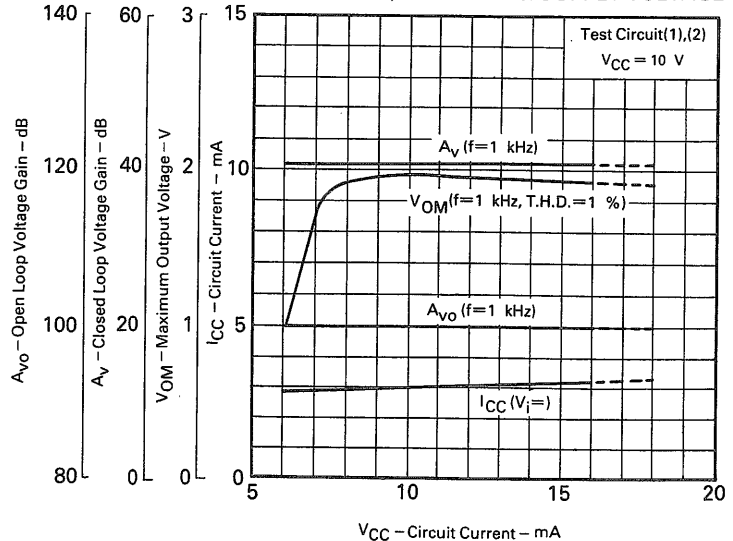


Fig.20 Maximum Output Voltage vs. Feedback Resistance

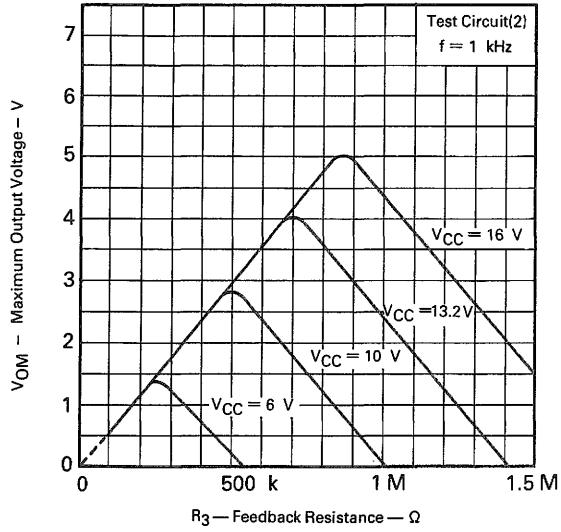


Fig.21 Maximum Output Voltage vs. Supply Voltage

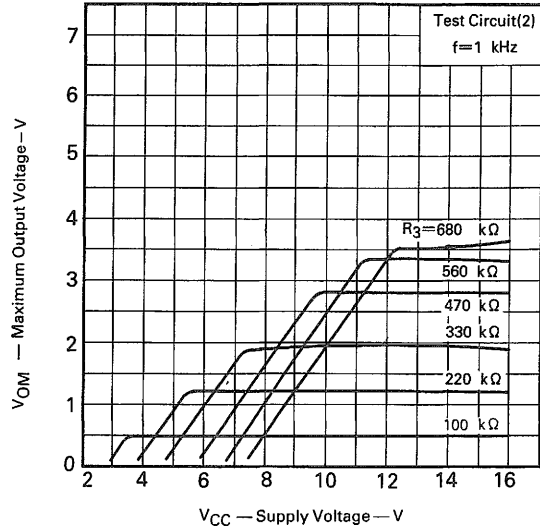


Fig.22 Voltage Gain vs. Frequency

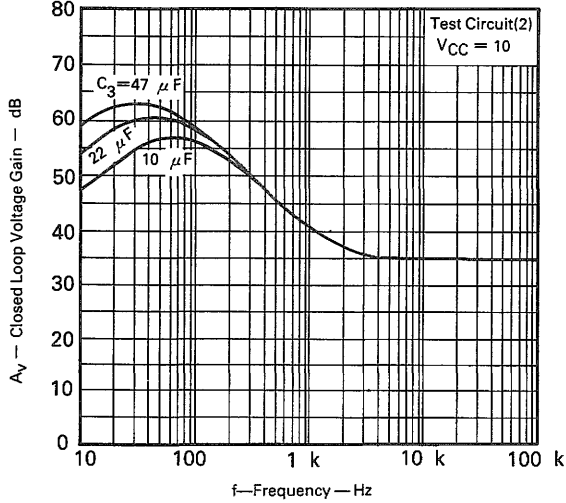


Fig.23 Voltage Gain vs. Frequency

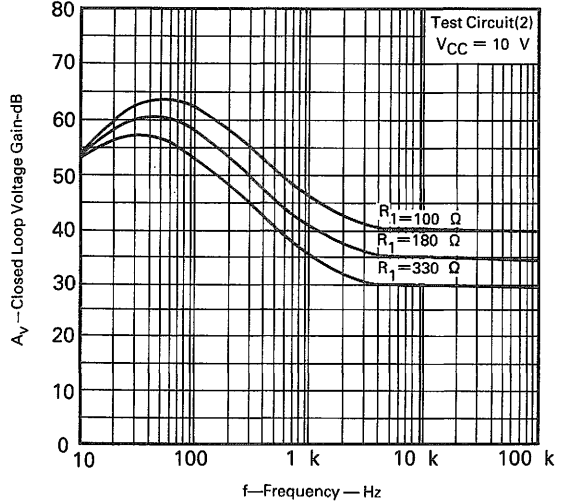


Fig.24 Equivalent Input Noise Voltage vs. Signal Source Resistance

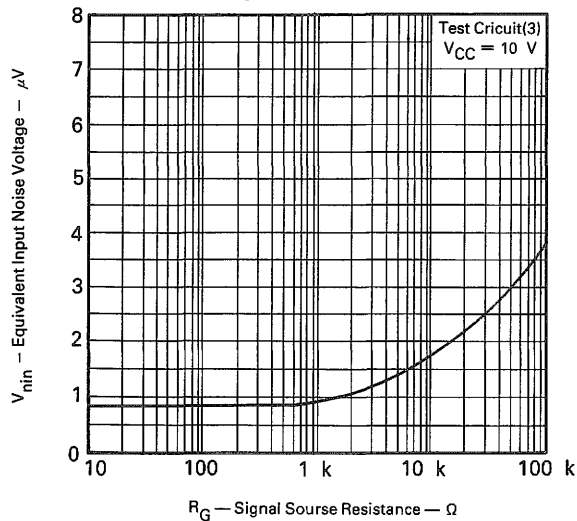


Fig.25 Cross Talk vs. Frequency

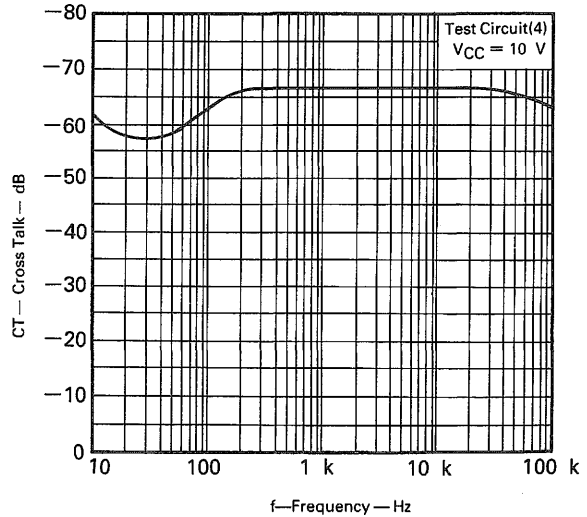


Fig.26 Open Loop Voltage Gain, Maximum Output Voltage, Circuit vs. Ambient Temperature


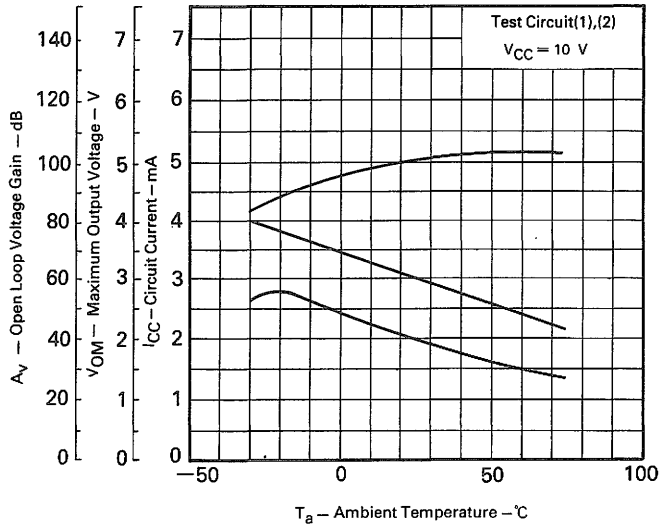


Fig.27 Maximum Output Voltage vs. Ambient Temperature

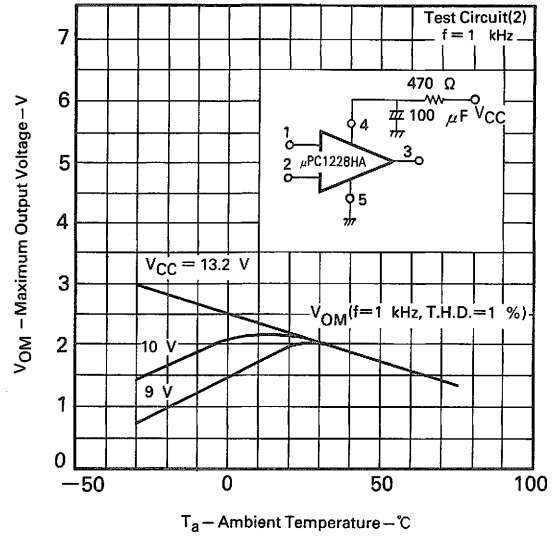

11. EXAMPLE OF APPLICATION CIRCUIT

11.1 APPLICATION 1 (NAB EQ, $V_{CC}=8\sim 17\text{ V}$, $V_{OM}=2\text{ V}$)


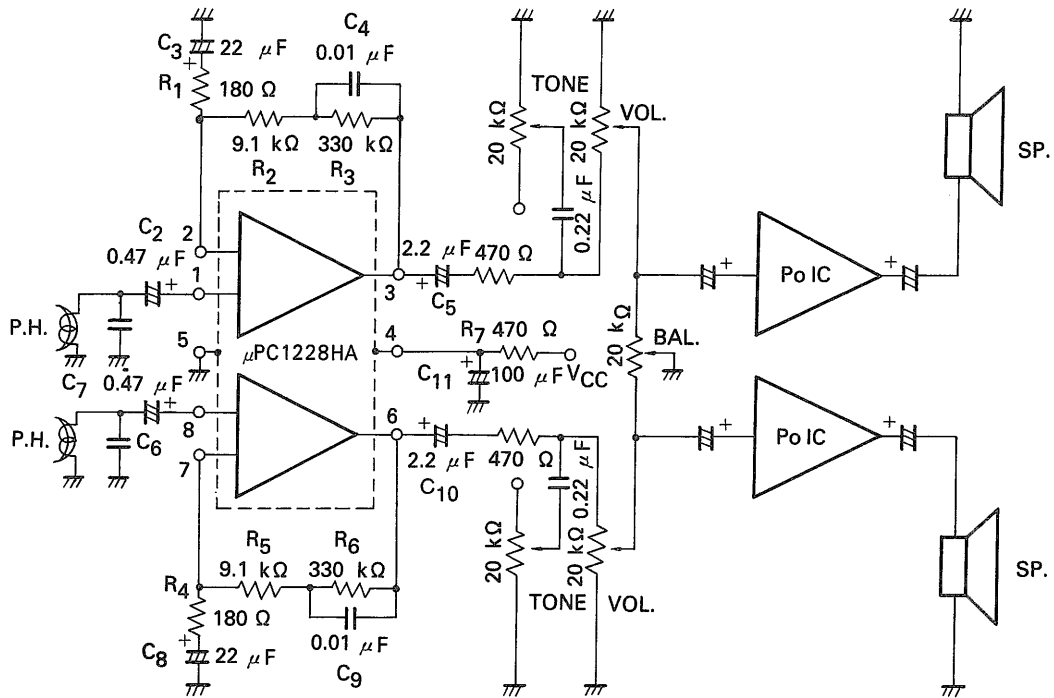


Fig.28 Application Circuit 1

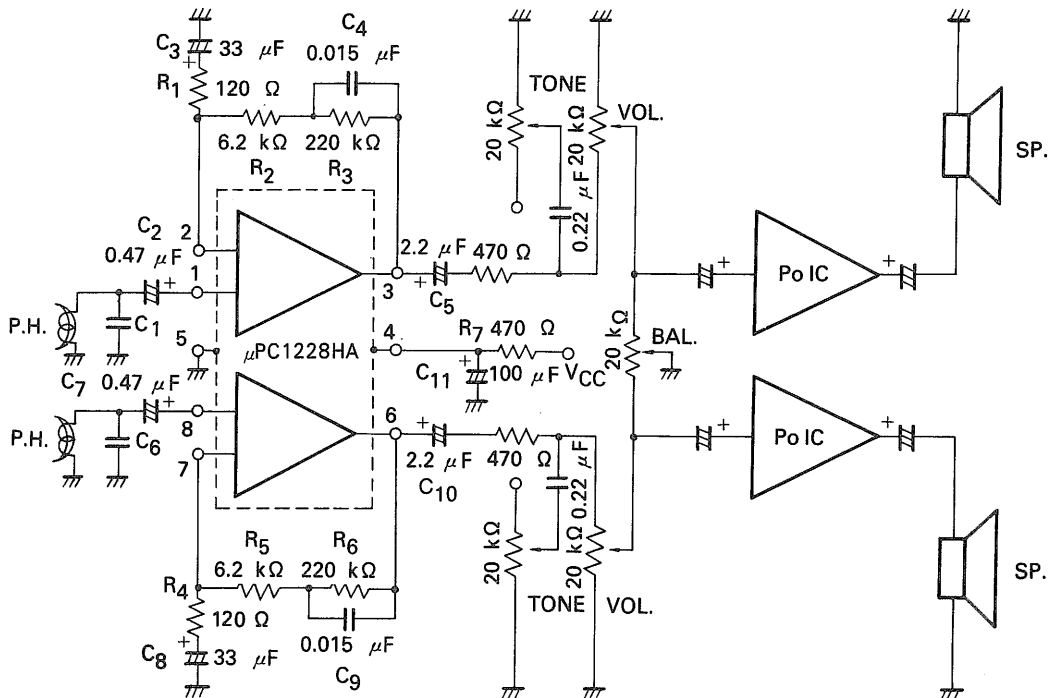11.2 APPLICATION 2 (NAB EQ, $V_{CC}=6\sim 17\text{ V}$, $V_{OM}=1.2\text{ V}$)



* When supply voltage of pin 4 is down to 6 V, please use TYPICAL APPLICATION 2.

Fig.29 Application Circuit 2

12.3 APPLICATION 3 (RIAA EQ, $V_{CC}=8\sim 18\text{ V}$, $V_{OM}=2\text{ V}$)

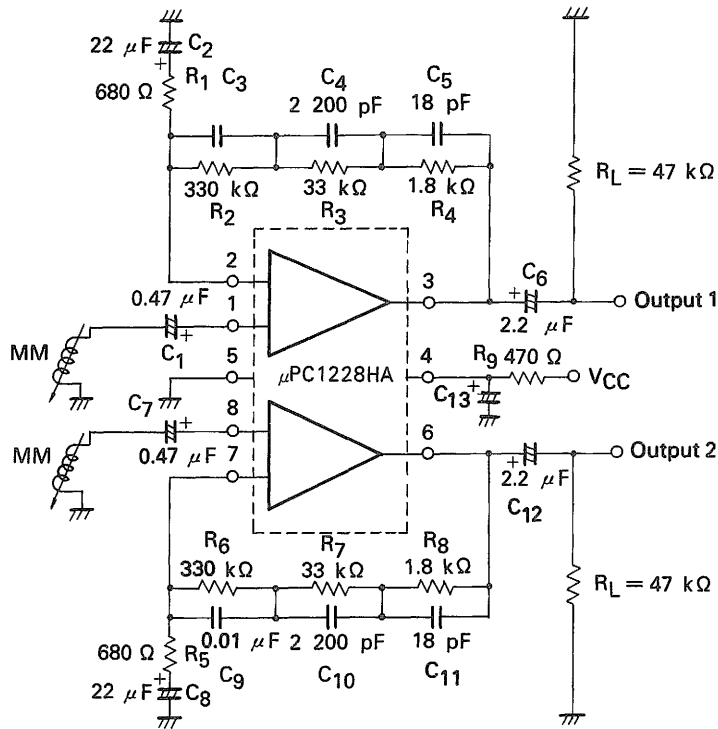


Fig.30 Application Circuit 3

13. TYPICAL PRINTED CIRCUIT BOARD PATTERN AND COMPONENT LAYOUT

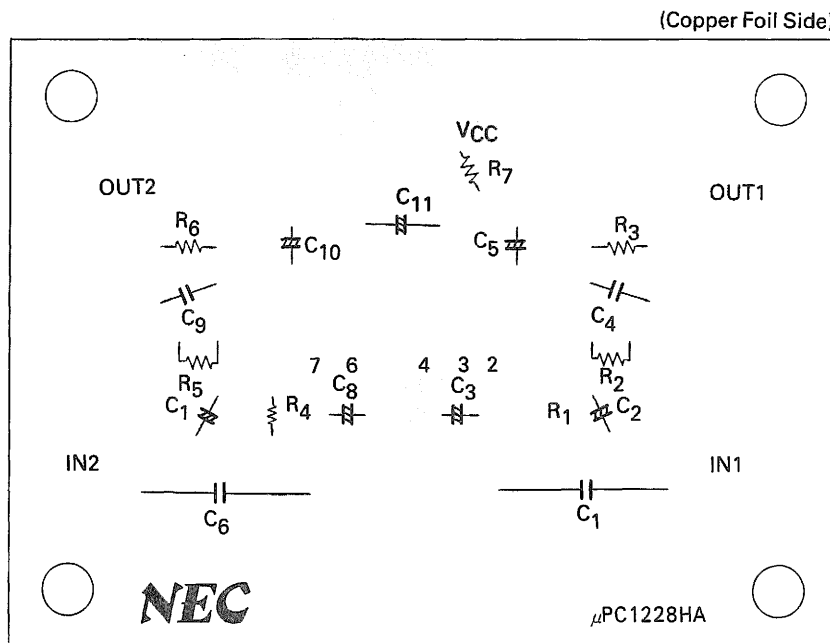


Fig.31 Printed Circuit Board

