

MOSFET

Precautions for parallel connection of power MOSFETs

Introduction

In this application note, we will explain the precautions for parallel connection of power MOSFETs.

Contents

1. Overview	2
2. Precautions during conduction (steady state)	3
3. Precautions during switching (transient state).....	3
3.1 Example of current imbalance during switching when samples with different $V_{GS(th)}$ are connected in parallel.....	3
4. Regarding parasitic oscillation	5
Revision History	6

1. Overview

In some cases, multiple devices may be connected in parallel to achieve higher power system or lower power MOSFET losses. In this case, it is important to balance the current flowing through each device, as if the current becomes unbalanced and concentrated on some devices, they may suffer excessive losses and be destroyed. Therefore, sufficient consideration is required for device characteristics variation, substrate layout symmetry, gate drive circuit, etc. Also, the problems that occur when using parallel connection can be classified into those that occur during the conduction period (steady state) of the power MOSFET and those that occur during the switching period (transient state) of the power MOSFET. These have different causes and require different countermeasures. The precautions for parallel connection are shown in Table 1-1.

Table 1-1. precautions for parallel connection of power MOSFETs

	During conduction (steady state)	During switching (transient state)
Circuit factors	<ul style="list-style-type: none">▪ Symmetry of board layout (resistance component)	<ul style="list-style-type: none">▪ Symmetry of board layout (resistance component)▪ Avoid avalanche operation▪ Gate oscillation
Power MOSFET factors	<ul style="list-style-type: none">▪ Variation of $R_{DS(on)}$	<ul style="list-style-type: none">▪ Variation of $V_{GS(th)}$

2. Precautions during conduction (steady state)

When power MOSFETs are turned on, the difference in $R_{DS(on)}$ of the parallel-connected devices and the resistance of the substrate and wiring cause an imbalance in the drain current. This current imbalance not only affects the loss of the devices during conduction, but also changes the current value during switching, affecting the transient loss. Therefore, it is necessary to take measures such as selecting devices from the same lot and minimizing the difference in $R_{DS(on)}$, and designing the parallel paths symmetrically. The $R_{DS(on)}$ of power MOSFETs has a positive temperature coefficient. Therefore, the current imbalance that occurs will self-balance to equalize, and the risk of failure due to heat generation during conduction is low.

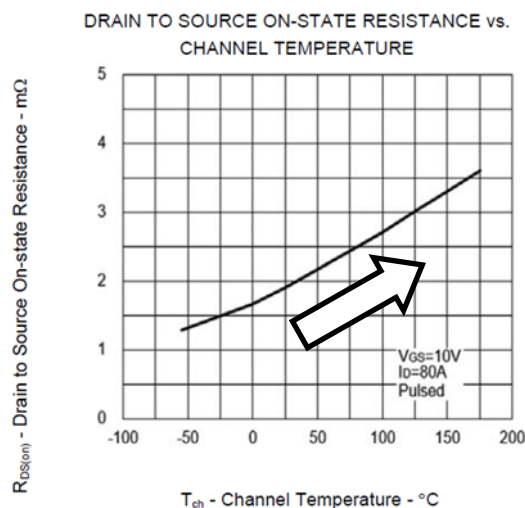


Fig. 2-1 $R_{DS(on)}$ Temperature characteristics

3. Precautions during switching (transient state)

When power MOSFETs are switching (transient state), the difference in $V_{GS(th)}$ of the parallel-connected devices and the difference in the inductance components of the substrate and wiring cause an imbalance in the drain current. Therefore, it is necessary to take measures such as selecting devices from the same lot and minimizing the difference in $V_{GS(th)}$, and designing the layout of the parallel paths symmetrically. When operating in avalanche mode in parallel connection, there is a possibility of destroying the device with low drain withstand voltage by concentrating all the current on it, so be careful.

3.1 Example of current imbalance during switching when samples with different $V_{GS(th)}$ are connected in parallel

The following figure shows the operation waveforms when samples with intentionally different $V_{GS(th)}$ are connected in parallel and switched. At turn-on, MOSFET2 with smaller $V_{GS(th)}$ turns on first, and at turn-off, MOSFET1 with larger $V_{GS(th)}$ turns off first, causing current imbalance. The current imbalance caused by the difference in $V_{GS(th)}$ can be prevented by using devices from the same lot and minimizing the difference in $V_{GS(th)}$ between MOSFETs.

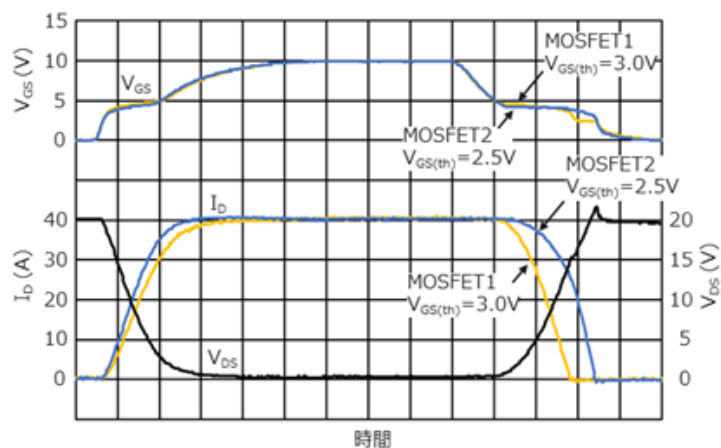


Fig. 3-1 Current imbalance waveforms during switching

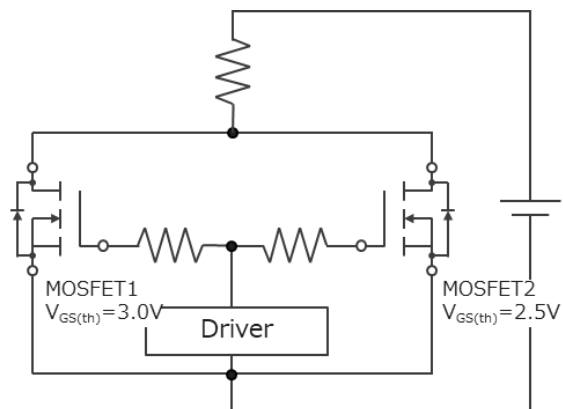


Fig. 3-2 Evaluation circuit

4. Regarding parasitic oscillation

When using power MOSFETs in parallel, parasitic oscillations are more likely to occur than when using a single power MOSFET. If the gates of the power MOSFETs are connected directly without resistance, oscillating waveforms may be seen on the gates because of parasitic parameters. These oscillating waveforms are caused by the voltage oscillation due to the drain wiring inductance (L_d) during switching (especially turn-off) and the resonant circuit composed of the gate-drain capacitance (C_{gd}) and the gate wiring inductance (L_g). Therefore, when there is no gate resistance, the Q factor (sharpness) of the resonant circuit becomes large, and when the resonance condition is met, a large oscillating voltage is generated between the gate-drain and the gate-source, causing parasitic oscillation. As a countermeasure, parasitic oscillation is suppressed by connecting a resistance (R_G) to the gate of each device.

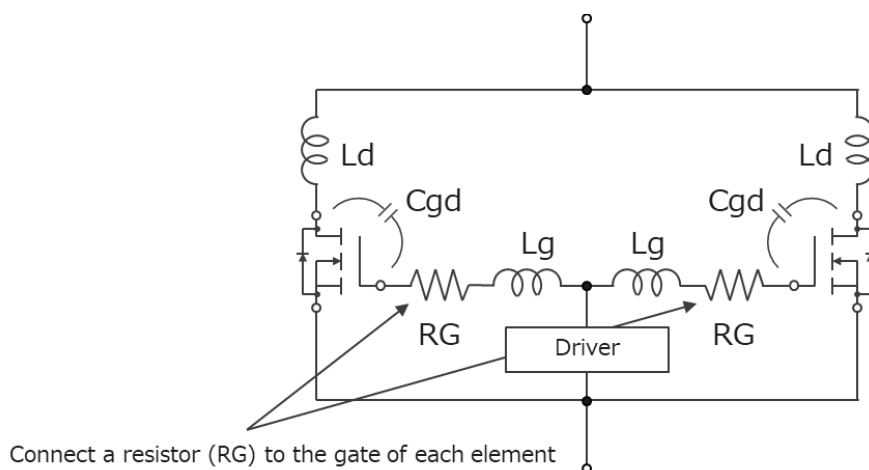


Fig. 4-1 Measures against gate oscillation

Revision History

Rev.	Date	Description	
		Page	Summary
Rev.1.00	Feb.29 2024	-	First edition

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/.