

R2A20135EVB-ND1 (Critical Conduction Mode)

R19AN0023EJ0100
Rev.1.00

R2A20135 Evaluation Board for Dimmable LED Lighting Application

Sep 27, 2013

1. Overview

The R2A20135EVB-ND1 is an evaluation board for LED driver IC, having capability of dimming control. All the components to control LED lighting system are onboard, it is easy to start evaluation by supplying power and connecting dimmer and LED load.


The board has a step-down and non-isolated high-side driving circuit, controls dimming, and features high efficiency, high power factor, low total harmonic distortion (THD), and low ripple voltage.

For evaluating this board, please refer to the R2A20135SP data sheet as well.

2. Specification


No.	Item	Specification
1	Input voltage range	85 to 132 VAC (single phase: 47 to 63 Hz)
2	Input power	9.5 W (typ.)
3	Output voltage (VF)	35 V
4	Output current	220 mA (typ.)
5	Efficiency	85% or more (when Vin = 100 VAC)
6	Power factor	0.9 or more (when Vin = 100 to 120 VAC)
7	Switching frequency	35 kHz (min.)
8	Operation mode	Critical Conduction Mode
9	Board	Two layers / glass epoxy (FR4) / dual-sided mount
10	Size (W ´ D ´ H)	36 mm ´ 41 mm ´ 20 mm (component side)

3. System Diagram and Connection

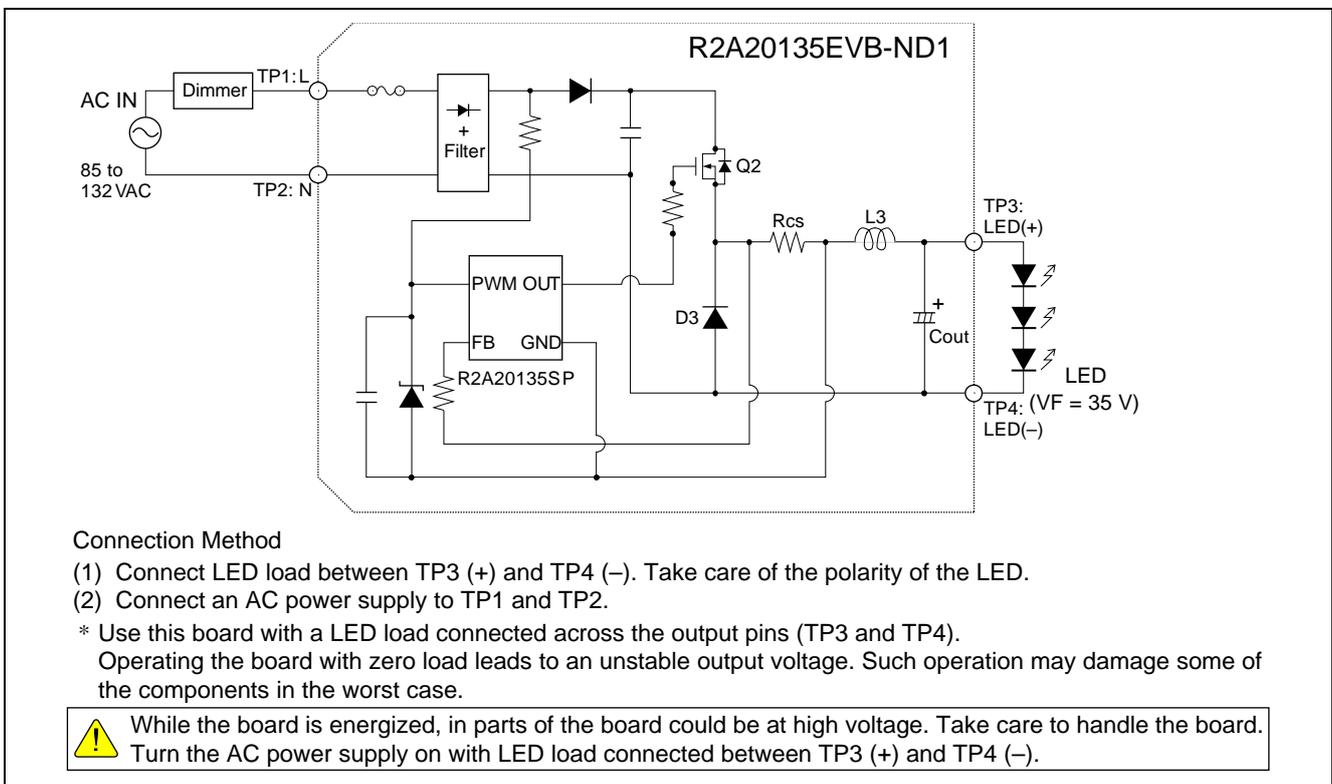


4. PCB Layout

4.1 PCB Layout

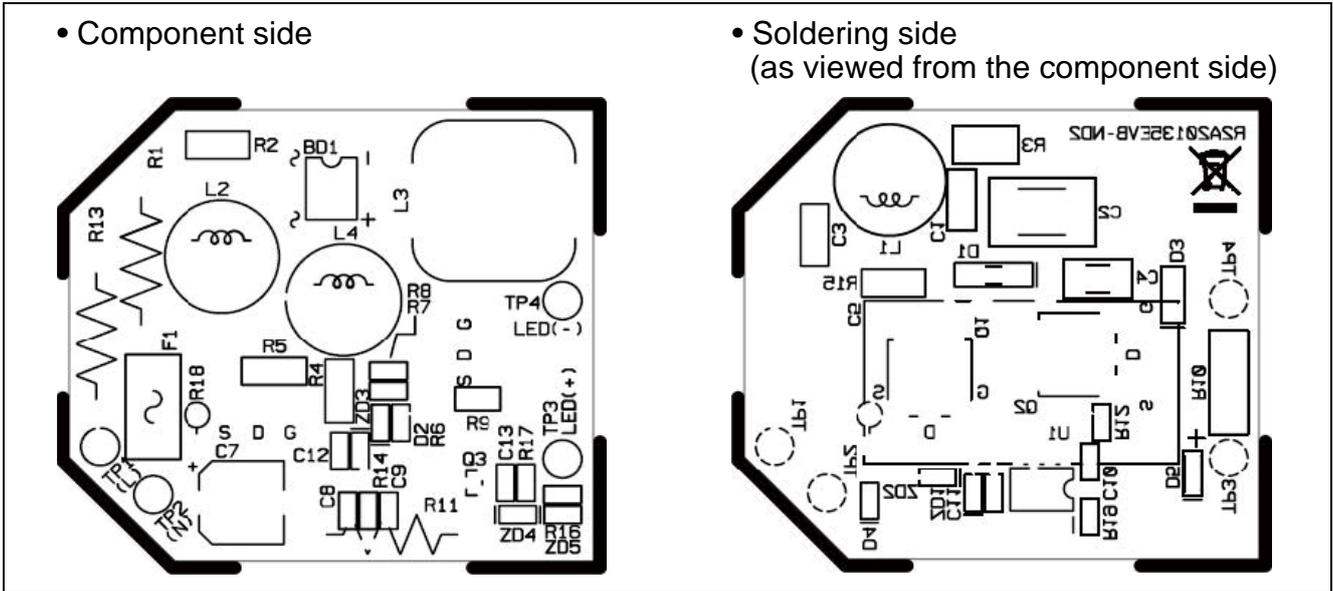


4.2 Circuit Patterns

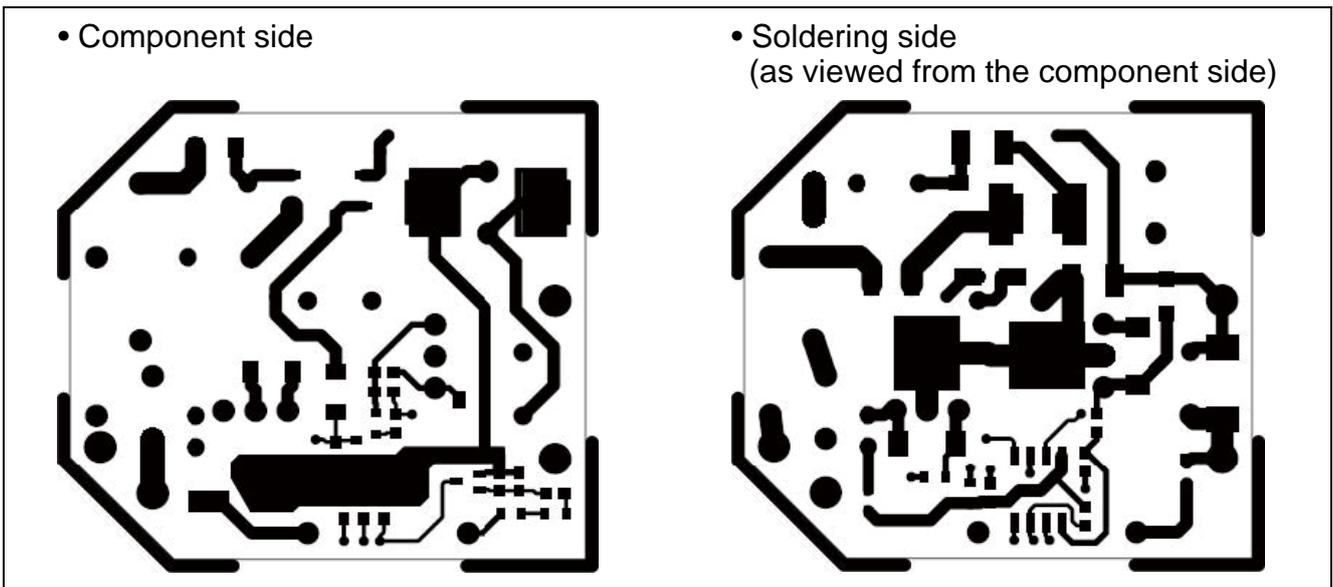


5. Performance Data


5.1 Operation Waveform

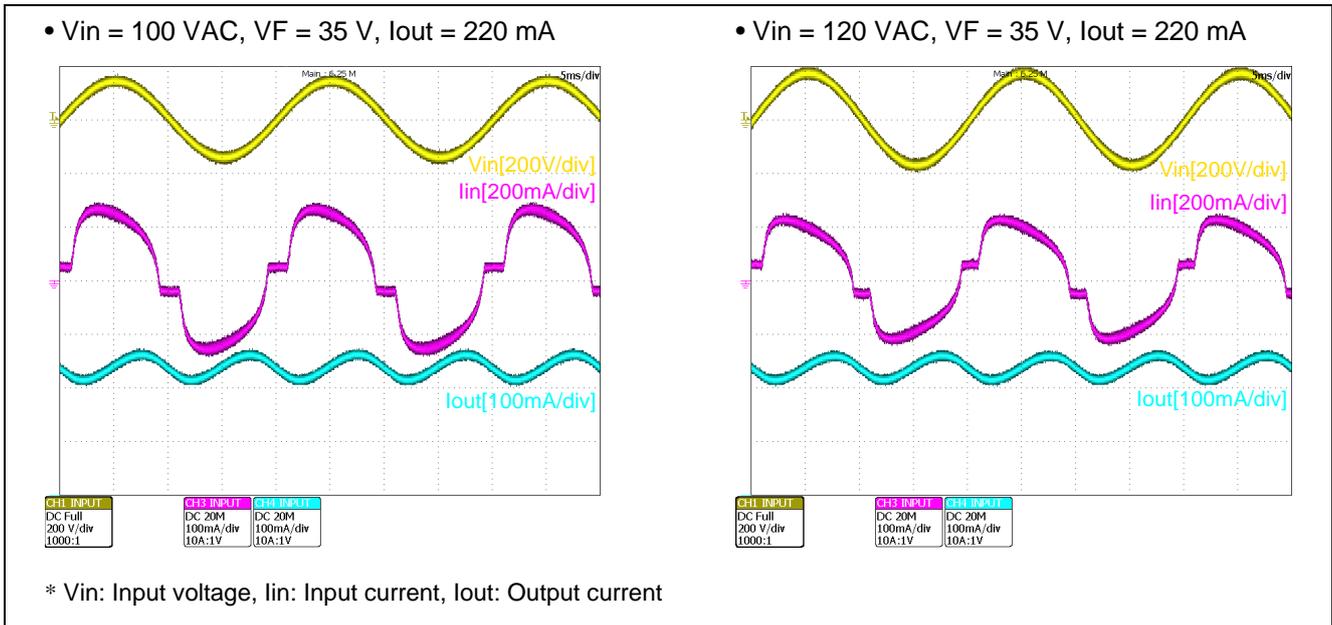


5.2 Power Factor

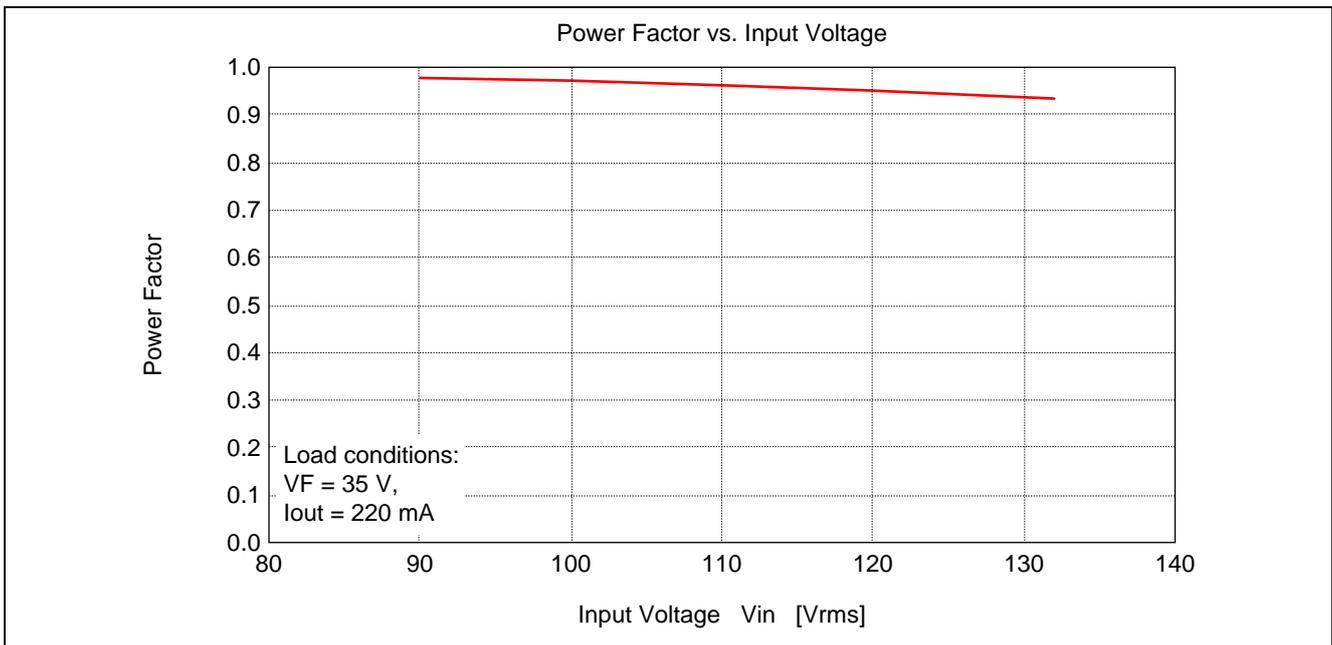


5.3 Efficiency

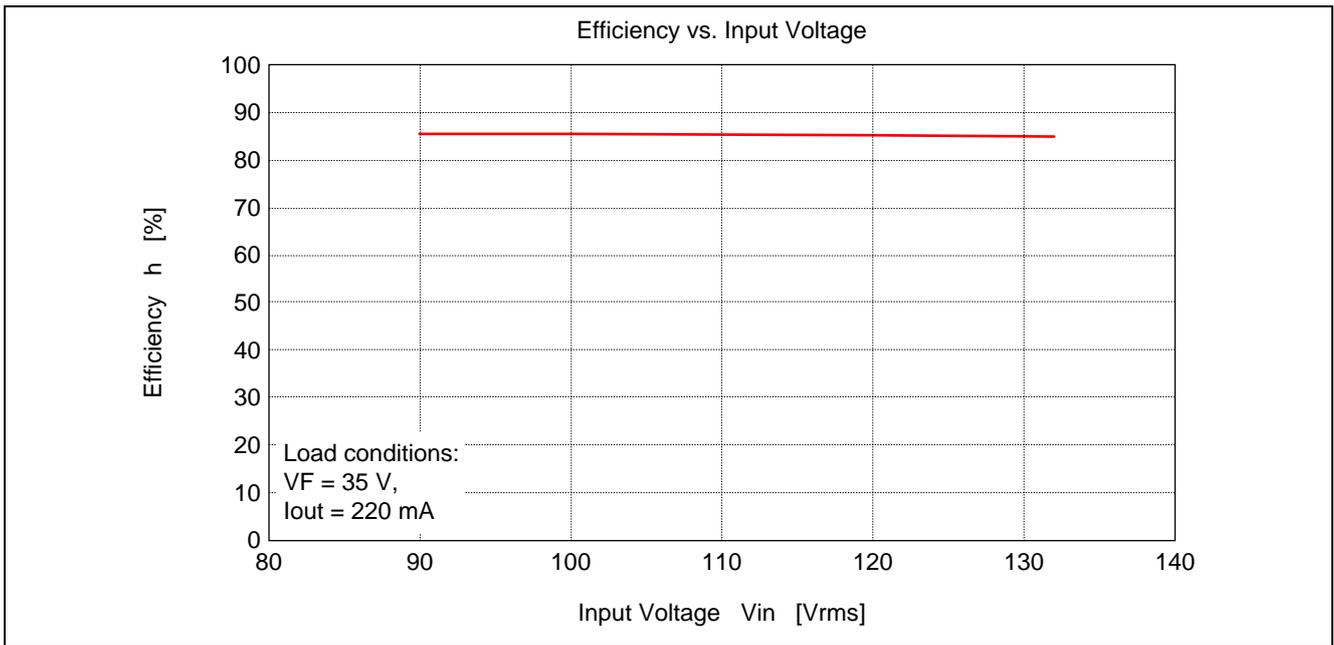


5.4 THD (Total Harmonic Distortion)

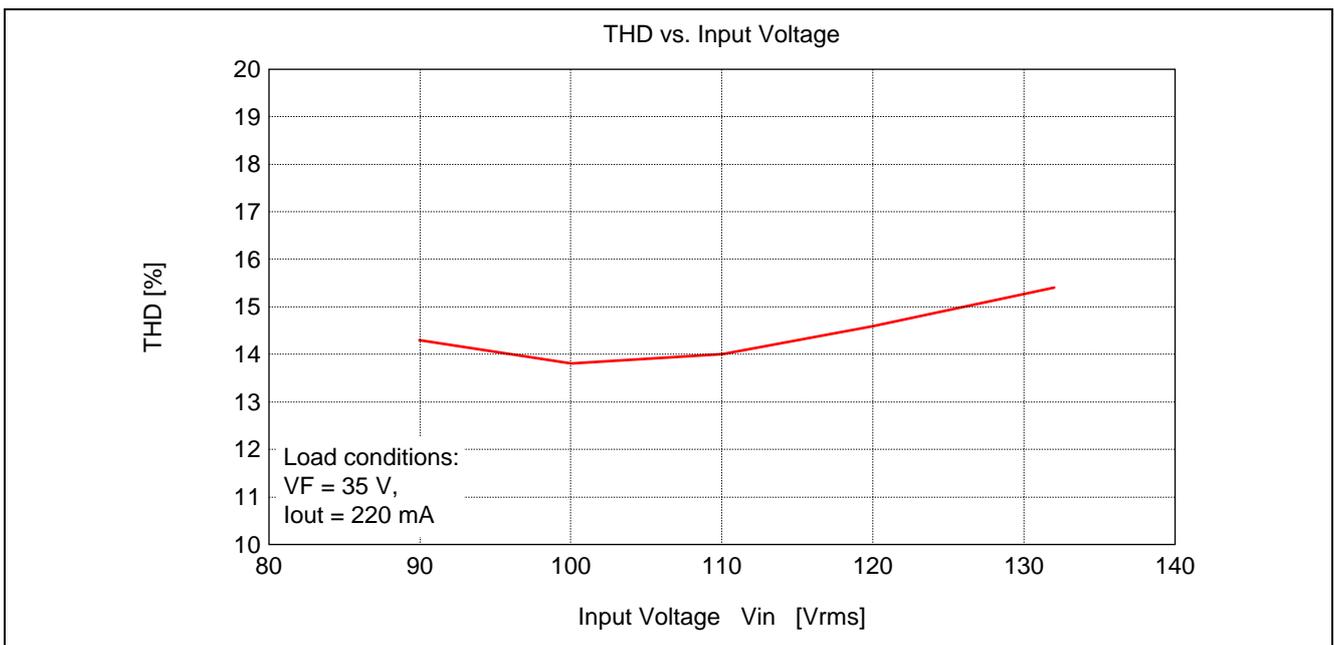


5.5 Input Power

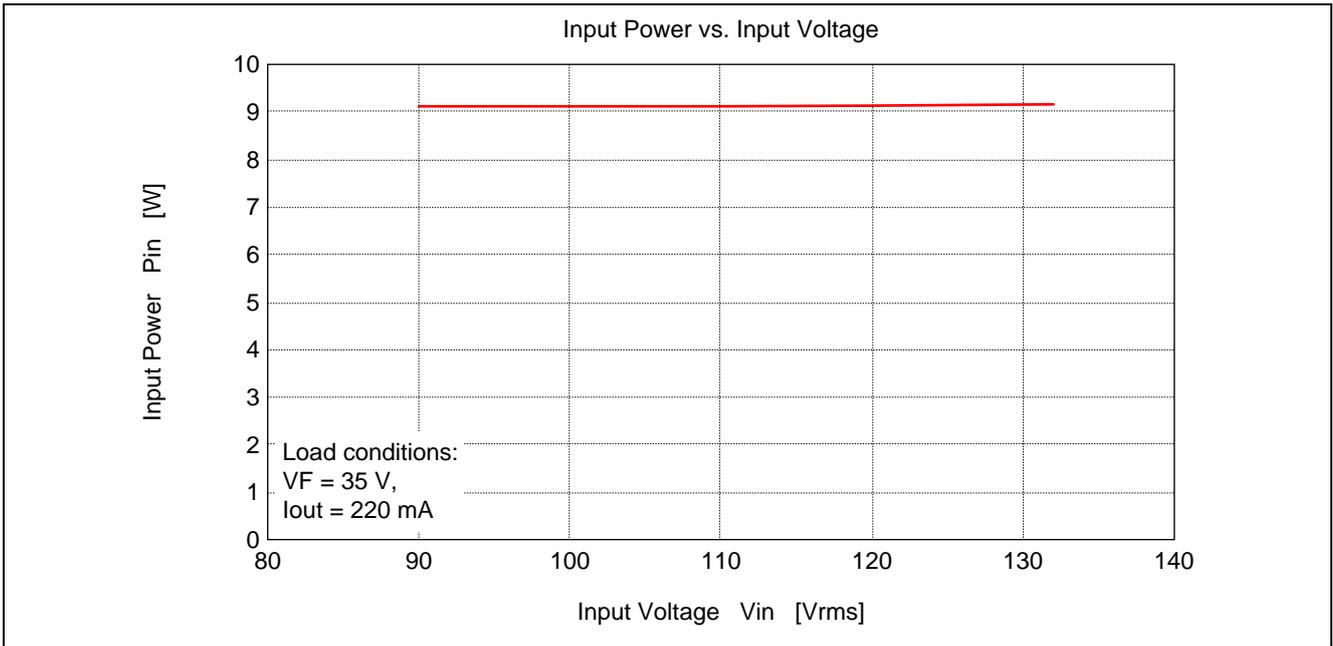


5.6 Output Current

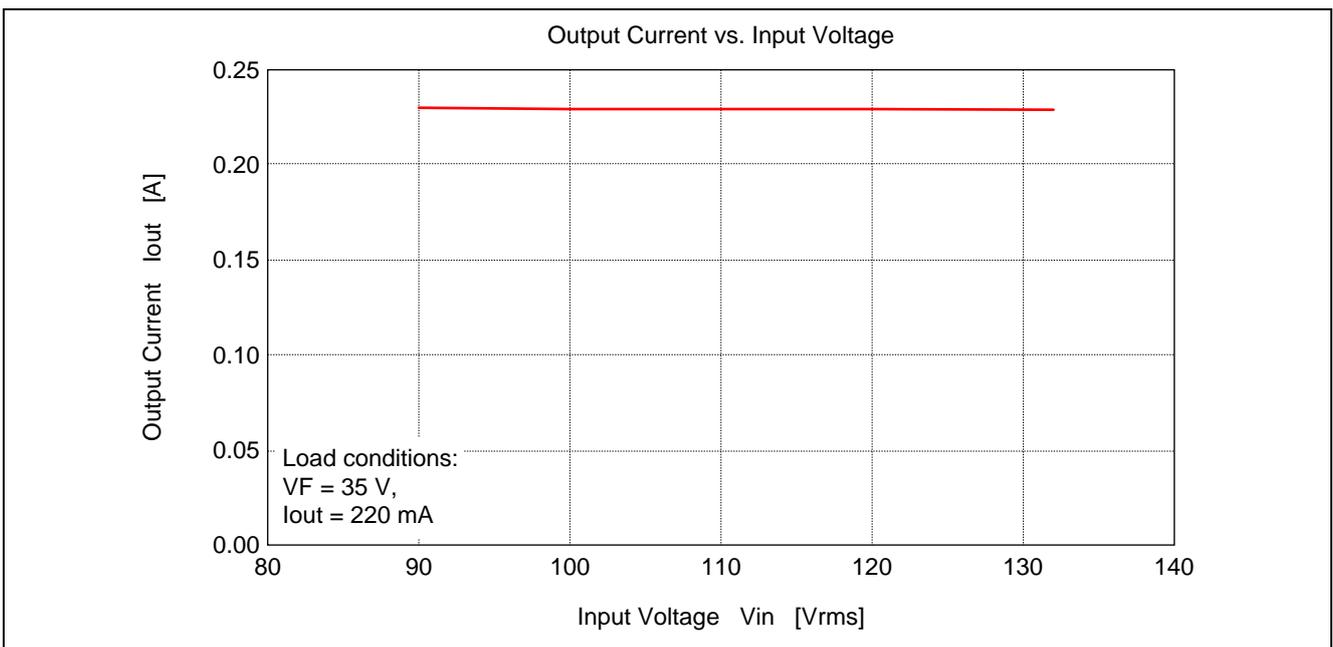

5.7 Dimming Characteristics

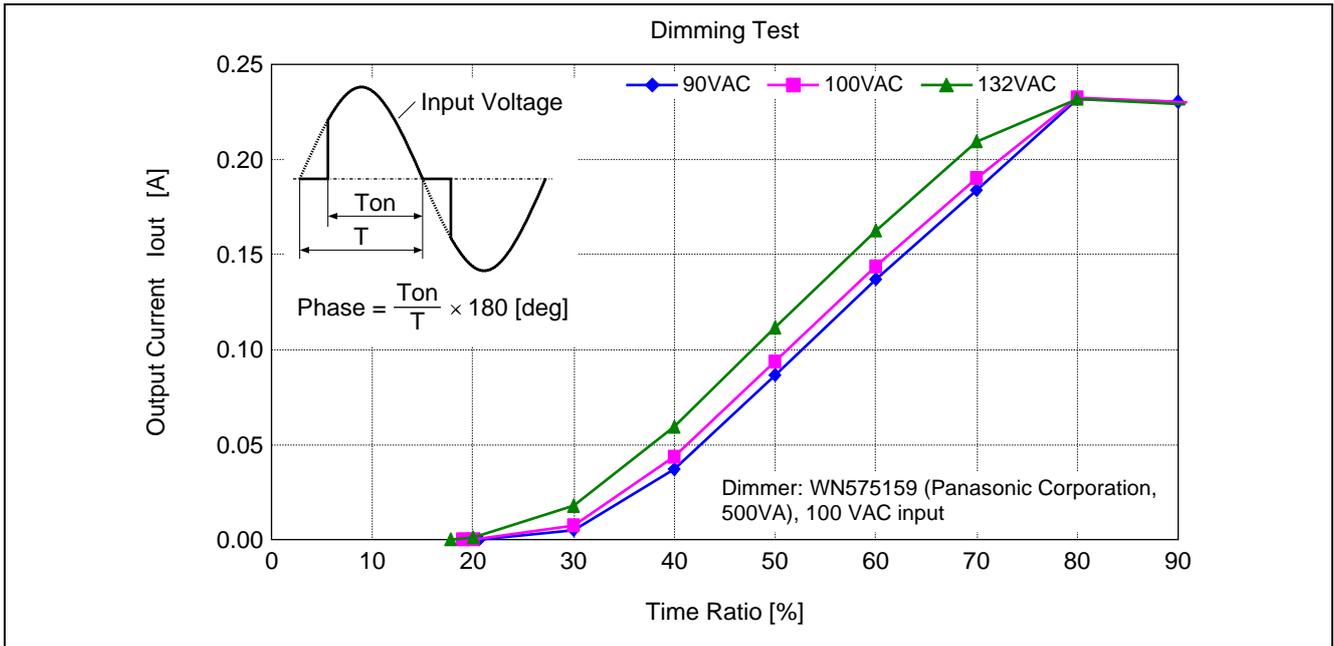

6. Schematic

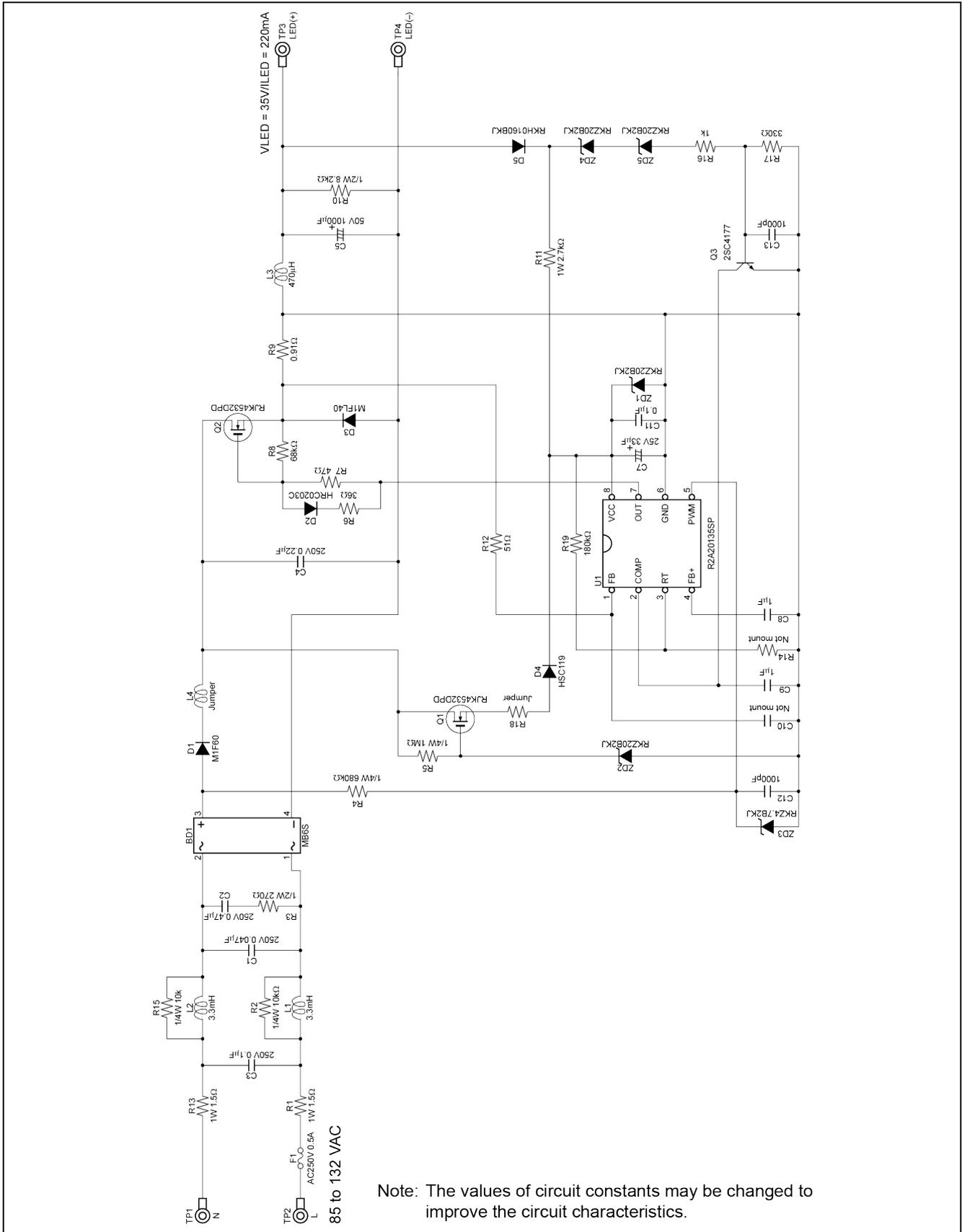

7. Bill of Materials

Symbol	Parts Name	Catalog No.	Q	Rating		Manufacturer	Note
PWB	Printed-wiring board	R2A20135EVB-ND1	1			Renesas Electronics	
U1	IC	R2A20135SP	1	24V		Renesas Electronics	SOP-8
Q1	FET	RJK4532DPD	1	450V	4A	Renesas Electronics	TO-252 (DPAK)
Q2	FET	RJK4532DPD	1	450V	4A	Renesas Electronics	TO-252 (DPAK)
Q3	Transistor	2SC4177	1	60V	0.1A	Renesas Electronics	3pin SSM
BD1	Bridge diode	MB6S	1	600V	0.5A	VISHAY	TO-269AA (MBS)
D1	Diode	M1F60	1	600V	1A	Shindengen	M1F
D2	SBD	HRC0203C-E	1	30V	0.2A	Renesas Electronics	UFP
D3	FRD	M1FL40	1	400V	1.5A	Shindengen	M1F
D4	Diode	HSC119	1	80V	100mA	Renesas Electronics	UFP
D5	Diode	RKH0160BKJ	1	600V	100mA	Renesas Electronics	URP
ZD1	Zener diode	RKZ20B2KJ	1	20V	5mA	Renesas Electronics	UFP
ZD2	Zener diode	RKZ20B2KJ	1	20V	5mA	Renesas Electronics	UFP
ZD3	Zener diode	RKZ4.7B2KJ	1	4.7V	5mA	Renesas Electronics	UFP
ZD4	Zener diode	RKZ20B2KJ	1	20V	5mA	Renesas Electronics	UFP
ZD5	Zener diode	RKZ20B2KJ	1	20V	5mA	Renesas Electronics	UFP
R1	Resistor		1	1W	1.5		Leaded
R2	Chip resistor		1	1/4W	10k		3216
R3	Chip resistor		1	1/2W	270		3225, Withstand pulse (SG73P by KOA, etc.)
R4	Chip resistor		1	1/4W	680k		3216, Withstand voltage of 400 V or more (HV73 by KOA, etc.)
R5	Chip resistor		1	1/4W	1M		3216, Withstand voltage of 400 V or more (HV73 by KOA, etc.)
R6	Chip resistor		1	1/10W	36		1608
R7	Chip resistor		1	1/10W	47		1608
R8	Chip resistor		1	1/10W	68k		1608
R9	Chip resistor		1	1/4W	0.91		2012, high accuracy (1 percent or better)
R10	Chip resistor		1	1/2W	8.2k		5025
R11	Resistor			1W	2.7k		Leaded
R12	Chip resistor		1	1/10W	51		1608
R13	Resistor		1	1W	1.5		Leaded
R14	Chip resistor		1	1/10W	150k		1608
R15	Chip resistor			1/4W	10k		3216
R16	Chip resistor		1	1/10W	1k		1608
R17	Chip resistor		1	1/10W	330		1608
R18			1				Leaded
R19	Chip resistor	No mount					1608
C1	Ceramic capacitor	GRM31	1	250V	0.047nF	Murata Manufacturing	3216
C2	Ceramic capacitor	GRM43	1	250V	0.47nF	Murata Manufacturing	4532
C3	Ceramic capacitor	GRJ31CR72E104KWJ3L	1	250Vdc	0.1nF		
C4	Ceramic capacitor	GRJ32DR72E224KWJ1L	1	250Vdc	0.22nF	Murata Manufacturing	3225
C5	Electrochemical capacitor	ECA1HHG102	1	50V	1000mF	Panasonic	f : (12.5' 25) or less, rated for 105°C
C7	Electrochemical capacitor	EMVL250ADA330MF60G	1	25V	33nF	Nippon Chemi-Con	f : (6.3' 8) or less, rated for 105°C
C8	Ceramic capacitor	GRM188	1	25V	1nF	Murata Manufacturing	1608
C9	Ceramic capacitor	GRM188	1	25V	1nF	Murata Manufacturing	1608
C10	Ceramic capacitor	GRM188	1	25V	0.1nF	Murata Manufacturing	1608
C11	Ceramic capacitor	GRM188	1	25V	0.1nF	Murata Manufacturing	1608
C12	Ceramic capacitor	GRM188	1	25V	1000pF	Murata Manufacturing	1608
C13	Ceramic capacitor	GRM188	1	25V	1000pF	Murata Manufacturing	1608
L1	Inductor	TSL0808S-332KR14-PF	1	0.14A	3.3mH	TDK	
L2	Inductor	TSL0808S-332KR14-PF	1	0.14A	3.3mH	TDK	
L3	Inductor	#B953AS-221M	1	1A	220mH	TOKO	
L4							
F1	Fuse	HTS 500mA	1	AC250V	0.5A	Skygate	
TP1	Test point	No mount	1				MAC8 ST-3-2 size
TP2	Test point	No mount	1				MAC8 ST-3-2 size
TP3	Test point	No mount	1				MAC8 ST-3-2 size
TP4	Test point	No mount	1				MAC8 ST-3-2 size

Note: The components may be changed to improve the circuit characteristics.

8.4 Selection of Inductor L

Calculate the inductance for the lowest switching frequency.

When the minimum V_{in} is 85 VAC and V_{out} is 80 V, duty cycle D_{ON} is calculated as follows:

$$D_{ON} = V_{out}/(V_{in}) = 35/(85 \cdot \sqrt{2}) = 0.291$$

Because the frequency is 40 kHz, ON time T_{on} is calculated as follows:

$$T_{on} = D_{ON}/f_{out} = 0.291/40\text{kHz} = 7.28\text{ms}$$

When input voltage V_{in} is 85 VAC, output power P_{out} is 7.7 W ($0.22 \cdot 35$), and conduction angle is 90%, average input current I_{in} (ave) is calculated as follows:

$$I_{in}(\text{ave}) = P_{out}/h/V_{in} = 7.7/0.90/85 = 101\text{mA}$$

The peak value of the coil current is calculated as follows:

$$I_L(\text{peak}) = I_{in}(\text{ave}) \cdot 2/D_{ON} = 0.101 \cdot 2/0.291 = 2.049\text{A}$$

Then, the value of inductor L is calculated as follows:

$$L = (V_{in} - V_{out}) \cdot T_{on}/I_L(\text{peak}) = (85 \cdot \sqrt{2} - 35) \cdot 3.64\text{ms}/0.687 = 1090\text{nH}$$

An inductor with a value of 1 mH is selected from the lineup of available standard inductors in consideration of allowable tolerance and size.

Note: *1 For the conduction angle, refer to the separate material (section headed "Selection of L" in the R2A20135SP application note).

8.5 External Circuit for FB and COMP Pins

Figure 8.4 shows the frequency characteristics of the R2A20135EVB-ND1.

This circuit is for stable operation in current mode (first-order lag). To improve the power factor, it is recommended to set the COMP pin in Figure 8.3 so that the loop gain is 0 dB at a frequency less than twice as the range of AC frequencies 50 to 60 Hz (100 to 120 Hz). C_{comp} is 1 μF on the evaluation board.

In the case that a CR filter for the FB pin is inserted to reduce noise influence, select R_{f1} so that the FB pin voltage is equal to or less than the zero-crossing detection threshold voltage in consideration of the current flowing into the FB pin. R_{f1} on the board is 51 Ω .

C_{f1} should have a value which produces a time constant much smaller than the switching frequency. It is left open circuit on the board.

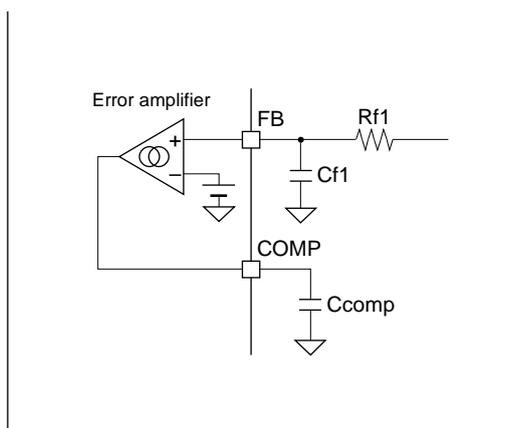


Figure 8.3 External Circuit for FB and COMP Pins

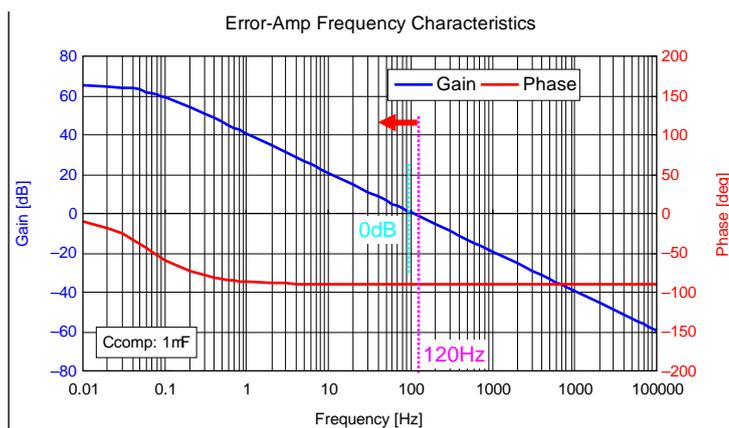


Figure 8.4 R2A20135EVB-ND1 Frequency Characteristics


9. Conducted EMI

9.1 Conducted Emission Standard (CISPR15) Adaptation

This evaluation board is possible to meet the conducted emission standard (CISPR15) by changing or adding some components.

However, basic characteristics such as power efficiency or power factor are trade-off for conducted emission, please adjust each components' value according to required performance.

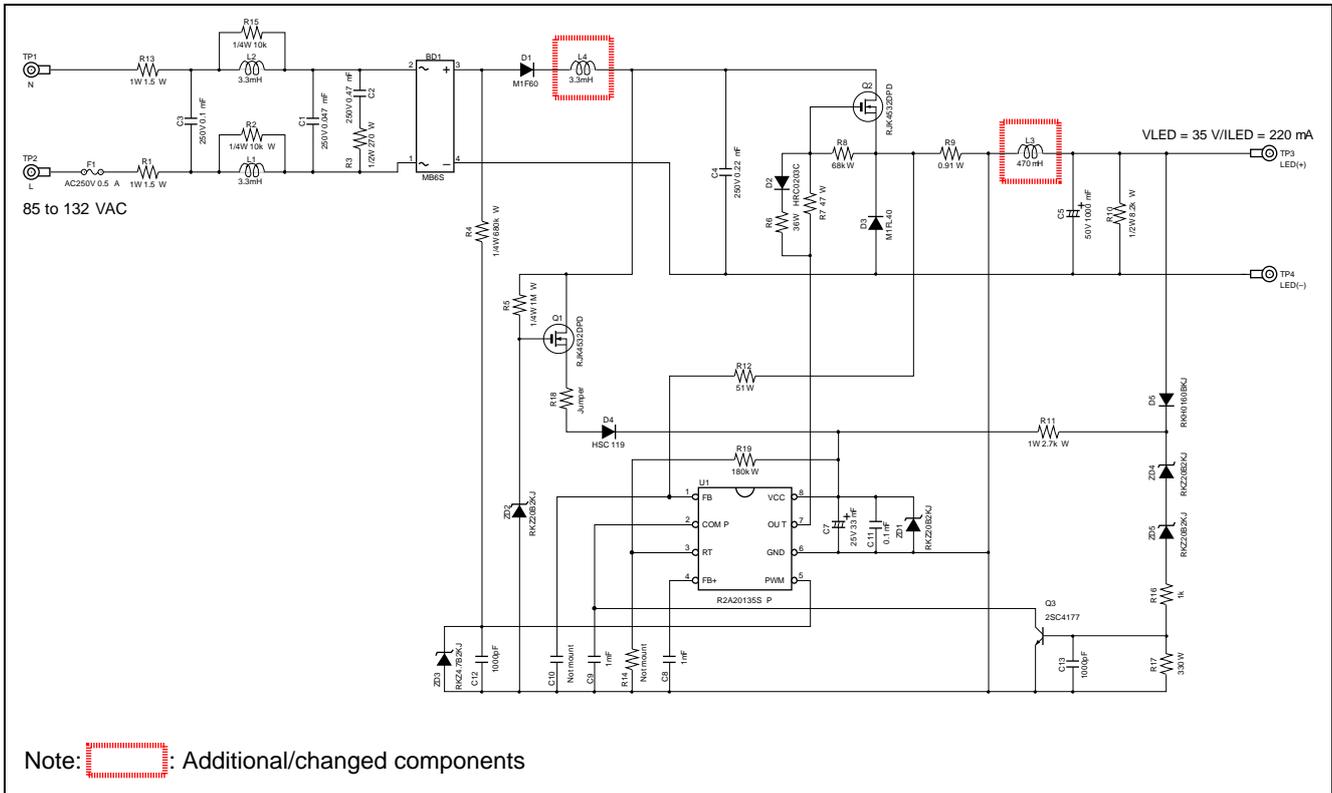9.1.1 Schematic with Conducted Emission Filter




9.1.2 Additional/Changed Parts to Meet Conducted Emission Standard


Symbol	Parts Name	Catalog No.	Q	Rating	Manufacturer
L3	Inductor	RCP1317NP-471L	1	1.35A 470mH	Sumida
L4	Inductor	TSL0808S-332KR14-PF	1	0.14A 3.3mH	Taiyo Yuden

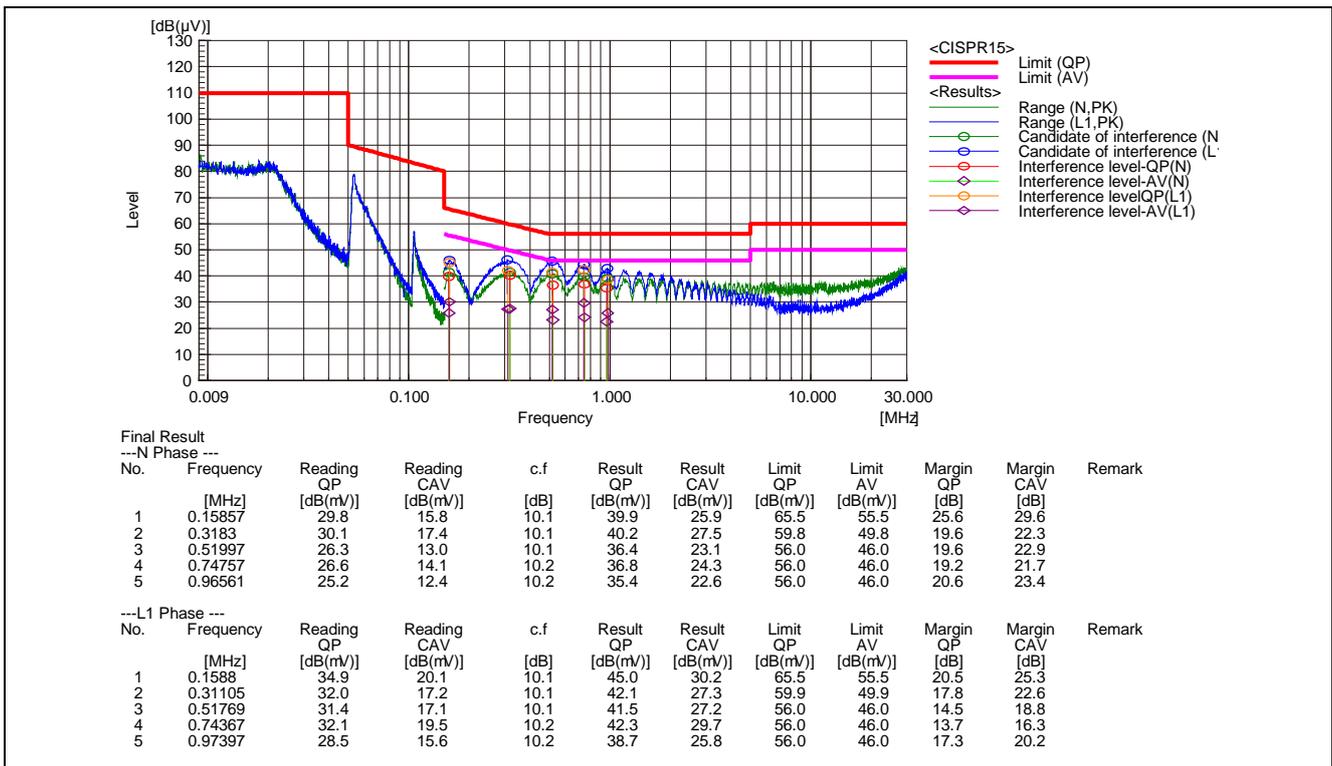9.2 Conducted EMI Performance Data (CISPR15)

• Vin = 100 VAC, 60 Hz, LED load (VF = 35 V), Iout = 220 mA



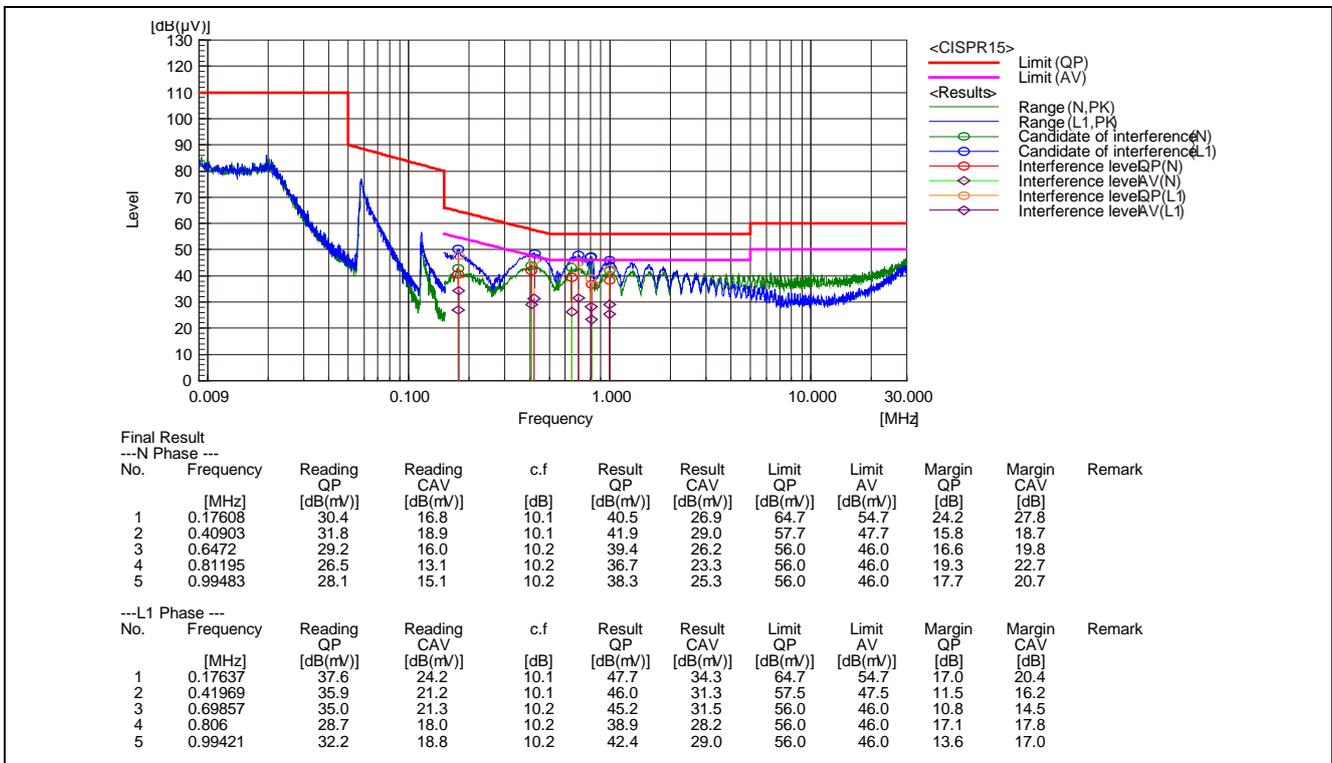• Vin = 120 VAC, 60 Hz, LED load (VF = 35 V), Iout = 220 mA




10.2 PCB Pattern Design

To reduce the effect of noise on the control IC, design the pattern by referring to the following example of design of the pattern around the control IC. The component numbers correspond to those of the circuits on the previous page and are common to both circuits.

These patterns are for reference and the operation of the circuit with components mounted is not guaranteed. The operation must be verified on an actual board.

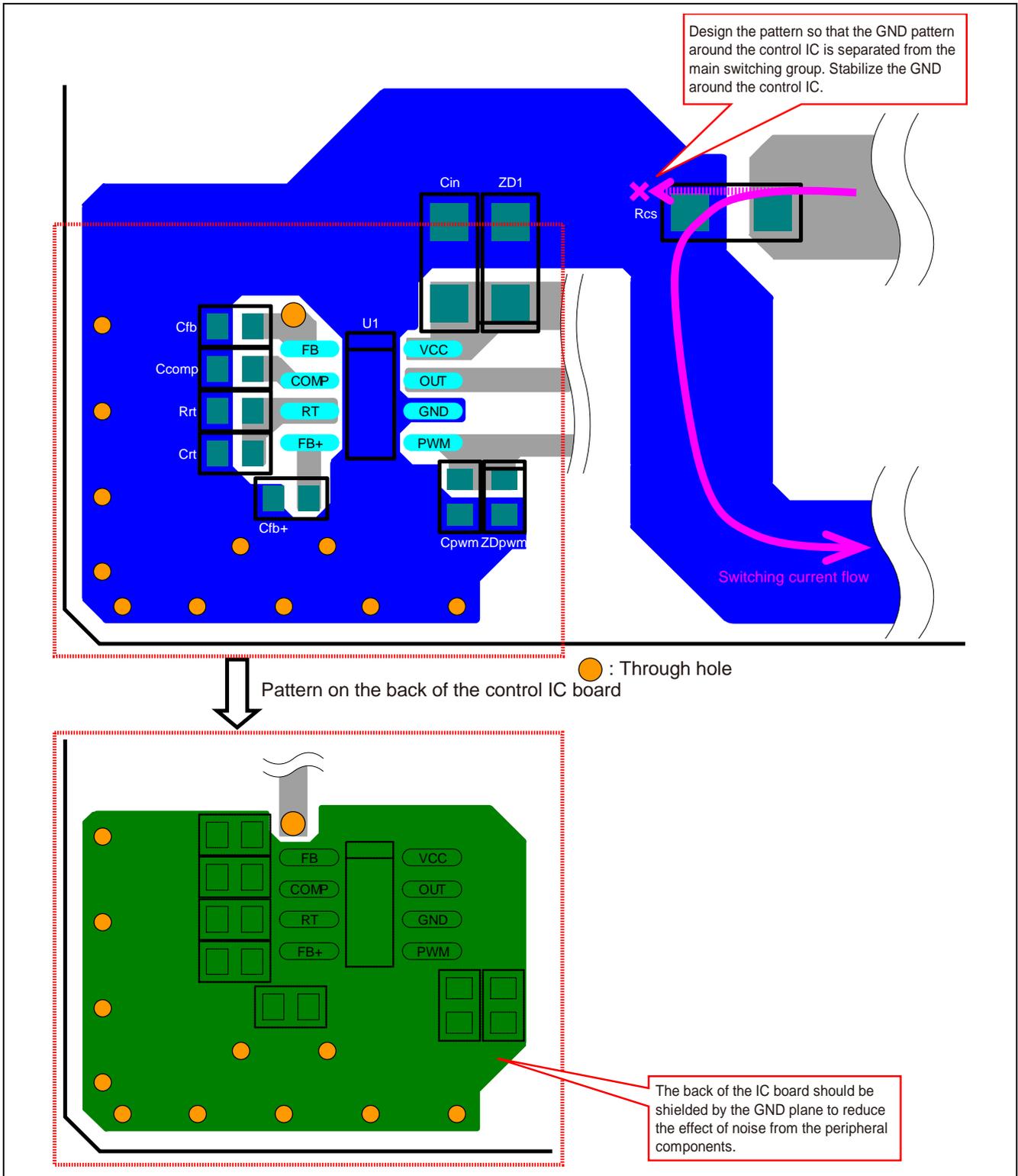Example of Design of Pattern around Control IC




10.3 Notes on Mounting Components

The occurrence of AC coupling may vary even with the same board and circuit constants according to the mounting of the components.

Mount the components so that none of them makes contact with the control IC.

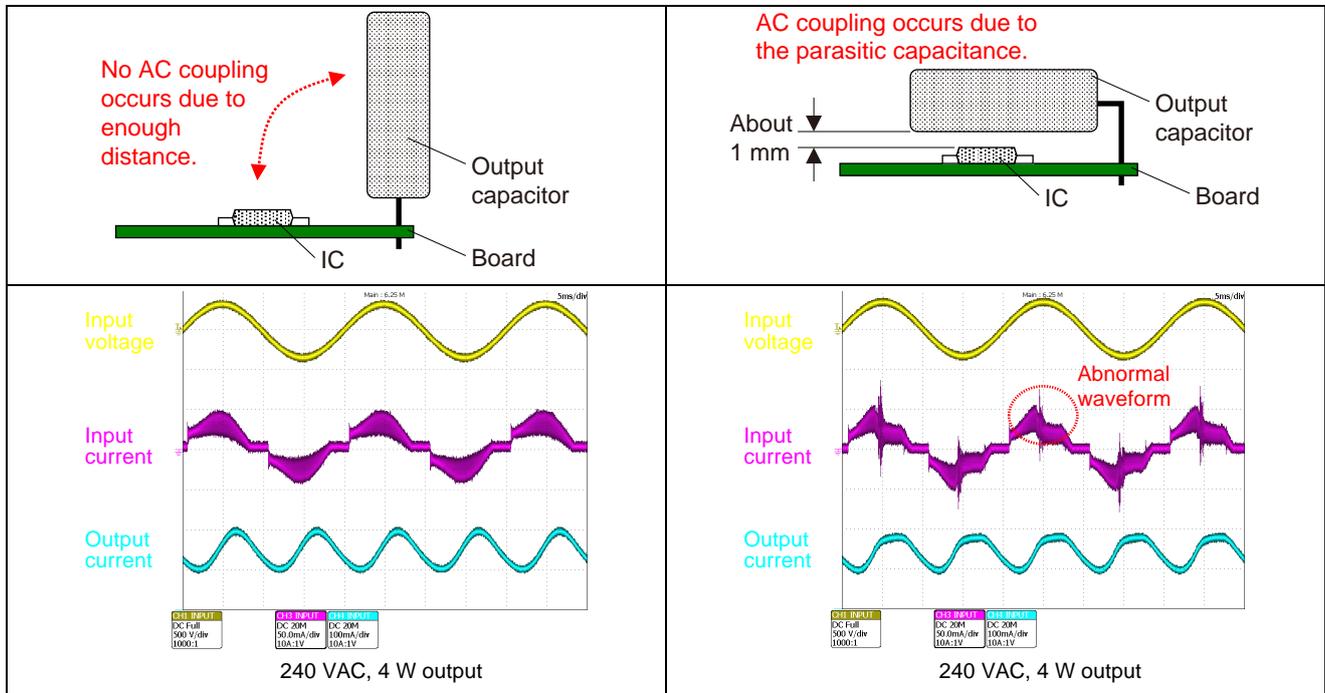The occurrence of AC coupling varies according to the mounting of the output capacitor as follows.



Website and Support

Renesas Electronics Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/contact/>

All trademarks and registered trademarks are the property of their respective owners.

Revision Record

Rev.	Date	Description	
		Page	Summary
Rev.1.00	Sep 27, 2013	—	First edition issued

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
 3. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from such alteration, modification, copy or otherwise misappropriation of Renesas Electronics product.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; and safety equipment etc.
Renesas Electronics products are neither intended nor authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems, surgical implantations etc.), or may cause serious property damages (nuclear reactor control systems, military equipment etc.). You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application for which it is not intended. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for which the product is not intended by Renesas Electronics.
 6. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You should not use Renesas Electronics products or technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. When exporting the Renesas Electronics products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, who distributes, disposes of, or otherwise places the product with a third party, to notify such third party in advance of the contents and conditions set forth in this document, Renesas Electronics assumes no responsibility for any losses incurred by you or third parties as a result of unauthorized use of Renesas Electronics products.
 11. This document may not be reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
2880 Scott Boulevard Santa Clara, CA 95050-2554, U.S.A.
Tel: +1-408-588-6000, Fax: +1-408-588-6130

Renesas Electronics Canada Limited
1101 Nicholson Road, Newmarket, Ontario L3Y 9C3, Canada
Tel: +1-905-898-5441, Fax: +1-905-898-3220

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-65030, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
7th Floor, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100083, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 204, 205, AZIA Center, No.1233 Lujiazui Ring Rd., Pudong District, Shanghai 200120, China
Tel: +86-21-5877-1818, Fax: +86-21-6887-7858 / -7898

Renesas Electronics Hong Kong Limited
Unit 1601-1613, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2886-9318, Fax: +852 2886-9022/9044

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei, Taiwan
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics Korea Co., Ltd.
11F., Samik Lavied' or Bldg., 720-2 Yeoksam-Dong, Kangnam-Ku, Seoul 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141