

Example of capacitor placement U2B10FCC BGA292

r01an5856ej0110-rh850u2b

Decoupling capacitors

- Capacitor placement and number of capacitors: Please refer page 3 to 4.
 - Capacitors has been kept as close as feasible to the related supply pin.


- Types of capacitors:
 - 0.1uF, 0.22uF, 10uF or higher*1 ceramic capacitor (Low ESR/ESL is required)
 - *1: This is expected value. Please follow the Power IC specification.
 - 10uF 3-terminal ceramic capacitor (Very low ESR/ESL is required)

- 3-terminal capacitor
 - 3-terminal capacitor is recommended for reduction of radiation noise.

Example of capacitor placement

U2B10FCC BGA292


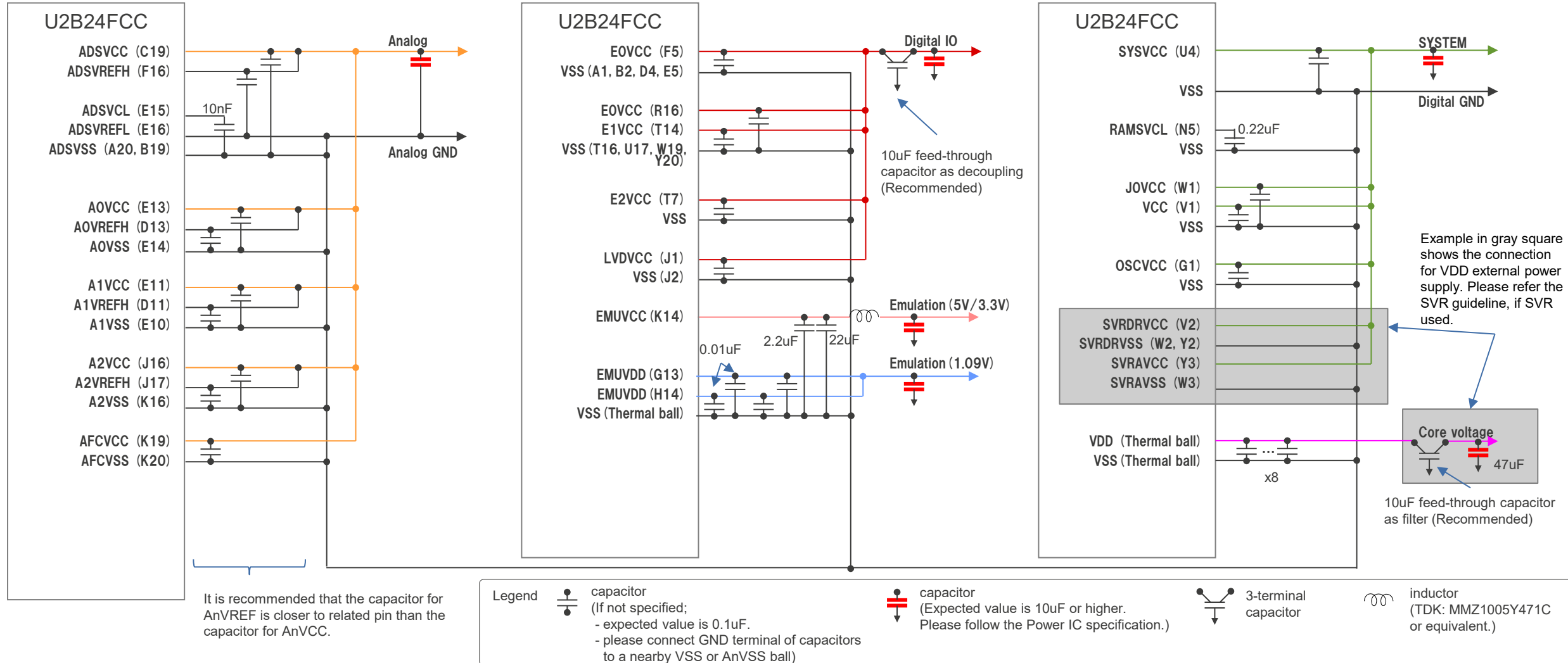
Example capacitor connection for BGA292 package.



PCB layout guidelines -Top layer / Bottom layer-

U2B10FCC BGA292

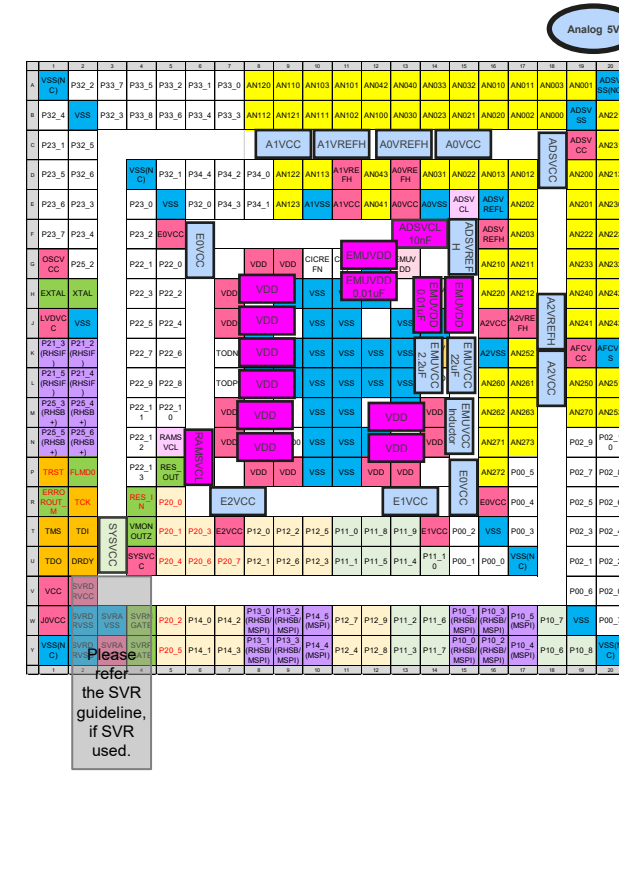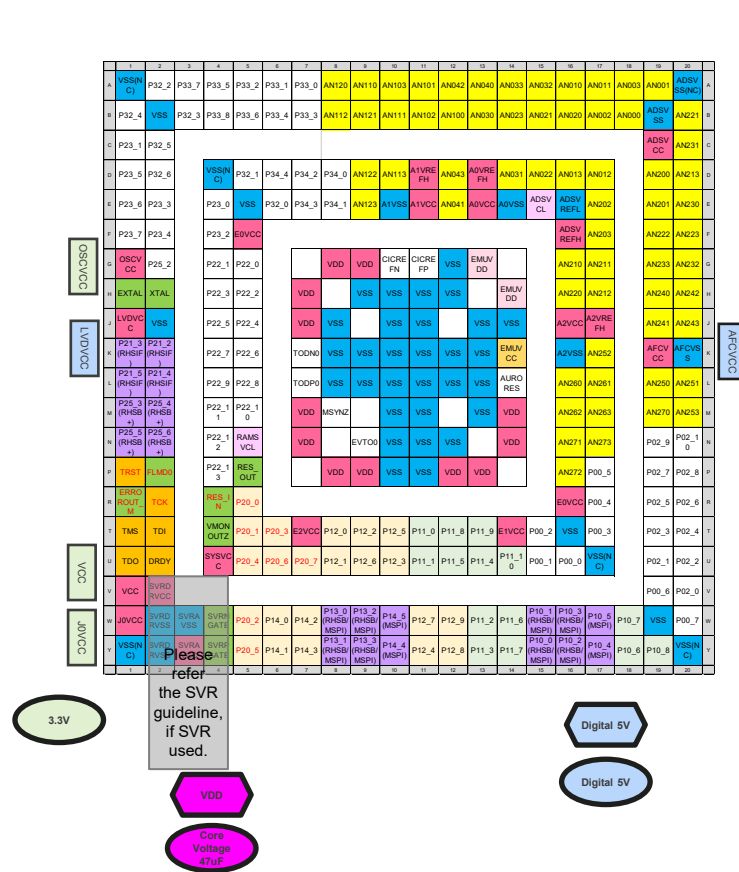Example capacitor placement for BGA292 package



- Legend
- capacitor (analog, Digital IO)
(The capacitance is 0.1uF if not specified.)
 - capacitor (system)
(The capacitance is 0.1uF if not specified.)
 - capacitor (Core voltage)
(The capacitance is 0.1uF if not specified.)
 - capacitor (analog, Digital IO)
(Expected value is 10uF or higher. Please follow the Power IC specification.)
 - capacitor (system)
(Expected value is 10uF or higher. Please follow the Power IC specification.)
 - capacitor (Core voltage)
(Expected value is 10uF or higher. Please follow the Power IC specification.)
 - 3-terminal capacitor (analog, Digital IO)
 - 3-terminal capacitor (Core voltage)

www.renesas.com