

RH850/U2B Group

Main Oscillator Application Note

R01AN6302EJ0110

Rev.1.10

Summary

This document describes precautions when using crystal Oscillator of RH850 / U2B series (after that, U2B).

It is the customer's responsibility to use the information contained in this document for designing the customer's equipment and system. We are not liable for any damages caused by these uses (including damages caused to either the customer or a third party).

Products

- RH850/U2B Group
 - RH850/U2B24
 - RH850/U2B10
 - RH850/U2B6

Contents

1.	Precautions for Crystal Oscillator Implementation	2
1.1	Recommended Circuit for Connecting Crystal Oscillator	2
1.2	Board Pattern Example for Stable Oscillation	3
1.3	Bad Example of Crystal Oscillator Connection	5
1.4	Target Oscillator and Reference Oscillator Circuit Constants	7

1. Precautions for Crystal Oscillator Implementation

When designing the substrate around the crystal Oscillator, it is necessary to pay attention to the contents in this application note for preventing the Oscillation margin of the Oscillator from designing and to suppress the EMI level.

1.1 Recommended Circuit for Connecting Crystal Oscillator

Figure 1 shows the recommended connection circuit of the crystal Oscillator.

U2B mounts the damping resistor (R_d), load capacity (C_{x1} , C_{x2}), and oscillation amplifier.

Basically, the damping resistor (R_d) and load capacity (C_{x1} , C_{x2}) are not necessary to mount showed by Figure 1 to set the internal damping resistor (R_d), load capacity (C_{x1} , C_{x2}), and oscillation amplifier. However, the damping resistor and road capacity may be required depending on the parasitic capacity of the oscillator and board. Please consult with the crystal Oscillator manufacture before making a decision.

Since the feedback resistor is built into the microcomputer, it does not need to be mounted on the board.

Please use an AT-cut fundamental wave specification crystal Oscillator.

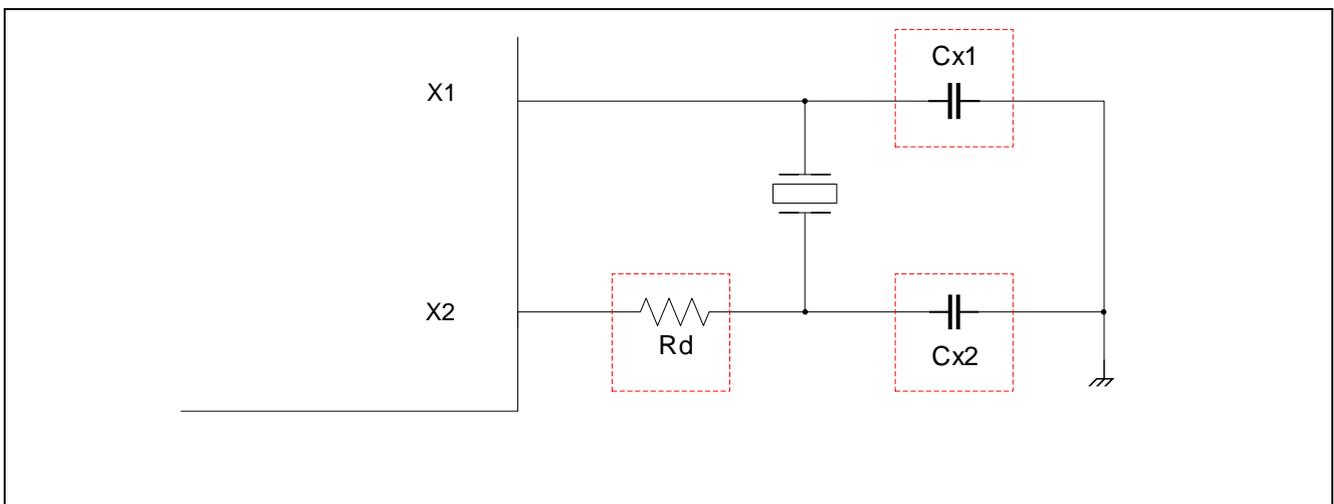


Figure 1 Recommended Connection Circuit of Crystal Oscillator

1.2 Board Pattern Example for Stable Oscillation

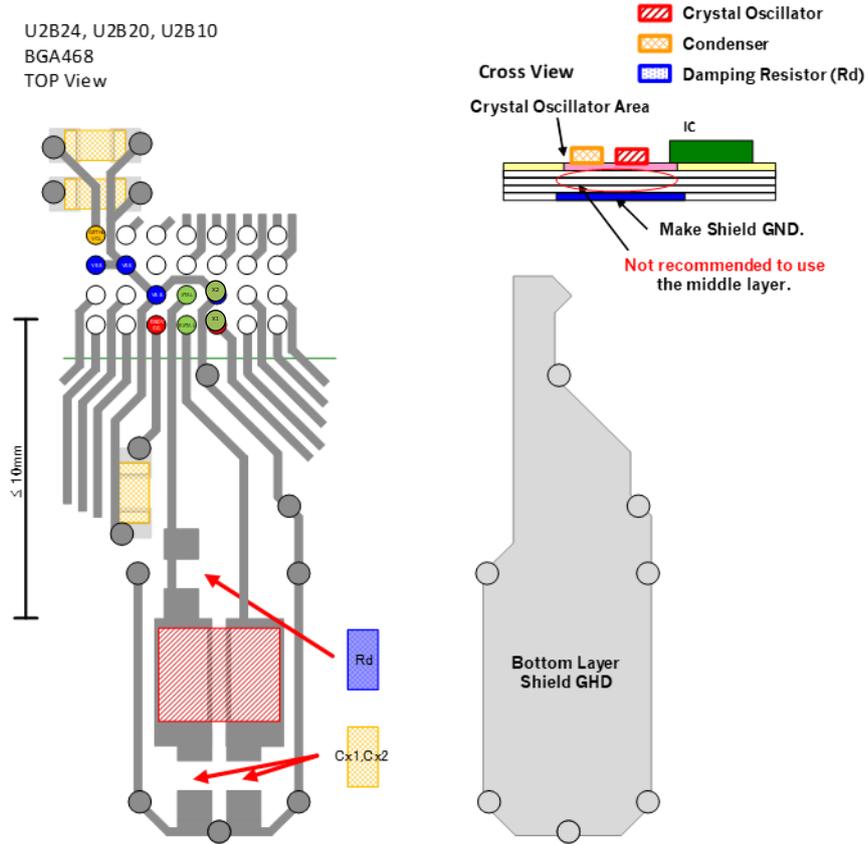


Figure 2 Bord Pattern Example for Stable Oscillation (U2B BGA468)

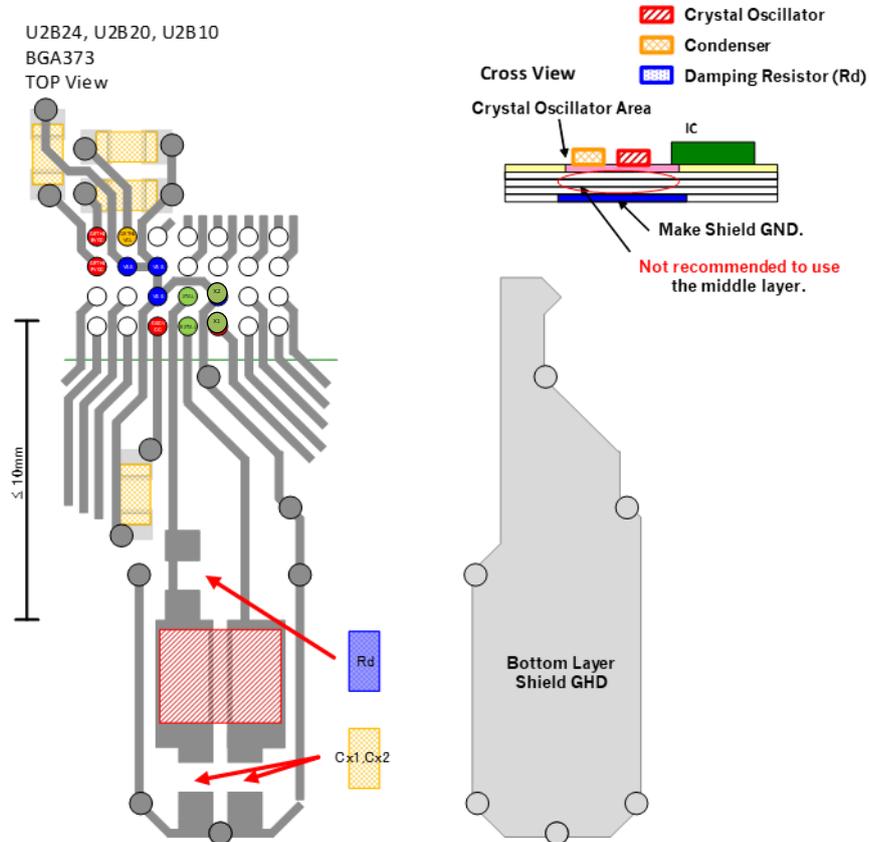


Figure 3 Bord Pattern Example for Stable Oscillation (U2B BGA373)

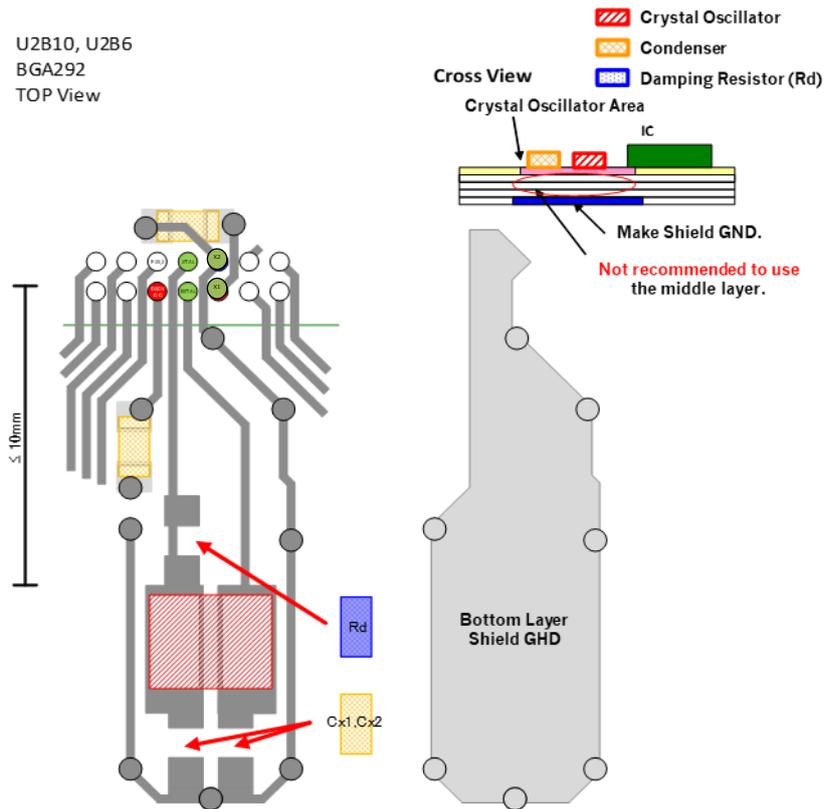



Figure 4 Board Pattern Example for Stable Oscillation (U2B BGA292)

Recommended Wiring Structure for Stable Oscillation

- Wire with metal of top layer board. (GND shield required)
- Place shield GND on bottom layer board.
- Not use middle layer board.
- Wiring length from pin to crystal oscillation is within 10mm.
- Signal wiring width is 0.1 to 0.3mm.
- Signal wiring should be separated from other wiring by 0.3mm or more.
(Wiring interval between X1 and X2 should be also 03 mm or more.)
- X1 and X2 wiring resistance $< 2\Omega$
- X1 and X2 wiring capacity $< 2\text{pF}$
- Connect about 0.1uF condenser between OSCVCC and VSS.

1.3 Bad Example of Crystal Oscillator Connection


Figure 6 and Figure 7 show the bad example of crystal oscillator connections.

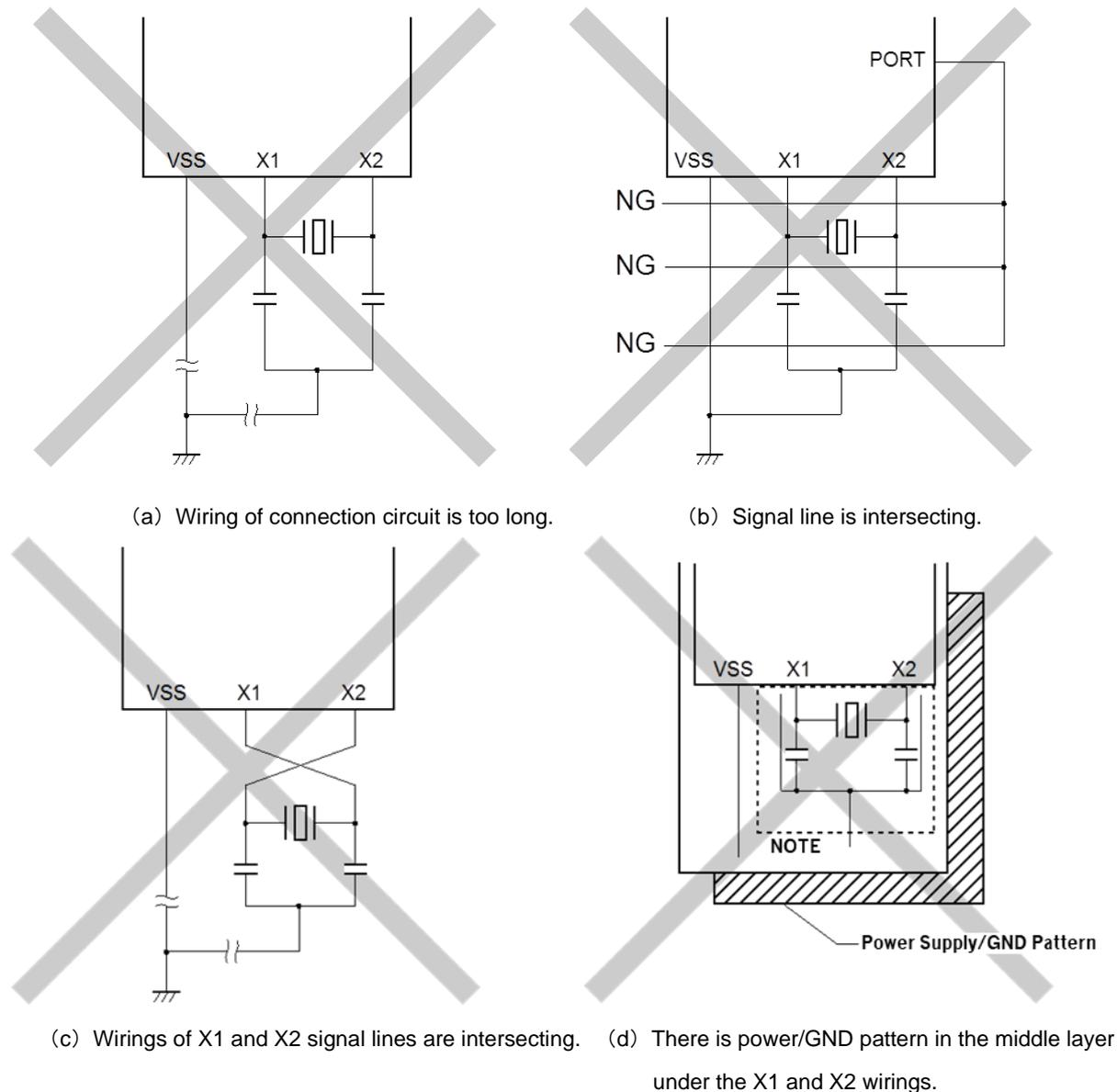


Note The capacitance between PINs between X1 and X2 may deteriorate the oscillation characteristics. Therefore, please avoid signal crossings. Also, when the wiring runs in parallel, pay attention to the wiring interval and parallel running distance so that the capacity during this period does not increase.

On multi-layer board, do not place the power supply/GND pattern under the wiring part between X1/X2 and crystal oscillation. (dotted line part in Figures) Also, secure a space of 0.5mm or more with the ground shield. If the space is not secured, the oscillation characteristics may be affected by the parasitic capacitance increase.


Figure 5 Bad Example of Crystal Oscillator Connection (1/2)

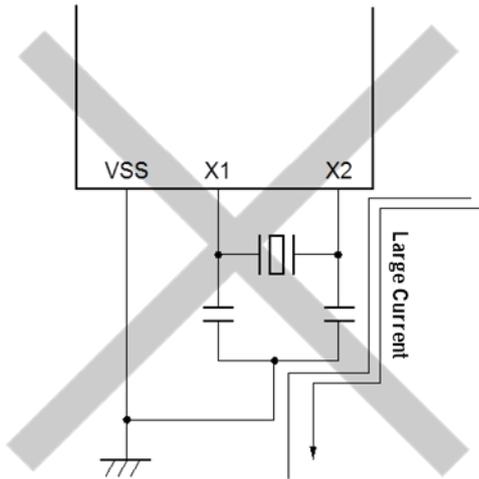

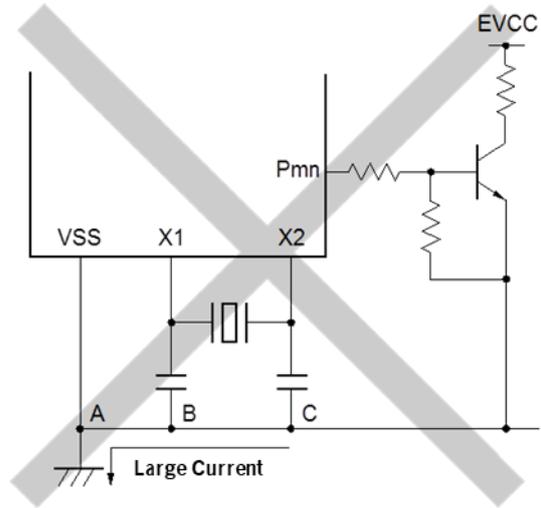(e) Large changing current is close To signal line.



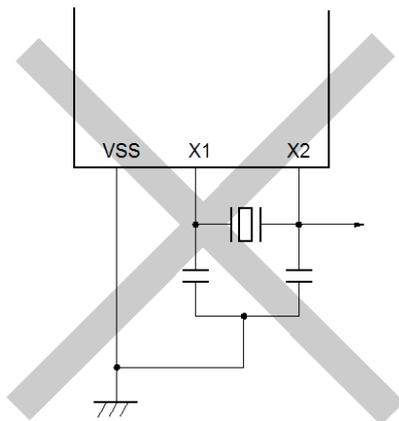(f) Current flows on ground line of oscillation circuit part. (Potentials at points A, B, and C fluctuate.)



(g) Taking out the signal.

Figure 6 Bad Example of Crystal Oscillator Connection (2/2)

1.4 Target Oscillator and Reference Oscillator Circuit Constants

The crystal currently the design target and its reference oscillation circuit constants are shown. This reference oscillation circuit constant was examined by our circuit simulation. To confirm that there is no problem with the oscillation characteristics in the actual application, ask the oscillator manufacturer to evaluate the actual product board.

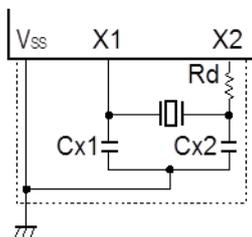


Figure 7 External Circuit Example

Table 1 Target Crystal Oscillator, Ceramic Oscillator and Its Reference Oscillation Circuit Constants^{*1}

Manufa cture	Name	CL (pF)	SMD/ Read	Frequen cy (MHz)	External Oscillator Circuit Constants (Reference) ^{*2}			OSCVCC Power Voltage (V)	OPBT10 Setting (Reference)								
					C _{x1} (pF)	C _{x2} (pF)	R _d (kΩ)		MOSC_EXCLKINPUT	MOSC_FREQ[2:0]	MOSC_CAP_SEL[3:0]	MOSC_SHTSTBY_A	MOSC_SHTSTBY_B	MOSC_AMP_SEL_A[2:0]	MOSC_AMP_SEL_B[2:0]	MOSC_RD_SEL_A[2:0]	MOSC_RD_SEL_B[2:0]
KDS	DSX320GE	8	SMD	16	—	—	—	3.0~5.5V	1	000	0000	1	0	111	111	000	000
		8	SMD	20	—	—	—	3.0~5.5V	1	001	0000	1	0	111	111	000	000
		8	SMD	24	—	—	—	3.0~5.5V	1	010	0000	1	0	111	111	000	000
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0000	1	0	100	111	000	000
		8	SMD	40	—	—	—	3.0~5.5V	1	011	0000	1	0	100	111	000	000
	DSX210GE	8	SMD	20	—	—	—	3.0~5.5V	1	001	0000	1	0	111	111	000	011
		8	SMD	24	—	—	—	3.0~5.5V	1	010	0000	1	0	111	111	000	100
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0000	1	0	100	111	000	000
Kyocer a	CX3225GA	8	SMD	16	—	—	—	3.0~5.5V	1	000	0010	1	0	000	001	001	000
		8	SMD	20	—	—	—	3.0~5.5V	1	001	0010	1	0	000	010	010	000
		8	SMD	24	—	—	—	3.0~5.5V	1	010	0010	1	0	010	011	000	000
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0010	1	0	100	101	000	000
		8	SMD	40	—	—	—	3.0~5.5V	1	011	0010	1	0	100	101	000	000
	CX2016GR	8	SMD	16	—	—	—	3.0~5.5V	1	000	0010	1	0	110	100	100	000
		8	SMD	20	—	—	—	3.0~5.5V	1	001	0010	1	0	001	011	010	000
		8	SMD	24	—	—	—	3.0~5.5V	1	010	0010	1	0	111	100	100	000
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0010	1	0	101	101	000	000
		8	SMD	40	—	—	—	3.0~5.5V	1	011	0010	1	0	101	101	000	000
NDK	NX3225GB	8	SMD	16	—	—	—	3.0~5.5V	1	000	0101	1	0	000	011	000	000
		8	SMD	20	—	—	—	3.0~5.5V	1	001	0101	1	0	011	100	000	000

		8	SMD	24	—	—	—	3.0~5.5V	1	010	0101	1	0	110	101	000	000
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0000	1	0	110	111	000	000
		6	SMD	40	—	—	—	3.0~5.5V	1	011	0000	1	0	110	111	000	000
	NX2016GC	8	SMD	16	—	—	—	3.0~5.5V	1	000	0010	1	0	111	111	100	100
		8	SMD	20	—	—	—	3.0~5.5V	1	001	0001	1	0	101	110	100	100
		8	SMD	24	—	—	—	3.0~5.5V	1	010	0000	1	0	100	111	000	100
		8	SMD	25	—	—	—	3.0~5.5V	1	1??	0000	1	0	111	111	000	010
		6	SMD	40	—	—	—	3.0~5.5V	1	011	0000	1	0	111	111	000	010

Note1. The target crystal oscillator, reference oscillation circuit constants, and OPBT settings are described as reference values based on information from the crystal oscillator manufacturer, and the contents are not guaranteed at all. Reference The oscillation circuit constants are measured and investigated by the oscillator manufacturer using our evaluation board under certain conditions. Since the oscillation operation depends on the oscillator and board, be sure to ask the oscillator manufacturer to evaluate the mounted circuit even in the actual system. In addition, the above conditions are conditions for the oscillator connected to the microcomputer to oscillate, and do not indicate the operating conditions of the microcomputer. For the operating conditions of the microcomputer, use it within the standards of DC and AC characteristics.

Note 2. Since the feedback resistor is built into the microcomputer, it does not need to be mounted on the board.

Our Company's Website and Inquiry

Website

<https://www.renesas.com/>

Inquiry

<https://www.renesas.com/contact/>

All trademarks and registered trademarks are the property of their respective owners.

Revision History

Rev.	Date	Description	
		Page	Summary
1.00	2021.4.26	-	Initial Edition
1.10	2025.4.7	1	Corrected the product list

Precautions for use of the product

This section describes the "Precautions" that apply to all microcontroller products. Please refer to this document and the Technical Update for precautions on individual products.

1. Treatment of unused pins

[Caution] Please dispose of unused pins according to "Handling of unused pins" in the text.

The impedance of the input pins of CMOS products is generally high impedance. If the unused pins are operated in an open state, noise around the LSI may be applied due to the induction phenomenon, a through current may flow inside the LSI, or it may be recognized as an input signal and malfunction may occur. Dispose of unused pins according to the instructions given in "Disposal of unused pins" in the text.

2. Treatment at power-on

[Caution] The state of the product is undefined when the power is turned on.

When the power is turned on, the state of the internal circuits of the LSI is indeterminate and the state of register settings and pins is undefined.

For products that are reset using the external reset pin, the pin state cannot be guaranteed from the time the power is supplied until the reset becomes valid.

Similarly, in the case of products that are reset using the built-in power-on reset function, the pin states cannot be guaranteed from the time the power is turned on until the voltage reaches a certain level.

3. Prohibition of Access to Reserved Addresses

[Caution] Access to reserved addresses is prohibited.

The address area has a reserved address allocated for future function expansion. The operation when these addresses are accessed cannot be guaranteed, so do not access them.

4. About clock

[Caution] When resetting, release the reset after the clock has stabilized.

When switching the clock during program execution, switch the clock after the switching destination clock is stable.

In a system that starts operating with a clock that uses an external oscillator (or external oscillator circuit) at reset, release the reset after the clock is sufficiently stable. Also, when switching to a clock that uses an external oscillator (or external oscillator circuit) in the middle of a program, make sure that the clock to be switched to is sufficiently stable before switching.

5. Differences between products

[Caution] When changing to a product with a different model name, perform a system evaluation test for each product model name.

Even if the MCUs in the same group have different model numbers, the characteristic values, operating margins, noise immunity, noise radiation, etc. may differ within the range of electrical characteristics due to differences in internal ROM and layout patterns. When changing to a product with a different model name, perform a system evaluation test for each individual product.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 "Standard": Computers, office equipment, communications equipment, test and measurement equipment, audio and visual equipment, home electronic appliances, machine tools, personal electronic equipment, industrial robots, etc.
 "High Quality": Transportation equipment (automobiles, trains, ships, etc.), traffic control (traffic lights), large-scale communication equipment, key financial terminal systems, safety control equipment, etc.
 Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations, etc.), or may cause serious property damage (space system, undersea repeaters, nuclear power control systems, aircraft control systems, key plant systems, military equipment, etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
 (Note 2) "Renesas Electronics products" means any product developed or manufactured by or for Renesas Electronics.

(Rev. 4.0-1, November 2011)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to <http://www.renesas.com> for the latest and detailed information.

Renesas Electronics America Inc.

1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
 Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited

9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
 Tel: +1-905-237-2004

Renesas Electronics Europe Limited

Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
 Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH

Arcadastrasse 10, 40472 Düsseldorf, Germany
 Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.

Room 1709 Quantum Plaza, No. 27 Zhichun Lu, Haidian District, Beijing, 100191 P. R. China
 Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.

Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
 Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited

Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
 Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.

13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
 Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.

80 Bendemeer Road, Unit #09-02 Hyflux Innovation Centre, Singapore 339949
 Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.

Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jin Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
 Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.

No 777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
 Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.

17F, KAM CO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
 Tel: +82-2-558-3737, Fax: +82-2-558-5338

© 2018 Renesas Electronics Corporation. All rights reserved.
 Colophon 7.0

