

ISL7184xSEH

Output Capacitance Considerations

Abstract

The ISL7184xSEH's output capacitance for the off channels does not follow a simple capacitance model. It presents a much more complex behavior that results in an anomalous current spike during an output transition. If the source impedance for the active channel is high enough, this added current can distort the output waveform. It is important to note that this phenomena does not affect DC leakage currents.

Contents

1. Anomalous Transient Current Signature.....	2
2. ISL7184xSEH vs HS-1840xRH and ISL7183xSEH.....	3
3. Assessing Peak Current in the ISL7184xSEH.....	4
4. Summary and Conclusion	4
5. Revision History.....	4

List of Figures

Figure 1. Normal Operation (0V to 15V on V_{OUT}) at 25°C	2
Figure 2. Anomalous Current Spike (-5V to 15V) at 25°C.....	2
Figure 3. Anomalous Current Spike (0V to 15V on V_{OUT}) at 125°C	2
Figure 4. Anomalous Current Spike (-5V to 15V) at 125°C.....	2
Figure 5. Anomalous Current Spike vs Output Slew Rate at 125°C	3
Figure 6. HS-1840xRH Behavior at 125°C	3
Figure 7. ISL71840SEH Behavior at 125°C	3
Figure 8. Normalized Peak I_{OUT} per Channel (125°C)	4

Related Literature

For a full list of related documents, visit our website:

- [ISL71840SEH](#), [ISL71841SEH](#) device pages

1. Anomalous Transient Current Signature

The anomalous current is exacerbated by three conditions: output voltage, temperature, and the output slew rate. For output voltage, the current spike may appear as the channel voltage transitions through 3V to 9V. For temperature, the higher the temperature, the larger the current is. For the output slew rate, the faster the slew rate, the larger the current spike. [Figure 1](#) shows the normal (expected) behavior at 25°C versus [Figure 3](#) at +125°C. Bench testing also showed that switching the output from below ground to some positive voltage ensured that the current spike would occur as shown in [Figure 2](#). The test circuit used to generate [Figures 1](#) and [2](#) was configured to drive the output of the multiplexer in a disabled condition with a voltage source through a 1kΩ resistor. The voltage drop across the resistor was used to measure the current going into the output.

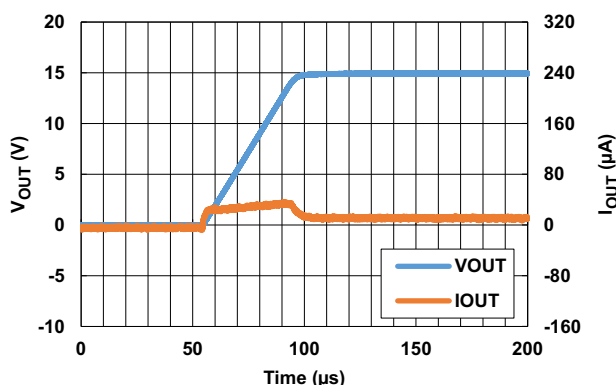


Figure 1. Normal Operation (0V to 15V on V_{OUT}) at 25°C

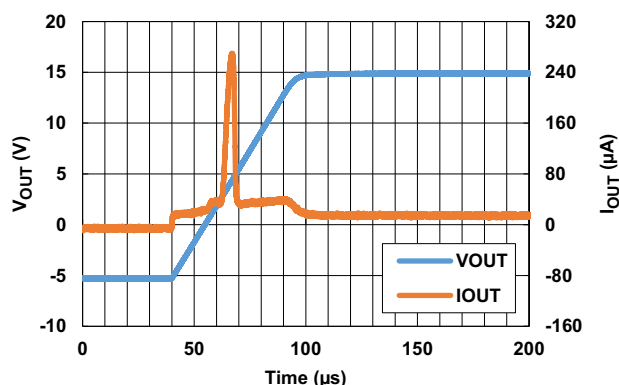


Figure 2. Anomalous Current Spike (-5V to 15V) at 25°C

When the temperature is increased to 125°C, the current spike appears regardless of how low the output voltage gets (as shown in [Figures 3](#) and [4](#)).

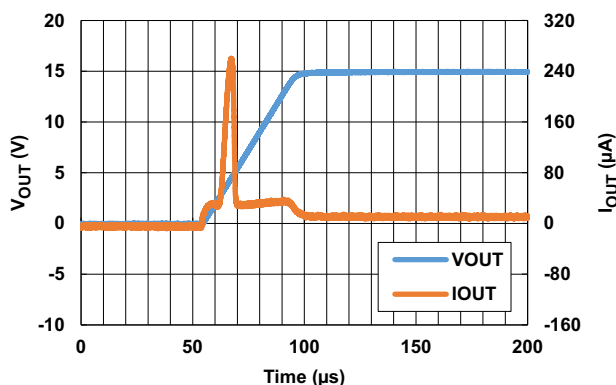


Figure 3. Anomalous Current Spike (0V to 15V on V_{OUT}) at 125°C

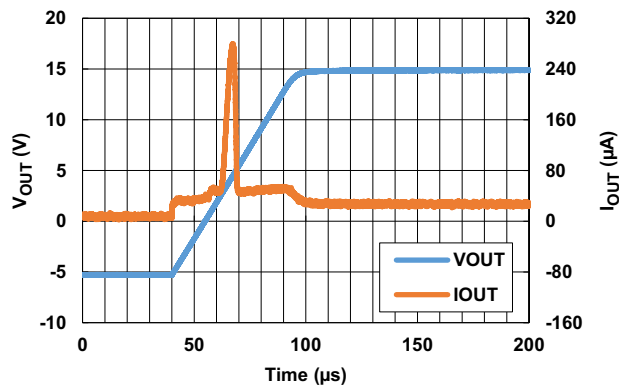


Figure 4. Anomalous Current Spike (-5V to 15V) at 125°C

As expected, the amount of current increases with increasing slew rate. The peak current versus output slew rate was plotted for both the ISL71840SEH and the ISL71841SEH. The peak current from [Figure 5 on page 3](#) shows how much current needs to be sourced from the selected multiplexer input for a given output slew rate to ensure the output waveform is not distorted.

[Figure 5](#) shows that the peak output current is higher for the ISL71841SEH compared to the ISL71840SEH. This is due to the increased number of inactive channels present on the ISL71841SEH. When paralleling multiple multiplexers to increase channel density, the increased current can present a significant load to the active channel.

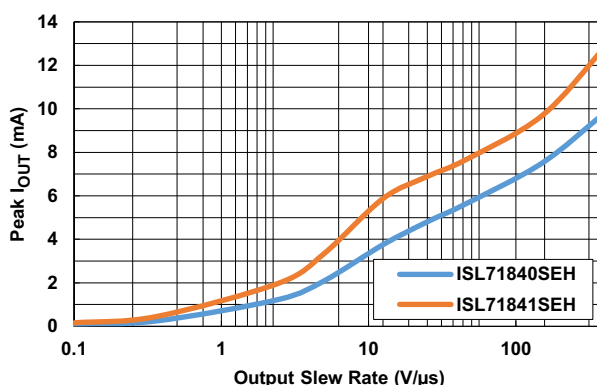


Figure 5. Anomalous Current Spike vs Output Slew Rate at 125°C

2. ISL7184xSEH vs HS-1840xRH and ISL7183xSEH

The ISL7184xSEH was a pin-for-pin replacement for the HS-1840xRH so it is good to see how it reacts under the same conditions. We considered the 0.36V/μs output ramp rate case at 125°C.

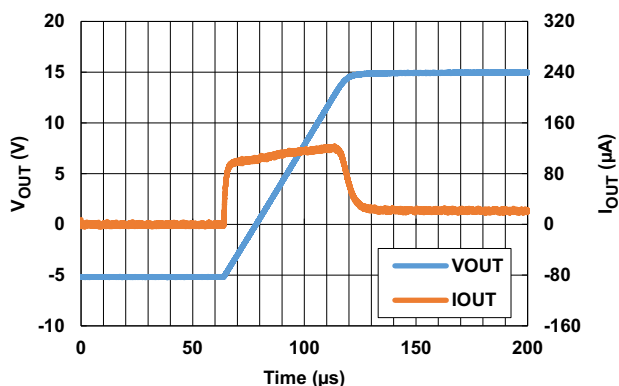


Figure 6. HS-1840xRH Behavior at 125°C

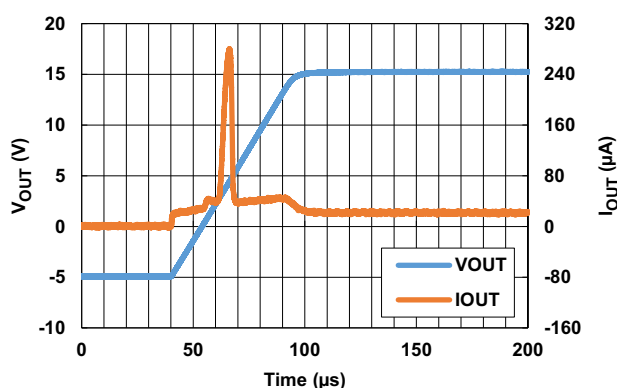


Figure 7. ISL71840SEH Behavior at 125°C

As it can be seen the plateau on I_{OUT} exists for both the HS-1840xRH and the ISL7184xSEH and is due to the inherent output capacitance of the multiplexer. For the HS-1840xRH, the current into the output is constant and in line with a simple capacitance model.

The ISL71830SEH and ISL71831SEH were tested for this anomalous current phenomena and were found to be free of it as well.

3. Assessing Peak Current in the ISL7184xSEH

Normalizing the data in [Figure 5](#) for the ISL71840SEH on a per channel basis we get [Figure 8](#). As the peak currents on a per channel basis are higher on the ISL71840SEH, they can be used as a worst case scenario for the ISL71841SEH.

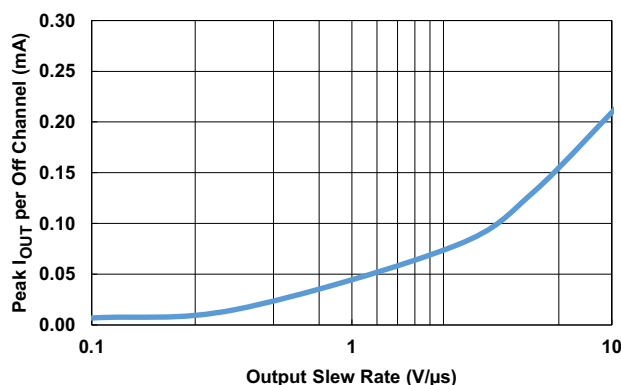


Figure 8. Normalized Peak I_{OUT} per Channel (125°C)

Multiplying the peak current in [Figure 8](#) by the number of off channels connected to the output in a system provides the anomalous current seen during an output transition. Imposing this current against the source impedance of the selected channel allows determination of whether the transient distortion is seen on V_{OUT} . An example of this distortion can be seen in [Figure 9](#) where the temperature is increased from +25°C (no distortion) to +125°C (with distortion).

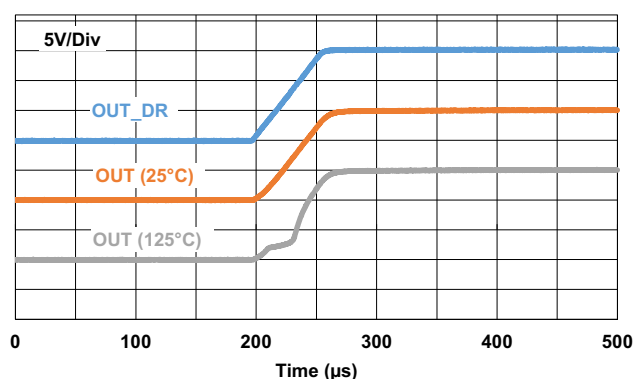


Figure 9. Transient Distortion

4. Summary and Conclusion

If the source impedance of the selected channel is high enough, the anomalous current can result in the output waveform being distorted. The distortion caused by the anomalous current needs to be accounted for during system design and can be quantified using [Figure 8](#). This distortion is a transient phenomenon and does not affect DC performance.

5. Revision History

Rev.	Date	Description
1.00	Dec.6.19	Initial release

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/