

# Trickle Charging Lithium Batteries with the ISL1208 and ISL1209 RTC Devices

TB456  
Rev.0.00  
Dec 7, 2005

## Introduction

The ISL1208 and ISL1209 Real Time Clock (RTC) devices include an active battery backup switchover function. This function allows a backup source tied to the  $V_{BAT}$  pin to assume powering the device once the main  $V_{DD}$  supply has dropped below the minimum operating voltage (see the RTC data sheet). A backup supply is crucial to the function of an RTC since it will enable the device to continue clocking and updating time while the RTC is powered off or during an AC blackout period.

The main options available for backup supplies include a super capacitor, a lithium coin cell, or a rechargeable lithium battery (usually Manganese Lithium or similar chemistry). These sources can provide the microamps of supply current needed by the RTC for extended backup operation yet are available in small, economical packaging.

Super capacitor backup is relatively straightforward. The super capacitor is charged by the main supply through a low leakage, low loss series diode, and the positive terminal is tied to  $V_{BAT}$ . In some cases a series resistor is included in the charging circuit to limit inrush current when power is applied. The ISL1208 and ISL1209 have redundant series elements in the path from  $V_{BAT}$  to  $V_{DD}$  so there is no need for a separate diode connecting the positive terminal of the supercap to the  $V_{BAT}$  pin (see the ISL1208 and ISL1209 datasheets for complete super capacitor backup information).

The lithium coin cell (usually 3.0V, but other types can be up to 3.6V) is connected directly to the  $V_{BAT}$  pin. Lithium batteries are to be protected from any type of charging currents in order to prevent failure (which can be spectacular). The battery switchover circuit containing redundant series protection elements in the RTC devices meets for UL recognition requirements for battery backup. Depending on the size, Lithium coin cells can provide continuous RTC backup for up to 10 years.

## Using Rechargeable Lithium Batteries

Rechargeable Lithium batteries require a trickle charge circuit to keep them near a fully charged state and ready for backup operation. This trickle charge circuit is not unlike the charging circuit for a supercap, except that there are severe restrictions on the voltage applied to the rechargeable Lithium battery. We will concentrate on Manganese Lithium devices here, but other chemistries such as Vanadium Pentoxide Lithiums have similar restrictions.

Rechargeable Lithium batteries do not like simple constant current charging circuits as with Nickel Cadmium batteries. The constant current circuits allow the voltage to drift upward

during trickle charge, and that causes problems with rechargeable Lithiums. Ideally, the voltage should be kept constant at a value from 3.0V to 3.3V in the normal operating temperature range (-20 to +60°C). Charging with a voltage higher than 3.3V not only reduces battery performance but can permanently damage the battery, and reduce the capacity. Charging below 3.0V will undercharge the battery, reducing available capacity and backup time for the RTC. These are the main guidelines for using rechargeable Lithiums, and some simple trickle charging circuits can be used safely with an RTC device to provide reliable long term backup power.

## Trickle Charging Circuits

Since rechargeable Lithiums prefer constant voltage, the simplest method of charging them involves using a low cost linear regulator to apply a regulated constant voltage to the device. Figure 1 shows the preferred circuit, which requires a low dropout regulator and a low-leakage Schottky diode to provide a regulated 3.6V output from a 3.7V to 5.5V input. The Schottky diode prevents excessive discharge currents when the main supply goes away and the series resistor limits maximum charge current when the battery is greatly discharged. Note that no Schottky diode is required between the battery and the  $V_{BAT}$  input, since the RTC device has redundant series elements in the path from  $V_{BAT}$  to  $V_{DD}$ .

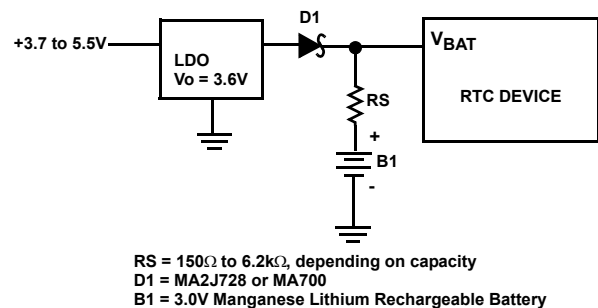


FIGURE 1.

With a regulated 3.6V output from the LDO, the battery should charge up to about 3.3V maximum, keeping it inside the safe operating range. Note that this circuit can be used with a 3.3V ±5% supply, which would replace the LDO output and connect directly to the anode of D1. Care should be taken, if the tolerance of the 3.3V supply is ±10%, then the battery could be subject to excessive charge voltage or significant undercharging.

Another more economical circuit uses a simple resistor divider to provide a charging voltage to the battery, yet keep it within the maximum guidelines allowable. Figure 2 shows this circuit and components used.

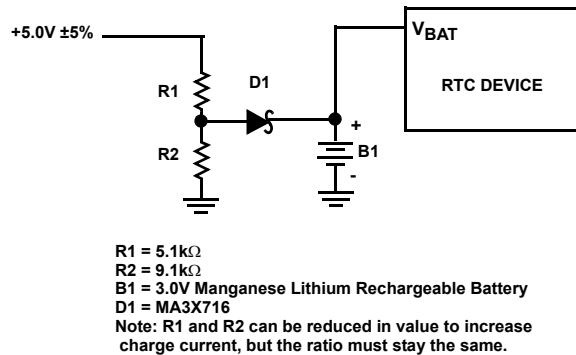


FIGURE 2.

In this circuit the battery will draw current up to where the resistor divider limits the voltage, thus providing a low trickle charge near that voltage. In this circuit, the resistor divider is set to slightly higher than 3.20V, and with the Schottky diode drop this essentially limits the charge voltage to about 3.0V max. Again, note that no Schottky diode is required between the battery and the  $V_{BAT}$  input, since the RTC device has redundant series elements in the path from  $V_{BAT}$  to  $V_{DD}$ . This circuit will allow the battery to charge very near 100% capacity, but will take much longer time than the circuit in Figure 1.

## References

Panasonic; Charging circuits for ML Lithium Coin Cells;  
[http://www.panasonic.com/industrial/battery/oem/images/pdf/Panasonic\\_Lithium\\_ML.pdf](http://www.panasonic.com/industrial/battery/oem/images/pdf/Panasonic_Lithium_ML.pdf)

## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
  2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
  3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
  4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
  5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
  6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
  7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
  8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
  9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
  10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
  11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
  12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



### SALES OFFICES

### Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

**Renesas Electronics America Inc.**  
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.  
Tel: +1-408-432-8888, Fax: +1-408-434-5351

**Renesas Electronics Canada Limited**  
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3  
Tel: +1-905-237-2004

**Renesas Electronics Europe Limited**  
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K  
Tel: +44-1628-651-700, Fax: +44-1628-651-804

**Renesas Electronics Europe GmbH**  
Arcadiastrasse 10, 40472 Düsseldorf, Germany  
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

**Renesas Electronics (China) Co., Ltd.**  
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China  
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

**Renesas Electronics (Shanghai) Co., Ltd.**  
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China  
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

**Renesas Electronics Hong Kong Limited**  
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong  
Tel: +852-2265-6688, Fax: +852-2886-9022

**Renesas Electronics Taiwan Co., Ltd.**  
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan  
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

**Renesas Electronics Singapore Pte. Ltd.**  
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949  
Tel: +65-6213-0200, Fax: +65-6213-0300

**Renesas Electronics Malaysia Sdn.Bhd.**  
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia  
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

**Renesas Electronics India Pvt. Ltd.**  
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India  
Tel: +91-80-67208700, Fax: +91-80-67208777

**Renesas Electronics Korea Co., Ltd.**  
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea  
Tel: +82-2-558-3737, Fax: +82-2-558-5338