

Replacing the Maxim DS1337 RTC with the ISL12057

TB480
Rev 0.00
June 9, 2009

Introduction

Intersil has recently introduced the ISL12057 Real Time Clock (RTC) devices. The device is pin-to-pin (8 Ld SOIC and 8 Ld MSOP package) and software compatible to Maxim DS1337 RTC. In fact, the ISL12057 is an enhancement because it provides:

- Fixed Default Register Values at Power-up
- Flexible Alarm Selection
- Stable Frequency Output vs V_{DD}
- Smaller Package Option - 2mmx2mm μ TDFN (Tiniest RTC available in the market)

The features are detailed in the data sheets. This Technical Brief provides information for an engineer wishing to use the ISL12057 to replace the DS1337 in their system.

Replacing the DS1337 with the ISL12057

The ISL12057 can drop into a DS1337 socket with no hardware and software changes required.

There is one difference that may affect hardware requirements. The DS1337 can operate at V_{DD} up to 5.5V, while the ISL12057 has an operating range up to 3.6V. The ISL12057 allows SDA, SCL, IRQ1 and IRQ2 to be pulled up to 5.5V.

A system that has the I²C lines pulled up to 5.5V (or other voltage higher than 3.6V), but has a 3.3V regulator on board requires a simple modification to connect the V_{DD} to 3.3V instead of 5.5V. Figure 1 shows an example circuit with V_{DD} to 3.3V and I²C lines and IRQx pulled up to 5.5V

A system that cannot connect V_{DD} to voltage lower than 3.6V can use a Zener diode on V_{DD} pin to lower the V_{DD} to 3.6V or below. Figure 2 shows an example circuit with a Zener diode to lower the 5.5V input voltage to 3.3V for V_{DD} .

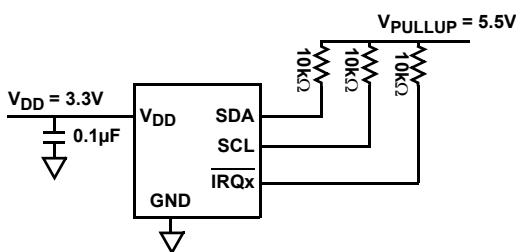


FIGURE 1. EXAMPLE CIRCUIT WITH V_{DD} AT 3.3V AND I²C AND IRQx PULLED UP TO 5.5V

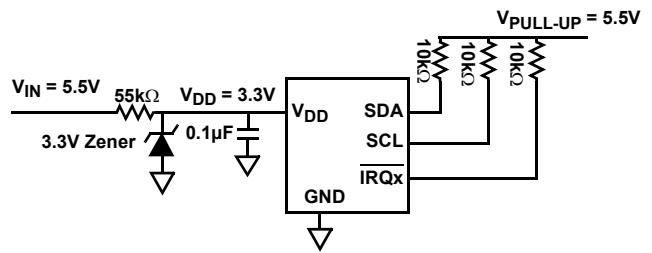


FIGURE 2. EXAMPLE CIRCUIT WITH ZENER DIODE ON V_{DD} TO REDUCE INPUT VOLTAGE TO 3.3V

Advantage on Using ISL12057 vs DS1337

The ISL12057 has a fixed default register value at power-up so a system can easily check for a power failure condition by examination the register value versus the default value.

The ISL12057 has a flexible alarm selection for the two alarms versus the fixed alarm selections for the DS1337. For Alarm1, the ISL12057 has a total of 24 alarm selections. For Alarm2, the ISL12057 has a total of 12 alarm selections. The Alarm can be set to any Clock/Calendar value for a match. For example, every minute, every Tuesday or at 5:23 AM on 1st day of a month.

The ISL12057 has more stable frequency output versus V_{DD} than the DS1337. Figure 3 shows the 32.768kHz F_{OUT} vs V_{DD} for ISL12057 and DS1337. As the graph shows, the ISL12057 32.768kHz F_{OUT} is flat across V_{DD} but the DS1337 has a linear slope on the 32.768kHz F_{OUT} across V_{DD} .

The ISL12057 has the 8 Ld SOIC and MSOP package that are pin-to-pin compatible to the DS1337. In addition to the SOIC and MSOP packages, the ISL12057 offers the tiniest 2mmx2mm μ TDFN package. A standard 8 Ld SOIC package occupies approximately 29.4mm² (4.9mmx6mm) of board space, and a standard 8 Ld MSOP package occupies approximately 14.7mm² (3mmx4.9mm) of board space. The ISL12057 2mmx2mm μ TDFN package only occupies 4mm² (2mmx2mm) of board space, which is equal to 86% space saving versus the 8 Ld SOIC package and 72% space saving versus the 8 Ld MSOP package. Figure 4 shows the package dimension for μ TDFN, MSOP, and SOIC.

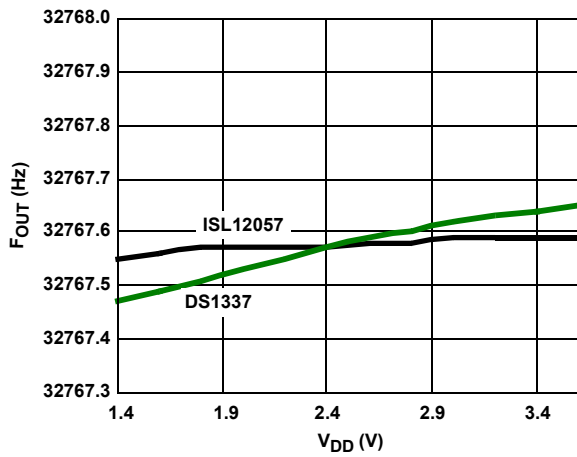


FIGURE 3. F_{OUT} vs V_{DD}

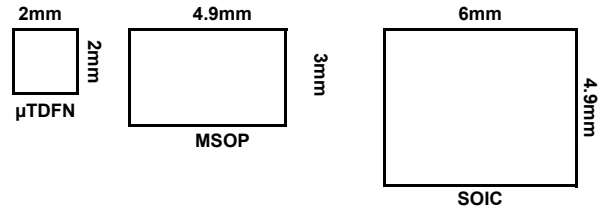


FIGURE 4. PACKAGE DIMENSION (NOT ACTUAL SIZE)

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338