

ISL6288x Products

VR_ON Timing Guidelines

TB496
Rev 0.00
August 6, 2013

Introduction

The rise time of the VR_ON signal must be designed such that the internal circuitry can tolerate noise dips to prevent improper soft-start of the controller. This document aids the user in designing the VR_ON circuitry.

The VR_ON signal is simply used by the controller to determine when to begin the soft-start sequence. Depending on the placement and layout of components around the controller, the magnitude of noise which could couple onto the VR_ON signal can vary. Typically a capacitor is placed on the VR_ON pin to provide decoupling of the signal from noise. Adjusting the rise time of the VR_ON signal can also address potential issues due to noise induced changes in the signal level.

Rise Time Analysis

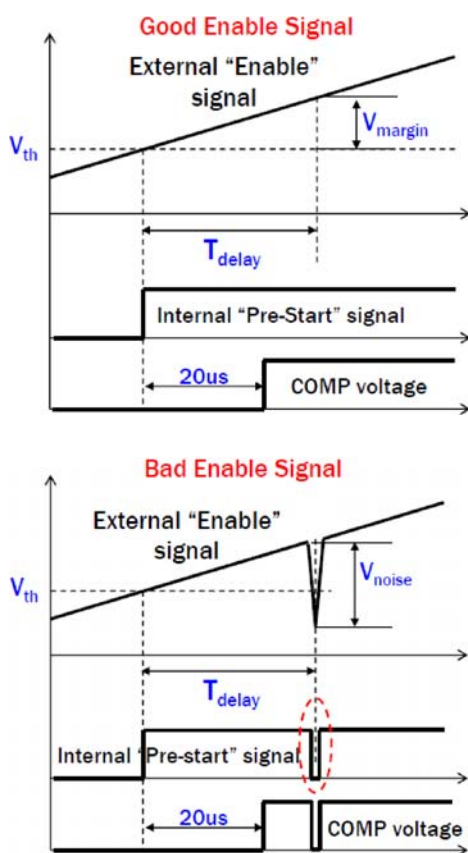


FIGURE 1.

Figure 1 shows two scenarios, one for a good and the other for a bad VR_ON signal. The V_{th} level represents the threshold at which the controller will begin the soft-start sequence as described in the datasheet. Once the VR_ON signal exceeds this threshold, an internal "Pre-Start" signal sets soft-start operation in motion. T_{delay} is a time delay which is typically 24 μ s, but has a minimum of 15 μ s. This is the delay in locking in the soft-start activity and this provides a measure of the

voltage margin the controller can tolerate, V_{margin} . The COMP pin voltage will begin to rise 20 μ s after VR_ON exceeds the V_{th} threshold as the internal circuitry is beginning to power up. This all occurs during the 800 μ s delay time shown in the datasheet during which time the output voltage is not moving.

In the case of a bad enable signal, a noise event occurs during the T_{delay} time which drops VR_ON more than the V_{margin} level. This results in an internal glitch on the Pre-Start signal since the V_{th} threshold has been exceeded again. This can result in a failure to soft-start properly due to the glitch on the Pre-Start signal. In order to prevent noise related glitches from occurring, V_{margin} must be greater than V_{noise} .

The rise time of the VR_ON signal cannot be faster than 12 μ s. This allows the internal soft-start circuitry time to wake up once VDD is applied. A 15 μ s rise time on VR_ON is recommended for applications which require a fast rise time to provide margin above the 12 μ s outlined previously. The rise time is not recommended to be slower than 500 μ s. This prevents slow moving VR_ON signals from encountering issues due to noise. If a slower rise time on VR_ON is needed, then Equation 1 must be met to prevent soft-start issues.

$$VR_ON \text{ Total Rise Time} < \frac{VR_ON \text{ Logic Level}}{\left[\frac{Noise \text{ Level}_{max}}{T_{delay_min}} \right]} \quad (EQ. 1)$$

For example, if a noise level of 30mV is the maximum in a design. Then, using a typical logic level of 3.3V that VR_ON is rising to and the T_{delay} minimum timing of 15 μ s, the total rise time VR_ON must be below calculates to be 1.65ms. See the calculation below in Equation 2:

$$\frac{3.3V}{\left[\frac{30mV}{15\mu s} \right]} = 1.65ms \quad (EQ. 2)$$

For a 30mV noise level, the rise time of VR_ON must be faster than 1.65ms for V_{margin} to be greater than V_{noise} to prevent soft-start issues due to noise glitches on VR_ON. The noise level used in the calculation must be worse case expectation to accurately predict and prevent soft-start issues.

A second area of concern with soft-start is the state of the VID pin pull-up voltage at the time VR_ON is applied or removed. The pull-up voltage must be present prior to VR_ON rising or enabling the controller. If the pull-up voltage is not present, the controller will read the improper VID code prior to soft-start. The pull-up voltage for the VID pins must also be present during the time VR_ON is falling until the controller is disabled. Without proper voltage available for the VID pins during either VR_ON event, the controller can get incorrect VID information which can result in improper operation. For example, if the pull-up voltage is not available prior to or during VR_ON rising and enabling the controller, the VID information decoded for soft-start output voltage would be all zeros for the VIDs. This results in the output voltage being programmed to 1.50V, which could be well beyond the level desired by design of the system.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338