

# IGBT, FRD

## How do smaller Co-Pack Diodes help improve IGBT Performance in UPS/PV Inverters?

### Introduction

Renesas G8H series IGBT+FRD co-pack discrete products are suitable for high frequency UPS/PV inverter applications. The product concept is to have a smaller current rating of co-packed FRD to achieve the best performance, especially at light to medium load operation and good cost.

### Target Device

IGBT & FRD

### Contents

|                                                         |   |
|---------------------------------------------------------|---|
| 1. Discrete IGBT products .....                         | 2 |
| 2. What is the current rating of Discrete devices ..... | 2 |
| 3. UPS and PV inverter operating conditions .....       | 3 |
| 4. Power loss in FRD .....                              | 4 |
| 5. G8H concept.....                                     | 5 |
| 6. Summary .....                                        | 6 |
| 7. References Application Note .....                    | 6 |
| Revision History .....                                  | 7 |

## 1. Discrete IGBT products

A wide range of IGBT products are utilized in the power electronics market. Especially in the industrial power converter market, there are a lot of discrete packaged products implemented. Almost all discrete IGBT products have a co-pack diode in the same package for reverse current conduction.

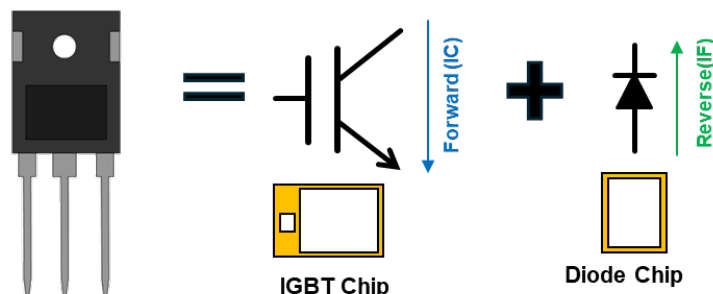


Figure 1 IGBT Diode co-pack device

The diode is mandatory for IGBT in inverter applications which require reverse current conduction to power devices. IGBT characteristics are very important for the efficiency of inverter circuit, but the co-pack diode is also important for the performance and the overall device cost. In this article, the Renesas G8H generation IGBT/FRD concept is explained in relation to its target applications, including UPS and PV inverters.

## 2. What is the current rating of Discrete devices

Power devices have absolute maximum ratings for voltage, current, and temperature. Renesas has a dedicated application note for each parameter definition. Design engineers refer to “Collector current  $I_C$ ” and “Diode forward current  $I_F$ ” individual ratings to find the correct device for their application. However, in practice, comparing the maximum current in the application with  $I_C$  and  $I_F$  is not meaningful. Those current ratings are DC current ratings defined by the formula below. Actual current in inverter applications is not DC current

$$I_C = \frac{(T_{jmax} - T_c)}{R_{th(j-c)} \times V_{CE(sat)}}$$

Equation 1: DC current rating definition.

IGBT and Diode can support higher current than the  $I_C$  &  $I_F$  ratings as long as the junction temperature does not exceed the junction temperature rating ( $T_{jmax}$ ) and peak current does not exceed  $I_C$  (peak) or  $I_F$  (peak).

### 3. UPS and PV inverter operating conditions

The UPS and Photovoltaics (PV) market is growing at a rapid pace. Those applications contribute to carbon dioxide emission reduction. Both applications have inverter circuits, requiring high voltage switch solutions, such as discrete IGBTs.

In inverter circuits, IGBT (and diode) work with the PWM gate control. Their conduction duty is dependent on the Power Factor (PF). In Figure 2, the blue area shows IGBT conduction duty, the green area shows diode duty. As depicted in Figure 2, They are the same duty under PF=0 condition and IGBT conduction area is bigger than diode in cases where PF>0.

In the inverter of UPS and PV applications case, PF is nearly +1.0, and never goes to the PF<0 condition. This means that the diode's forward voltage, which contributes to conduction loss, has minimal impact on the performance of UPS and PV systems. On the other hand, switching loss and diode recovery loss are independent of the power factor (PF) and are instead influenced by the switching frequency.

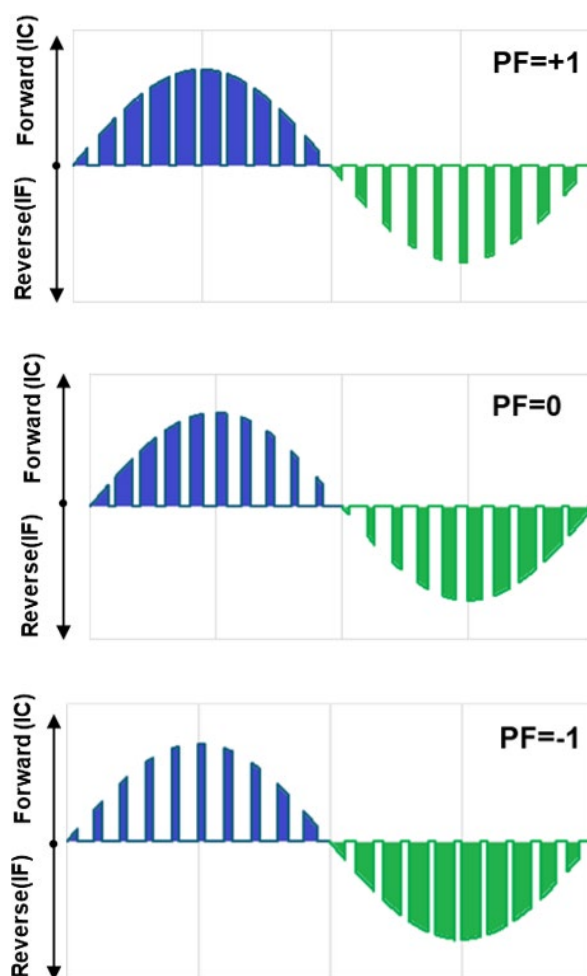


Figure 2 PF dependency of IGBT and Diode conduction duty.

#### 4. Power loss in FRD

Conduction loss by  $V_F$  and Recovery loss by  $Q_{rr}$  are the power loss factors in diode characteristics. They are in a trade-off relationship such that if we design the diode to focus on low recovery loss, that affects Forward voltage and vice versa. In addition, both power losses depend on chip size. Generally speaking, a bigger chip has lower  $V_F$  and higher  $Q_{rr}$ . Chip size directly relates to  $I_F$  rating.

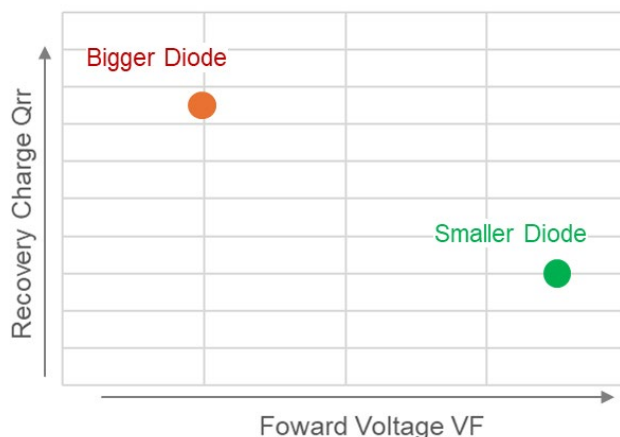


Figure 3 Chip size dependency of Diode characteristics.

Another important point is that  $Q_{rr}$  also impacts the IGBT turn-on loss. The basic half bridge configuration is shown in Figure 4. The high side diode is in conduction state before the turn-on of the low side IGBT. Then, recovery current appears in the turn-on current waveform and affects turn-on loss.

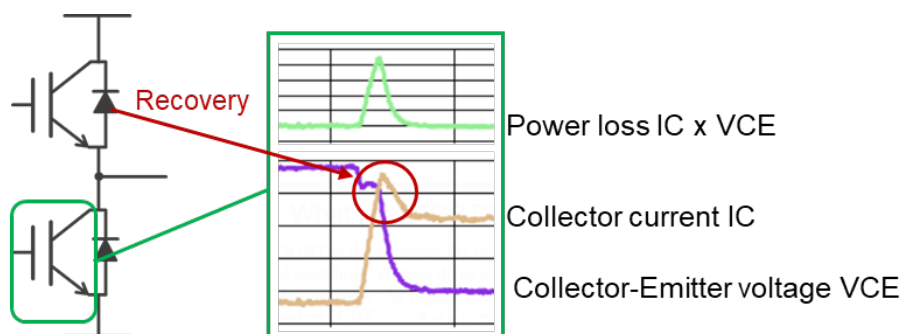


Figure 4 Turn-on waveform, recovery affects turn-on loss

This indicates that for UPS and PV inverters, a smaller co-pack diode rating compared to the IGBT might be more suitable, as the diode's conduction duty is lower than that of the IGBT. Additionally, a smaller diode can help reduce both recovery loss and IGBT turn-on loss.

## 5. G8H concept

Renesas conducted an investigation to determine the optimal diode size for UPS and PV applications. Renesas simulated the total power loss of the IGBT and diode based on an evaluation of switching characteristics. The device consists of a 650V 50A class IGBT. Two different co-pack diode sizes, 30A (smaller) and 50A (larger), were evaluated in combination with the IGBT with the same voltage class. Those current classes refer to the IC and IF rating. As you can see in Figure 5, IGBT + Smaller diode configuration shows smaller Power loss thanks to low recovery loss and low Turn-ON loss. Even though diode conduction loss is higher, smaller diode can contribute 2.5% improvement in efficiency. Another important point is that we can save diode chip cost by 20% with a smaller chip. This achieves a good cost and performance balanced solution.

Note, a smaller chip has a smaller IF rating, and higher thermal resistance, but power loss of the diode is sufficiently small due to low duty (Figure 2) and Tj of the diode that it does not exceed its Tj maximum rating.



**Figure 5 Total power loss simulation conditions and results**

This is one of the Renesas G8H series key concepts. Based on this result and application requirements, Renesas has optimized its IGBT product lineups as shown in Table 1, where the co-pack diode has smaller current rating than the IGBT for better performance in UPS and PV applications.

**Table 1 Renesas G8H series lineups**

| Part Number       | VCES[V] | IC [A] | IF[A] |
|-------------------|---------|--------|-------|
| RBN25H125S1FPQ-A0 | 1250    | 25     | 15    |
| RBN40H125S1FPQ-A0 | 1250    | 40     | 25    |
| RBN75H125S1FP4-A0 | 1250    | 75     | 50    |
| RBN40H65T1FPQ-A0  | 650     | 40     | 30    |
| RBN50H65T1FPQ-A0  | 650     | 50     | 50    |
| RBN75H65T1FPQ-A0  | 650     | 75     | 50    |

## 6. Summary

The inverter circuit in UPS and PV are operated under high PF conditions. In high PF operation, diode conduction duty is low, so a smaller diode should be better for circuit efficiency. Renesas confirmed by power loss simulation. A smaller diode contributes to total performance as well as cost improvement. Furthermore, a smaller diode has higher thermal resistance, but power loss is low enough in high PF operation that we can keep lower junction temperature than the  $T_j$  max rating. So a smaller IF rating diode can work with a higher IC rating IGBT.

Renesas G8H series is focused on UPS and PV applications. The lineup includes smaller diodes to improve cost and efficiency. Renesas next generation IGBT discrete series is currently under development. Renesas has plans for a larger lineup to support additional applications, such as UPS, PV, EV charging system, motor drive and more, while keying in on further performance improvement.

## 7. References Application Note

- [1] [IGBT Application Note](#): Renesas.com
- [2] [IGBT Usage Notes on Gate Drive](#): Renesas.com
- [3] [Renesas automotive IGBT technology improvement](#): Renesas.com

**Revision History**

| Rev. | Date       | Description |               |
|------|------------|-------------|---------------|
|      |            | Page        | Summary       |
| 1.00 | 12.02.2024 | -           | First edition |

## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall be responsible for determining what licenses are required from any third parties, and obtaining such licenses for the lawful import, export, manufacture, sales, utilization, distribution or other disposal of any products incorporating Renesas Electronics products, if required.
5. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
6. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.

7. No semiconductor product is absolutely secure. Notwithstanding any security measures or features that may be implemented in Renesas Electronics hardware or software products, Renesas Electronics shall have absolutely no liability arising out of any vulnerability or security breach, including but not limited to any unauthorized access to or use of a Renesas Electronics product or a system that uses a Renesas Electronics product. RENESAS ELECTRONICS DOES NOT WARRANT OR GUARANTEE THAT RENESAS ELECTRONICS PRODUCTS, OR ANY SYSTEMS CREATED USING RENESAS ELECTRONICS PRODUCTS WILL BE INVULNERABLE OR FREE FROM CORRUPTION, ATTACK, VIRUSES, INTERFERENCE, HACKING, DATA LOSS OR THEFT, OR OTHER SECURITY INTRUSION ("Vulnerability Issues"). RENESAS ELECTRONICS DISCLAIMS ANY AND ALL RESPONSIBILITY OR LIABILITY ARISING FROM OR RELATED TO ANY VULNERABILITY ISSUES. FURTHERMORE, TO THE EXTENT PERMITTED BY APPLICABLE LAW, RENESAS ELECTRONICS DISCLAIMS ANY AND ALL WARRANTIES, EXPRESS OR IMPLIED, WITH RESPECT TO THIS DOCUMENT AND ANY RELATED OR ACCOMPANYING SOFTWARE OR HARDWARE, INCLUDING BUT NOT LIMITED TO THE IMPLIED WARRANTIES OF MERCHANTABILITY, OR FITNESS FOR A PARTICULAR PURPOSE.
8. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
12. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
13. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
14. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.5.0-1 October 2020)

## Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan

[www.renesas.com](http://www.renesas.com)

## Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

## Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:

[www.renesas.com/contact/](http://www.renesas.com/contact/).