

RX62T Group

R01AN0638EJ0100

Rev.1.00

Notes on Analog Power Supply Printed Circuit Board Patterns

Sep 27, 2011

Introduction

This application note discusses the layout of the analog power supply lines on printed circuit boards used for RX62T Group microcontroller applications.

Target Device

RX62T Group

This application note also applies to other microcontrollers in the RX Family that have the same A/D converter as the RX62T Group microcontroller. Note, however, that since certain aspects of the functions used may be changed in other devices, the documentation for the device used must be checked carefully before using the information provided in this application note.

Contents

- | | | |
|----|---------------------------------------|---|
| 1. | Notes on Power Supply Pin Layout..... | 2 |
| 2. | Reference Documents..... | 9 |

1. Notes on Power Supply Pin Layout

1.1 Separating Digital and Analog Circuits

Digital and analog circuits should be separated as much as possible. In particular, avoid allowing digital signal lines to run close to or to cross analog signal lines so that digital circuit signals do not appear as noise in analog circuits.

The 12-bit A/D converter analog input pins (AN000 to AN003 and AN100 to AN103), the analog reference power supply (VREFH0 and VREFL0), and the analog supply voltage (AVCC0) should be separated from the digital circuits by the analog ground (AVSS0). Furthermore, the analog reference ground (VREFL0) and the analog ground (AVSS0) should be connected to a stabilized ground (VSS) on the board at a single point.

Similarly, the 10-bit A/D converter analog input pins (AN00 to AN11), the analog reference power supply (VREF), and the analog supply voltage (AVCC) should be separated from the digital circuits by the analog ground (AVSS). Furthermore, the analog ground (AVSS) should be connected to a stabilized ground (VSS) on the board at a single point.

To acquire high-quality analog inputs, the analog ground plane and the digital ground plane should be allocated to separate individual layers in the PCB.

The table below lists the setting ranges for the analog pins. If the A/D converters are not used, do not leave any of the following pins open: the AVCC0, AVSS0, VREFH0, and VREFL0 pins for the 12-bit A/D converter and the AVCC, AVSS, and VREF pins for the 10-bit A/D converter.

Table 1 Analog Pin Setting Ranges (3 V Version)

Analog Pin	When an A/D converter is used	When the A/D converter is not used
AVCC0, AVCC	AVCC0 = AVCC = 3.0 V to 3.6 V or 4.0 V to 5.5 V	AVCC0 = AVCC = VCC
AVSS0, AVSS	AVSS0 = AVSS = VSS ^{*1}	AVSS0 = AVSS = VSS
VREFH0	VREFH0 = 3.0 V to AVCC0 or 4.0 V to AVCC0	VREFH0 = AVCC0
VREFL0	VREFL0 = AVSS0 ^{*1}	VREFL0 = AVSS0
AN000 to AN003 AN100 to AN103	VREFL0 ≤ VAN ≤ VREFH0 ^{*2}	^{*3}
VREF	VREF = 3.0 V to AVCC or 4.0 V to AVCC	VREF = AVCC
AN00 to AN11	AVSS ≤ VAN ≤ VREF ^{*2}	^{*3}

Notes: 1. AVSS0, AVSS, and VREFL0 should be connected to a stable ground (VSS) at a single point.

2. VAN: Voltage applied to the analog input pin ANn.

3. Unused pins must be handled as directed in the Hardware Manual for the device used.

Table 2 Analog Pin Setting Ranges (5 V Version)

Analog Pin	When an A/D converter is used	When the A/D converter is not used
AVCC0, AVCC	AVCC0 = AVCC = 4.0 V to 5.5 V	AVCC0 = AVCC = VCC
AVSS0, AVSS	AVSS0 = AVSS = VSS ^{*1}	AVSS0 = AVSS = VSS
VREFH0	VREFH0 = 4.0 V to AVCC0	VREFH0 = AVCC0
VREFL0	VREFL0 = AVSS0 ^{*1}	VREFL0 = AVSS0
AN000 to AN003 AN100 to AN103	VREFL0 ≤ VAN ≤ VREFH0 ^{*2}	^{*3}
VREF	VREF = 4.0 V to AVCC	VREF = AVCC
AN00 to AN11	AVSS ≤ VAN ≤ VREF ^{*2}	^{*3}

Notes: 1. AVSS0, AVSS, and VREFL0 should be connected to a stable ground (VSS) at a single point.

2. VAN: Voltage applied to the analog input pin ANn.

3. Unused pins must be handled as directed in the Hardware Manual for the device used.

1.2 Power Supply Pin Capacitors

Insert a $0.1\ \mu\text{F}$ capacitor between each of the following pairs: between VCC and VSS, between AVCC0 and AVSS0, between VREFH0 and VREFL0, between AVCC and AVSS, and between VREF and AVSS. Furthermore, these noise countermeasures can be improved further by inserting a $0.1\ \mu\text{F}$ capacitor between AVCC0 and VREFL0. Design the layout so that each of these power supply capacitors forms the shortest closed loop possible. The lengths of these lines between capacitor and power supply pin must be made as equal as possible and furthermore, as short as possible. Also, the power supply lines and ground lines should be made as wide as possible.

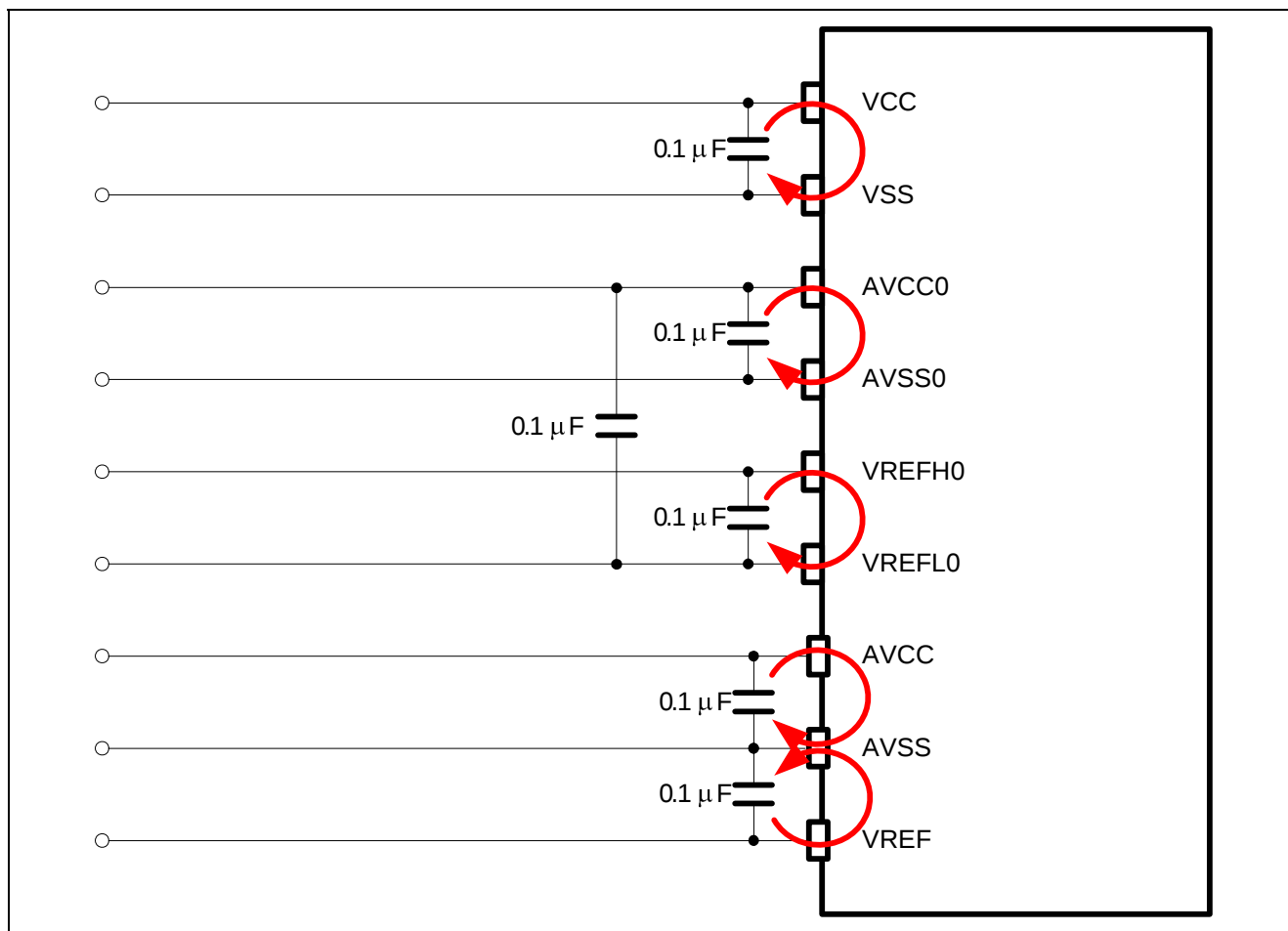


Figure 1 Power Supply Pin Capacitors and Closed Loops

1.3 Power Supply Pin Layout Examples

This section presents examples of analog power supply pin capacitor layouts using 4-layer printed circuit boards.

The board surfaces are allocated as follows: the top surface is the component plane, layer 2 is the ground plane, layer 3 is the power supply plane, and the back surface is the solder plane. After capacitor decoupling, each of the AVCC0, VREFH0, AVSS0, VREFL0, AVCC, VREF, and AVSS pins should be connected to the corresponding power supply plane. Although this example only shows the analog power supply pins, similar decoupling should also be used between VCC and VSS.

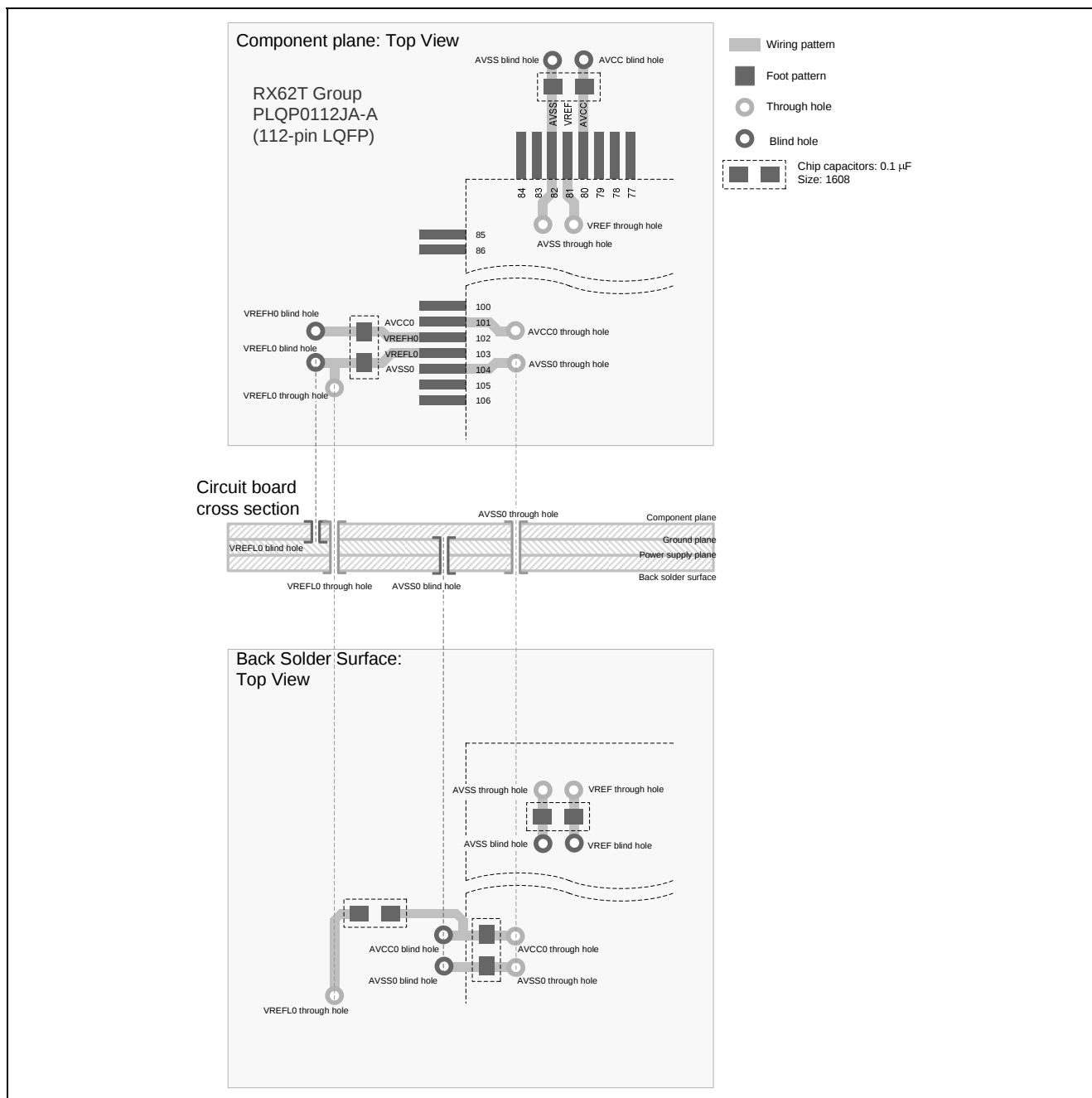


Figure 2 RX62T 112-Pin LQFP Package Power Supply Pin Capacitor Layout Example

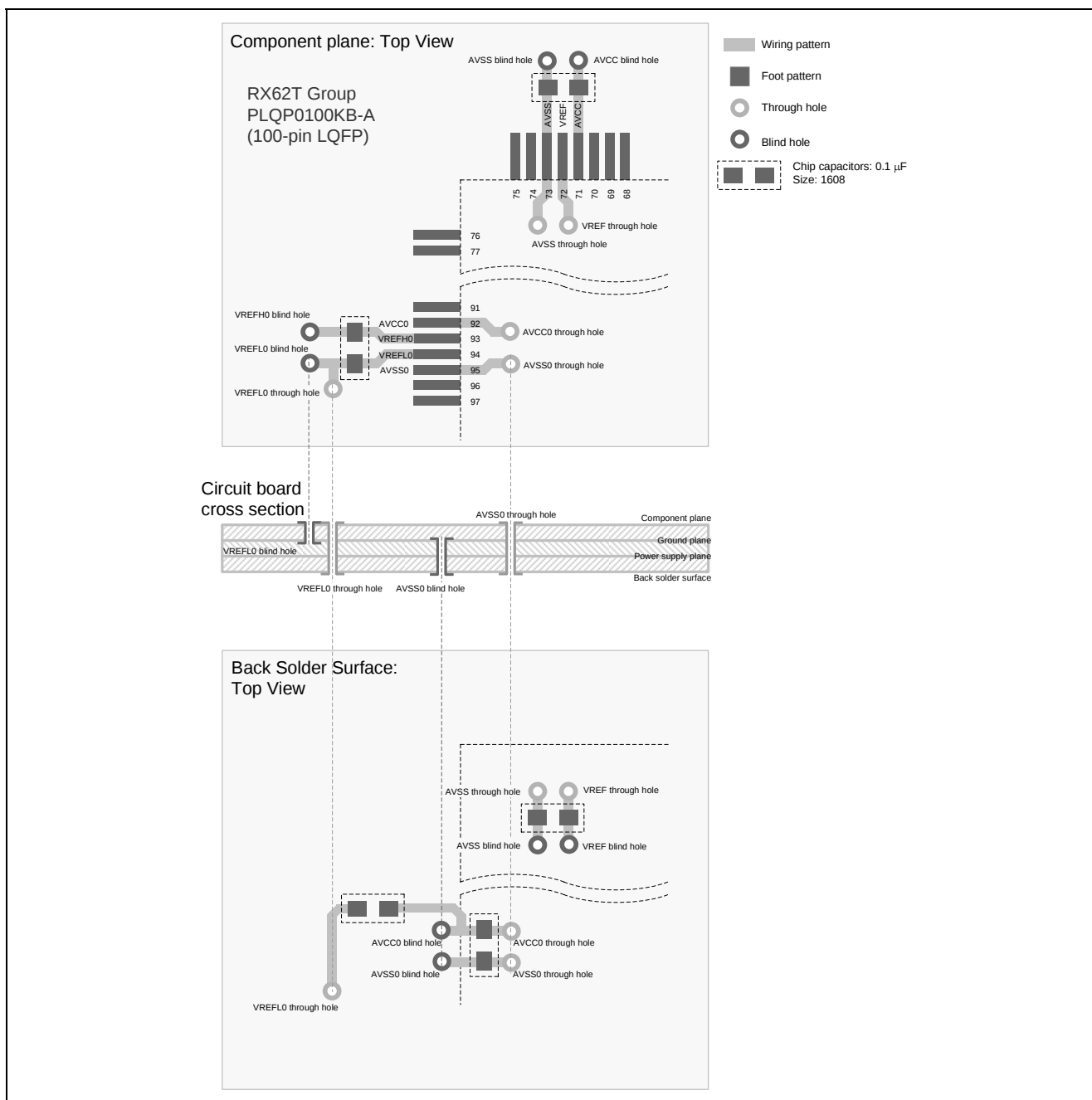


Figure 3 RX62T 100-Pin LQFP Package Power Supply Pin Capacitor Layout Example

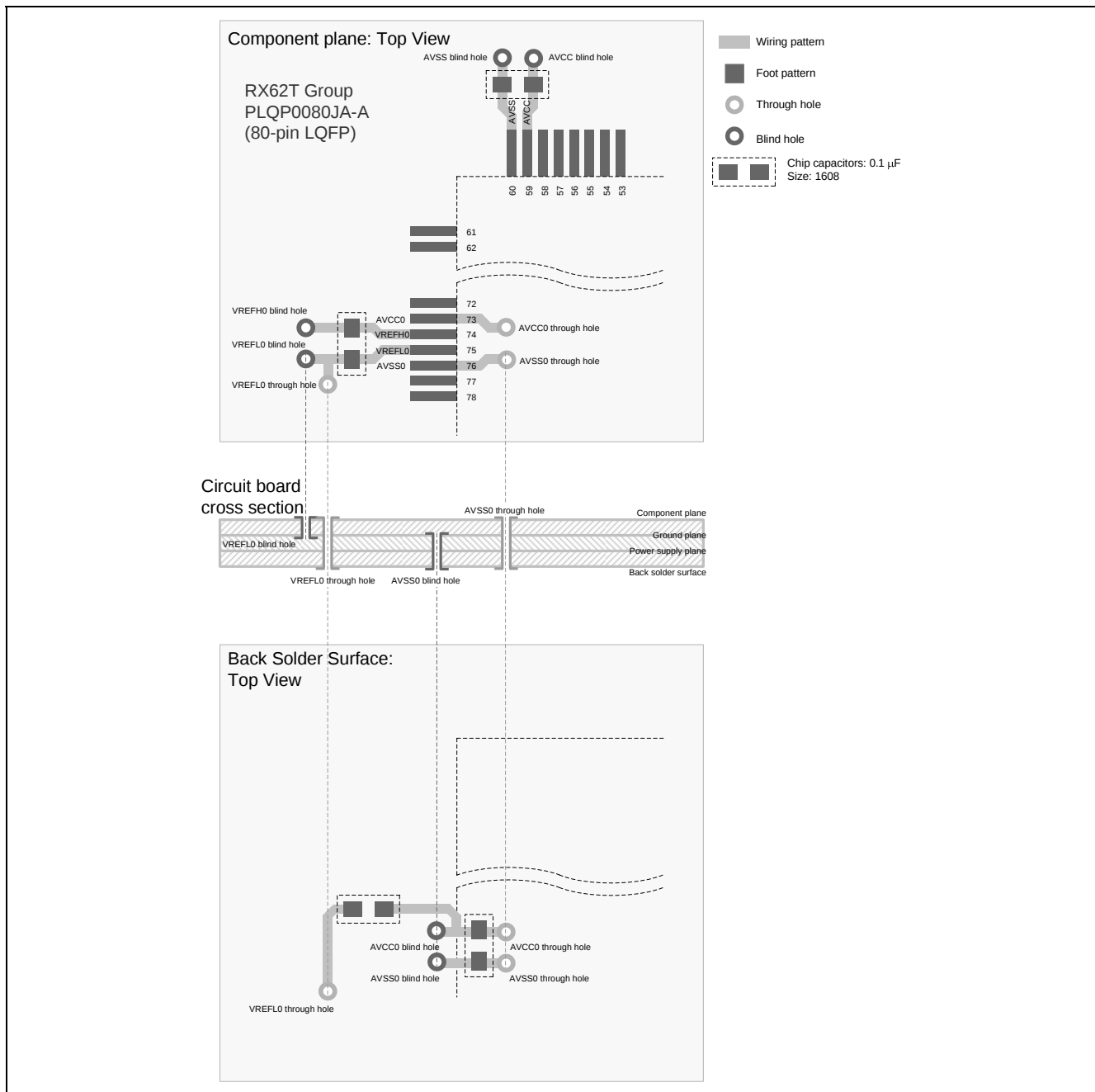


Figure 4 RX62T 80-Pin LQFP Package Power Supply Pin Capacitor Layout Example

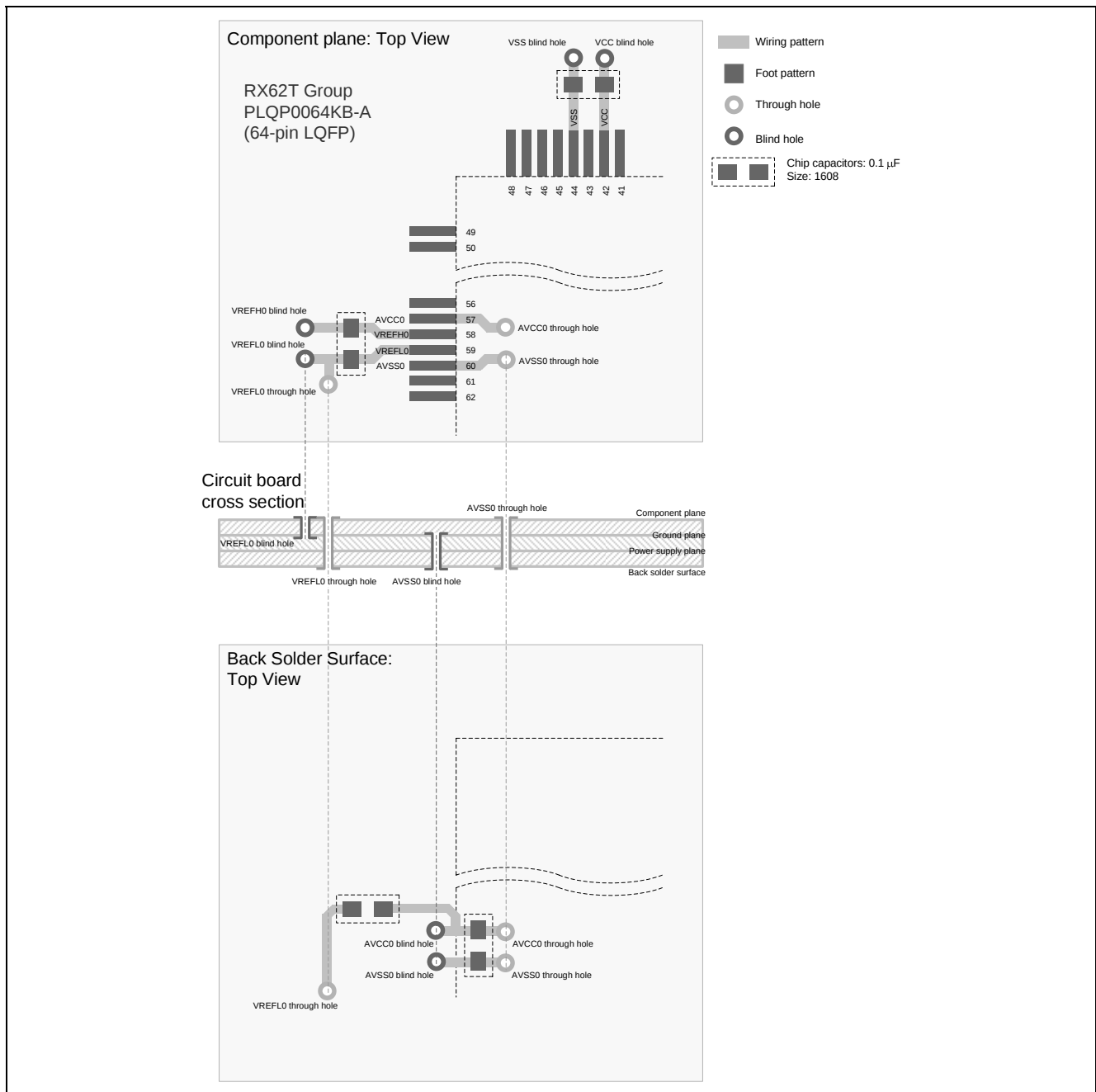


Figure 5 RX62T 64-Pin LQFP Package Power Supply Pin Capacitor Layout Example

1.4 Reducing Noise in Power Supply Lines

The 10 μF and 0.01 μF (values provided for reference purposes) capacitors shown in the circuit diagrams in the Hardware Manual for each microcontroller product are included as bypass capacitors for the analog power supply lines. The actual capacitances and layout details for these capacitors must be analyzed in conjunction with the end product or system characteristics (for example locating them near the power supply itself).

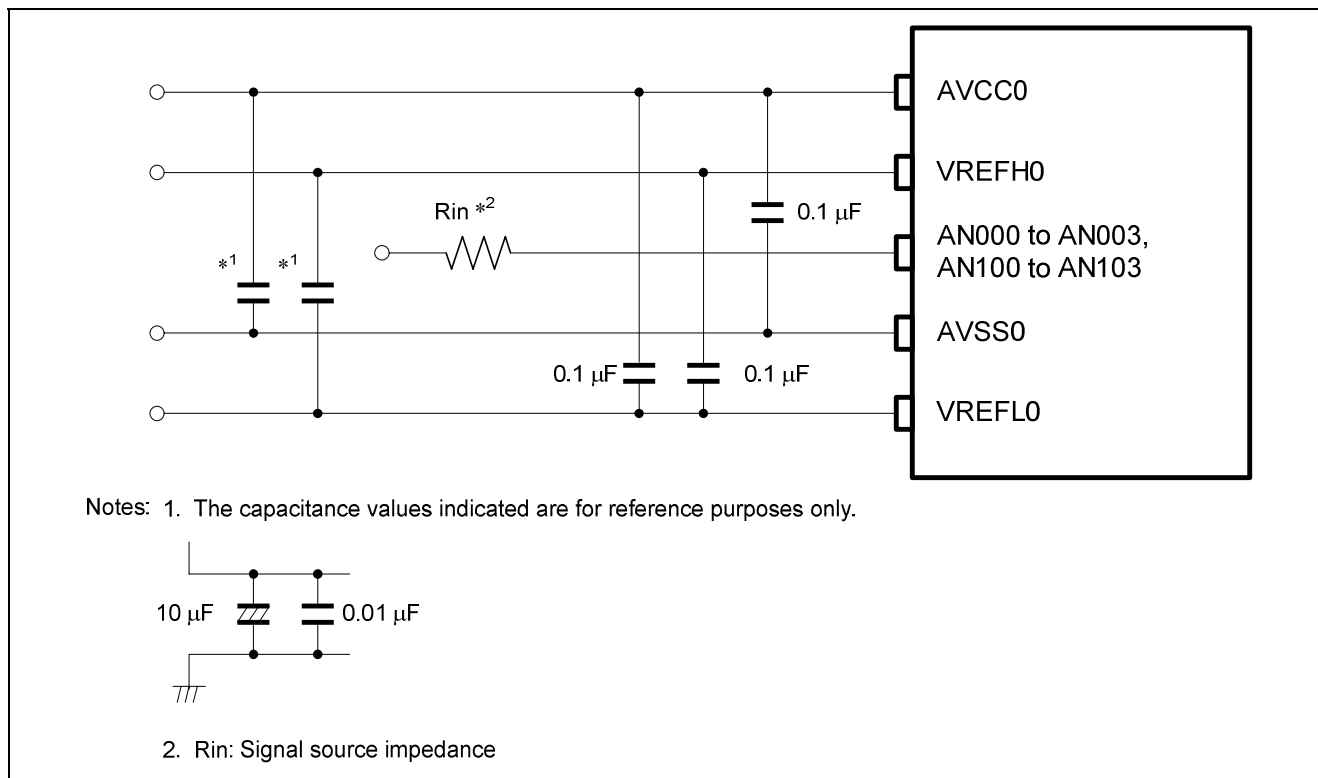


Figure 6 Reducing Noise in Power Supply Lines (12-bit A/D converter)

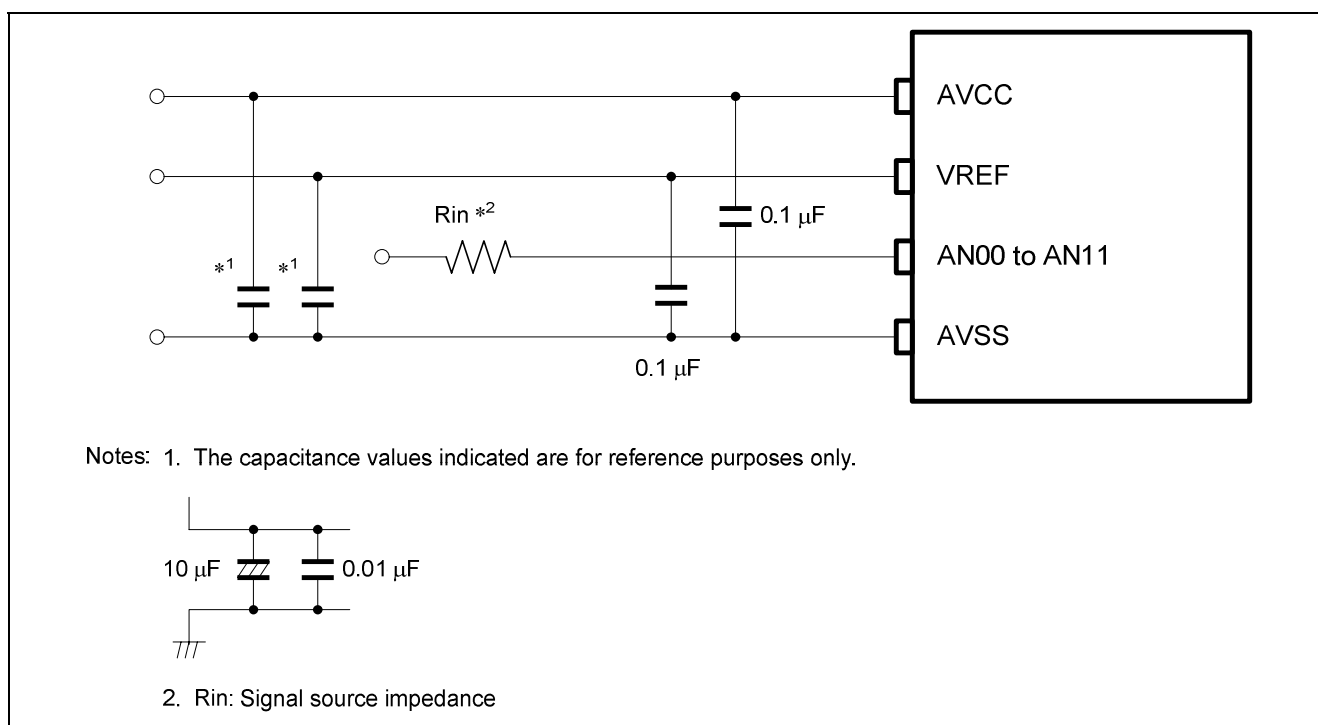


Figure 7 Reducing Noise in Power Supply Lines (10-bit A/D converter)

2. Reference Documents

- Hardware Manual
RX62T Group User's Manual: Hardware Rev.1.10
(The latest version can be downloaded from the Renesas Electronics Web site.)
- Technical Updates
(The latest information can be downloaded from the Renesas Electronics Web site.)

Website and Support

Renesas Electronics Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

All trademarks and registered trademarks are the property of their respective owners.

Revision Record

Rev.	Date	Description	
		Page	Summary
1.00	Sep.27.11	—	First edition issued

General Precautions in the Handling of MPU/MCU Products

The following usage notes are applicable to all MPU/MCU products from Renesas. For detailed usage notes on the products covered by this document, refer to the relevant sections of the document as well as any technical updates that have been issued for the products.

1. Handling of Unused Pins

Handle unused pins in accord with the directions given under Handling of Unused Pins in the manual.

- The input pins of CMOS products are generally in the high-impedance state. In operation with an unused pin in the open-circuit state, extra electromagnetic noise is induced in the vicinity of LSI, an associated shoot-through current flows internally, and malfunctions occur due to the false recognition of the pin state as an input signal become possible. Unused pins should be handled as described under Handling of Unused Pins in the manual.

2. Processing at Power-on

The state of the product is undefined at the moment when power is supplied.

- The states of internal circuits in the LSI are indeterminate and the states of register settings and pins are undefined at the moment when power is supplied.
In a finished product where the reset signal is applied to the external reset pin, the states of pins are not guaranteed from the moment when power is supplied until the reset process is completed. In a similar way, the states of pins in a product that is reset by an on-chip power-on reset function are not guaranteed from the moment when power is supplied until the power reaches the level at which resetting has been specified.

3. Prohibition of Access to Reserved Addresses

Access to reserved addresses is prohibited.

- The reserved addresses are provided for the possible future expansion of functions. Do not access these addresses; the correct operation of LSI is not guaranteed if they are accessed.

4. Clock Signals

After applying a reset, only release the reset line after the operating clock signal has become stable. When switching the clock signal during program execution, wait until the target clock signal has stabilized.

- When the clock signal is generated with an external resonator (or from an external oscillator) during a reset, ensure that the reset line is only released after full stabilization of the clock signal. Moreover, when switching to a clock signal produced with an external resonator (or by an external oscillator) while program execution is in progress, wait until the target clock signal is stable.

5. Differences between Products

Before changing from one product to another, i.e. to a product with a different part number, confirm that the change will not lead to problems.

- The characteristics of an MPU or MCU in the same group but having a different part number may differ in terms of the internal memory capacity, layout pattern, and other factors, which can affect the ranges of electrical characteristics, such as characteristic values, operating margins, immunity to noise, and amount of radiated noise. When changing to a product with a different part number, implement a system-evaluation test for the given product.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
 2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
 4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
 5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
 6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
 7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
"Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
 8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
 9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
 10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.

2880 Scott Boulevard Santa Clara, CA 95050-2554, U.S.A.
Tel: +1-408-588-6000, Fax: +1-408-588-6130

Renesas Electronics Canada Limited

1101 Nicholson Road, Newmarket, Ontario L3Y 9C3, Canada
Tel: +1-905-898-5441, Fax: +1-905-898-3220

Renesas Electronics Europe Limited

Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-585-100, Fax: +44-1628-585-900

Renesas Electronics Europe GmbH

Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-65030, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.

7th Floor, Quantum Plaza, No.27 ZhichunLu Haidian District, Beijing 100083, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.

Unit 204, 205, AZIA Center, No.1233 Lujiazui Ring Rd., Pudong District, Shanghai 200120, China
Tel: +86-21-5877-1818, Fax: +86-21-6887-7858 / -7898

Renesas Electronics Hong Kong Limited

Unit 1601-1613, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2886-9318, Fax: +852 2886-9022/9044

Renesas Electronics Taiwan Co., Ltd.

13F, No. 363, Fu Shing North Road, Taipei, Taiwan
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

Renesas Electronics Singapore Pte. Ltd.

1 HarbourFront Avenue, #06-10, Keppel Bay Tower, Singapore 098632
Tel: +65-6213-0200, Fax: +65-6278-8001

Renesas Electronics Malaysia Sdn.Bhd.

Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jin Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics Korea Co., Ltd.

11F., Samik Lavied' or Bldg., 720-2 Yeoksam-Dong, Kangnam-Ku, Seoul 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141