

Introduction

Crystal drive level is the amount of power dissipated in a crystal which is usually specified in microwatts or milliwatts. It can be calculated by measuring the excitation current flowing through the crystal. The maximum drive level is the most power the crystal can dissipate while still maintaining operation with all electrical parameters guaranteed. Drive level should be maintained at the minimum levels necessary to initiate proper start-up and assure steady state oscillation. Some of the larger crystal packages like HC49 tend to have higher drive level limits while the smaller crystal packages like 5x7mm and 2.5 x 3.2mm have lower drive level. To ensure that premature aging or damage to the crystal does not occur, drive level should be considered.

Though drive level is specified in most quartz crystal datasheets, at times it is overlooked. Drive level is an important factor when designing or evaluating an oscillator circuit.

Measuring Drive Level

There are multiple ways of measuring drive level. Using a current probe is most reliable which is similar to current flowing through a resistor. Using a FET probe is also common but has disadvantages on an inverter type oscillator, like a Pierce. On an inverter type oscillator, there is phase difference between the signal at the crystal input and output which make it difficult to accurately measure the voltage across the crystal. The equations and examples below will show the requirements for measuring drive level using a current probe.

The drive level can be calculated by using the RMS drive current (I_d) and the load resonance resistance (R_L). Refer to equation 1.

$$Power = I_d^2 \times R_L \quad (watts) \quad (1) \quad \begin{array}{l} I_d = \text{RMS drive current} \\ R_L = \text{Load resonance frequency} \end{array}$$

Since R_L varies with load capacitance, equation 2 can be used to calculate R_L .

$$R_L = R_R \left(1 + \frac{C_o}{C_L} \right)^2 \quad (\Omega) \quad (2) \quad \begin{array}{l} C_o = \text{Shunt Capacitance} \\ C_L = \text{Load Capacitance} \\ R_R = \text{Resistance at series resonant} \\ \text{frequency} \end{array}$$

Combining equation 1 and 2 yields equation 3.

$$Power = I_d^2 \times R_R \left(1 + \frac{C_o}{C_L} \right)^2 \quad (watts) \quad (3)$$

When R_R is at FS (series resonance frequency), R_R is equal to R_1 (Motional Resistance).

$$Power = I_d^2 \times R_1 \left(1 + \frac{C_o}{C_L} \right)^2 \quad (watts) \quad (4) \quad R_1 = \text{Motional Resistance}$$


If using a series resonance crystal, C_L goes to infinity.

$$Power = I_d^2 \times R_1 \quad (watts) \quad (5)$$

Example Calculation

For this example, a Tektronix CT-6 probe was used to measure the drive current. When placing the current probe, special attention should be given to the orientation. For inverter type oscillators, the drive current should be measured on the output side of the crystal in order to contain the influence of the oscillator. Refer to [Figure 1](#).


Figure 1. Oscilloscope and current probe connection

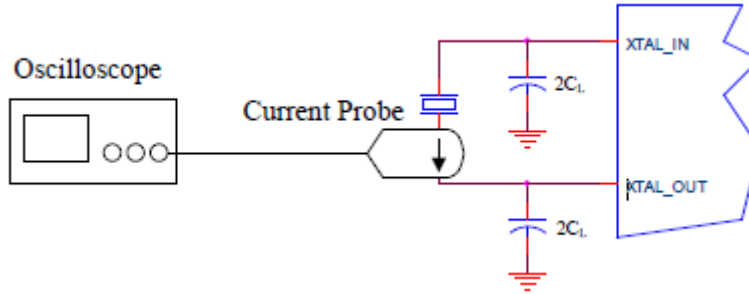

Oscilloscopes measure voltage versus time, though the display value is in mV, the current probe converts the electric field to AC current. The voltage can be ignored; in reality it is current. Oscilloscopes can display AC current in peak, peak to peak, or RMS. For most cases, we can assume the waveform is a pure sine-wave, hence the equation 6 applies. Refer to equation 6 and [Figure 2](#).

$$I_{RMS} = \frac{I_{pk}}{\sqrt{2}} = \frac{I_{pkpk}}{2\sqrt{2}} \quad (A) \quad (6)$$

Figure 2. Sample AC Current waveform. IRMS = 1.74mA

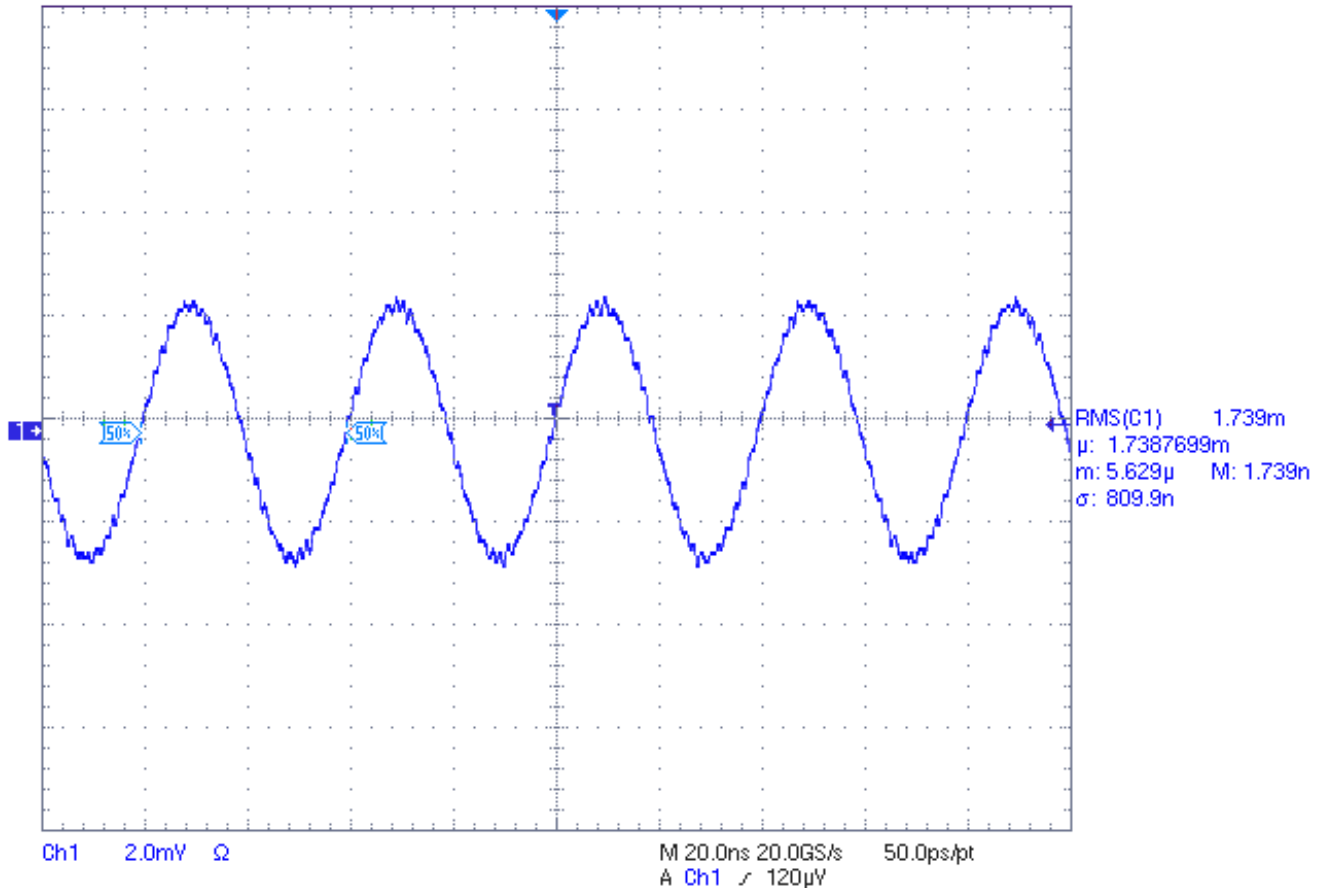

Using a Saunders & Associates 250B Network Analyzer, the relevant crystal parameters can be characterized. For this example, a 25MHz, HC49 type crystal was used. Refer to [Figure 3](#).

Figure 3. S&A Crystal Parameters, 25MHz

Description: S&A 250B			
Reference F: 25,000,000 Hz			
Power: 1.00 mW into 25.00 Ohms			
CL: 18.00 pF Using: Calculated FL			
RR	RL	CO	C1
Ohms	Ohms	pF	fF
14.0	19.0	2.9	11.4

Using equation 3 in combination with IRMS from figure 2 and RL from values in [Figure 3](#) yields the drive level below.

$$Power = I_d^2 \times R_R \left(1 + \frac{C_O}{C_L} \right)^2 = (1.74mA)^2 \times 14\Omega \left(1 + \frac{2.9pf}{18pf} \right)^2 = 57.14uW$$

The drive level contains variables from both the crystal and oscillator; hence both the crystal type and frequency will affect the drive level. When characterizing an oscillator, it should be verified across minimum and maximum frequency, CL, and RL. For the example above, the drive level is 57.14µW for a 25MHz, HC49 crystal on this specific oscillator.

This example yielded 57.14µW of drive level. In order to avoid poor aging or crystal damage, this value should be compared to the maximum level recommended by the crystal manufacturer.

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01 Jan 2024)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.