

**Introduction**

For battery-powered applications, minimizing current consumption is a critical parameter of the design. So, keeping current consumption as low as possible is crucial. This can be achieved by using a WS (Wake/Sleep) timing block for controlling on-chip circuit block powerdown. The most power consuming blocks in GreenPAK IC's are those that work with analog signals (ACMPs, ADC).

**Wake/Sleep Function Operation Example**

The wake/sleep function switches on and off the relevant circuit blocks. In the SLG46140 IC, these are ACMPs and ADC blocks. The block that creates a Wake/Sleep signal is CNT0 switched into 'Wake Sleep ratio control' mode (it morphs into the WS Ctrl block). In this mode this block operates as a counter, but supplies ACMPs and ADC with power on and latch signals.

 


Fig.1. SLG46140 based design with all blocks wake/sleep controlled

To make this function operational just set its type to 'Wake sleep control'. The on time is defined by the clock frequency (LF OSC) and lasts one clock cycle. The ratio is controlled by changing the Counter data value, so the on time is constant, but the overall period could be changed. This design example provides the control of all possible external signals that influence the blocks with wake/sleep function.

*NOTE: The on time can be controlled by the clock frequency of LF OSC, and there is a post clock divider behind the LF OSC. One can change the LF OSC clock frequency by changing the output divider. The WS Ctrl input clock is from the output of this divider.*

## ACMP Wake and Sleep

To turn on the Wake/Sleep function in ACMP, change the 'ACMPx Wake sleep' option to 'Enable' in the properties of any of the WS Ctrl block.

This function is shared between both ACMPs in SLG46140 IC, which means the WS function will be turned on in both ACMPs if any has this option enabled. The operation of WS is the following: the PWR UP input signal of the ACMP should be HIGH to enable block's operation. Setting the PWR UP input (ACMP0\_PWRUP or ACMP1\_PWRUP) LOW will latch the previous data on the output. After the block is powered up, it will periodically turn on. On the falling edge of the WS signal, the ACMP will latch the output and will not change it until the next WS pulse comes. The ACMP operation can be stopped in several ways: set PWR UP signal LOW, SET or RESET the WS control block, power down the LF OSC. These events have the priorities shown in table 1.

*NOTE: For correct ACMPs operation the PWR UP input should be sourced from WS Ctrl output. We recommend using LUTs logic cells for full ACMPs operation control.*

Priority	Event	State	Action
1	ACMP Power	Up (W/S <sup>1</sup> )	ACMP with W/S
		Down (LOW)	ACMP is OFF
2	LF OSC Power	Up (LOW)	ACMP with W/S
		Down (HIGH)	ACMP is ON or OFF <sup>2</sup>
3	WS Ctrl	SET/ RESET <sup>3</sup>	ACMP always ON or OFF
		none	ACMP with W/S

**Table 1. The ACMP operation**

---


<sup>1</sup> sourced from WS Ctrl output

<sup>2</sup> depends on 'Wake sleep output state' configuration in WS Ctrl block

<sup>3</sup> depends on WS Ctrl 'Q mode' configuration

Operation of the W/S function in ACMP with LF OSC always turned on shown below.

## ADC Wake and Sleep

 

**Fig 2. Timing diagrams of the wake/sleep function. A – ACMP always in W/S mode; B – ACMP forced to power down by ACMP PWRUP in LOW; C – ACMP forced to be always on by WS Ctrl RESET IN in SET mode; D – ACMP forced to power down by WS Ctrl RESET in in RESET mode**

*NOTE: Because the W/S function is shared in both ACMPs, there only possible operation cases use 3 control signals (ACMP PWR UP, WS Ctrl RESET/SET IN, LFOSC PWR DOWN). Note that there is no way for one ACMP to be turned on and another ACMP to be in W/S mode:*

ACMP0	ACMP1
ON	ON
OFF	OFF
W/S	W/S
W/S	OFF
OFF	W/S

**Table 2. ACMP in W/S mode**

In this example DCMP0 is used to compare the ADC parallel data with its Register0 value ('127', corresponds to 0.5V).

According to the SLG46140 datasheet, the signal to ADC comes from PGA which should be powered down if WS function will be used.

Unlike ACMPs ADC power down signal becomes inactive when W/S function is turned on. The rest operates the same as ACMPs with WS function turned on. So the ADC could be turned always ON, always OFF or Wake/Sleep depending on WS Ctrl RESET/SET and LF OSC PWR DOWN signals.

### Conclusion

The W/S function is very useful if analog blocks are used and low power consumption is desired. Wake and sleep itself not only powers up and down

ACMPs and ADC dynamically, but also latches the outputs while blocks are in sleep mode. All blocks share the same W/S signal generation source – WS Ctrl/CNT0. It is shared for ACMPs together, while ADC is independent.

## IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01 Jan 2024)

### Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan  
[www.renesas.com](http://www.renesas.com)

### Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

### Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit [www.renesas.com/contact-us/](http://www.renesas.com/contact-us/).