

---

# Application Note

## Propagation Delay Considerations

**AN-CM-283**

### **Abstract**

*This application note illustrates the concept of propagation delay and how to estimate the propagation delay of different circuit blocks. It includes techniques that foster a more robust design implementation.*

---

## Propagation Delay Considerations

### Contents

|  |   |
|--|---|
| <b>Abstract</b> .....  | 1 |
| <b>Contents</b> .....  | 2 |
| <b>Figures</b> .....   | 2 |
| <b>Terms and Definitions</b> .....                             | 2 |
| <b>1 References</b> .....                                      | 2 |
| <b>2 Introduction</b> .....                                    | 3 |
| <b>3 Propagation Delay Considerations in GreenPAK</b> .....    | 3 |
| 3.1    Estimating Propagation Delay for Different Blocks ..... | 4 |
| <b>4 Conclusions</b> .....                                     | 7 |
| <b>Revision History</b> .....                                  | 8 |

### Figures

|   |   |
|---|---|
| Figure 1: Opening Datasheet via Help Window .....                                       | 3 |
| Figure 2: Typical Delay Estimated for Macrocells in SLG46826 .....                      | 4 |
| Figure 3: Example for Signal Delay.....   | 5 |
| Figure 4: Serial Block Propagation Delay.....   | 5 |
| Figure 5: Design Example .....  | 5 |
| Figure 6: Design Example Simulation Result.....   | 6 |
| Figure 7: Filtering Glitches Dependent on Propagation Delay (Using P DLY (FILTER))..... | 6 |
| Figure 8: Filtering Glitches Dependent on Propagation Delay (Using LUT Buffer) .....    | 6 |

### Terms and Definitions

|       |                    |
|-------|--------------------|
| Tpd   | Propagation Delay  |
| LUT   | Look-Up Table      |
| P DLY | Programmable Delay |

### 1 References

- [1] SLG46826, Datasheet, Renesas Electronics.
- [2] AN-1046, Various Edge Detector Circuits, Application Note, Renesas Electronics.

## Propagation Delay Considerations

### 2 Introduction

In digital electronics, the time needed to transmit a signal from one point (element) to another is called propagation delay (Tpd). The main factors that determine additional propagation delay of a signal through an integrated circuit are diode and transistor capacitances between the components of the ICs and inertia of the switching process in diode and transistors. This problem is exacerbated in synchronous systems, where the propagation of a signal through the IC is dependent upon the global clock frequency.

In practice, propagation delay is variable and depends on different factors including environment (for temperature) and electrical characteristics (for example supply voltage). GreenPAK, just like any other IC, has propagation delay resulting from its internal components like LUTs, DFFs, and others.

### 3 Propagation Delay Considerations in GreenPAK

The question of whether propagation delay is advantageous or detrimental is heavily dependent upon the specific circuit. On one hand, the signal delay caused by LUT propagation gives us the possibility to create helpful designs such as edge detectors in reset functions (see application note AN-1046), signal filters, or high frequency oscillators.

On the other hand, propagation can lead to undesirable and unpredictable logic combinations (often called "signal race"), which can negatively influence design functionality. Furthermore, Tpd limits the maximum frequency with which circuits can function. There are a lot of devices and applications that work on a minimum allowable switching frequency, like transmission protocols (I<sup>2</sup>C, UART, SPI), Levels Shifters, and more. Depending upon the minimum propagation delay, certain applications may not be feasible.

We are going to consider this issue and give simple hints that can help to calculate propagation delay of different blocks and their combinational delay. We will also show problems that can be caused by propagation delay, along with the methods to avoid these problems.

To start, we must know where propagation delay timings can be found. To find a typical estimated propagation time for different blocks go to the datasheet. It is very easy to do it via GreenPAK designer. Choose the necessary IC (let's say SLG46826). GreenPAK Designer automatically downloads the datasheet after clicking «Datasheet» in the «Help» window (see Figure 1).

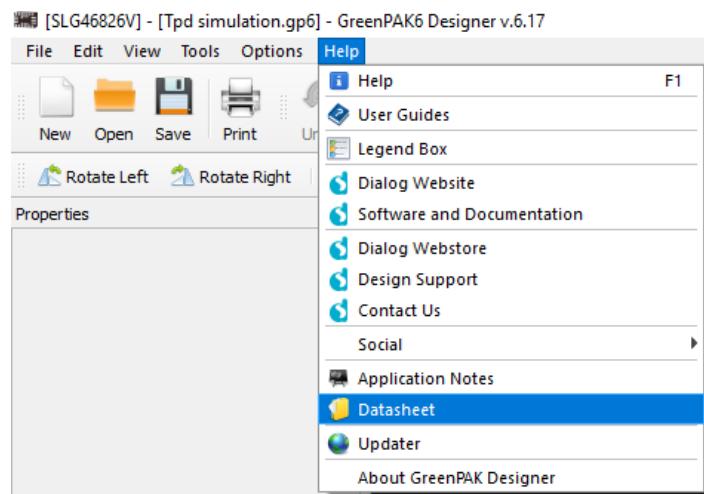


Figure 1 Opening Datasheet via Help Window

## Propagation Delay Considerations

In the datasheet navigate to chapter 3.4 Timing Characteristics of propagation delay can be determined in Table 8 Typical Delay Estimated for Each Macrocell (**Note 1**: Chapter and table number example is for the SLG46826 IC, it varies from chip to chip). Looking through the table, the datasheet of a certain block specifies the propagation delay variation for different voltage ranges at 25 °C (**Note 2**: All data shown are worst case and includes 6-sigma coverage factor).

### 3.4 TIMING CHARACTERISTICS

Table 8: Typical Delay Estimated for Each Macrocell at T = 25°C

| Parameter | Description | Note   | V <sub>DD</sub> = 2.5 V |         | V <sub>DD</sub> = 3.3 V |         | V <sub>DD</sub> = 5 V |         | Unit |
|-----------|-------------|--|-------------------------|---------|-------------------------|---------|-----------------------|---------|------|
|           |             |  | Rising                  | Falling | Rising                  | Falling | Rising                | Falling |      |
| tpd       | Delay       | Multi-Function DFF Q                           | 23                      | 21      | 16                      | 15      | 11                    | 11      | ns   |
| tpd       | Delay       | Multi-Function DFF nQ                          | 23                      | 21      | 17                      | 15      | 12                    | 11      | ns   |
| tpd       | Delay       | Multi-Function DFF nRESET Q                    | --                      | 29      | --                      | 21      | --                    | 15      | ns   |
| tpd       | Delay       | Multi-Function DFF nRESET nQ                   | 31                      | --      | 22                      | --      | 16                    | --      | ns   |
| tpd       | Delay       | 2-bit LUT                                      | 17                      | 16      | 12                      | 12      | 8                     | 8       | ns   |
| tpd       | Delay       | 3-bit LUT                                      | 17                      | 17      | 12                      | 12      | 8                     | 9       | ns   |
| tpd       | Delay       | 4-bit LUT                                      | --                      | --      | --                      | --      | --                    | --      | ns   |
| tpd       | Delay       | Digital input to Low Voltage to PP 1X          | 35                      | 222     | 24                      | 150     | 16                    | 96      | ns   |
| tpd       | Delay       | Digital input to with Schmitt Trigger to PP 1x | 26                      | 30      | 19                      | 22      | 13                    | 16      | ns   |
| tpd       | Delay       | Digital input to 1xPP                          | 27                      | 31      | 19                      | 22      | 13                    | 16      | ns   |
| tpd       | Delay       | Digital input to 2xPP                          | 24                      | 29      | 18                      | 21      | 12                    | 15      | ns   |
| tpd       | Delay       | Digital input to 1xNMOS                        | --                      | 27      | --                      | 20      | --                    | 14      | ns   |
| tpd       | Delay       | Digital input to 2xNMOS                        | --                      | 26      | --                      | 19      | --                    | 14      | ns   |
| tpd       | Delay       | Digital input to 1x3-State (Z to 0)            | --                      | 24      | --                      | 17      | --                    | 12      | ns   |

Figure 2: Typical Delay Estimated for Macrocells in SLG46826

### 3.1 Estimating Propagation Delay for Different Blocks

Frequently, questions are asked: "what is the maximum frequency that GreenPAK can work with?" or "how do I estimate the delay of an input signal?". To answer these questions, refer to the following Example 1 and Example 2.

#### Example 1

The datasheet of a certain block specifies that for 2-bit LUT (SLG46826), at the V<sub>DD</sub> = 3.3 V rising edge delay, tpd (rising) = 12 ns, falling edge delay tpd (falling) = 12 ns. What is the maximum frequency that can go through the LUT?

$$t_{\min} = t_{\text{pd}}(\text{rising}) + t_{\text{pd}}(\text{falling}) = 12 \text{ ns} + 12 \text{ ns} = 24 \text{ ns}$$

$$f_{\max} = \frac{1}{t_{\min}} = \frac{1}{24 \text{ ns}} = \frac{1}{24 \times 10^{-9}} = 41.66 \times 10^6 \text{ Hz} = 41.66 \text{ MHz}$$

As a result, the received frequency f<sub>max</sub> = 41.66 MHz is the highest frequency that can pass through the 2 bit-LUT.

#### Example 2

Given: Logic circuit in Figure 3. Find: signal delay at the output pin (V<sub>DD</sub> = 5 V).

## Propagation Delay Considerations

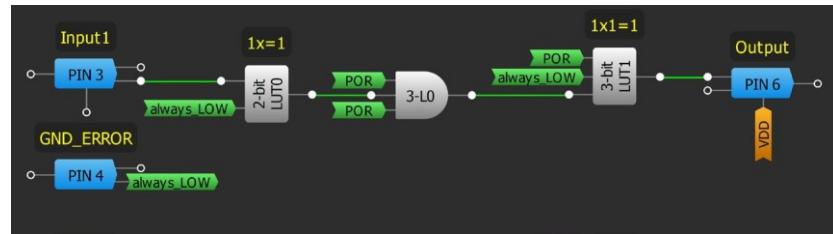


Figure 3: Example for Signal Delay

The solution includes two parts: rising edge delay and falling edge delay calculation.

$$t_{\text{rising\_edge}} = t_{\text{pd}}(\text{rising}_{\text{DI\_to\_1xPP}}) + t_{\text{pd}}(\text{rising\_2bitLUT}) + 2t_{\text{pd}}(\text{rising\_3bitLUT}) = 13 \text{ ns} + 8 \text{ ns} + 2 \cdot 8 \text{ ns} = 37 \text{ ns}$$

$$t_{\text{falling\_edge}} = t_{\text{pd}}(\text{falling}_{\text{DI\_to\_1xPP}}) + t_{\text{pd}}(\text{falling\_2bitLUT}) + 2t_{\text{pd}}(\text{falling\_3bitLUT}) = 16 \text{ ns} + 8 \text{ ns} + 2 \cdot 9 \text{ ns} = 42 \text{ ns}$$

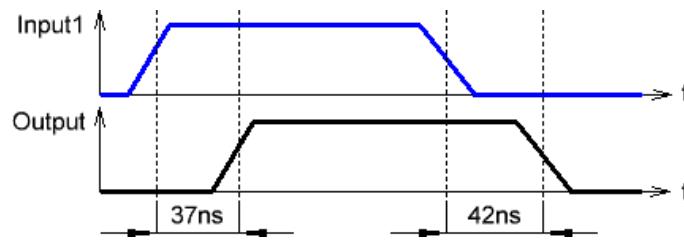


Figure 4: Serial Block Propagation Delay

Result: rising and falling edges of applied input signal are delayed 37 ns and 42 ns accordingly.

To fully understand potential issues related to Tpd, let's consider the simple logic circuit designed in SLG46826 (Figure 5). A signal that is applied to Input2 goes through an XOR block. The signal is fed into the XOR through IN0 directly, and with IN1 it passes via an AND-cell (Input1 is enable signal).

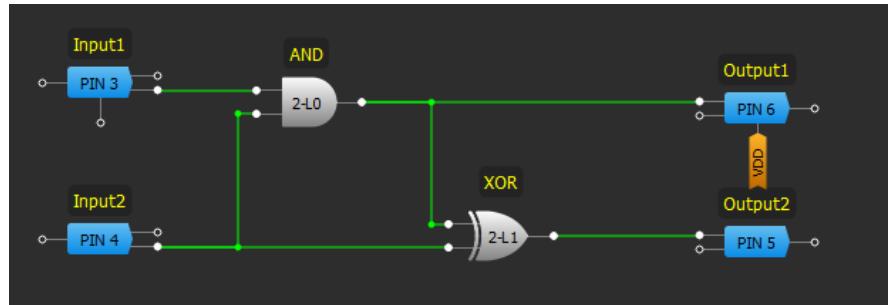


Figure 5: Design Example

So, how will propagation delay factor into this delay? When Input1 is Low, the XOR-gate works to buffer the Input2 signal. But, when it is High, XOR's IN1 will be applied with the signal from Input2, which will be delayed by AND cell propagation delay. This construction generates a short duration glitch on Output2 (Figure 6). Not good, especially for edge-dependent logic on the output.

## Propagation Delay Considerations

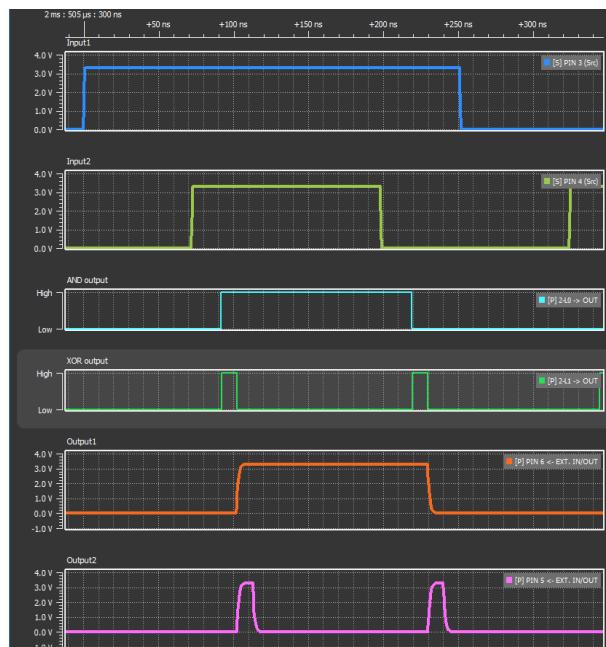


Figure 6: Design Example Simulation Result

The first and the easiest way to overcome glitches caused by this circuit scenario is to filter it using either P DLY block (configured as both edge delay) or FILTER (configured as filter) (see [Figure 7](#)). This method is reliable because of long delay time (up 834 ns for 4 cells P DLY, according to the datasheet). However, these specialized blocks may already be used for other functions or the input frequency is too high to use P DLY, so another method for filtering propagation glitches should be applied.

The second method is based upon providing the equivalent signal delay for the 2 XOR inputs. In order to implement this, a 2-bit LUT (2-bit LUT is an example, any other block can be used) is added between Input2 and the XOR's In0 (see [Figure 8](#)). The extra block equalizes the delays on XOR's inputs, which prevents that logic from creating short glitches on Output2 pin. **Note 3:** Because of the internal structure of LUT's, their inputs have different propagation delay times. The higher the input label number, the shorter the propagation delay it has. For example, IN1 has shorter propagation delay time than IN0.

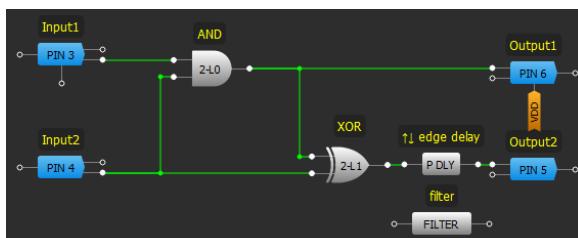


Figure 7: Filtering Glitches Dependent on Propagation Delay (Using P DLY (FILTER))

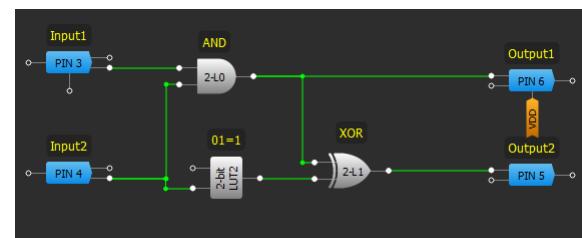


Figure 8: Filtering Glitches Dependent on Propagation Delay (Using LUT Buffer)

## 4 Conclusions

In this article, we considered the sensitivity of Tpd, and how to calculate total propagation delay time in GreenPAK designer. Two examples with maximum frequency and signal delay calculation were presented. Two different methods of filtering glitches caused by propagation delay were shown.

---

## Propagation Delay Considerations

---

### Revision History

| Revision | Date        | Description     |
|----------|-------------|-----------------|
| 1.0      | 13-Jun-2019 | Initial version |

## IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01)

### Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan  
[www.renesas.com](http://www.renesas.com)

### Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

### Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit [www.renesas.com/contact-us/](http://www.renesas.com/contact-us/).