
RL78 Family

Notes and Countermeasures Against Noise

R01AN0839EJ0100

Rev.1.00

Oct. 4, 2011

Abstract

This document describes notes and countermeasures against noise for the RL78 Family. The countermeasures are generally effective countermeasures against noise, however a careful system evaluation should be performed after using these countermeasures.

Product

MCU: RL78 Family

Contents

- 1. Notes on Noise 3
 - 1.1 Shortest Wiring Length 3
 - 1.1.1 Wiring for the RESET Pin 3
 - 1.1.2 Wiring for Clock Input/Output Pins 4
 - 1.2 Connection of Bypass Capacitor Across VSS Line and VDD Line 5
 - 1.3 Wiring to Analog Input Pins 6
 - 1.4 Oscillator Concerns 7
 - 1.4.1 Avoid Large Current Signal Lines 7
 - 1.4.2 Avoid Signal Lines Where Potential Levels Change Frequently 8
 - 1.5 Setup for I/O Ports 9
- 2. Reference Documents 10

1. Notes on Noise

1.1 Shortest Wiring Length

The wiring on a printed circuit board can function as an antenna, which attracts noise into an MCU. The shorter the total wiring length (in mm units), the less the possibility of noise being attracted into the MCU.

1.1.1 Wiring for the $\overline{\text{RESET}}$ Pin

Make the length of the wiring connected to the $\overline{\text{RESET}}$ pin as short as possible. When connecting a capacitor between the $\overline{\text{RESET}}$ pin and Vss pin, and when connecting the reset IC to its corresponding pins, the wire length should be especially short (within 20 mm).

Reason:

The width of a pulse input into the $\overline{\text{RESET}}$ pin is determined by the timing requirements. If noise having a shorter pulse width than the standard is input to the $\overline{\text{RESET}}$ pin, the reset is released before the internal state of the MCU is completely initialized. This may cause a program runaway.

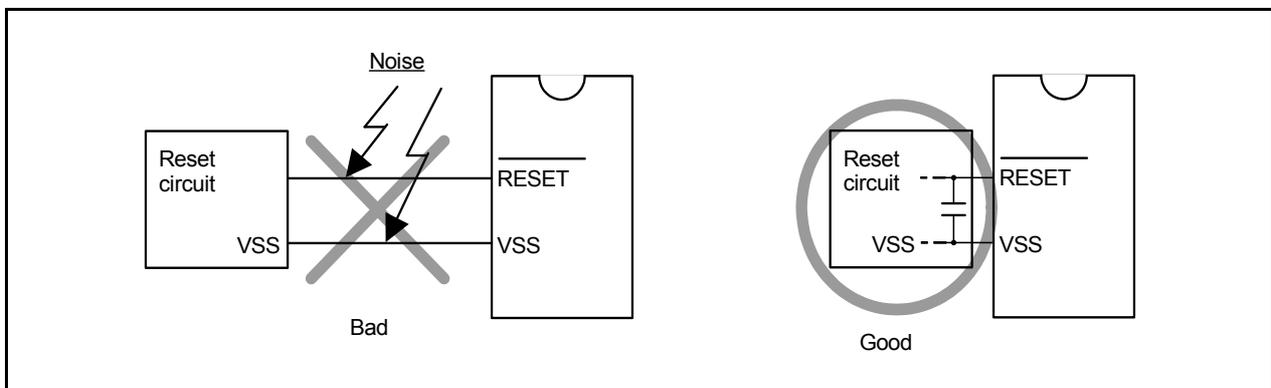


Figure 1.1 Wiring for the $\overline{\text{RESET}}$ Pin

1.1.2 Wiring for Clock Input/Output Pins

- Make the length of wiring connected to clock I/O pins as short as possible.
- Make the length of wiring (within 20 mm) across the grounding lead of a capacitor which is connected to an oscillator and the VSS pin of an MCU as short as possible.

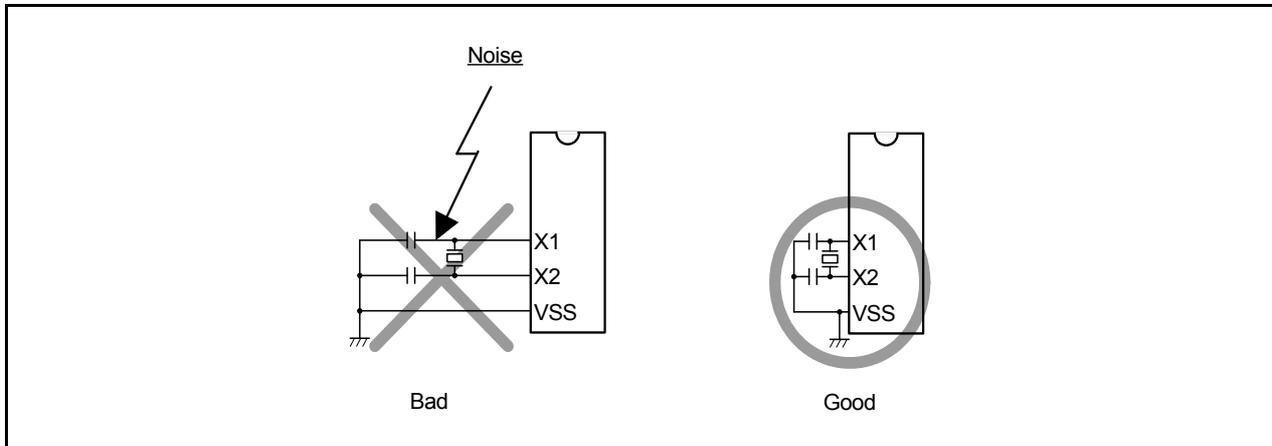


Figure 1.2 Wiring for Clock Input/Output Pins

Reason:

If noise enters clock input/output pins, clock waveforms may be unstable. This may cause a program failure or program runaway. Also, if a potential difference is caused by the noise between the VSS level of the MCU and the VSS level of an oscillator, the correct clock will not be input in the MCU.

1.2 Connection of Bypass Capacitor Across VSS Line and VDD Line

Connect a bypass capacitor that is approximately 0.1 μF across the VSS line and VDD line as follows:

- Connect a bypass capacitor across the VSS pin and VDD pin at equal length.
- Connect a bypass capacitor across the VSS pin and VDD pin with the shortest possible wiring.
- Use lines with a diameter larger than other signal lines for VSS line and VDD line.
- Connect the power source wiring via a bypass capacitor to the VSS pin and the VDD pin.

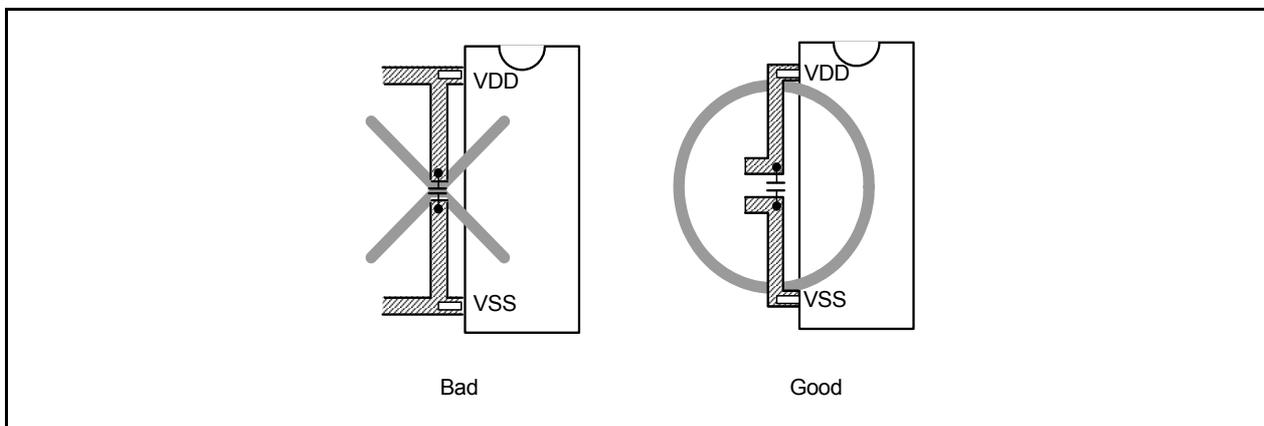


Figure 1.3 Bypass Capacitor Across the VSS Line and VDD Line

1.3 Wiring to Analog Input Pins

- Connect a resistor that is approximately $100\ \Omega$ to $1\ \text{k}\Omega$ to an analog signal line which is connected to an analog input pin in series. Connect the resistor to the MCU as close as possible.
- Insert a capacitor that is approximately $1000\ \text{pF}$, between the analog input pin and Vss pin, placing it as close to the Vss pin as possible. The wire between the analog input pin and the capacitor, and the wire between the Vss pin and the capacitor should be equal length.

Reason:

Signals input to an analog input pin are usually output signals from a sensor. Most sensors that detect events are placed further away from boards that have mounted MCUs. Wiring to analog input pins is inevitably longer. This long wiring functions as an antenna which attracts noise into the MCU, which causes noise to the analog input pin.

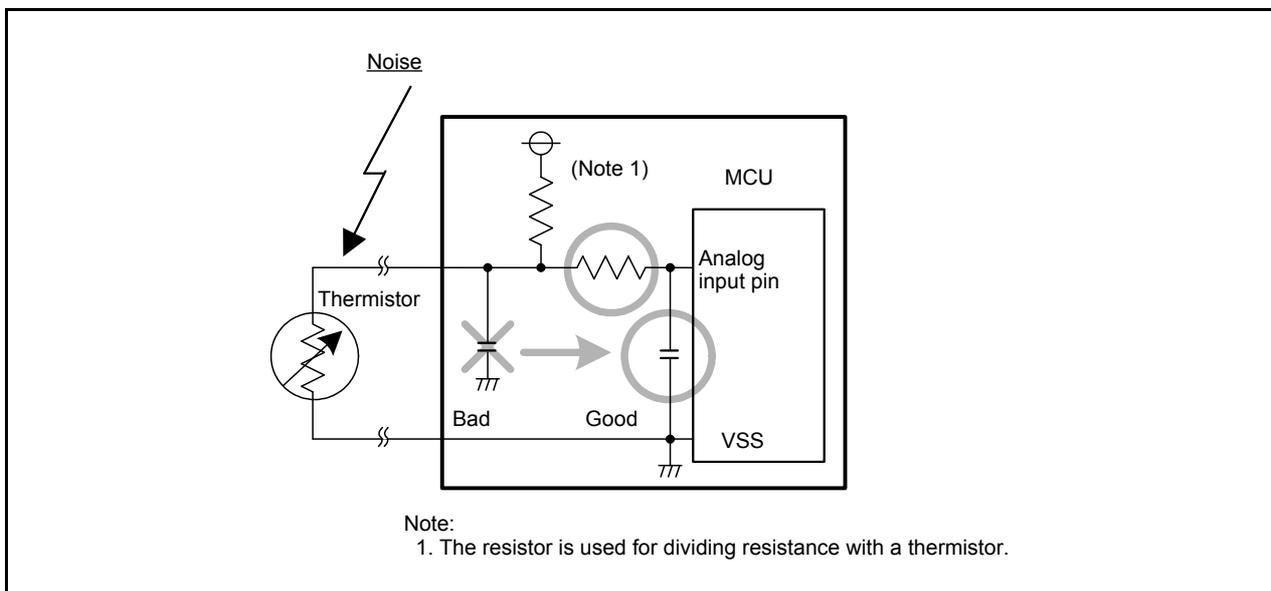


Figure 1.4 Analog Signal Line, a Resistor, and a Capacitor

1.4 Oscillator Concerns

Oscillators that generate clocks for the main operation of the MCU need special attention as to not be affected by other signals.

1.4.1 Avoid Large Current Signal Lines

Place the MCU (and especially the oscillator) as far away as possible from signal lines where a current larger than the tolerance of current value flows.

Reason:

In a system using an MCU, there are signal lines for controlling things such as motors, LEDs, and thermal heads. When a large current flows through those signal lines, noise occurs because of mutual inductance.

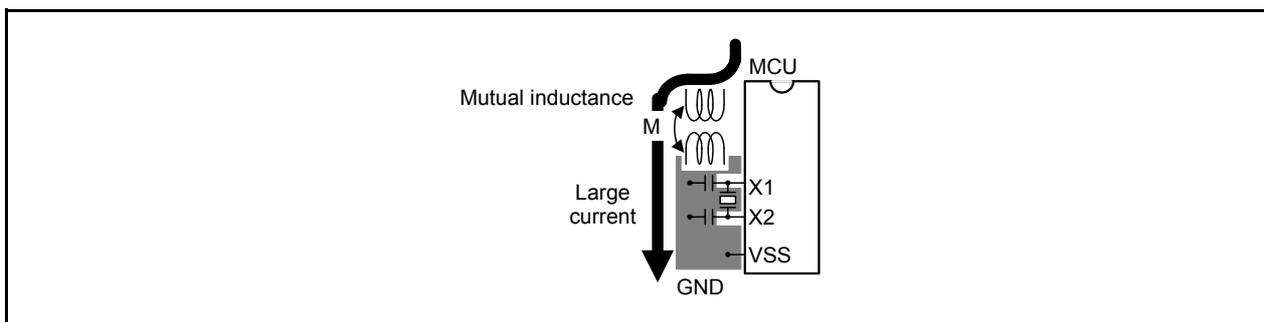


Figure 1.5 Wiring of a Large Current Signal Line

1.4.2 Avoid Signal Lines Where Potential Levels Change Frequently

Place an oscillator and a connecting pattern of an oscillator away from signal lines where potential levels change frequently. The layout for signal lines where potential levels change frequently should not cross signal lines such as clock related signal lines and other signal lines that are easily affected by noise; and the signal lines should not run long in parallel.

Reason:

Signal lines where potential levels change frequently (such as the TO01 pin signal line) may affect other lines at the rising edge or falling edge of a signal. If such lines cross over a clock line, clock waveforms may be unstable, which causes an MCU failure or a program runaway.

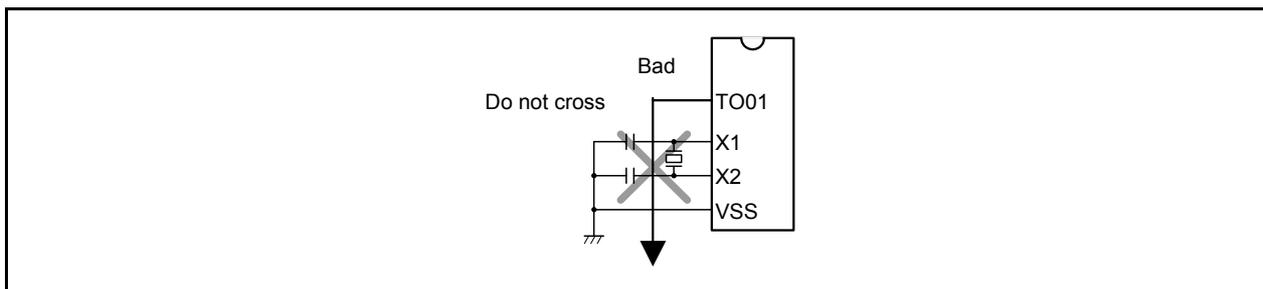


Figure 1.6 Wiring of Signal Lines Where Potential Levels Change Frequently

1.5 Setup for I/O Ports

Setup I/O ports using hardware and software as described below:

Hardware

- Connect a resistor that is 100 Ω or more to a signal line which is connected to an I/O port in series. Connect the resistor as close to the MCU as possible.

Software

- For input ports, read data several times by a program to check whether input levels are equal or not.
- For output ports, since the output data may inverse due to noise, rewrite data to its port register at fixed periods.
- Rewrite data to the register that controls port functions at fixed periods.

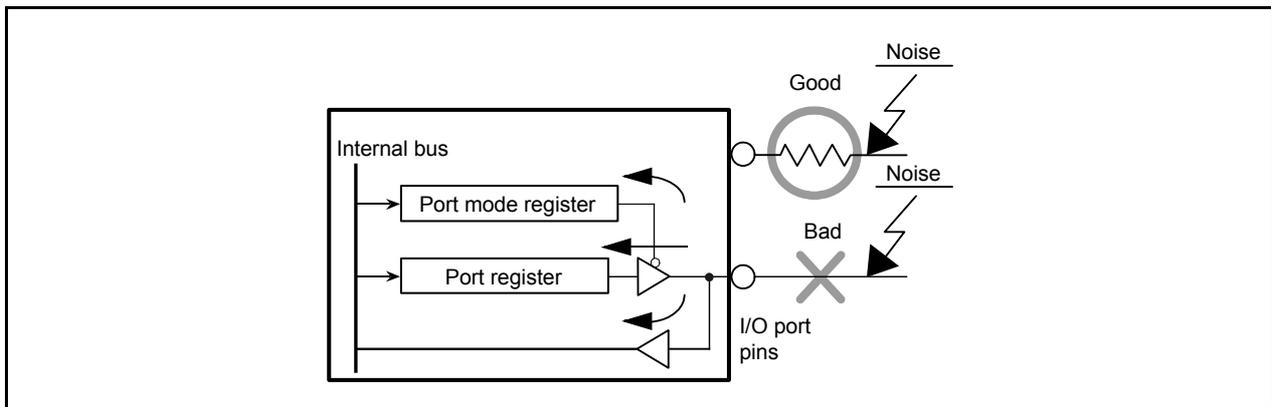


Figure 1.7 Setup for I/O Ports

2. Reference Documents

Each product User's Manual: Hardware

The latest version can be downloaded from the Renesas Electronics website.

Technical Update/Technical News

The latest information can be downloaded from the Renesas Electronics website.

Website and Support

Renesas Electronics website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

Revision History	RL78 Family Notes and Countermeasures Against Noise
------------------	--

Rev.	Date	Description	
		Page	Summary
1.00	Oct. 4, 2011	—	First edition issued

All trademarks and registered trademarks are the property of their respective owners.

General Precautions in the Handling of MPU/MCU Products

The following usage notes are applicable to all MPU/MCU products from Renesas. For detailed usage notes on the products covered by this manual, refer to the relevant sections of the manual. If the descriptions under General Precautions in the Handling of MPU/MCU Products and in the body of the manual differ from each other, the description in the body of the manual takes precedence.

1. Handling of Unused Pins

Handle unused pins in accord with the directions given under Handling of Unused Pins in the manual.

- The input pins of CMOS products are generally in the high-impedance state. In operation with an unused pin in the open-circuit state, extra electromagnetic noise is induced in the vicinity of LSI, an associated shoot-through current flows internally, and malfunctions occur due to the false recognition of the pin state as an input signal become possible. Unused pins should be handled as described under Handling of Unused Pins in the manual.

2. Processing at Power-on

The state of the product is undefined at the moment when power is supplied.

- The states of internal circuits in the LSI are indeterminate and the states of register settings and pins are undefined at the moment when power is supplied.

In a finished product where the reset signal is applied to the external reset pin, the states of pins are not guaranteed from the moment when power is supplied until the reset process is completed.

In a similar way, the states of pins in a product that is reset by an on-chip power-on reset function are not guaranteed from the moment when power is supplied until the power reaches the level at which resetting has been specified.

3. Prohibition of Access to Reserved Addresses

Access to reserved addresses is prohibited.

- The reserved addresses are provided for the possible future expansion of functions. Do not access these addresses; the correct operation of LSI is not guaranteed if they are accessed.

4. Clock Signals

After applying a reset, only release the reset line after the operating clock signal has become stable. When switching the clock signal during program execution, wait until the target clock signal has stabilized.

- When the clock signal is generated with an external resonator (or from an external oscillator) during a reset, ensure that the reset line is only released after full stabilization of the clock signal. Moreover, when switching to a clock signal produced with an external resonator (or by an external oscillator) while program execution is in progress, wait until the target clock signal is stable.

5. Differences between Products

Before changing from one product to another, i.e. to one with a different part number, confirm that the change will not lead to problems.

- The characteristics of MPU/MCU in the same group but having different part numbers may differ because of the differences in internal memory capacity and layout pattern. When changing to products of different part numbers, implement a system-evaluation test for each of the products.

Notice

- All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
- Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
- You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
- Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
- When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
- Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
- Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
"Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
- You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
- Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
- Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
- Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
2880 Scott Boulevard Santa Clara, CA 95050-2554, U.S.A.
Tel: +1-408-586-6000, Fax: +1-408-586-6130

Renesas Electronics Canada Limited
1101 Nicholson Road, Newmarket, Ontario L3Y 9C3, Canada
Tel: +1-905-898-5441, Fax: +1-905-898-3220

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: +44-1628-585-100, Fax: +44-1628-585-900

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-65030, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
7th Floor, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100083, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 204, 205, AZIA Center, No.1233 Lujiazui Ring Rd., Pudong District, Shanghai 200120, China
Tel: +86-21-5877-1818, Fax: +86-21-6887-7858 / -7898

Renesas Electronics Hong Kong Limited
Unit 1601-1613, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2886-9318, Fax: +852 2886-9022/9044

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei, Taiwan
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
1 HarbourFront Avenue, #06-10, Keppel Bay Tower, Singapore 098632
Tel: +65-6213-0200, Fax: +65-6276-8001

Renesas Electronics Malaysia Sdn.Bhd.
Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics Korea Co., Ltd.
11F., Samik Lavied' or Bldg., 720-2 Yeoksam-Dong, Kangnam-Ku, Seoul 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141