

Application Note

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

AN-CM-263

Abstract

This application note presents how to make a capacitive charge pump with a programmable, regulated output voltage using GreenPAK IC and a couple of low-cost external components. Single stage charge pump may be configured as voltage booster or voltage inverter. GreenPAK charge pump operates at input voltages 1.8 V to 5 V and load currents up to 145 mA. Overall performance peaks at input voltages 3 V to 5 V and output currents 1 mA to 5 mA, using Schottky external diodes. The advantage of GreenPAK solution is the flexibility to shift the design to meet the system priorities, such as a focus on power consumption, ripple etc.

This application note comes complete with design files which can be found in the References section.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

Contents

Abstract	1
Contents	2
Figures.....	2
Tables	3
1 Terms and Definitions.....	4
2 References	4
3 Introduction.....	5
4 Charge Pump Circuit Design.....	5
4.1 Operating Frequency & Capacitor Selection	6
4.2 Diode Selection	6
4.3 Feedback Design for Voltage Booster	6
4.4 Feedback Design for Voltage Inverter	8
4.5 Feedback Design for Input Referenced Inverter	8
5 GreenPAK Design	9
5.1 Oscillator Design & Output Pins Design	9
5.2 Comparator Design & Programming Output Voltage.....	9
5.3 GreenPAK Design Schematic.....	10
5.4 Powerdown Feature	11
6 Circuit Performance	12
7 Testing & Results	13
7.1 Graphs	14
8 Optional Design Modifications and Optimizations	18
9 Key Advantages and Commercial Viability	20
10 Conclusion.....	21
Revision History	22

Figures

Figure 1: Single Stage Charge Pump Regulated Voltage Booster and Inverter	5
Figure 2: Input Referenced Regulated Inverter	8
Figure 3: Comparator Settings	10
Figure 4: GreenPAK Based Regulated Charge Pump - Basic Design.....	11
Figure 5: Programmable Output Regulated Charge Pump GreenPAK Design	11
Figure 6: Regulated CP with Full Shutdown.....	12
Figure 7: GreenPAK Design for DUT	14
Figure 8: Load Regulation 5 V Lin.....	16
Figure 9: Load Regulation 3.3 V Lin	16
Figure 10: Load Regulation 5 V Log.....	16
Figure 11: Load Regulation 3.3 V Log.....	16
Figure 12: Efficiency vs Load 5 V.....	17

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

Figure 13: Efficiency vs Load 3.3 V	17
Figure 14: Line Regulation 5 V	17
Figure 15: Line Regulation 3.3 V	17
Figure 16: Efficiency vs Line 5 V	18
Figure 17: Efficiency vs Line 3.3 V	18
Figure 18: Quiescent Current	18
Figure 19: Shutdown Current	18
Figure 20: Replacing Diodes with MOSFETs	19
Figure 21: Reusing Reference Pin for Multiple Outputs	19

Tables

Table 1: Analog Comparator Input Characteristics	7
Table 2: Circuit Performance Specifications	12

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

1 Terms and Definitions

BOM	Bill of materials
CMOS	Complementary metal oxide semiconductor
DUT	Device under test
EMI	Electromagnetic interference
ESR	Equivalent series resistance
GPIO	General purpose input output
I2C	Inter-integrated circuit
IC	Integrated circuit
IoT	Internet of things
LDO	Low drop out regulator
LUT	Lookup table
MLCC	Multi-layer ceramic capacitor
MOSFET	Metal oxide semiconductor field effect transistor
NFET	N-channel field effect transistor
PFET	P-channel field effect transistor
R_{dson}	Resistance drain-source while FET is ON
SPI	Serial peripheral interface

2 References

For related documents and software, please visit:

[GreenPAK™ Programmable Mixed-Signal Products | Renesas](#)

Download our free [GreenPAK™](#) Designer software [1] to open the .gp files [2] and view the proposed circuit design. Use the [GreenPAK](#) development tools [3] to freeze the design into your own customized IC in a matter of minutes. Find out more in complete library of application notes [4] featuring design examples as well as explanations of features and blocks within the GreenPAK IC.

- [1] [GreenPAK Designer Software](#), Software Download and User Guide
- [2] [AN-CM-263 Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK.gp](#), [GreenPAK](#) Design File
- [3] [GreenPAK Development Tools](#), [GreenPAK](#) Development Tools Webpage
- [4] [GreenPAK Application Notes](#), [GreenPAK](#) Application Notes Webpage
- [5] Capacitive Charge Pump using [GreenPAK](#), Application Note
- [6] SLG46533, Datasheet
- [7] MCP1252/3 Low-Noise, Positive-Regulated Charge Pump, Datasheet, Microchip Technology
- [8] LTC1751/LTC1751-3.3/LTC1751-5, Datasheet, Linear Technology.
- [9] TPS6013x Regulated 5-V, 300-mA High-Efficiency Charge Pump DC-DC Converters, Datasheet, Texas Instruments.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

3 Introduction

Many battery powered applications in the IoT market require additional voltage levels for powering specific interface circuits, sensors, etc. This application note presents how to make a regulated capacitive charge pump using a **GreenPAK** IC and a couple of low cost external components. A single stage charge pump may be configured as a voltage doubler or inverter. Multistage charge pumps enable higher output voltages, both positive and negative (inverting doubler, tripler etc). The output is a regulated voltage source, independent of input voltage level variations and load variations, provided that input voltage and load are within defined limits. Maximum output current is in the milliamps range. This application note is a continuation of the app note “Capacitive Charge Pump using **GreenPAK**” for unregulated charge pumps.

The **GreenPAK** power supply voltage is used as the charge pump input. The **GreenPAK** outputs a driving signal for the external bootstrap capacitor. For multistage charge pumps, the **GreenPAK** outputs two anti-phase driving signals. A control signal is optional to start/stop (power down) the charge pump and can be added as an IO or through serial communication protocols. When using I2C-enabled **GreenPAK** s the output voltage level can be programmed by controlling the internal reference voltage over I2C communication. If tight output voltage tolerance is required, external precision reference may be applied.

One **GreenPAK** IC can control multiple charge pumps with various output voltages. Independent programmability may be limited to some of the outputs, depending on the **GreenPAK** part selected. In the case of low input voltages, **GreenPAK** s may be cascaded to obtain higher output voltages with fewer external components.

Basic diagram is shown in [Figure 1](#).

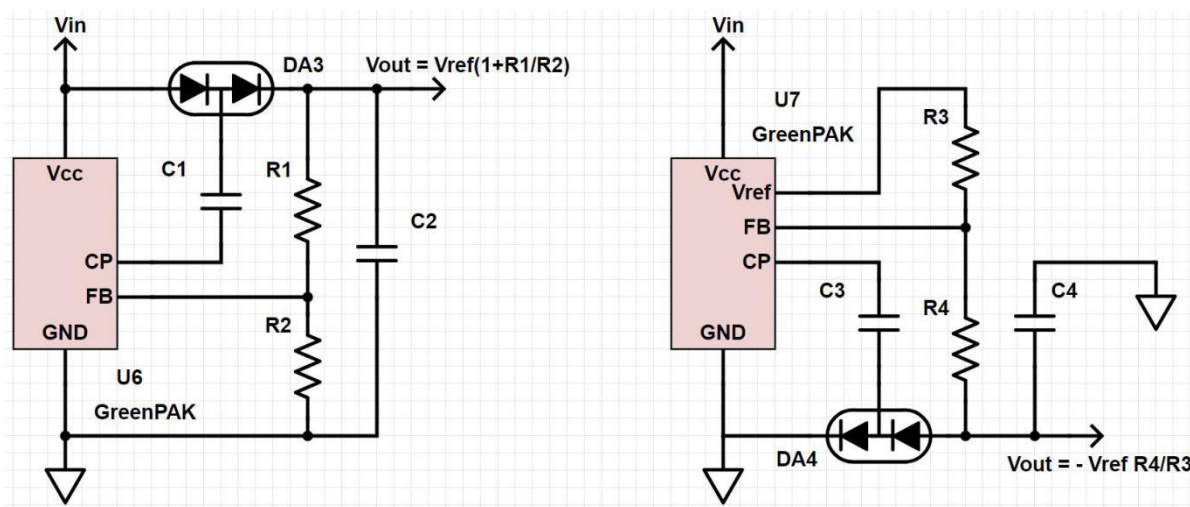


Figure 1: Single Stage Charge Pump Regulated Voltage Booster and Inverter

4 Charge Pump Circuit Design

The implementation is founded on the unregulated charge pump design. A comparator is added to detect when the desired output voltage is met and consequently stop charging the output capacitor. In this way the output voltage is limited without an additional LDO or other type of dissipative regulator. Since analog comparators are available inside most **GreenPAK**s only a resistive voltage divider is needed.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

The circuit performance of a regulated charge pump is like the unregulated charge pump design procedure. A designer needs to make sure that charge pump in unregulated configuration can provide high enough output voltage at all working conditions (input voltage and load current). Introduced feedback will regulate the output voltage. Necessary voltage margin is negligible.

4.1 Operating Frequency & Capacitor Selection

Operating frequency and capacitor selection is explained in the application note for unregulated charge pumps; these principles all apply to regulated charge pumps. Additionally, we will examine how operating frequency and capacitance affects output voltage regulation.

Output voltage regulation is performed by controlling the peak output voltage value, so the average value of output voltage depends on the ripple. At no load, ripple is zero, so average voltage equals peak voltage. At full load, the ripple at maximum, and average value is the peak value minus half of the peak-to-peak ripple. Regulation “zero to full load” equals half of the maximum peak-to-peak ripple.

Ripple depends on load, operating frequency and capacitance. Load cannot typically be altered by design, but operating frequency and capacitance can be set for correct operation.

Increasing operating frequency reduces ripple and improves output voltage regulation. However, it also increases power losses and reduces efficiency. Increasing output capacitance reduces ripple and improves output voltage regulation. However, bigger capacitors are usually larger in size and higher in cost. Note that a bigger output capacitor also means a longer startup time, as well as a longer transition time between regulated output voltages. At light loads and large output capacitance a transition to a lower voltage level might take a very long time.

For top efficiency, improve regulation by increasing output capacitance. For low price, low size, and fast response improve regulation by increasing operating frequency.

4.2 Diode Selection

Diode selection is explained in the application note for unregulated charge pumps. However, regulated charge pumps lack the influence of diode forward voltage to output regulation, so diodes only affect the maximum achievable output voltage. After regulation is introduced, diodes will only marginally affect the power efficiency, provided the circuit is “in regulation”. Efficiency will not be much higher if diodes with lower forward voltage drop are applied (schottky diodes), but the dissipation will shift from the diodes to the GreenPAK itself. In certain applications standard diodes with higher forward voltage drop may help reduce the heat of the GreenPAK IC.

4.3 Feedback Design for Voltage Booster

Feedback design is simple for the case of the voltage doubler. The output voltage peak is directly determined by the resistive divider ratio and the reference voltage is provided by the GreenPAK internal blocks. Reference voltage performance is best around 1 V, which is also a handy value for calculations. Divider ratio to obtain V_{out} at V_{ref} :

$$R_1 / R_2 = V_{out} / V_{ref} - 1$$

Using $V_{ref} = 1 \text{ V}$ gives $R_1/R_2 = V_{out} - 1$

For example, $V_{out} = 5 \text{ V}$ and $V_{ref} = 1 \text{ V}$, $R_1/R_2 = 4$.

Regarding the resistance of the divider, an easy approach is to make divider current 1% of maximum output current.

$$V_{ref} / R_2 = I_{outmax} * 1\%$$

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

For example, $I_{outmax} = 1 \text{ mA}$, $R_2 = 1 \text{ V} / 10 \text{ } \mu\text{A} = 100 \text{ K}\Omega$ and $R_1 = 4 * R_2 = 400 \text{ K}\Omega$.

A resistive divider loads the charge pump and increases quiescent current thus reducing the circuit efficiency. Therefore, it's better to aim for high resistance. However, too high a resistance makes the circuit susceptible to electromagnetic interference and introduces noise that reflects to the output voltage. Additionally, input characteristics of a GreenPAK comparator at high divider resistance become less negligible and may affect output voltage regulation.

Comparator input impedance is very high at gain 1x, but much lower when using an internal divider:

Table 1: Analog Comparator Input Characteristics

Gain	1x	0.5x		0.33x		0.25x	
Input resistance	100 M Ω	1 M Ω	2 M Ω	0.8 M Ω	2 M Ω	1 M Ω	2 M Ω
Input current @1V	10 nA	1 μA	0.5 μA	1.25 μA	0.5 μA	1 μA	0.5 μA

With internal divider on, input current is around 1 μA . To keep it below 1%, divider current should be at least 100 μA , which is too high for low power applications. It is better to use comparator with divider switched off, when input current is around 10nA and it is below 1% for divider currents of 1 μA and above.

Leakage current is 1 nA typical, making it 10 times less than comparator input current. However, leakage current is strongly dependent on temperature and may reach 1 μA at high temperatures. Charge pump losses heat up the GreenPAK IC and temperature may raise considerably even at moderate ambient temperatures. For most applications, leakage current will stay below 0.1 μA ; still 10x higher than comparator input current. To keep the error below 1%, divider current should be at least 10 μA .

Recommendation: design divider current to be 10 μA or more, except in the case GreenPAK works at high ambient temperatures or in the case of high-power charge pump (high losses) when 100 μA divider current is the preferred option.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

4.4 Feedback Design for Voltage Inverter

In the voltage inverter circuit, an output voltage divider referred to ground yields a sense voltage below ground – outside the **GreenPAK** supply voltage range. Such a sense signal cannot be applied to the comparator input, so a voltage divider must be biased to a reference potential above ground. One solution is to take advantage of **GreenPAK** internal reference wired to an output pin. In this configuration, the circuit works with 2 reference voltages, one reference used for comparator threshold (call it “threshold voltage”) and the other reference used for feedback (call it “reference voltage”).

Output voltage peak value is determined by the ratio of resistive divider and the difference between reference voltage and threshold voltage and referred to reference voltage.

$$V_{out} = V_{th} - R_f (V_{ref} - V_{th}) / R_r = V_{th} (1 + R_f / R_r) - V_{ref} * R_f / R_r$$

Programming **GreenPAK**'s internal references V_{ref} and V_{th} set the output voltage level, with fixed voltage divider ratio.

Taking $V_{th} \sim 0$, greatly simplifies the expression for output voltage:

$$V_{out} \sim -V_{ref} * R_f / R_r$$

When considering voltage divider resistance in the case of a voltage inverter, the designer must consider current capacity of the **GreenPAK** reference output. Current capacity is relatively low and resistance must be high enough to avoid overload.

4.5 Feedback Design for Input Referenced Inverter

In the common case when input voltage is regulated (tight tolerance) and it's satisfactory for the output voltage regulation to match input voltage regulation, the input voltage may be used to generate a reference voltage. The circuit is simplified and resembles the voltage doubler configuration:

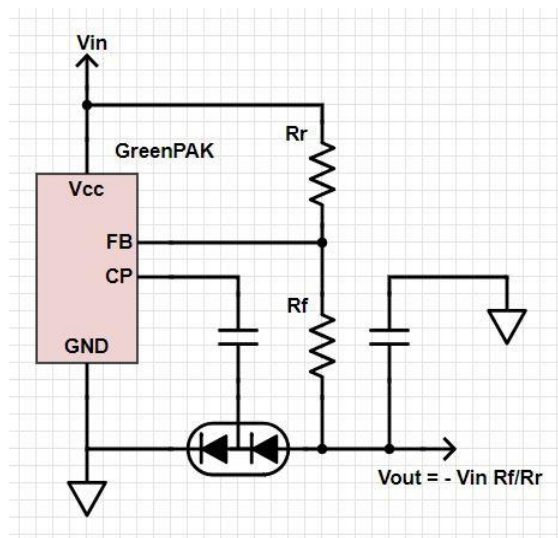


Figure 2: Input Referenced Regulated Inverter

Replacing reference voltage with input voltage gives the formula for output voltage:

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

$$V_{out} = V_{th} - R_f (V_{in} - V_{th}) / R_r = V_{th} (1 + R_f / R_r) - V_{in} * R_f / R_r$$

Programming V_{th} sets the negative output voltage.

Choosing $V_{th} \sim 0$, greatly simplifies the expression for output voltage:

$$V_{out} \sim -V_{in} * R_f / R_r$$

For a single stage voltage inverter, R_f must be less than R_r , because the absolute value of the output voltage cannot be higher than the input voltage.

The same principles that apply for choosing resistor values for the voltage doubler also apply to the inverter configuration.

5 GreenPAK Design

The **GreenPAK** Design adds one analog comparator and a couple of gates to the unregulated charge pump design. Operating frequency affects regulation, since feedback controls the output peak value rather than the average level, so output voltage declines with raising output ripple. Keeping output ripple low by selecting higher operating frequency and/or large output capacitor improves output voltage regulation.

5.1 Oscillator Design & Output Pins Design

Oscillator and output pin design are explained in the application note for unregulated charge pumps. However, the voltage drop introduced by an output pin's serial resistance is neutralized by regulation, so output pin configuration only affects maximum output voltage. Output pin configuration still affects efficiency like an unregulated charge pump. Efficiency will be better if pins with lower resistance are used, if multiple pins are wired in parallel, and also if a GreenPAK with better IO performance is selected.

5.2 Comparator Design & Programming Output Voltage

Hysteresis: Enable and set to minimum available value (25 mV). Hysteresis raises effective reference voltage V_{IH} , presented in the ACMP settings dialog box, in the Information section.

Low bandwidth: Enables low pass filter on feedback input. Use in noisy environments.

IN+ gain: Disable for high input impedance.

IN+ source: Select feedback input pin.

IN- source: Set initial V_{ref} value as absolute value (mV), V_{dd} fraction or ext. V_{ref} as desired. This initial value may be changed via I²C command.

The output voltage can be programmed via serial communication by setting internal reference voltage at the comparator input. Through I²C the internal reference can be set between 50 mV and 1200 mV in 50 mV steps. Using the feedback resistor divider the regulation can be set to regulate the output voltage to different values

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

Properties [X]

A CMP1

100uA pullup on input: Disable

Hysteresis: 25 mV

Low bandwidth: Disable

IN+ gain: Disable

Connections

IN+ source: PIN 10 (IO8)

IN- source: 1000 mV

Information

Typical ACMP thresholds

V _{IH} (mV)	V _{IL} (mV)
1013	988

ACMP start time [\(Summary\)](#)

Min, us	Typ, us	Max, us
-	294.698	2736.73

Power ctrl. settings

i ↶ ↷ Apply

Figure 3: Comparator Settings

5.3 GreenPAK Design Schematic

Figure 4 shows the basic design with only one pin used to drive the Dickson charge pump. The output voltage is not programmable, but the design includes a shutdown feature. Such design simplicity is enabled by GreenPAK built-in features. The basic design fits into any GreenPAK that offers an analog comparator block. To increase drive strength, add output pins as available and wire them to the LUT output.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

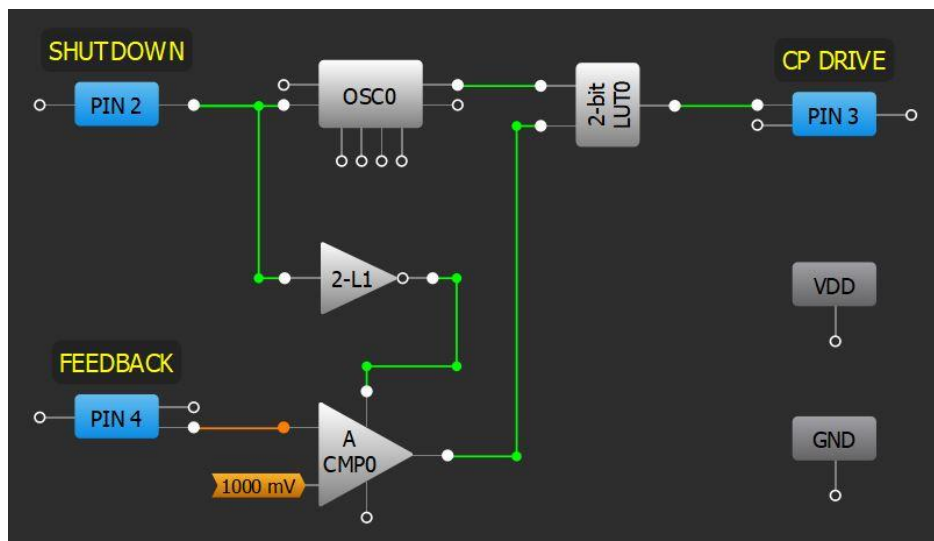


Figure 4: GreenPAK Based Regulated Charge Pump - Basic Design

Figure 5 shows a design with a programmable output voltage and two shutdown inputs: one direct input, like in the first design, and another via I²C. They are wired through an OR gate so each one can shut down the charge pump independently. If priority logic for shutdown commands is needed, change LUT0 accordingly. This design requires I²C capabilities and it fits into any [GreenPAK](#) SLG465xx or SLG468xx. To enable the programmable output the I²C block must be enabled.

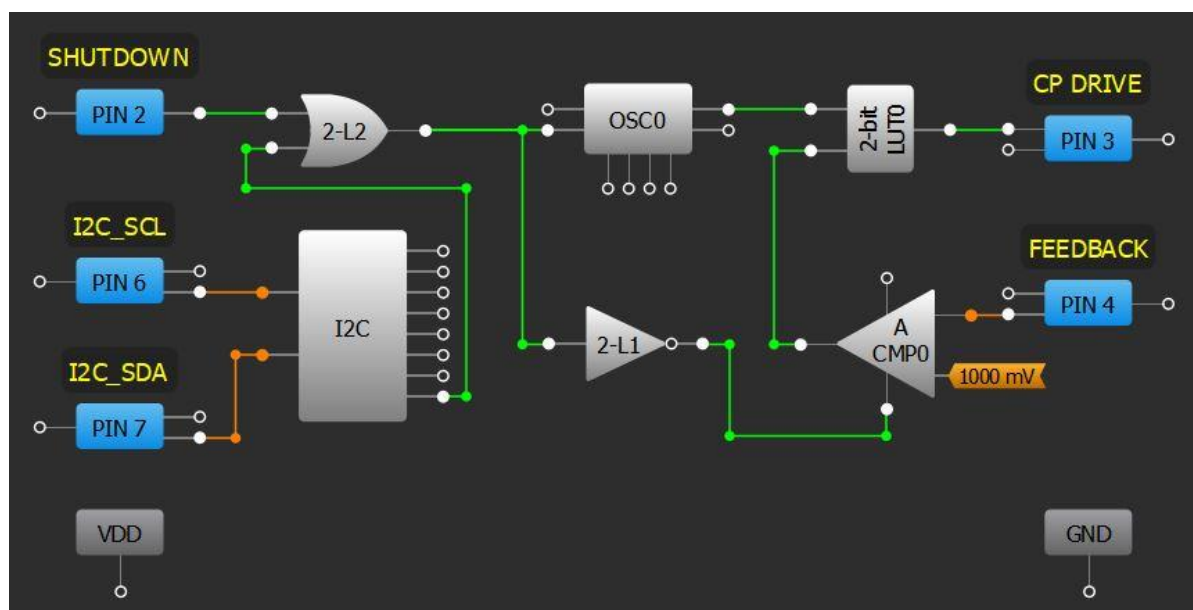


Figure 5: Programmable Output Regulated Charge Pump GreenPAK Design

5.4 Powerdown Feature

Design issues regarding a powerdown feature are explained in the application note for unregulated charge pumps. Extra design steps are needed to power down the comparator block that performs the regulation, as shown in [Figure 4](#).

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

If a powerdown feature is not needed, PWR UP input of the comparator (ACMP0) must be wired HI. The POR block is recommended as the HI source in this scenario.

When designing a voltage booster with full shutdown (see the application note for unregulated charge pumps), connect the feedback divider across the load, otherwise it will draw current from the supply rail during powerdown.

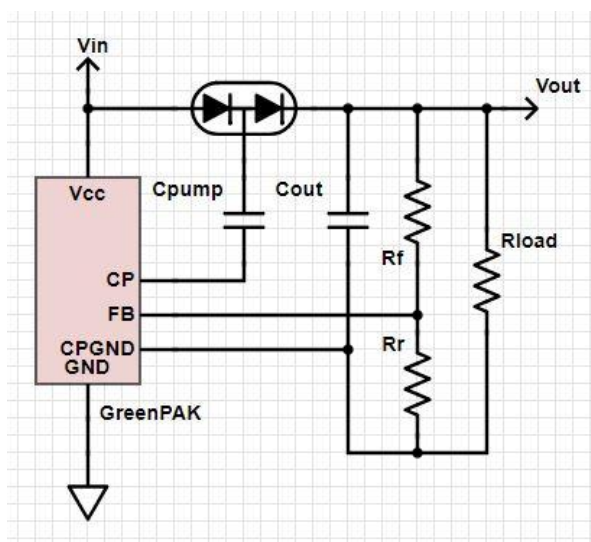


Figure 6: Regulated CP with Full Shutdown

6 Circuit Performance

Circuit performance specification: $C_{\text{pump}} = C_{\text{out}} = 1 \mu\text{F}$ X7R, D = schottky,

$T_A = 25^\circ\text{C}$, $f_{\text{osc}} = 125 \text{ kHz}$; $I_{\text{fb}} = 10 \mu\text{A}$; $R_r = 100 \text{ K}\Omega$; $R_f = 400 \text{ K}\Omega$ ($5 V_{\text{out}}$) or $230 \text{ K}\Omega$ ($3.3 V_{\text{out}}$); $V_{\text{ref}} = 1000 \text{ mV}$ unless otherwise noted.

Table 2: Circuit Performance Specifications

Symbol	Parameter	Note	Min	Typ	Max	Unit
V_{in}	Supply Voltage		1.71	---	5.5	V
I_{qsc}	Quiescent current	$R_L = \infty$, 125kHz	---	100	---	μA
I_{shdn}	Shutdown current (Note 1)	SLG46533	0.31	0.57	0.89	μA
f_{osc}	Oscillator frequency 25kHz OSC 2M OSC	selectable (Note 2)	0.048 -3.4% -9.4%	$25/2^n$ $2000/2^n$	2000 4.7% 14.4%	kHz
I_{out}	Output current (Note 3)		5	10	45	mA
V_{out}	Output voltage accuracy	in regulation	-3	-	+3	%
FB_{imp}	Feedback pin impedance	(Note 4)	0.8	100	-	$\text{M}\Omega$
P_{eff}	Power conversion efficiency	$R_L = 5\text{K}\Omega$	51	63	76	%

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

Symbol	Parameter	Note	Min	Typ	Max	Unit
V_{th}	Shutdown input threshold High State, Device Shutdown Low State, Device Operating	$V_{in}=3.3V$, selectable (Note 5)	1.06 0.67	1.81 1.31		V
T_A	Operating Temperature		-40	25	85	°C

- Note 1** I_{shdn} : specified for SLG46533, see relevant datasheet for other Renesas parts; considers leakage and other parasitics outside GreenPAK negligible; for measured shutdown current which includes feedback current, leakages and other parasitic parameters in a real circuit, not just the GreenPAK IC, check Figure 19.
- Note 2** Selectable to frequencies derived by dividing 25 kHz or 2 MHz: 25 kHz / 2 n or 2 MHz / 2 n, n=0..9
- Note 3** Column "min": single pin 2x drive, "typ": 2 pins in parallel 2x drive, "max": multiple pins in parallel 2x drive; specified for SLG46533, see relevant datasheet for other Renesas parts;
- Note 4** Depends on comparator configuration, for detailed info refer to Table 1.
- Note 5** GreenPAK input levels may be programmed for Logic Input (min HIGH-Level and max LOW-Level shown in column typ) or Low-Level Logic Input (min HIGH-Level and max LOW-Level shown in column min). Third option is Logic Input with Schmitt Trigger, see GreenPAK datasheet for voltage levels.

7 Testing & Results

The regulated voltage doubler charge pump external circuit was assembled on a breadboard and connected to a GreenPAK Universal Development Board. SLG46533 has enough GPIO pins to test multiple pins in parallel. A programmable DC voltage source is connected to the charge pump input. A programmable load is connected to the charge pump output. Two professional high accuracy multimeters were connected to measure input and output parameters.

For final measurements, the GreenPAK Universal Development Board is removed because it introduces effects in the circuit that impact the measurement results, such as the series resistance of the analog switches. For complete test setup schematics and photos please refer to unregulated charge pump application note.

Since the testing includes various configurations, GreenPAK design for a DUT device is adapted accordingly, so that the charge pump configuration may be changed by digital signals sent from an automated test setup. The GreenPAK design is presented in Figure 7 and it is intended only for testing purposes.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

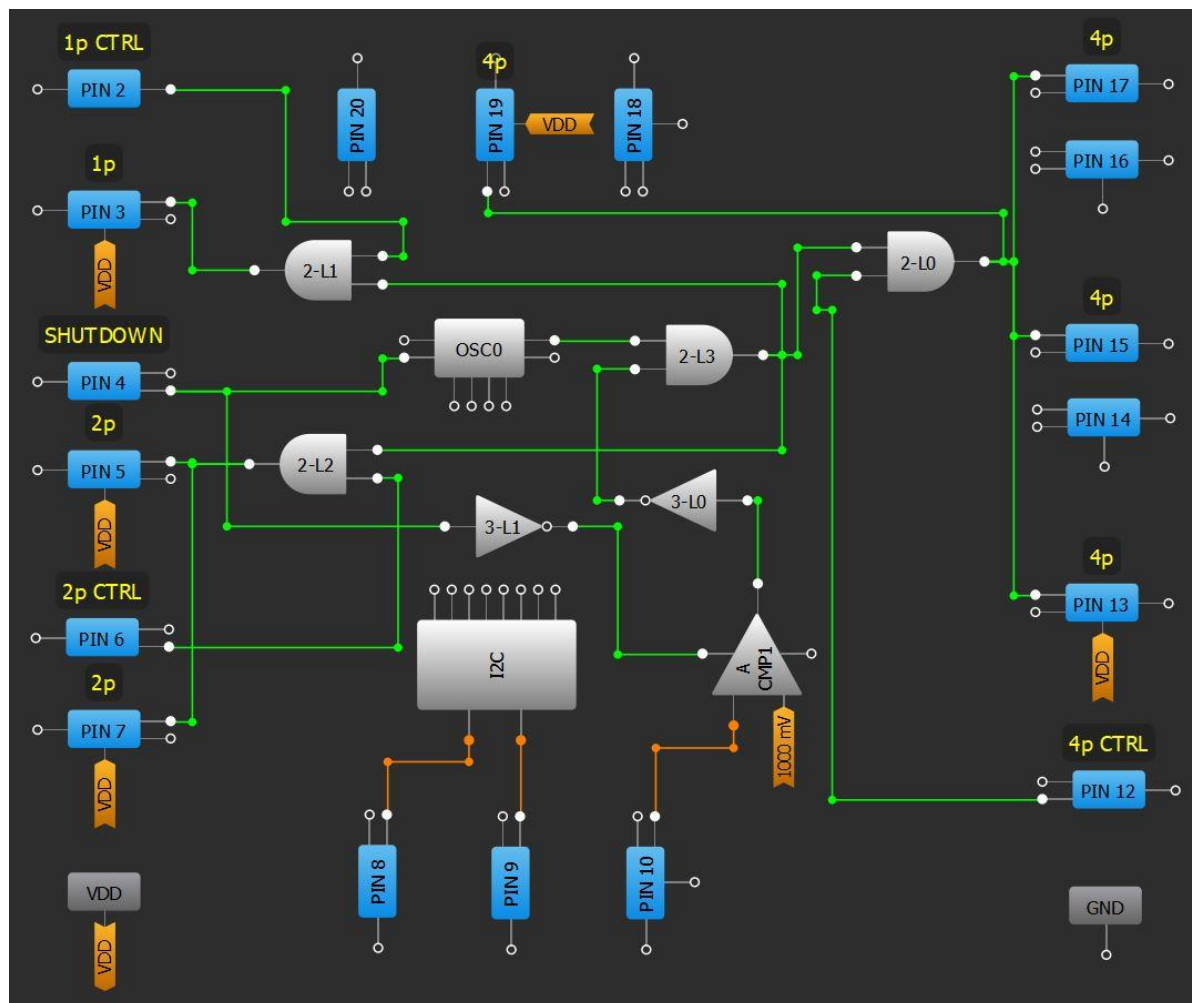


Figure 7: GreenPAK Design for DUT

7.1 Graphs

Measurements were obtained for two popular low cost diode options: standard silicon fast switching diodes 1N4148 and schottky diodes BAT42. Results are presented graphically.

All Graphs:

$C_{\text{pump}} = C_{\text{out}} = 1 \mu\text{F}$ X7R ceramic multilayer; $T_A = 25^\circ\text{C}$; $f_{\text{osc}} = 125 \text{ kHz}$

Feedback:

$I_{\text{fb}} = 10 \mu\text{A}$; $R_r = 100 \text{ K}\Omega$; $R_f = 400 \text{ K}\Omega$ ($5 V_{\text{out}}$) or $230 \text{ K}\Omega$ ($3.3 V_{\text{out}}$); $V_{\text{ref}} = 1000 \text{ mV}$

Configuration: Voltage booster (doubler); full shutdown: no; programmable ($I^2\text{C}$): yes

Graphs vs Load Current, parameter: V_{in} ; $f=125 \text{ kHz}$; drive = 2 pin 2x:

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

- 8) 5 V Output voltage vs Load current (Load regulation) @ $V_{in} = 4.5\text{ V}, 3.7\text{ V}, 3.0\text{ V}$; D = standard, schottky; linear scale
- 9) 3.3 V Output voltage vs Load current (Load regulation) @ $V_{in} = 3.7\text{ V}, 3.0\text{ V}, 2.5\text{ V}$; D = standard, schottky; linear scale
- 10) 5 V Output voltage vs Load current (Load regulation) @ $V_{in} = 4.5\text{ V}, 3.7\text{ V}, 3.0\text{ V}$; D = standard, schottky; log scale
- 11) 3.3 V Output voltage vs Load current (Load regulation) @ $V_{in} = 3.7\text{ V}, 3.0\text{ V}, 2.5\text{ V}$; D = standard, schottky; log scale
- 12) Efficiency vs Load current @ $V_{out} = 5\text{ V}$; $V_{in} = 4.5\text{ V}, 3.7\text{ V}, 3.0\text{ V}$; D = standard, schottky
- 13) Efficiency vs Load current @ $V_{out} = 3.3\text{ V}$; $V_{in} = 3.7\text{ V}, 3.0\text{ V}, 2.5\text{ V}$; D = standard, schottky

Graphs vs V_{in} , parameter I_{out} : V_{in} ; $f=125\text{ kHz}$; drive = 2 pin 2x:

- 14) 5 V Output voltage vs Input voltage (Line regulation) @ $I_{out} = 1\text{ mA}, 3\text{ mA}, 10\text{ mA}$; D = standard, schottky
- 15) 3.3 V Output voltage vs Input voltage (Line regulation) @ $I_{out} = 1\text{ mA}, 3\text{ mA}, 10\text{ mA}$; D = standard, schottky
- 16) 5 V Output Efficiency vs Input voltage @ $I_{out} = 1\text{ mA}, 3\text{ mA}, 10\text{ mA}$; D = standard, schottky
- 17) 3.3 V Output Efficiency vs Input voltage @ $I_{out} = 1\text{ mA}, 3\text{ mA}, 10\text{ mA}$; D = standard, schottky
- 18) Quiescent current vs Input voltage @ $V_{out} = 5\text{ V}, 3.3\text{ V}$; D = standard, schottky
- 19) Shutdown current vs Input voltage @ $V_{out} = 5\text{ V}, 3.3\text{ V}$; D = standard, schottky

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

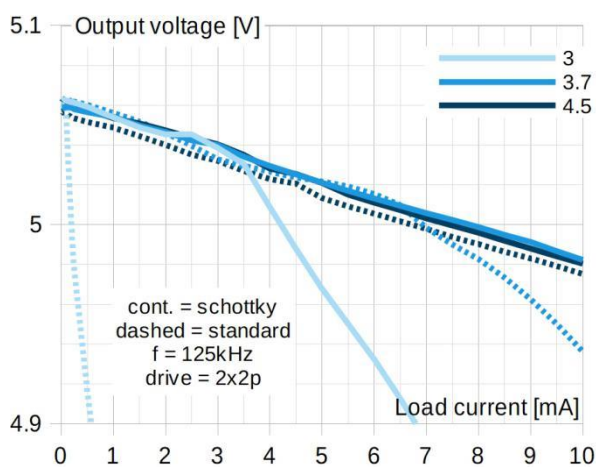


Figure 8: Load Regulation 5 V Lin

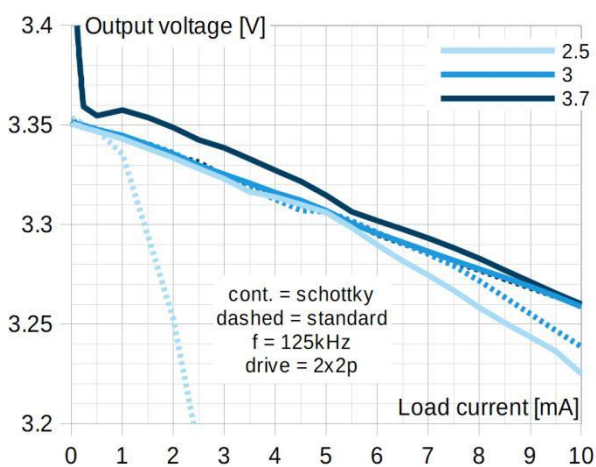


Figure 9: Load Regulation 3.3 V Lin

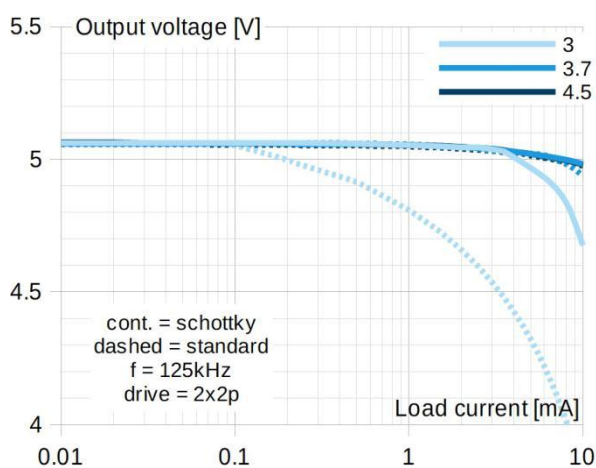


Figure 10: Load Regulation 5 V Log

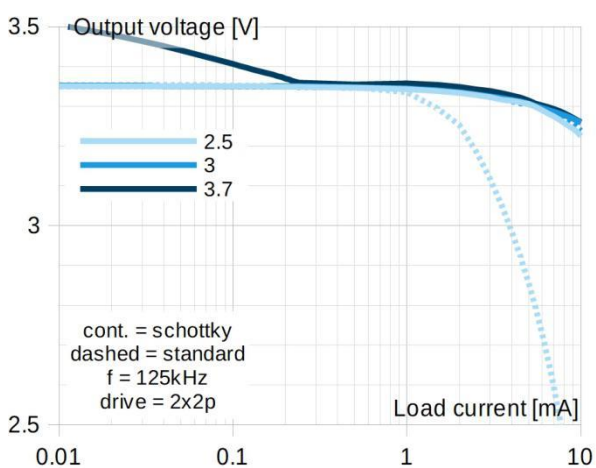


Figure 11: Load Regulation 3.3 V Log

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

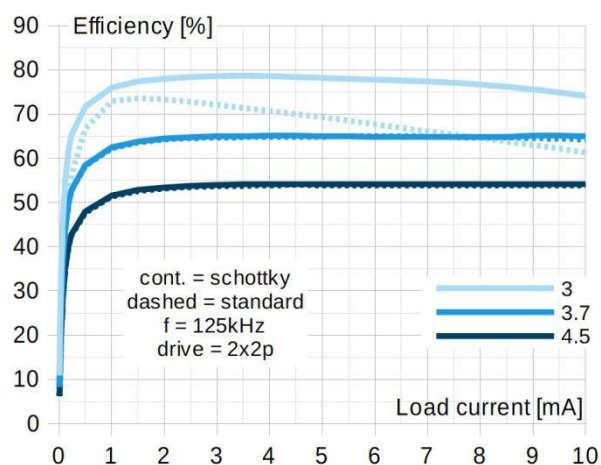


Figure 12: Efficiency vs Load 5 V

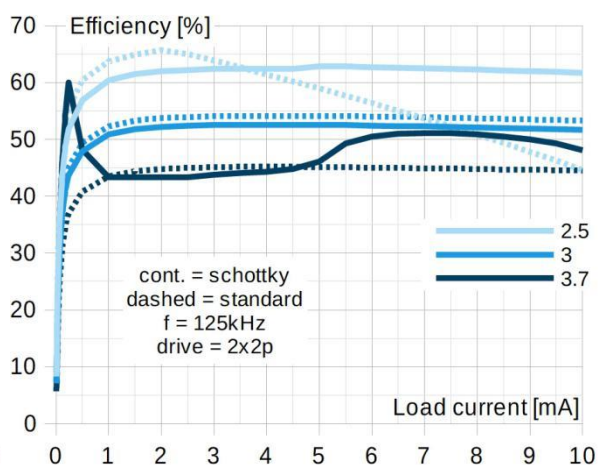


Figure 13: Efficiency vs Load 3.3 V

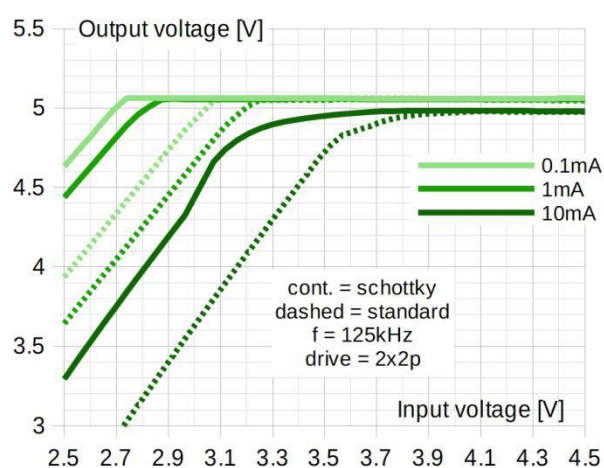


Figure 14: Line Regulation 5 V

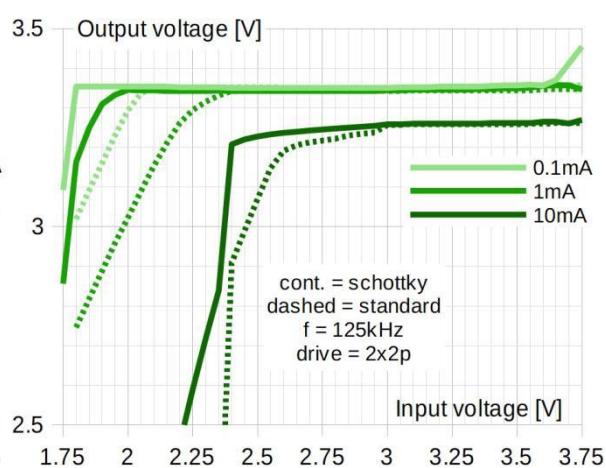


Figure 15: Line Regulation 3.3 V

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

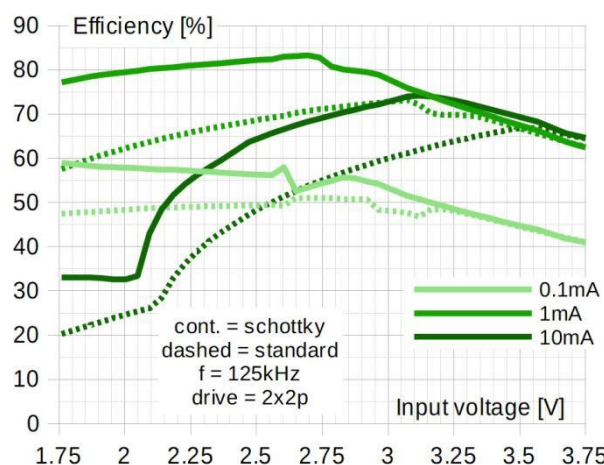


Figure 16: Efficiency vs Line 5 V

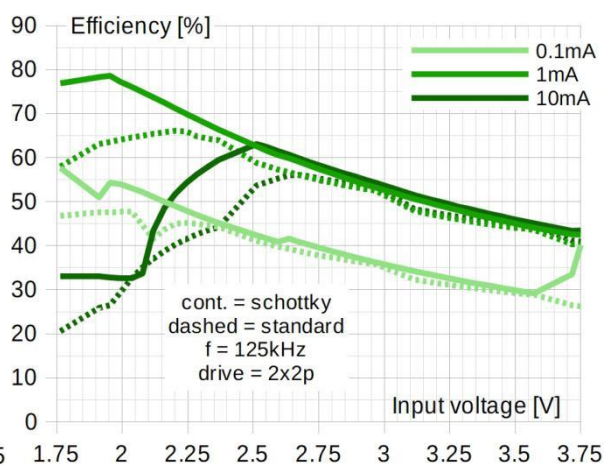


Figure 17: Efficiency vs Line 3.3 V

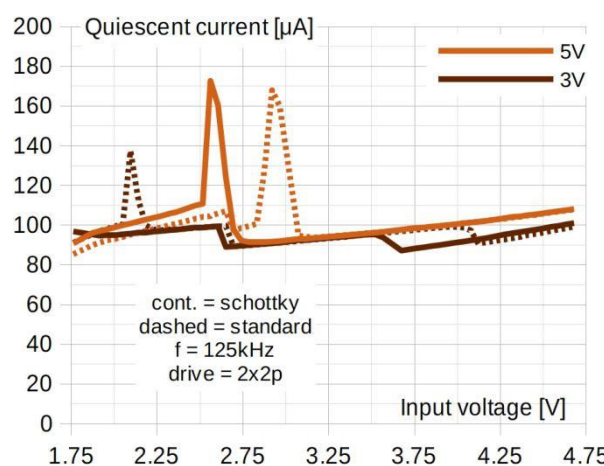


Figure 18: Quiescent Current

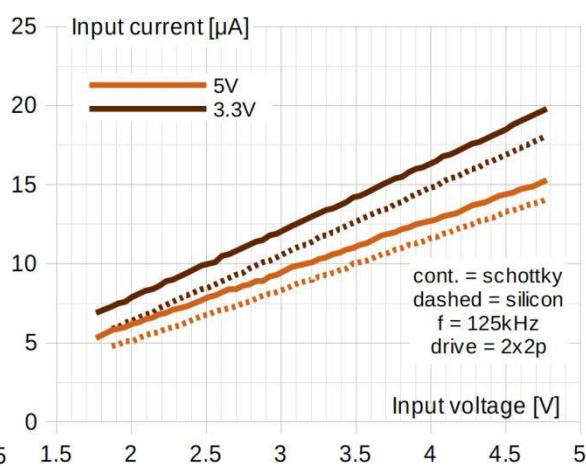


Figure 19: Shutdown Current

8 Optional Design Modifications and Optimizations

External diodes may be replaced by MOSFET's or analog switches to reduce voltage drop (increase output voltage) and improve efficiency. In this case the unregulated output voltage is higher than required regulated voltage, only efficiency will be affected.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

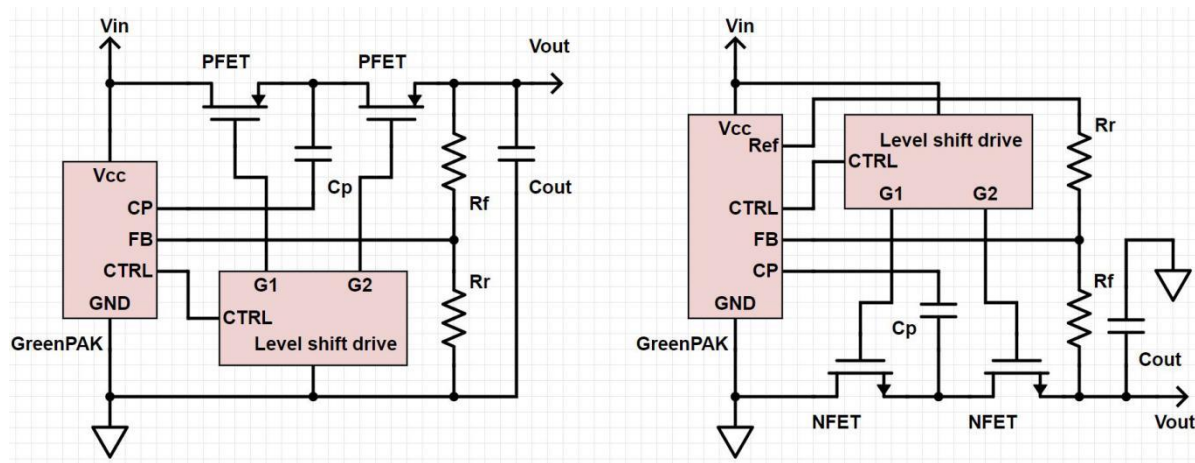


Figure 20: Replacing Diodes with MOSFETs

Output voltage may be regulated by LDO's or Zener diodes to eliminate output ripple. With a regulated charge pump there is no need to compensate for input voltage and load variations. When using LDOs, output characteristics are similar for regulated as well as for unregulated charge pumps, so a regulated circuit isn't often necessary. However, using a regulated charge pump with an LDO has the advantages of lower aggregate losses and less heat on the LDO. Higher efficiency is important for battery powered circuits where configuration "regulated charge pump + LDO" may double battery autonomy compared to "unregulated charge pump + LDO" configuration.

Looking at design modifications and optimizations presented for unregulated charge pumps, it is important to note that with unregulated charge pumps, it is possible to reuse same driving pins for all charge pumps, if several outputs are required. This is NOT possible for regulated charge pumps, because driving pins are used for regulation and pulse widths for different outputs will not be equal. With regulated charge pumps, you have to use at least one driving pin and one feedback pin for each output. However, it is possible to use the same internal voltage reference for multiple negative outputs, as shown in the [Figure 21](#).

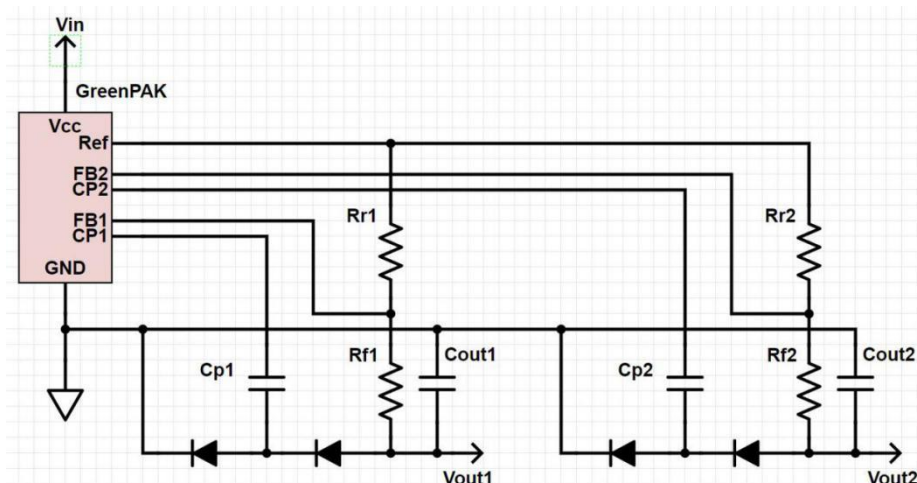


Figure 21: Reusing Reference Pin for Multiple Outputs

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

9 Key Advantages and Commercial Viability

If you already have GreenPAK IC in your circuit performing other functions, with a couple of unused pins and some free blocks inside GreenPAK, then it is absolutely commercially viable to implement a GreenPAK regulated charge pump solution because it will take just a couple of additional diodes, capacitors and resistors. Total cost of such a solution at production quantities comes down to cents, 5 to 10 times less than a specialized charge pump IC.

GreenPAK charge pump solution is also competitive if it is applied solely for a charge pump function. In this case, select a low cost GreenPAK such as SLG46110 and you can reach a cost 2 times less than a specialized charge pump IC solution.

One GreenPAK can control multiple regulated charge pump circuits or a combination of regulated and unregulated charge pumps. The cost of each additional charge pump comes down to additional external components, which is a couple of cents. With commercial charge pump ICs, each pump comes at full price. With GreenPAK solution for multiple charge pumps, parameters of each circuit may be programmed independently. Multiple outputs with the same voltage level might be required if separate on/off control is needed or cross regulation effects must be avoided.

With GreenPAK 4 and 5, it is possible to control the charge pump circuit via serial communication. GreenPAK 4 offers SPI, while GreenPAK 5 offers I²C. On/off control, operating frequency, wake/sleep regime are some parameters to set via serial comms. GreenPAKs with I²C provide far more configurability from the serial protocol.

Key advantages of GreenPAK charge pump solution:

- lower cost,
- smaller size,
- multiple outputs with the same IC,
- programmable operating frequency,
- serial comm control,
- lower quiescent current,
- surplus logic for additional functions.

GreenPAK solution offers similar or better performance and some additional features at a fraction of the price.

For the solution presented in this application note to be commercially viable,

certain requirements must be within performance level range that is achievable by GreenPAK solution. That range is dependent on supply voltage and for exact data please refer to graphs in this application note. General requirements are summarized as follows:

- output current in the milliamps range (<10 mA)
- power conversion efficiency <90 %.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

10 Conclusion

This application note presented a high performance, small size capacitive charge pump with regulated output voltage that can be built easily using a [GreenPAK](#) IC and a couple of low-cost external components. A [GreenPAK](#) charge pump operates with input voltages 1.8 V to 5 V and load currents up to 145 mA. Overall performance peaks at input voltages 3 V to 5 V and output currents 1 mA to 5 mA while using schottky diodes.

There are certain “basic charge pump” feature sets where the proposed [GreenPAK](#) solution offers lower cost, smaller size or lower quiescent current than specialized ICs. Other applications where a [GreenPAK](#) based charge pump solution is favorable are ones needing specific functions not available in standardized charge pump ICs. The surplus circuitry in [GreenPAK](#), unused in a charge pump circuit, can be utilized in those applications to implement such specific functions. Specific functions could be directly or closely related to charge pump function but may just as easily be completely independent hardware functions of the target device.

This application note does not cover all performance ranges of capacitive charge pumps, but the [GreenPAK](#) ecosystem offers the right solution to cover all of them with appropriate design.

Regulated Capacitive Charge Pump with Programmable Output and Powerdown using GreenPAK

Revision History

Revision	Date	Description
1.0	16-Nov-2018	Initial Version

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD-PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers who are designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only to develop an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third-party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising from your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.01 Jan 2024)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit www.renesas.com/contact-us/.

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.