

Development of a Voltage Feedback Spice Op-Amp Macromodel

Introduction

A voltage-feedback amplifier macromodel has been developed that simulates the most common effects, such as transient response, frequency response, voltage noise and input/output slew rate limiting. Detailed descriptions of each stage in the model will be presented with examples of model performance and correlation to actual device behavior.

Macromodels are developed for the customer instead of releasing full transistor schematics. Of course, the most accurate simulations are conducted from fully-extracted 3-D device models. Not only would it be impractical to share these models because of the need to accommodate the numerous simulation platforms, but also because of proprietary reasons.

One of the first op-amp macromodel techniques was developed by Boyle in 1974 and used only two transistors, a few diodes and linear elements [1]. Linear elements like resistors, capacitors, inductor and voltage/current control sources simulate much faster than active elements and are used to provide poles, zeros and any gain. For a DC model, a voltage-controlled voltage source can represent the amplifier while resistances can be added to better represent the input and output impedance. Capacitors, inductors, diodes and transistors can then provide the proper AC response. If you want more information on the development of simulation models, see Alexander and Bowers [2] and [3]. We will follow their model here.

The ISL28133

As an example, we are going to investigate the ISL28133. The ISL28133 is a zero-drift operational amplifier with voltage feedback topology. Intended for low frequency and power precision applications, the gain bandwidth product is 400kHz, the slew rate is 0.1V/ μ s, and the supply current is 18 μ A. A five-stage model represents the actual circuit, the block diagram for which is shown in Figure 1. The five stages are the input stage, the gain stage, the frequency-shaping stage, the output stage, and the noise module.

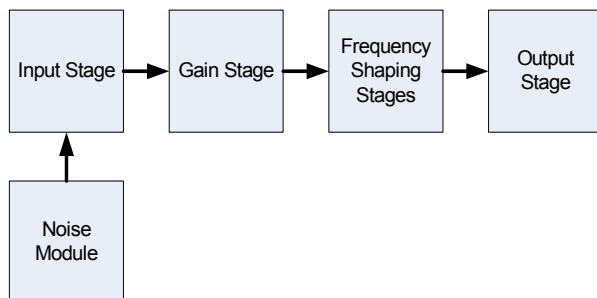


FIGURE 1. ISL28133 MACROMODEL BLOCK DIAGRAM

The Input Stage

The input stage of the zero-drift amplifier is shown in Figure 2. The $100\mu\text{A}$ current source 'I2' feeds the PMOS input pair. Normally, I2 should be chosen less than the quiescent current. Remember, the ISL28133's typical supply current ($R_L = \text{open}$) is only $18\mu\text{A}$. However, a small I2 ($\sim 10\mu\text{A}$) would make the input voltage noise too large to emulate. This will be discussed later in the noise analysis section of this document. Choose $I2 = 100\mu\text{A}$ and use I1 to compensate back to the total quiescent current. C_{in1} and C_{in2} are the input common mode capacitance and C_{diff} is the input differential mode capacitance.

 


FIGURE 2. INPUT STAGE

The Gain Stage (Figure 3)

This stage performs several important functions in the model:

1. This stage sets the DC gain of the part. All the subsequent stages provide unity DC gain.
2. It provides slew rate limiting.
3. It adds the dominant pole to the AC characteristic.
4. It level shifts the signal from two voltages referred to the supplies to a single voltage referred to the mid-point.
5. It limits the full scale output swing.

 


FIGURE 3. GAIN STAGE

Referring to Figure 3, G_a is the gain of block G1 and G2. G_b is the gain of block G3 and G4.

$$SlewRate = \frac{I2 \cdot R3 \cdot G_a \cdot R5 \cdot G_b}{C1} \quad (EQ. 1)$$

Changing the value of V3 and V4 limits the slew rate. Also, R8/C1 and R7/C2 decide the dominant pole of this model. E1 is used to set the reference level at the middle of Vcc and Vee.

Frequency-Shaping Stages

The "telescopic" frequency shaping techniques used here are very common in op-amp modeling. It is easy to add more poles and zeros. Each frequency-shaping block provides unity gain. A zero-pole pair is included in this model and shown in Figure 4.

$$R10 = R11 = 1M\Omega \quad (EQ. 2)$$

$$R9 = R12 = R10 \cdot \left(\frac{f_p}{f_z} - 1 \right) \quad (EQ. 3)$$

$$L1 = L2 = \frac{R9}{2\pi f_p} \quad (EQ. 4)$$

A higher order pole stage is shown in Figure 5, G7/8, R13/14 and C3/4.

 


FIGURE 4. ZERO-POLE PAIR STAGE

 


FIGURE 5. HIGHER ORDER POLE STAGE

Noise Simulation

The ISL28133 input current noise is very small (~70fA), so it is neglected in this model. The voltage noise of the MOSFET can be modeled using the following equations.

$$V_i^2(f) = 4kT \left(\frac{2}{3} \right) \frac{1}{g_m} + \frac{K}{WLC_{ox} f} \quad (\text{EQ. 5})$$

$$g_m \propto \sqrt{I_D} \quad (\text{EQ. 6})$$

I_D is the drain current. High bias current in the model is needed to emulate the low voltage noise. At the input stage, the tail current is set high enough to generate the low input voltage noise. Before the noise sources are added, the model has to be rendered lower noise than the spec or typical performance noise curve in the [ISL28133 datasheet](#). The noise-voltage module of Figure 6 generates 1/f and white noise by using a 0.1V voltage source biasing a diode-resistor series combination. White noise is generated by the thermal noise-current.

$$i_n^2 = \frac{4kT}{R} \quad (\text{EQ. 7})$$

where k is the Boltzmann's constant. So, the required value of the resistor for a given noise-voltage spectral density is:

$$R = \frac{e_n^2}{2 \times 4kT} \quad (\text{EQ. 8})$$

where e_n is the spectral density of the white noise voltage. The design of the chopper stabilized amplifier greatly reduces 1/f noise. 1/f noise (flicker noise) refers to the noise exhibiting power spectral density inversely proportional to the frequency.

More generally, the noise with the spectral density

$$S_N \propto \frac{1}{|f|^\beta} \quad \beta > 0 \quad (\text{EQ. 9})$$

is also called 1/f noise. Normally, the frequency where the flicker noise curve crosses the white noise curve is defined as the corner frequency. The small amount of flicker noise that remains is modeled within the SPICE diode model. Referring to Figure 6,

$$i_n^2 = 2qI_d + KF \cdot \frac{I_d^{AF}}{\text{frequency}} \quad (\text{EQ. 10})$$

I_d is the DC diode current. AF and KF are the model parameters of the SPICE diode and q is the charge of the electron. The flicker noise exponent (AF) is set to 1 and the flicker noise coefficient (KF) is set

$$KF = \frac{E_a^2}{2R^2 \cdot I_d} \quad (\text{EQ. 11})$$

where E_a is the noise-voltage spectral density at 1Hz. The simulated voltage noise will show the 1/f noise-voltage spectral density with the correct corner frequency.

 


FIGURE 6. NOISE VOLTAGE MODULE

Output Stage

After the frequency shaping-stages, the signal appears at Node VV5, which is referenced to the midpoint of two supply rails. Each controlled source can generate enough current to support the desired voltage drop across its paralleled resistor. R15 and R16 are equal to twice of the open loop output resistance, so their parallel combination gives the correct Z_{out} . D5-D8 and G9/10 are used to force a current from the positive rail to the negative rail to correct the real current sink or source in the supply pins.

$$G9 = G10 = G11 = G12 = \frac{1}{2Z_{out}} \quad (\text{EQ. 12})$$

$$R15 = R16 = 2Z_{out} \quad (\text{EQ. 13})$$

 


FIGURE 7. OUTPUT STAGE

Simulation Results

Some SPICE simulation results are compared with the typical performance curve from the [ISL28133 datasheet](#) in the following. (Figure 8b is from the datasheet).

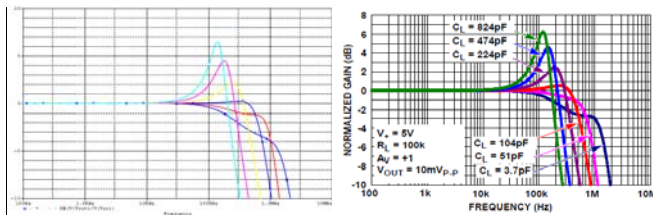


FIGURE 8. GAIN vs FREQUENCY vs LOAD CAPACITANCE. IT CANNOT BE VERY ACCURATE BECAUSE THE PARASITIC CAPACITANCE ON THE BOARD WASN'T INCLUDED IN THE MODEL. THE ERROR IS LESS THAN 5%

 


FIGURE 9. FREQUENCY RESPONSE OF CLOSED LOOP GAIN WITH DIFFERENT GAIN. AT GAIN = 100, THE BANDWIDTH IS 3.94kHz AND THE ERROR IS LESS THAN 5%. AT LOW GAIN, THE BANDWIDTH IS EXPANDED BECAUSE OF THE ZERO POLE PAIR

 


FIGURE 10. LARGE SIGNAL STEP RESPONSE. THE SLEW RATE SIMULATED IS 0.198V/μs AND THE ERROR IS 1%

 


FIGURE 11. INPUT NOISE VOLTAGE vs FREQUENCY. AT 1kHz, THE SIMULATED INPUT NOISE VOLTAGE IS 64.9 nV/Hz, VERY CLOSE TO THE VALUE IN THE DATASHEET 65nV/Hz. THE SIMULATED CURVE CANNOT CATCH THE PEAK NEAR 10kHz

Conclusion

A truly comprehensive SPICE macromodel for a voltage feedback amplifier is developed. This macromodel includes effects such as transfer response, accurate AC response, DC offset and voltage noise. It is easy to add more features like CMRR, PSRR, input current-noise, etc. Also it is convenient to change the parameters of the model to fit other voltage feedback amplifiers. Actually, several of Intersil's voltage feedback amplifiers use the same model topology.

ISL28133 Macromodel Netlist

* ISL28133 Macromodel

* Revision B, July 2009 by Jian Wang

* This model simulates AC characteristics, Voltage Noise, Transient Response

* Connections: +input -input +Vsupply -Vsupply Vout

.subckt ISL28133 3 2 7 4 6

*Input Stage

C_Cin1 8 0 1.12p

C_Cin2 2 0 1.12p

C_Cd 8 2 1.6p

R_R1 9 10 10

R_R2 10 11 10

R_R3 4 12 100

R_R4 4 13 100

M_M1 12 8 9 9 pmosil

+ L=50u

```

+ W=50u
M_M2 13 2 11 11 pmosisil
+ L=50u
+ W=50u
I_I1 4 7 DC 92uA
I_I2 7 10 DC 100uA
*Gain stage
G_G1 4 VV2 13 12 0.0002
G_G2 7 VV2 13 12 0.0002
R_R5 4 VV2 1.3Meg
R_R6 VV2 7 1.3Meg
D_D1 4 14 DX
D_D2 15 7 DX
V_V3 VV2 14 0.7Vdc
V_V4 15 VV2 0.7Vdc
*SR limit first pole
G_G3 4 VV3 VV2 16 1
G_G4 7 VV3 VV2 16 1
R_R7 4 VV3 1meg
R_R8 VV3 7 1meg
C_C1 VV3 7 12u
C_C2 4 VV3 12u
D_D3 4 17 DX
D_D4 18 7 DX
V_V5 VV3 17 0.7Vdc
V_V6 18 VV3 0.7Vdc
*Zero/Pole
E_E1 16 4 7 4 0.5
G_G5 4 VV4 VV3 16 0.000001
G_G6 7 VV4 VV3 16 0.000001
L_L1 20 7 0.3H
R_R12 20 7 2.5meg
R_R11 VV4 20 1meg
L_L2 4 19 0.3H
R_R9 4 19 2.5meg
R_R10 19 VV4 1meg
*Pole
G_G7 4 VV5 VV4 16 0.000001
G_G8 7 VV5 VV4 16 0.000001
C_C3 VV5 7 0.12p
C_C4 4 VV5 0.12p
R_R13 4 VV5 1meg
R_R14 VV5 7 1meg
*Output Stage
G_G9 21 4 6 VV5 0.0000125
G_G10 22 4 VV5 6 0.0000125
D_D5 4 21 DY
D_D6 4 22 DY
D_D7 7 21 DX
D_D8 7 22 DX
R_R15 4 6 8k
R_R16 6 7 8k
G_G11 6 4 VV5 4 -0.000125
G_G12 7 6 7 VV5 -0.000125
*Voltage Noise
D_DN1 102 101 DN
D_DN2 104 103 DN
R_R21 0 101 120k
R_R22 0 103 120k
E_EN 8 3 101 103 1
V_V15 102 0 0.1Vdc
V_V16 104 0 0.1Vdc
.model pmosisil pmos (kp=16e-3 vto=10m)
.model DN D(KF=6.4E-16 AF=1)
.MODEL DX D(IS=1E-18 Rs=1)
.MODEL DY D(IS=1E-15 BV=50 Rs=1)
.ends ISL28133

```

References

- [1] BOYLE, G.R., "Macromodeling of integrated circuit operational amplifiers", IEEE J. 1974, SC-9.
- [2] Derek Bowers, Mark Alexander, Joe Buxton, "A Comprehensive Simulation Macromodels for 'Current Feedback' Operational Amplifiers," IEEE Proceedings, Vol. 137, April 1990 pp.137-145
- [3] Mark Alexander, Derek Bowers, "AN-138 SPICE-Compatible Op Amp Macro-Models", Analog Devices Inc., Application Note 138.
- [4] "AN-840 Development of an Extensive SPICE Macromodel for 'Current-Feedback' Amplifiers", National Semiconductor Corp., Application Note 840.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338