

## White Paper

# Comparing the Benefits of Using an Integrated Power Module versus a Discrete Regulator

## Introduction


Today's power systems for communications and computing infrastructure support high current loads from increasingly power hungry FPGAs, ASICs and microprocessors. To supply these high current circuits, equipment makers often rely on discrete power solutions that are complicated, take up valuable real-estate and may have significant power output limitations.

Step-down (buck) regulators are used to convert power from a distributed power bus to the individual point-of-loads (POLs) in infrastructure systems. Step-down converters convert a voltage from an input source to a lower output voltage and are capable of converting a voltage source (typically 5V to 25V or higher) into a lower regulated voltage (typically 0.5V to 5V). More recent infrastructure systems may utilize 20-40 point-of-load (step-down) converters in one system, each with different output voltage and output current needs, creating a challenge for system power supply design engineers.

To meet the challenge of designing the power sub-system for these systems, many designers are considering using power modules instead of traditional discrete POL designs, with time to market, size constraints, reliability and design capabilities being motivating factors. In this paper, we will compare the benefits of using an integrated power module vs. a discrete step-down switching regulator.

## Design of a Discrete Non-Isolated Step-Down Regulator

The building blocks of a non-isolated switching power supply are shown in Figure 1.

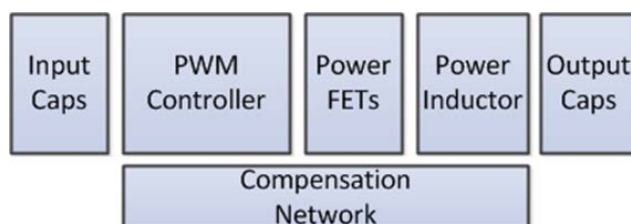

**Figure 1: Discrete Power Supply Block Diagram**

A discrete power supply requires a number of external components to build: a PWM controller, switching power MOSFETs, input capacitors, output capacitors and a power inductor. All of these components vary for each design. For example, if a system has 20 different power supply rails, the selection of these components must be done for each design, which makes the job of designing a power sub-system very challenging.

Let's look at an example of a non-isolated buck regulator. All of the components for the non-isolated buck regulator design in Figure 2 should be carefully selected to meet the design requirements.

Calculating the inductor value is most critical in designing a step-down switching converter. First, assume the converter is in continuous conduction mode (CCM), which is usually the case. CCM implies that the inductor

does not fully discharge during the switch-off time. Peak current through the inductor determines the inductor's required saturation-current rating, which in turn dictates the approximate size of the inductor. Saturating the inductor core decreases the converter efficiency, while increasing the temperatures of the inductor, the MOSFET and the diode.

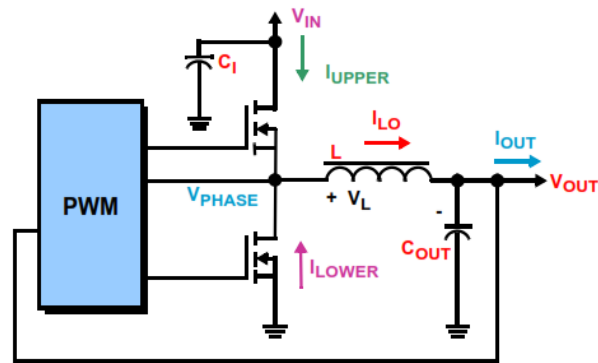


Figure 2: Basics of a Synchronous Buck Converter

The output capacitor selection is also a critical part of the design. The output capacitance determines the load transient performance of the power supply. Output capacitance is required to minimize the voltage overshoot and ripple present at the output of a step-down converter. Poor load transient performance or instability is caused by insufficient output capacitance, and large voltage ripple is caused by insufficient capacitance as well as a high equivalent-series resistance (ESR) in the output capacitor. The maximum allowed output voltage overshoot and ripple are usually specified at the time of design. Thus, to meet the ripple specification for a step-down converter circuit, you must include an output capacitor with ample capacitance and low ESR.

The input capacitor is used to suppress noise at the input of the power supply and reduce the ripple voltage seen at the input. Load current, duty cycle and switching frequency are some of the factors used to determine the magnitude of the input ripple voltage. Ceramic capacitors placed directly at the input of the regulator reduce ripple voltage amplitude. Only ceramics have the extremely low ESR that is needed to reduce the ripple voltage amplitude. These capacitors must be placed close to the regulator input pins to be effective.

Careful selection of the upper and lower MOSFETs will determine the overall efficiency of the buck converter. The on-resistance of the power MOSFETs and switching losses will affect the overall efficiency. The compensation components must be selected to ensure that the design meet the stability criteria over the required operating conditions. Placement of the external components can also affect the performance of the power supply. Designers must use an optimal layout to minimize noise and maximize system efficiency.


This entire process must be repeated for each power rail. If there are 20 point-of-load power rails in the system, the process must be repeated 20 times, which can quickly become a daunting task for a power sub-system designer.

## Use of a Power Module

System designers will make tradeoffs between cost, design effort and performance when selecting a power module. For systems with 1-5 power rails, designers may opt to use a discrete regulator to save cost and meet the time to market schedule. However, as the number of power rails increases and the current rating increases, the design of the power sub-system becomes challenging and requires significantly more design

effort. To meet this challenge, designers may opt to use a power module solution. Designers will also consider the cost of ownership of a discrete design. The cost of ownership is the bill of materials (BOM) cost in addition to the power designer’s time required to design and test the design. Potential re-design changes, manufacturing and assembly costs are additional expenses for discrete designs.


Figure 3 shows how a power module can integrate many of the blocks of the discrete design shown in Figure 1. A power module integrates the PWM controller, power MOSFETs, inductor and compensation network into the package. The designer typically only needs to select the input and output capacitors to complete a design.

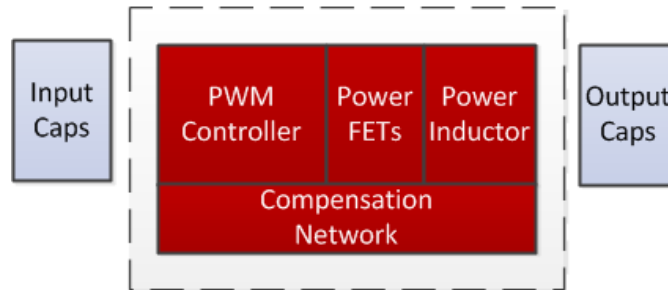

**Figure 3: Power Module Implementation**

Intersil offers a comprehensive portfolio of digital and analog point-of-load power modules to address the needs of infrastructure systems. Intersil power modules are complete DC/DC power sub-systems as shown in Figure 3. With industry-leading power technology, these modules reduce design time, lower cost and save board space. Intersil’s optimized thermal packaging technology provides excellent thermal performance, providing high current operation and high power density without the need for an external heat sink or fan, reducing system cost.

Figure 4 shows the ISL8216M, Intersil’s first high voltage power module. The ISL8216M supports a wide 10V to 80V input voltage range with an adjustable 2.5V to 30V output range, and delivers 4A of output current. The ISL8216M is an ideal choice for systems with a 12V, 24V, 36V or 48V input rail, making it well suited for infrastructure and industrial systems.

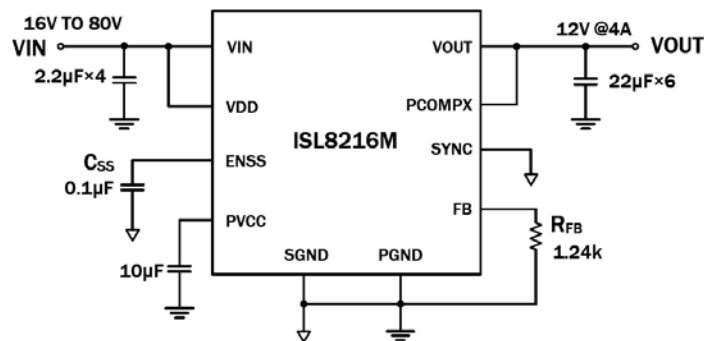

**Figure 4: ISL8216M Application Circuit**

Intersil offers two pin-to-pin compatible step-down power modules for maximum design flexibility. The popular ISL8225M dual 15A/single 30A step-down power module delivers up to 100W output power from a tiny 17mm x 17mm thermally enhanced QFN package. The two 15A outputs may be used independently or combined to deliver a 30A output.

If you need high voltage or more headroom, you can move to the ISL8240M dual 20A/single 40A step-down power module, which is well suited for power hungry ASIC, FPGA and microprocessor loads in infrastructure systems. Current sharing and phase interleaving allow up to 6 modules to be paralleled for up to 240A of current. Both power modules offer excellent efficiency and low thermal resistance to permit full power operation without heat sinks or fans.

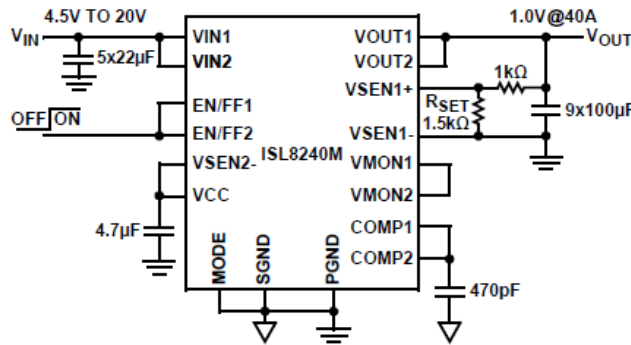


Figure 5. ISL8240M Single 1V/40A Output Application Diagram

## Conclusion

The initial cost of implementing a discrete design may be cheaper than using a power module, but when considering time to market and long-term engineering and maintenance costs, a power module shows significant advantages, particularly for systems with 10 or more power rails. The cost of ownership, reduced design complexity, and a simplified and more flexible PCB layout are all important factors to consider. Intersil offers a rich portfolio of digital and analog power modules to address the wide input voltage range and load current range of infrastructure systems.

## Next Steps

- [Learn more about Renesas' power module solutions](#)
- [Generate a board-level power module design with iSim](#)
- [Search for power module parts using our parametric search](#)

###

© 2018 Renesas Electronics America Inc. (REA). All rights reserved. All trademarks and trade names are those of their respective owners. REA believes the information herein was accurate when given but assumes no risk as to its quality or use. All information is provided as-is without warranties of any kind, whether express, implied, statutory, or arising from course of dealing, usage, or trade practice, including without limitation as to merchantability, fitness for a particular purpose, or non-infringement. REA shall not be liable for any direct, indirect, special, consequential, incidental, or other damages whatsoever, arising from use of or reliance on the information herein, even if advised of the possibility of such damages. REA reserves the right, without notice, to discontinue products or make changes to the design or specifications of its products or other information herein. All contents are protected by U.S. and international copyright laws. Except as specifically permitted herein, no portion of this material may be reproduced in any form, or by any means, without prior written permission from Renesas Electronics America Inc. Visitors or users are not permitted to modify, distribute, publish, transmit or create derivative works of any of this material for any public or commercial purposes.

