

There are several ways to recover the common mode voltage (CMV) range of video sent from the EL4543 which has 2.5V of offset that uses most of the input CMV range of the receiver amp.

- The first way is to use AC cap coupling at the receiver, but this will lose the DC ref level for the RGB that normally has the back porch at ground. Some displays require back porch at or near ground. A DC restore can be added but it will increase cost. AC coupling can also cause droop on each horizontal line. Video YPbPr are bipolar signals and are often AC coupled, then normally DC restored in the displays. AC coupling is well known and will not be discussed in this application note.
- The second way is to use an offsetting resistor network at the receiver. This retains the DC ref level of the video with back porch near ground with only small DC offsets and no droop. The network will have some gain loss, about 30%, so the receiver has to have more gain to recover for the loss. Yet, this added gain may cause a small reduction in the maximum usable cable length, up to 5% less.

The EL4543 solves the problem of sending RGB video plus HSYNC and VSYNC down three twisted pairs of a CAT-5 cable. The RGB video is sent differentially on three twisted pairs with the HSYNC and VSYNC is encoded as differential common mode on the RGB pairs. The sync data, which is encoded on the RGB pairs, will manifest itself as a CMV on each pair. The EL4543, when used with a $\pm 5V$ supply, will have a sync data CMV (common mode voltage) offset of $\pm 0.5V$.

Yet, a typical configuration for the EL4543 is a single 5V supply operation. The single supply output has a positive DC offset of about mid supply or 2.5V with no signal applied. The problem manifests itself at the receiver when using a dual supply receiver, such as the EL9110 or EL9111, each having a wide CMV range of 7.5V. The EL4543 directly driving a cable to the EL9110 or EL9111 input, will have a positive DC offset from the EL4543. This will limit the operational common mode range for video transmission.

This document addresses the CMV problem and offers a solution to balance the EL4543 CMV output signal to take full advantage of the wide input CMV range of the EL9110 or EL9111. We will also discuss simple circuits for:

- LF and HF noise rejection,
- HSYNC jitter caused by CAT-5 cable delay difference, and
- A unique solution for circuit instability.

Even though this document discusses the CMV, LF and HF noise, HSYNC jitter, and other issues using the EL4543 and EL9110 or EL9111 for video transmission, the information in

this document is applicable to any video transmission down cables.

CMV Range Computation

EL4543 – the typical output CMV for the single supply EL4543 includes the HSYNC or VSYNC data along with a DC offset. Single supply operation will offset the output to half the supply voltage range, 2.5V on a 5V supply. Embedding sync, we add $\pm 0.5V$ on this mid point. Therefore the CMV would be:

$$+CMV = 2.5V + 0.5V = +3V$$

$$-CMV = 2.5V - 0.5V = +2V$$

The EL4543 CMV, while driving a CAT-5 wire pair differentially, will be 2V to 3V above ground.

Details of the EL4543 Non-Symmetrical Impact on the EL9111

EL9110 or EL9111 — the CMV range is specified in the data sheet 'CMIR' from -4V to +3.5V. The usable CMV is the input CMV range minus the input signal. The input signal equals Video plus sync.

A typical video example to look at is the white RGB components. Red is by far the predominate color in white. In this case, red is about 60% of full scale or about $400mV_{p-p}$. The transmitted signal common mode voltage (EL4543), as before, would be 2V to 3V. Now, adding in the Video input and sync, the range would be the lower -CMV minus the video and the upper range would be +CMV plus the video or:

$$\text{Signal min} = 2V - 0.4V = 1.6V$$

$$\text{Signal max} = 3V + 0.4V = 3.4V$$

Since the EL9110 or EL9111 upper input CMV range is 3.5V, the CMV offset limits the input range of the EL9110 or EL9111 to about 100mV. Thus, the non-symmetrical output of the EL4543 could cause distortion at the output of the EL9110 or EL9111 if the CMV overhead of the video input is just a few 100mV. So, the issue is how to balance the 2.5V CMV offset so we can recover the usable CMV range of the EL9111.

Goals of this design are to:

1. Terminate the CAT-5 cable properly and improve HF noise rejection. See "Terminate the CAT-5 Cable" on page 2 and "Reduce the HF Common Mode Components" on page 2.
2. Balance the cable driver offsets and improve the CMV symmetry. See "Balance the CMV Cable Offsets" on page 2.

3. Reduce LF CMV noise due to long cable lengths. See "Minimize DC Loading and Reduce CMV Noise" on page 2.

Balance the Cable Driver Offset/ Recovering Usable CMV Range

The single supply EL4543 offset CMV range can be corrected by using a simple resistor network after the cable termination to offset the CMV at the cable output to level shift CMV towards ground. Offsetting the input by about -2.5V will recover the usable CMV range at the EL9110 or EL9111 receiver input.

Terminate the CAT-5 Cable

A cable input termination network is needed to properly terminate the CAT-5. This can be accomplished with two resistors, 51Ω in series across each twisted pair output (see Figure 1).

Reduce the HF Common Mode Components

The two 51Ω terminating resistors junction point has a third 51Ω resistor connected that is in series with a large capacitor to ground (0.1μF) (see Figure 1). Thus, supplying a path for cable HF common mode termination and the two series 51Ω terminates the differential pairs. The two series 51Ω match the 100Ω of the CAT-5 cable. The series RC network provides both the differential common mode termination and HF path to ground for HF rejection.

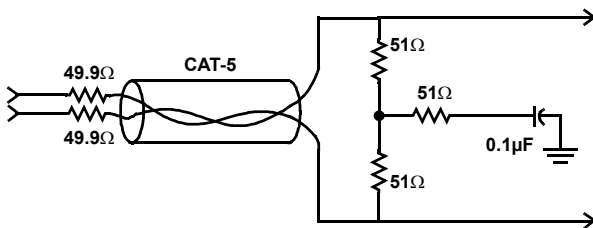


FIGURE 1. TERMINATING CAT-5 CABLE

Balance the CMV Cable Offsets

The incoming signal is offset by about +2.5V. Using a simple voltage divider to pull down the incoming signal by the same amount as the offset and thus, the input signal CMV would be about ground. You need to consider a few restrictions when selecting the resistor divider values:

- The divider should minimize the DC loading of the EL4543.
- The divider must not attenuate the signal below the useful range of the receiver.

The offset circuit consists of two matched/balanced circuits. We will discuss one half of the circuit as it is applicable to the other side as well. Let's start with the key problem, recovering the usable CMV range of the EL9111.

Minimize DC Loading and Reduce CMV Noise

A simple series 1:2 voltage divider to a negative supply would pull down the EL4543 offset on each leg to about 0V. One limit is to keep the divide impedance high enough not to draw too much DC current from the EL4543 outputs.

Series 1k with a 2k tied to -5V would bias the junction to a level removing the input offset as shown in Figure 2. The series 3k, on parallel with the 51Ω input, changes the input impedance seen by the EL4543 by less than 2%. Yet, the EL9110 or EL9111 CMV is non-symmetrical; its mid point is -0.25V below ground. To gain back an additional 0.25mV, we need to adjust the circuit. The circuit shown in Figure 2 reflects this adjustment, the 1.05k resistor series to a 2k resistor to -5V. The series circuit is 49.9Ω source resistance from the cable source, the 1.05k, and the 2k to -5V. The overall offset at the junction will result in CMV at input to the EL9110 or EL9111 to be -0.25V, and not 0V. The EL4543 CMV offset is -2.5V. Adding -0.25V plus the original adjustment, -2.5V, the circuit compensates for the total asymmetry.

We selected -5V supply for termination because the EL9110 or EL9111 requires ±5V supply and it was readily available. Not only does this network balance the CMV DC offset, it also supplies the DC termination for low frequency rejection.

The circuit does not impact the DC loading of the EL4543, as it appears as about 1.5k impedance to the cable. That, in parallel with the 51Ω, results in a termination which appears as 49.4Ω per line. Thus, this circuit will improve the CMV symmetry and reduce LF CMV noise due to long cable.

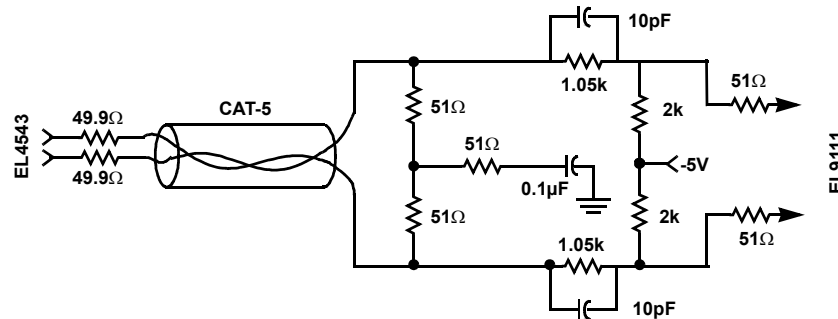


FIGURE 2. CMV OFFSET CORRECTION AND HF/LF REJECTION

Attenuating the Input Signal

The circuit does attenuate the signal by 33% (1k:2k). Yet, the EL9110 or EL9111 can cleanly reproduce the video signal of these levels using the adjustable internal gain.

Why the added 51Ω at input to the EL9110 or EL9111?

EL9110 or EL9111 gain is 1k at 100MHz at the maximum comp level. At this frequency range, the network may look like a resonance circuit. If you have feedback as little as 1/1000th of the output, the circuit may become unstable. The simplest way of lowering the 'Q' of the resonant circuit is to place the two 51Ω in series at the input to the EL9110 or EL9111 as shown in Figure 2. Thus, you will have dampened the feedback and improved the stability. This also increases ESD protection.

10pF Cable Comp

The 1.05k resistors in series from the cable pair lines to the amp inputs have 10pF caps in parallel to prevent excessive high frequency loss or color phase shift resulting in moray fringes.

The 10pF cap also helps prevent increased noise with long cables. It generates about 3.6dB peaking (33% voltage loss)

that will compensate about 75 feet cables and, with short cables, the peaking effect is small enough not to impact the signal quality.

CMV Input Range

The input offset network will offset the input CMV to the EL9110 or EL9111 by -2.75V. It will also attenuate the CMV $\pm 0.5V$ sync data to $\pm 0.32V$ and the video signal from $\pm 0.4V$ to $\pm 0.26V$ so the total input signal range is -0.83V to 0.33V. The EL9110 or EL9111 CMV range is $\pm 3.17V$. The CMV plus input signal is -4V to +3.5V and matches the EL9110's or EL9111's input amp CMV range.

ESD Protection

Long cables are subject to ESD so basic protection should be used, and under bad conductions, added protection may be needed. Basic ESD protection uses logic diodes reverse connected from the supplies to the input of the 51Ω resistor in series with the receiver amp input pin. The 51Ω are located very close to the amp input pin. This will give increased ESD protection and more stable EL9110 amps at very high cable comp levels.

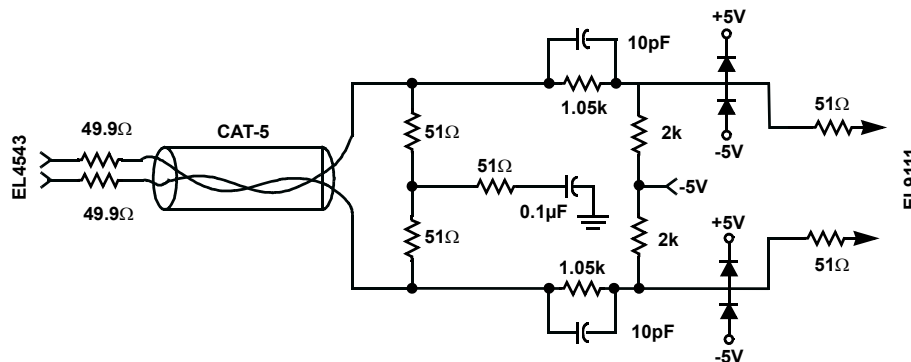


FIGURE 3. ESD PROTECTION DIODES

Sync Decode

The EL9110 or EL9111 can use the configuration in Figure 4 at their input to offset the CMV from the EL4543. They detect the CMV for HSYNC and VSYNC and are decoded in the EL9111.

Correcting for HSYNC Jitter

What is the cause of HSYNC Jitter? The HSYNC is transmitted differentially down the CAT-5 cable using three twisted wire pairs:

- RED twisted wire pairs carry Red video and -HSYNC and +VSYNC
- BLUE twisted wire pairs carry Blue video, +HSYNC inverted and +VSYNC
- GREEN twisted wire pairs carry Green video and -VSYNC inverted.

The CAT-5 cable twisted wire pairs have different twist rates resulting in up to 30nS difference between them at the receiver. The HSYNC uses the Red wire pair and HSYNC inverted is on the Blue wire pair. The HSYNC differential comparator (EL8101 seen on page 15 of the EL4543 data sheet, FN7325) could receive the HSYNC and HSYNC inverted such that both signals are at 0V for up to 30ns at the same time. The HSYNC recovery circuit could induce HSYNC jitter as the diff-comparator attempts to determine which of the HSYNCs is more positive. A simple 30mV offset imposed on one of the HSYNC differential inputs eliminates the HSYNC jitter.

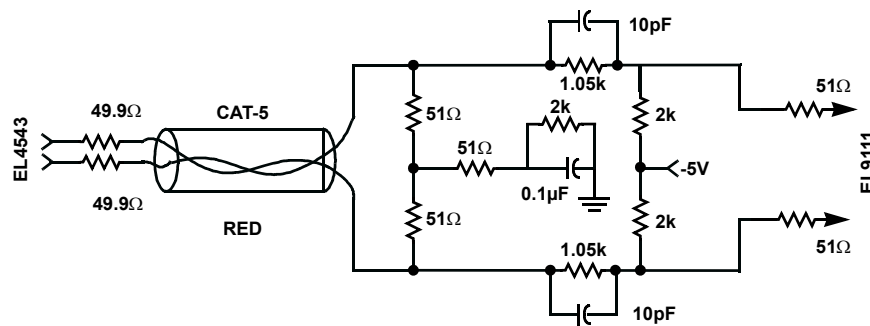


FIGURE 4. HSYNC JITTER COMPENSATION

We use the Red CMV termination circuit to add the 30mV DC offset. The input to the CMV circuit is 25 Ω (the two 51 Ω in parallel) through a 51 Ω resistor to the 0.1 μ F cap. We need 1.2mA through this 25 Ω equivalent resistor to generate the 30mV offset. Since the input is 2.5V (no video), we can place a

resistor in parallel with the 0.1 μ F cap to ground for the DC path. Computing the resistor, 1.2mA through a resistor dropping 2.47V to ground would require 2k Ω . This will prevent HSYNC jitter caused by the cable skew between twisted pair.

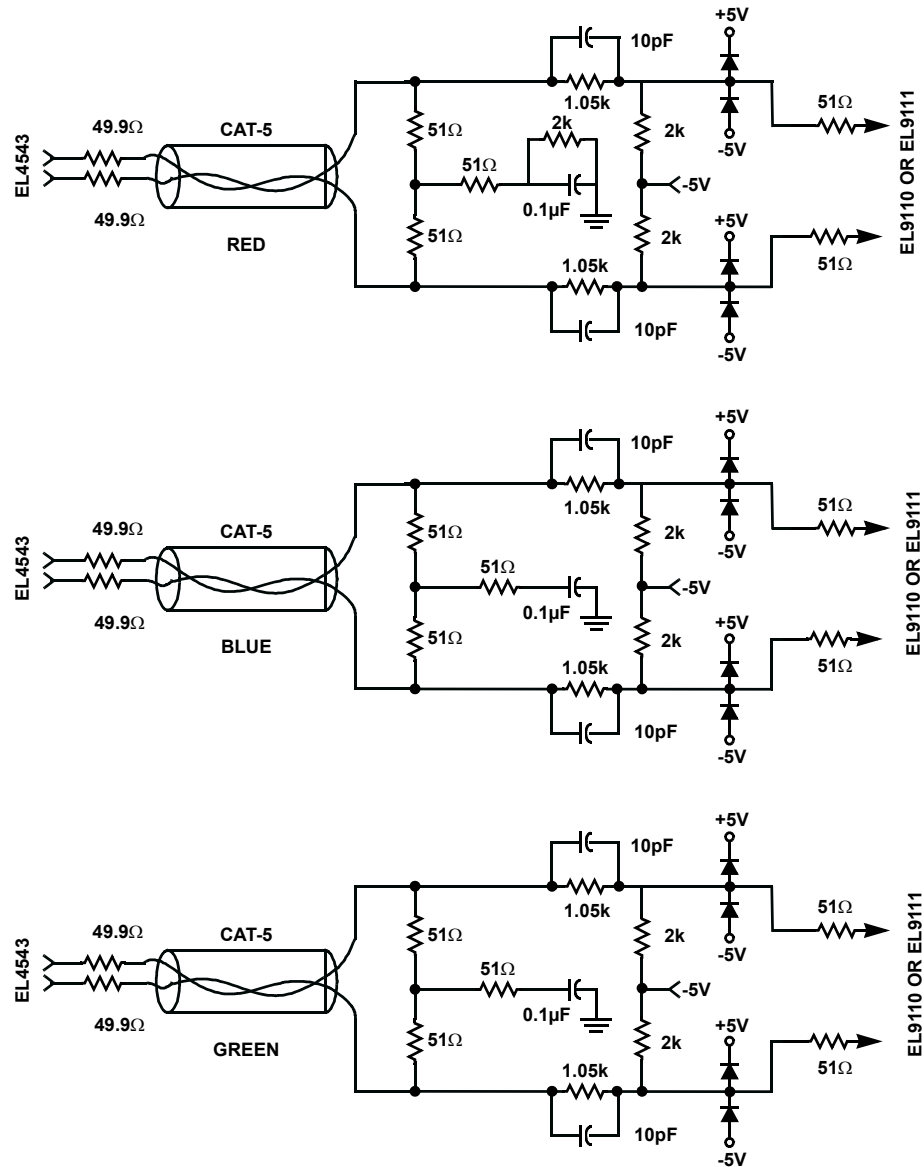


FIGURE 5. FINAL RGB BALANCE NETWORKS

Attenuation Correction

The Input offset network reduces the input video by 33.3%. To compensate for the loss, the receiver amp should have an additional gain of 1.5. The EL9110 or EL9111 has gain controls to add 1.5 gain.

Figure 6 is the implementation of the CMV restore circuit for a typical cable driver/receiver application circuit. Refer to the

EL4543 data sheet, FN7325, page 15. Instead of using the EL9110 or EL9111, this circuit uses the EL5375. The EL8201 is the HSYNC recovery differential comparator circuit.

EL5375 Gain recovers the 33% loss: The EL5375 2k fixed gain resistors are replaced with 1k resistors. This changes the gain from $A = 2$ to $A = 3$, compensating for input offset circuit loss.

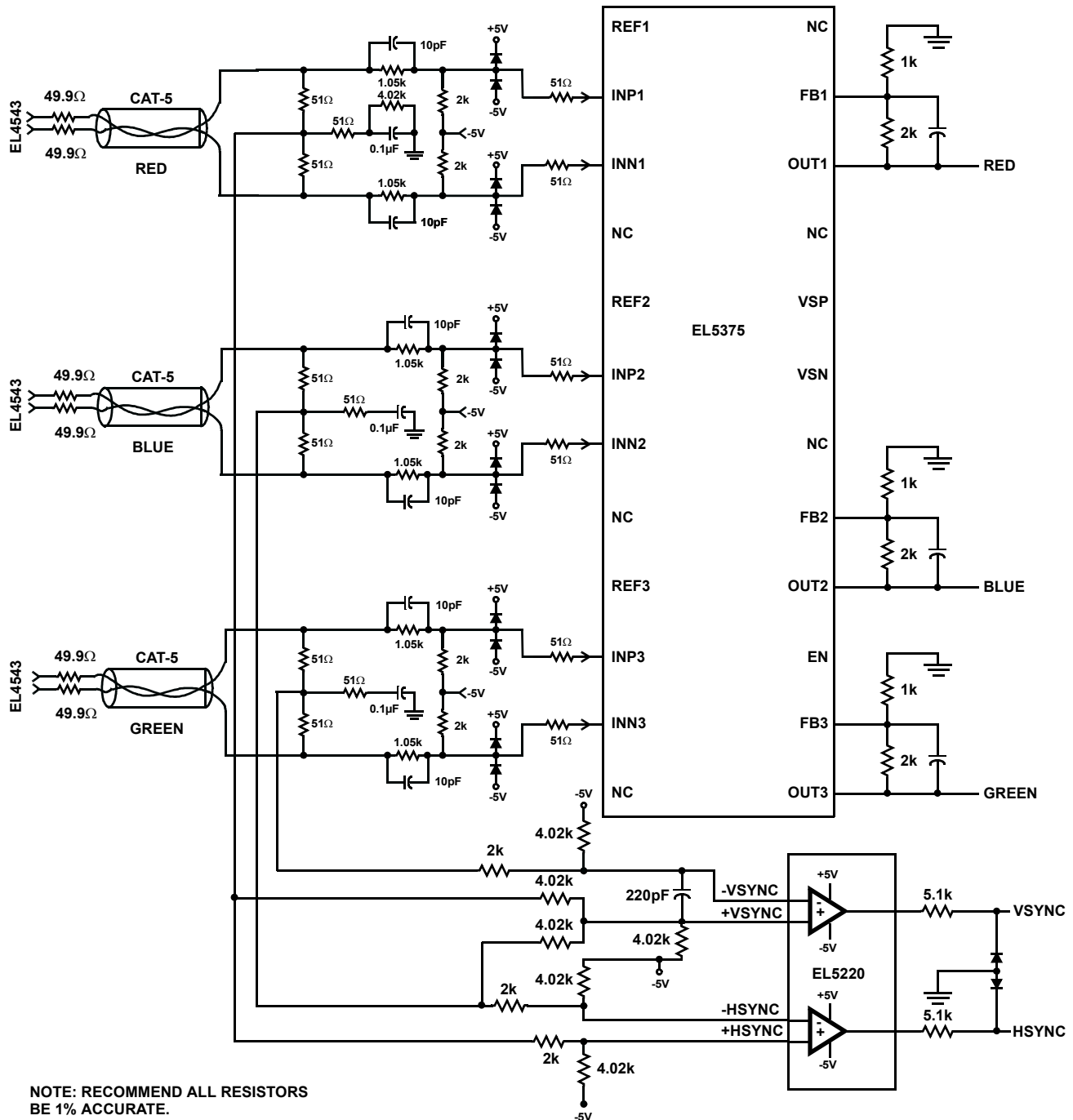


FIGURE 6. SOLUTION USING THE EL5375

Cross Talk Attenuation

The CAT-5 cable will have cross talk when transmitting digital data. A longer cable will have more cross talk. The HSYNC and VSYNC signals are basically a digital signal with fast rise and fall times causing cross talk in the CAT-5 cable. The HSYNC cross talk will appear as digital noise to the other pairs. The HSYNC is in sync with the video signal so the noise is always in a blanked part of the video signal and will not be seen on the display. The HSYNC also couples in to the VSYNC cable pairs and causes false HSYNC spikes on the VSYNC decoded data output. This will appear as failure to VSYNC. The VSYNC noise can be suppressed using a 220pF cap across the VSYNC comparator amp input to filter out the HSYNC noise spikes.

Summary

Single supply drivers interfacing into dual supply receivers may have limited CMV range due to CMV offset. Using simple balanced resistor networks, you can recover the full CMV range of the receiver. At the same time, using a few capacitors, you can improve the HF and LF rejection. We introduced two subtle issues to consider and their solutions:

- HSYNC Jitter — solved by offsetting one of the HSYNC differential signals by more than the detector's input offset voltage.
- Circuit Instability — solved by adding two 51 Ω dampening resistors at the input to the differential receiver to reduce the 'Q' of the entire circuit.

Thus, you can successfully interface a single supply cable driver to a dual supply receiver.

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338