

HC55185 Ringing SLIC & the AK2306/2306LV Dual PCM CODEC

AN9991
Rev 0.00
Dec 21, 2001

The purpose of this application note is to provide a reference design for the HC55185 and AK2306/2306LV Dual PCM CODEC.

The network requirements of many countries require the analog subscriber line circuit (SLIC) to terminate the subscriber line with an impedance for voiceband frequencies which is complex, rather than resistive (e.g. 600Ω). The HC55185 accomplishes this impedance matching with a single network (R_S Figure 1) connected between the VTX pin and the -IN pin.

The AK2306/2306LV Dual PCM CODEC includes Selectable A-law/ μ -law function, Internal Gain Adjustment from +6dB to -18dB by 1dB steps control and a selectable 16Hz/20Hz Ring Tone Generator.

Discussed in this application note are the following:

- 2-wire impedance matching
- Receive gain (4-wire to 2-wire) and transmit gain (2-wire to 4-wire) calculations
- Reference design for both 600Ω and 220Ω + 820Ω//115nF Complex Impedance

Impedance Matching

Impedance matching of the HC55185 to the subscriber load is important for optimization of 2 wire return loss, which in turn cuts down on echoes in the end to end voice communication path. Impedance matching of the HC55185 is accomplished by making the SLIC's impedance (Z_O , Figure 1) equal to the desired terminating impedance Z_L , minus the value of the protection resistors (R_P). The formula to

calculate the proper R_S for matching the 2-wire impedance is shown in Equation 1.

$$R_S = 133.3 \cdot (Z_L - 2R_P) \quad (\text{EQ. 1})$$

Equation 1 can be used to match the impedance of the SLIC and the protection resistors (Z_{TR}) to any known line impedance (Z_L). Figure 1 shows the calculations of R_S to match a resistive and 2 complex loads.

EXAMPLE 1:

Calculate R_S to make $Z_{TR} = 600\Omega$ in series with 2.16μF.
 $R_P = 49\Omega$.

$$R_S = 133.3 \left(600 + \frac{1}{j\omega 2.16 \times 10^{-6}} - (2)(49) \right) \quad (\text{EQ. 2})$$

$R_S = 66.9k\Omega$ in series with 16.2nF. Note: Some impedance models, with a series capacitor, will cause the op amp feedback to behave as an open circuit DC. A resistor with a value of about 10 times the reactance of the R_S capacitor (2.16μF/133.3 = 16.2nF) at the low frequency of interest (200Hz for example) can be placed in parallel with the capacitor in order to solve the problem (491kΩ for a 16.2nF capacitor).

EXAMPLE 2:

Calculate R_S to make $Z_{TR} = 220 + 820\Omega//115nF$
 $R_P = 49\Omega$.

$$Z_T = 133.3 \left(200 + \frac{820}{1 + j\omega 820(115) \times 10^{-9}} - (2)(49) \right) \quad (\text{EQ. 3})$$

$R_S = 16.26k\Omega$ in series with the parallel combination of 109.3kΩ and 862pF.

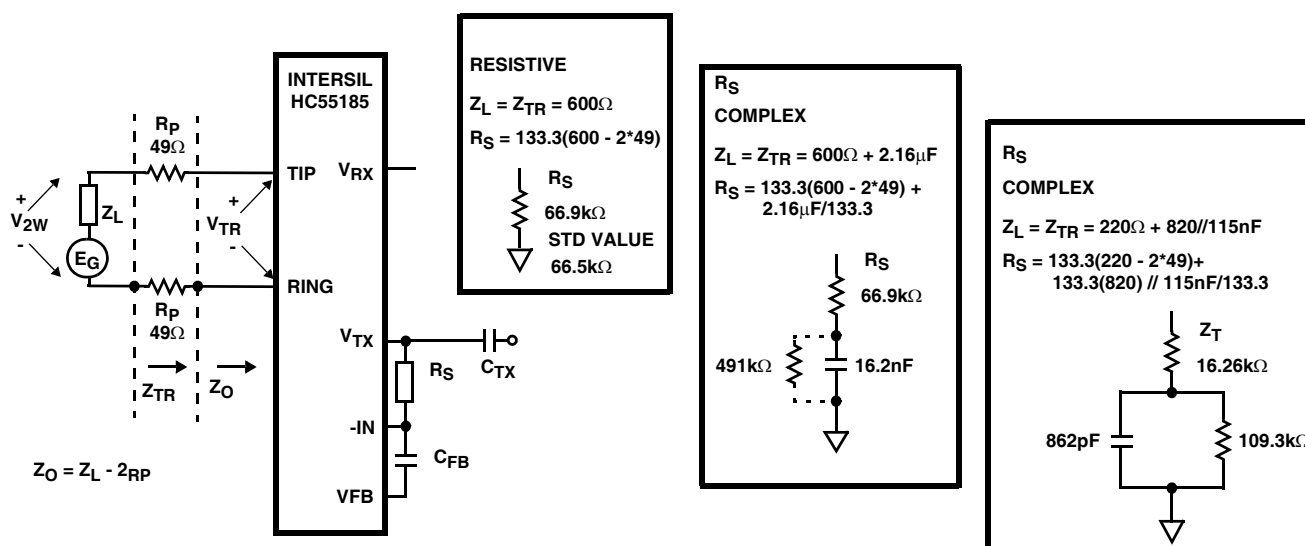


FIGURE 1. IMPEDANCE MATCHING

SLIC in the Active Mode

Figure 2 shows a simplified AC transmission model of the HC55185 and the connection of the AK2306 to the SLIC. Figure 3 shows a simplified AC transmission model of the HC55185 and the connection of the “Low Voltage” AK2306LV to the SLIC. The Low Voltage AK2306LV CODEC requires a different connection to the HC55185 to achieve the voltage gain required at tip and ring without clipping the output signal of the CODEC.

The following analysis is performed with the AK2306 CODEC connection. Circuit analysis of the “Low Voltage” circuit is left for the reader. Circuit analysis of the HC55185 yields the following design equations:

The Sense Amplifier is configured as a 4 input differential amplifier with a gain of 3/4. The voltage at the output of the sense amplifier (V_{SA}) is calculated using superposition. V_{SA1} is the voltage resulting from V_1 , V_{SA2} is the voltage resulting from V_2 and so on (reference Figure 2).

$$V_{SA1} = \frac{3}{4}(V_1) \quad (\text{EQ. 4})$$

$$V_{SA2} = \frac{3}{4}(V_2) \quad (\text{EQ. 5})$$

$$V_{SA3} = \frac{3}{4}(V_3) \quad (\text{EQ. 6})$$

$$V_{SA4} = \frac{3}{4}(V_4) \quad (\text{EQ. 7})$$

$$V_{SA} = [(V_2 - V_1) + (V_4 - V_3)] \frac{3}{4} = [\Delta V + \Delta V] \frac{3}{4} \quad (\text{EQ. 8})$$

Where ΔV is equal to $I_M R_{SENSE}$ ($R_{SENSE} = 20\Omega$)

$$V_{SA} = 2(\Delta I_M \times 20) \frac{3}{4} = \Delta I_M 30 \quad (\text{EQ. 9})$$

The voltage at V_{TX} is equal to:

$$V_{TX} = -V_{SA} \left(\frac{R_S}{8K} \right) = - \left(\frac{R_S}{8K} \right) \Delta I_M 30 \quad (\text{EQ. 10})$$

V_{TR} is defined in Figure 2, note polarity assigned to V_{TR}

$$V_{TR} = 2(V_{RX} + V_{TX}) \quad (\text{EQ. 11})$$

Setting V_{RX} equal to zero, substituting Equation 10 into Equation 11 and defining $Z_O = -V_{TR}/\Delta I_M$ will enable the user to determine the require feedback to match the line impedance at V_{2W} .

$$Z_O = \frac{1}{133.33} R_S \quad (\text{EQ. 12})$$

Z_O is the source impedance of the device and is defined as $Z_O = Z_L - 2R_P$. Z_L is the line impedance. R_S is defined as:

$$R_S = 133.33(Z_L - 2R_P) \quad (\text{EQ. 13})$$

Node Equation at HC55185 V_{RX} input

$$I_X = \frac{V_{RX}}{R} + \frac{V_{TX}}{R} \quad (\text{EQ. 14})$$

Substitute Equation 10 into Equation 14

$$I_X = \frac{V_{RX}}{R} - \left(\frac{R_S \Delta I_M 30}{8K} \right) \quad (\text{EQ. 15})$$

Loop Equation at HC55185 feed amplifiers and load

$$I_X R - V_{TR} + I_X R = 0 \quad (\text{EQ. 16})$$

Substitute Equation 15 into Equation 16

$$V_{TR} = 2V_{RX} - \left(\frac{R_S \Delta I_M 60}{8K} \right) \quad (\text{EQ. 17})$$

Substitute Equation 12 for R_S and $-V_{2W}/Z_L$ for ΔI_M into Equation 17.

$$V_{TR} = 2V_{RX} + \frac{Z_O V_{2W}}{Z_L} \quad (\text{EQ. 18})$$

Loop Equation at Tip/Ring interface

$$V_{2W} - I_M 2R_P + V_{TR} = 0 \quad (\text{EQ. 19})$$

Substitute Equation 18 into Equation 19 and combine terms

$$V_{2W} \left[\frac{Z_L + Z_O + 2R_P}{Z_L} \right] = -2V_{RX} \quad (\text{EQ. 20})$$

where:

V_{RX} = The input voltage at the V_{RX} pin.

V_{SA} = An internal node voltage that is a function of the loop current and the output of the Sense Amplifier.

I_X = Internal current in the SLIC that is the difference between the input receive current and the feedback current.

I_M = The AC metallic current.

R_P = A protection resistor (typical 49.9 Ω).

R_S = An external resistor/network for matching the line impedance.

V_{TR} = The tip to ring voltage at the output pins of the SLIC.

V_{2W} = The tip to ring voltage including the voltage across the protection resistors.

Z_L = The line impedance.

Z_O = The source impedance of the device.

HC55185 Receive Gain (V_{RX} to V_{2W})

4-wire to 2-wire gain across the HC55185 is equal to the V_{2W} divided by the input voltage V_{RX} , reference Figure 2. The receive gain is calculated using Equation 20.

Equation 21 expresses the receive gain (V_{RX} to V_{2W}) in terms of network impedances. From Equation 13, the value of R_S was set to match the line impedance (Z_L) to the HC55185 plus the protection resistors ($Z_O + R_P$). This results in a 4-wire to 2-wire gain of -1, as shown in Equation 21.

$$G_{4-2} = \frac{V_{2W}}{V_{RX}} = -2 \frac{Z_L}{Z_L + Z_O + 2R_P} = -2 \frac{Z_L}{Z_L + Z_L} = -1 \quad (\text{EQ. 21})$$

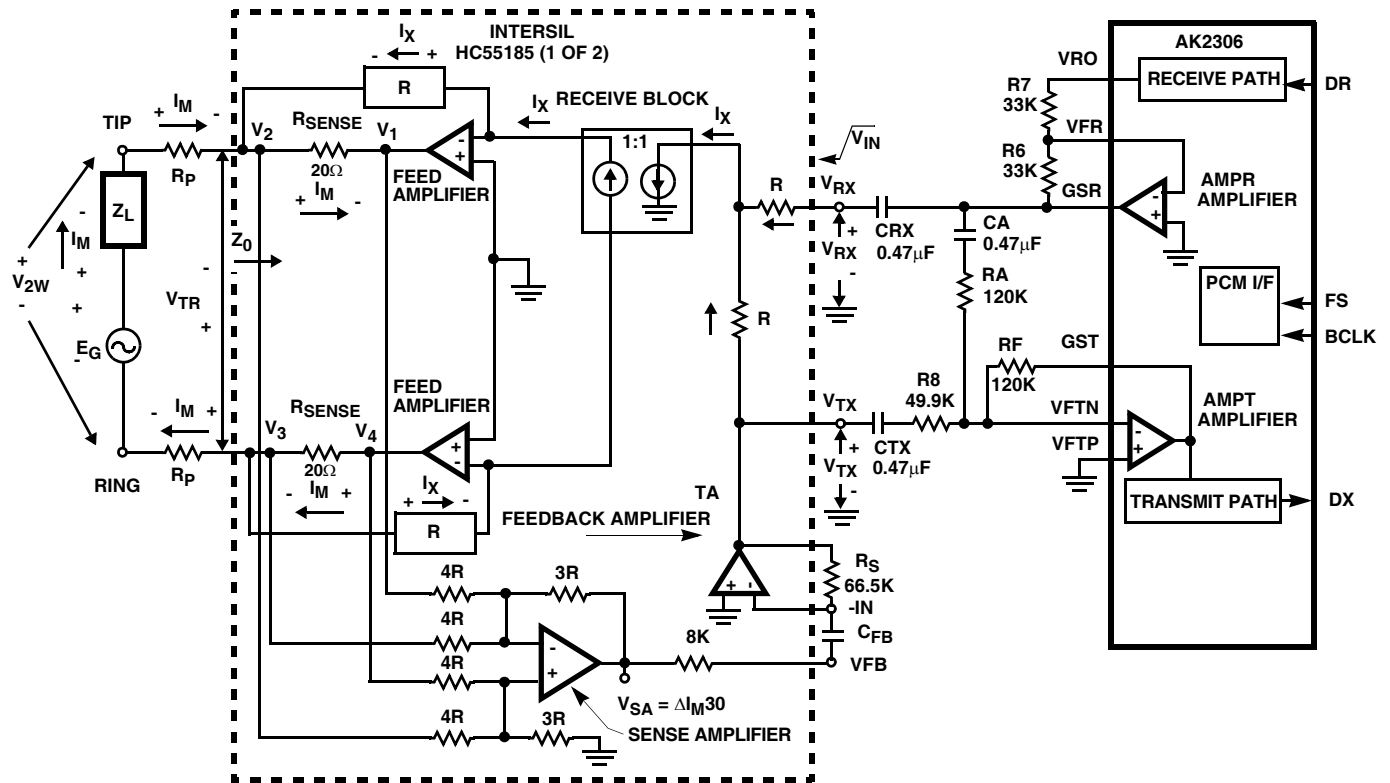


FIGURE 2. HC55185 SIMPLIFIED AC TRANSMISSION CIRCUIT AND AK2306

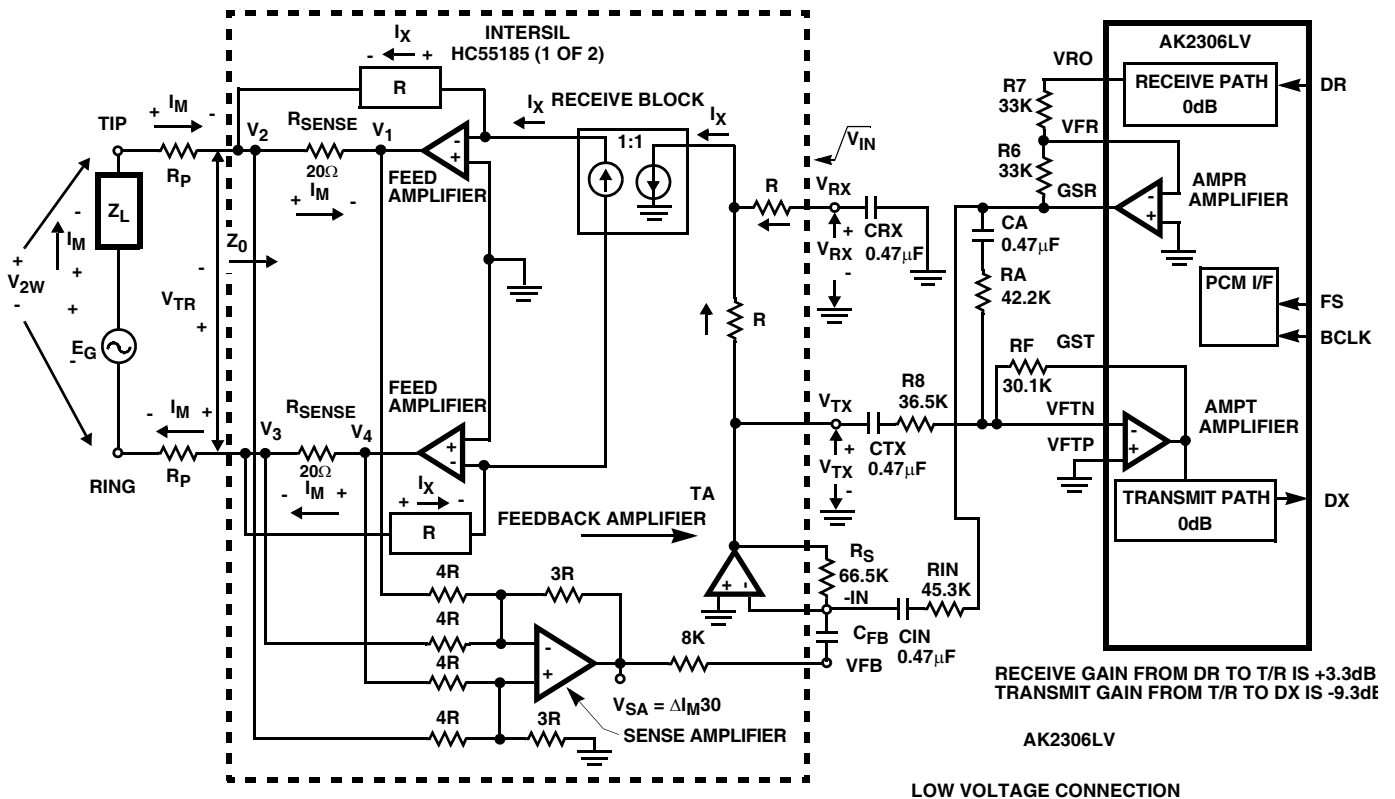


FIGURE 3. HC55185 SIMPLIFIED AC TRANSMISSION CIRCUIT AND AK2306LV

Receive Gain Across the System

The receive gain across the system is defined as the gain from DR to the phone (V_{2W}). With the receive gain through the HC55185 set to 1, the receive gain across the system is entirely controlled by programming the AK2306. The AK2306 can program the receive gain across the system from +6dB to -18dB in 1 dB increments (reference Figure 4).

If more precise gain increments are required, the AMPR amplifier can be used to adjust the overall Receive gain ($R6/R7$).

Transmit Gain Across HC55185 (E_G to V_{TX})

The 2-wire to 4-wire gain is equal to V_{TX}/E_G with $V_{RX} = 0$, reference Figure 2.

$$\text{Loop Equation} \quad (EQ. 22)$$

$$-E_G + Z_L I_M + 2R_P I_M - V_{TR} = 0$$

From Equation 18 with $V_{RX} = 0$

$$V_{TR} = \frac{Z_O V_{2W}}{Z_L} \quad (EQ. 23)$$

Substituting Equation 23 into Equation 22 and simplifying.

$$E_G = -V_{2W} \left[\frac{Z_L + 2R_P + Z_O}{Z_L} \right] \quad (EQ. 24)$$

Substituting Equation 12 into Equation 10 and defining $\Delta I_M = -V_{2W}/Z_L$ results in Equation 25 for V_{TX} .

$$V_{TX} = \frac{V_{2W}}{2} \left[\frac{Z_L - 2R_P}{Z_L} \right] \quad (EQ. 25)$$

Combining Equations 24 and 25 results in Equation 26.

$$G_{2-4} = \frac{V_{TX}}{E_G} = -\frac{Z_L - 2R_P}{2(Z_L + 2R_P + Z_O)} = -\frac{Z_O}{2(Z_L + 2R_P + Z_O)} \quad (EQ. 26)$$

A more useful form of the equation is rewritten in terms of V_{TX}/V_{2W} . A voltage divider equation is written to convert from E_G to V_{2W} as shown in Equation 27.

$$V_{2W} = \left(\frac{Z_O + 2R_P}{Z_L + Z_O + 2R_P} \right) E_G \quad (EQ. 27)$$

Substituting $Z_L = Z_O + 2R_P$ and rearranging Equation 27 in terms of E_G results in Equation 28.

$$E_G = 2V_{2W} \quad (EQ. 28)$$

Substituting Equation 28 into Equation 26 results in an equation for 2-wire to 4-wire gain that's a function of the synthesized input impedance of the SLIC and the protection resistors.

$$G_{2-4} = \frac{V_{TX}}{V_{2W}} = -\frac{Z_O}{(Z_L + 2R_P + Z_O)} = 0.416 \quad (EQ. 29)$$

Z_L is set to 600Ω , Z_O is programmed with R_S to be 498.76Ω ($66.5k\Omega/133.33$), and R_P is equal to 49.9Ω . This results in a 2-wire to 4-wire gain of 0.416 or -7.6dB.

Transmit Gain Across the System

The transmit gain across the system is defined as the gain from the phone or 2-wire side (V_{2W}) to the PCM highway (DX). Setting the gain of the AK2306 will have to account for the attenuated signal through the HC55185. The system gain is entirely controlled by programming the AK2306. The AK2306 can program the transmit gain across the system from +6dB to -18dB in 1 dB increments (reference Figure 4).

If more precise gain increments are required, the AMPT amplifier can be used to adjust the overall Transmit gain (R_f/R_8).

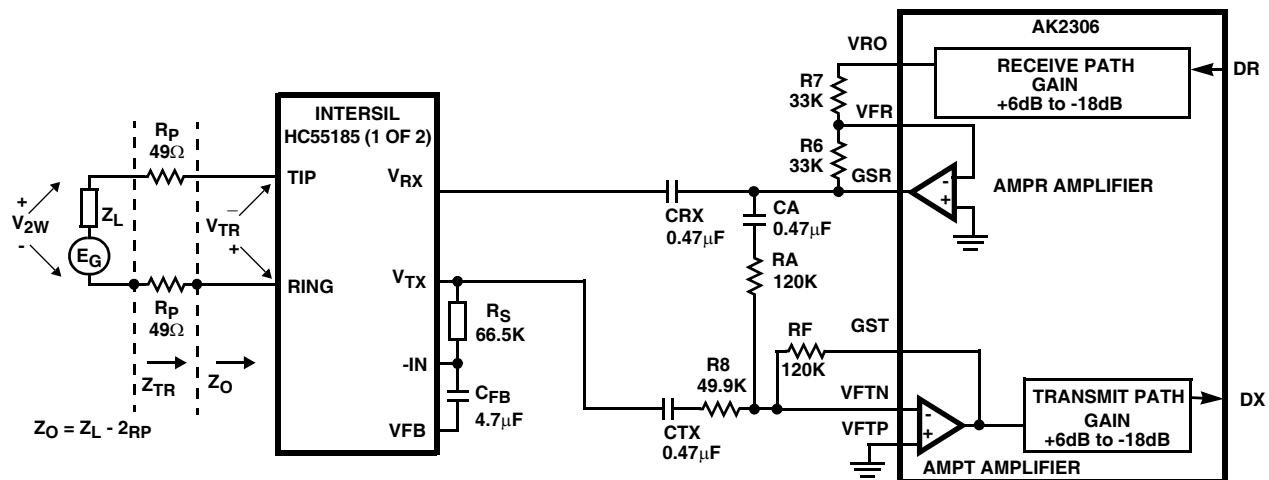


FIGURE 4. RECEIVE GAIN G(4-2), TRANSMIT GAIN (2-4)

Transhybrid Balance G(4-4)

Transhybrid balance is a measure of how well the input signal is canceled (that being received by the SLIC) from the transmit signal (that being transmitted from the SLIC to the CODEC). Without this function, voice communication would be difficult because of the echo.

The signals at V_{GSR} and V_{TX} (Figure 4) are opposite in phase. Transhybrid balance is achieved by summing two signals that are equal in magnitude and opposite in phase into the AMPT amplifier inside the AK2306.

Transhybrid balance is achieved by summing the V_{GSR} signal with the output signal from the HC55185 when proper gain adjustments are made to match V_{GSR} and V_{TX} magnitudes.

For discussion purpose, the AMPT amplifier is redrawn with the external resistors in Figure 5.

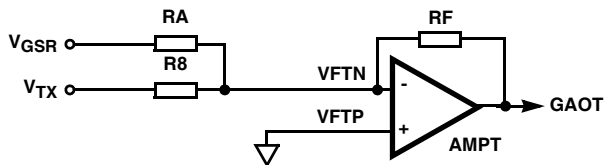


FIGURE 5. TRANSHYBRID BALANCE CIRCUIT

Transhybrid balance is achieved by adjusting the magnitude from both V_{TX} and V_{GSR} so their equal to each other.

The gain across the system is set by the gain through the SLIC (0.416) and the AMPT amplifier through $RF/R8$. RF is randomly selected to be 120k Ω . To achieve a 0dB gain across

the system, with the transmit gain of the AK2306 set to 0dB, we set $R8$ equal to 49.9k Ω , as shown in Equation 30.

$$G_{V_{TX}} = G_{4-4} \left(\frac{RF}{R8} \right) = G_{4-4} \left(\frac{120k}{49.9k} \right) = 0.416(2.404) = 1.0 \quad (\text{EQ. 30})$$

The gain through the AMPT amplifier from V_{GSR} must equal the gain from V_{TX} to achieve transhybrid balance. RA is therefore equal to RF , as shown in Equation 31.

$$G_{V_{GSR}} = V_{GSR} \left(\frac{RF}{RA} \right) = V_{GSR} \left(\frac{120k}{120k} \right) = 1 \quad (\text{EQ. 31})$$

Reference Design of the HC55185 and the AK2306 With a 600 Ω Load

The design criteria is as follows:

- 4-wire to 2-wire gain (DR to V_{2W}) equal 0dB
- 2-wire to 4-wire gain (V_{2W} to DX) equal 0dB
- $R_p = 49.9\Omega$

Figure 6 gives the reference design using the Intersil HC55185 and the AK2306 Dual PCM CODEC. Also shown in Figure 6 are the voltage levels at specific points in the circuit.

Impedance Matching

The 2-wire impedance is matched to the line impedance Z_0 using Equation 1, repeated here in Equation 32.

$$R_S = 133.3 \cdot (Z_L - 2R_P) \quad (\text{EQ. 32})$$

For a line impedance of 600 Ω , R_S equals:

$$R_S = 133.3 \cdot (600 - 98) = 66.9k\Omega \quad (\text{EQ. 33})$$

The closest standard value for R_S would be 66.5k Ω .

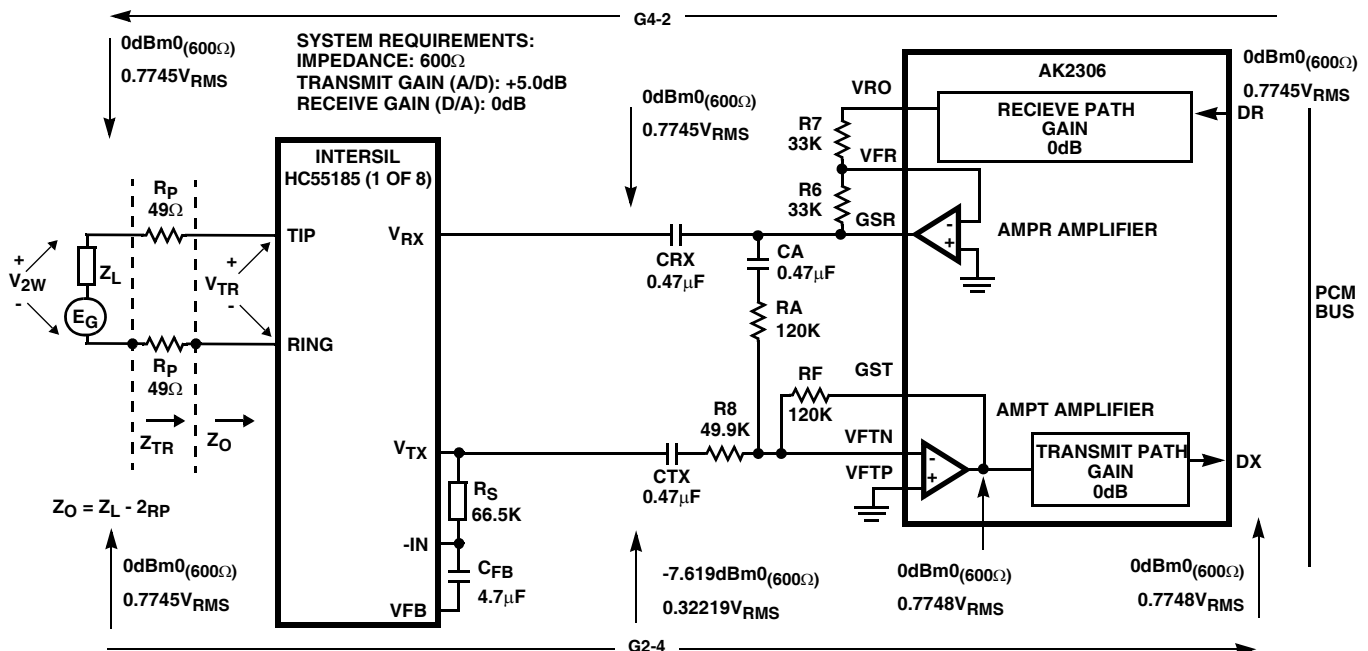


FIGURE 6. REFERENCE DESIGN OF THE HC55185 AND THE AK2306/2306LV WITH A 600 Ω LOAD IMPEDANCE

Reference Design of the HC55185 and the AK2306 With a Complex Load

The design criteria for a Complex load solution are as follows:

- Desired line circuit impedance is $220 + 820j/115nF$
- Receive gain V_{2W} / DR is -3.5dB
- Transmit gain DX / V_{2W} is 0dB
- 0dBm0 is defined as 1mW into the complex impedance at 1020Hz
- $R_p = 49.9\Omega$

Figure 7 gives the reference design using the Intersil HC55185 and the AK2306 Dual PCM CODEC. Also shown in Figure 7 are the voltage levels at specific points in the circuit. Note: The transmit gain of the system is 0dB ($-1.79dB_{(897\Omega)} = -3.5dB_{(600\Omega)}$) as explained in the following section.

Adjustment to Get -3.5dBm0 at the Load Referenced to 600Ω

The voltage equivalent to 0dBm0 into 897Ω ($0dBm0_{(897\Omega)}$) is calculated using Equation 34 (897Ω is the impedance of complex load at 1020Hz).

$$0dBm_{(897\Omega)} = 10 \log \frac{V^2}{897(0.001)} = 0.9471V_{RMS} \quad (EQ. 34)$$

The gain referenced back to $0dBm0_{(600\Omega)}$ is equal to:

$$GAIN = 20 \log \frac{0.9471V_{RMS}}{0.7745V_{RMS}} = 1.747dB \quad (EQ. 35)$$

The adjustment to get -3.5dBm0 at the load referenced to 600Ω is:

$$Adjustment = -3.5dBm0 + 1.747dBm0 = -1.75dB \quad (EQ. 36)$$

The voltage at the load (referenced to 600Ω) is given in Equation 37

$$-1.75dBm_{(600\Omega)} = 10 \log \frac{V^2}{600(0.001)} = 0.63306V_{RMS} \quad (EQ. 37)$$

Setting the Receive Path Gain equal to -1dB and adjusting R6/R7 with standard resistor values results in a voltage of 0.62969Vrms or -1.70dBm0 (600Ω).

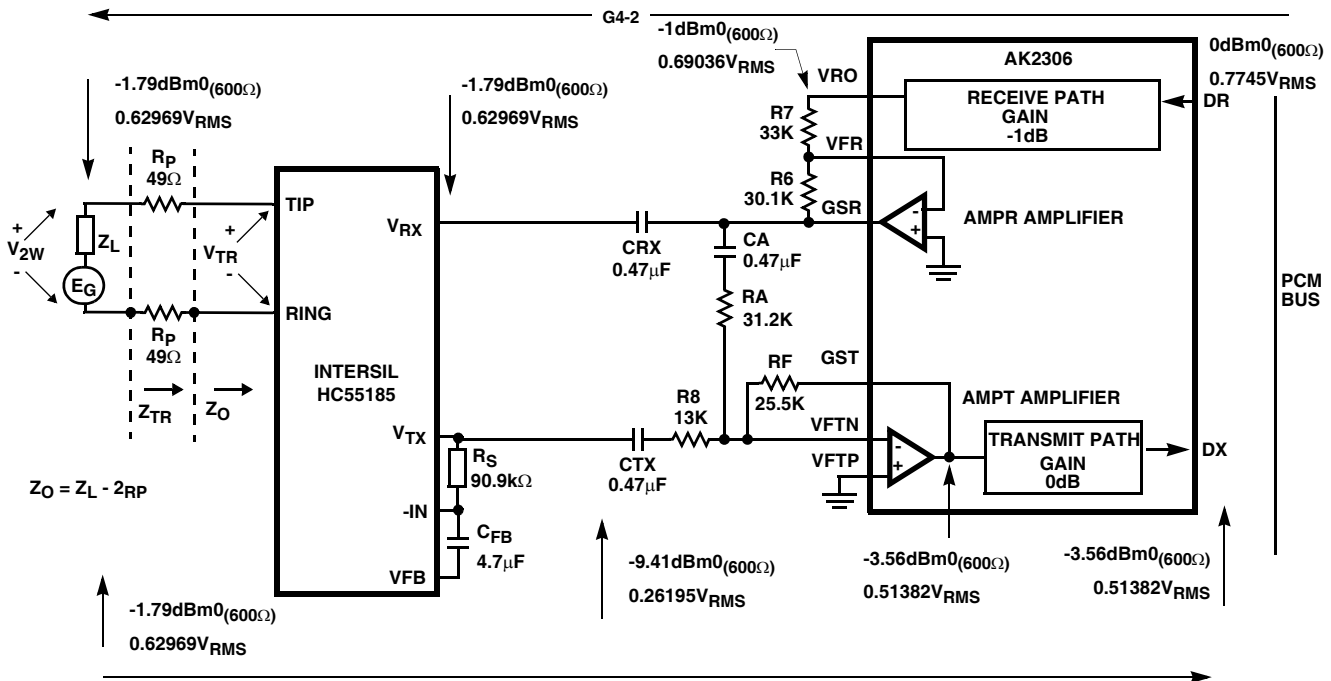


FIGURE 7. REFERENCE DESIGN OF THE HC55185 AND THE AK2306 WITH A COMPLEX LOAD IMPEDANCE

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338