

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

H8/300H, H8/300L Super Low Power Series

Example of Driving an MCU from a Low-Voltage Power Supply by Using a Step-Up DC/DC Converter and Start-Up IC

Introduction

A minimum operating voltage applies to LSI circuits in general, and not just to the Super Low Power Series. Operation will not proceed when the power-supply voltage is at a lower value. However, constraints of the following types may apply, according to the system.

- Power-supply voltages can fall because batteries are drained.
- Operation with a small solar panel may necessitate operation with a low power-supply voltage.

To satisfy such constraints, examples of using a step-up circuit to drive an MCU are introduced in this application note.

Contents

1. Step-Up Circuit.....	2
2. Example of Using a Step-Up DC/DC Converter to Drive an MCU	5
3. Reference Documents	7

1. Step-Up Circuit

In this application note, a switching regulator with an on-chip FET for step-up PWM control (S-8353 Series) and a charge-pump IC with super-low-voltage operation for starting up step-up DC/DC converters (S-882Z Series), both manufactured by Seiko Instruments Inc., are used in a step-up circuit.

Normally, a circuit will be drivable by a step-up DC/DC converter on its own. However, using the charge-pump IC with super-low-voltage operation to start the converter up allows the operation of circuits from even lower power-supply voltages (as low as 0.3 V). More detailed descriptions of the ICs used in the step-up circuit follow.

1.1 Switching Regulator with On-Chip Step-Up PWM Control FET: S-8353 Series

The S-8353 Series is a CMOS step-up switching regulator, the main components of which are a reference-voltage source, oscillator circuit, power MOS FET, error amplifier, phase compensation circuit, and PWM control circuit.

Configuring a step-up switching regulator simply requires the addition of an external coil, capacitor, and diode.

- Low-voltage operation: Startup at 0.9 V ($I_{OUT} = 1$ mA) guaranteed
- Low current drawn: 18.7 μ A (3.3 V, 50 kHz, typ.) during operation
0.5 μ A (max.) during shutdown
- Duty cycle: On-chip PWM control circuit
0% to 83% (30-kHz and 50-kHz models)
0% to 78% (250-kHz models)
- External parts: Coil, capacitor, and diode
- Output voltage: Selectable in 0.1-V steps between 1.5 and 6.5 V (for separate V_{DD}/V_{OUT} types)
Selectable in 0.1-V steps between 2.0 and 6.5 V (for types without separate V_{DD}/V_{OUT})
- Oscillation frequency: 30 kHz, 50 kHz, and 250 kHz selectable
- Soft-start function: 6 ms (50 kHz, typ.)

 


Figure 1 Block Diagram of S-8353 Series

1. In the S-882Z Series, input of a power-supply voltage of 0.3 V or more to the V_{IN} pin makes the oscillator start operation, producing the CLK signal as an output signal.
2. This CLK signal drives the charge pump, and the power from the V_{IN} pin is converted to stepped-up electrical power in the charge-pump circuit.
3. The stepped-up electric power output from the charge pump circuit gradually charges to the startup capacitor (C_{CPOUT}) connected to the CPOUT pin, the voltage on the pin gradually rises.
4. When the CPOUT pin voltage (V_{CPOUT}) reaches or exceeds the discharge-start voltage (V_{CPOUT1}), the output signal of the comparator (COMP1) changes from high to low level. This switches the discharge-control switch (M1) from off to on.
5. When M1 is switched on, the step-up electric power stored in C_{CPOUT} is discharged from the OUT pin.
6. When discharging proceeds until V_{CPOUT} falls to the level of the discharge-stop voltage (V_{CPOUT2}), M1 is switched off, and the discharge is stopped.
7. When the VM pin voltage (V_{VM}) reaches or exceeds the shutdown voltage (V_{OFF}), the output signal (EN-) of the comparator (COMP2) changes from low level to high. This makes the oscillator circuit stop, and the device enters the shutdown state.
8. When V_{VM} does not reach or exceed V_{OFF} , the step-up electric power from the charge-pump circuit reaches C_{CPOUT} again (from here, return to the step 3).

Note: When discharge to the OUT pin stops and recharging of the startup capacitor (C_{CPOUT}) is restarted, C_{CPOUT} must be charged until the voltage on the CPOUT pin (C_{CPOUT}) falls below the discharge-stop voltage (V_{CPOUT2}). In this case, the following condition must be met:

Condition: OUT pin voltage (V_{OUT}) < Discharge-stop voltage (V_{CPOUT2}).

 


Figure 3 Example of Operation for S-882Z Series

2. Example of Using a Step-Up DC/DC Converter to Drive an MCU

In the example given below, the switching regulator with on-chip step-up PWM control FET (S-8353 Series) and charge-pump IC with super-low-voltage operation for starting up step-up DC/DC converters (S-882Z Series) are combined to drive a Super Low Power Series MCU from an input voltage of 0.3 V.

Figure 4 shows the connections between the MCU and the S-8353 Series and S-882Z Series devices.

 


Figure 4 Example of Using a Step-Up Circuit to Drive an MCU

Table 1 shows the major parts used.

Table1 Major Parts Used

Part Name	Symbol	Manufacturer	Part No.
Super Low Power Series MCU	—	Renesas Technology Corp.	(Various; depends on the products)
S-882Z Series	—	Seiko Instruments Inc.	S-882Z20-M5T1G (Discharge-start voltage setting: 2.0 V)
Step-up DC/DC converter	—	Seiko Instruments Inc.	S-8353D30MC (Output voltage setting: 3.0 V)
Inductor	L	Sumida Corporation	CDRH5D18-101 (100 μH)
Schottky diode	SD1, SD2	Rohm Co., Ltd.	RB551V-30
Startup capacitor	C_{CPOUT}	—	10 μF (ceramic type)
Input capacitor	C_{IN}	—	47 μF
Output capacitor	C_L	—	33 μF (ESR $\geq 50\text{ m}\Omega$)
Power smoothing capacitor	C_{VDD}	—	1 μF (ceramic type)

Note: Following the above connection diagram and constants does not guarantee successful operation. Set the actual constants after thoroughly evaluating operation with the actual application.

The above figure shows an application circuit example with targeted values of $V_{IN} = 0.3\text{ V}$, $V_{OUT} = 3.0\text{ V}$, and $I_{OUT} = 1\text{ mA}$.


In order to operate the Super Low Power Series MCU, increasing output current of step-up DC/DC converter and reducing current drawn by the MCU is required.

To reduce the current drawn by the MCU, the following countermeasures can be considered.

- Reduce the number of operating power-supply voltage of the MCU
- Reduce the operating frequency for the MCU
- Use the on-chip oscillator for system clock (in case of product with on-chip oscillator for system clock)
- Switch the LSI circuit from the active (high-speed) mode to the active (middle-speed) mode after a reset. Switch it to the sub-active mode after stabilization of sub-clock oscillation.
- When the software does not operate, transit to the standby mode or watch mode.


The following chart shows the transition from the active (high-speed) mode to the active (middle-speed) mode after a reset, the transition to the sub-active mode after the sub-clock oscillation is stabilized, and then the transition to the watch mode.

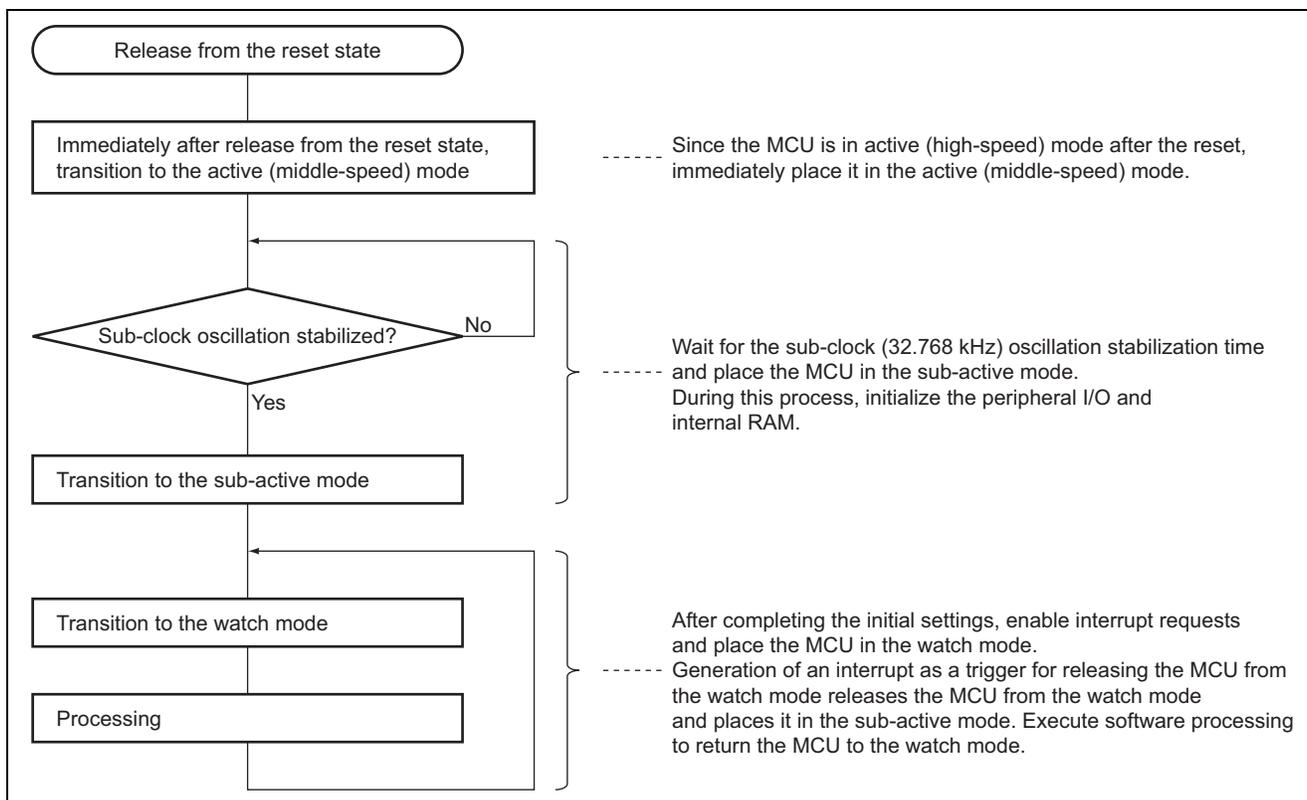- Flow which minimizes the current drawn by general products of the Super Low Power Series



The products for which the on-chip oscillator can be used as the sub-clock enable the transition to the sub-active mode to be made without waiting for the oscillation of the external sub-clock to be stabilized.

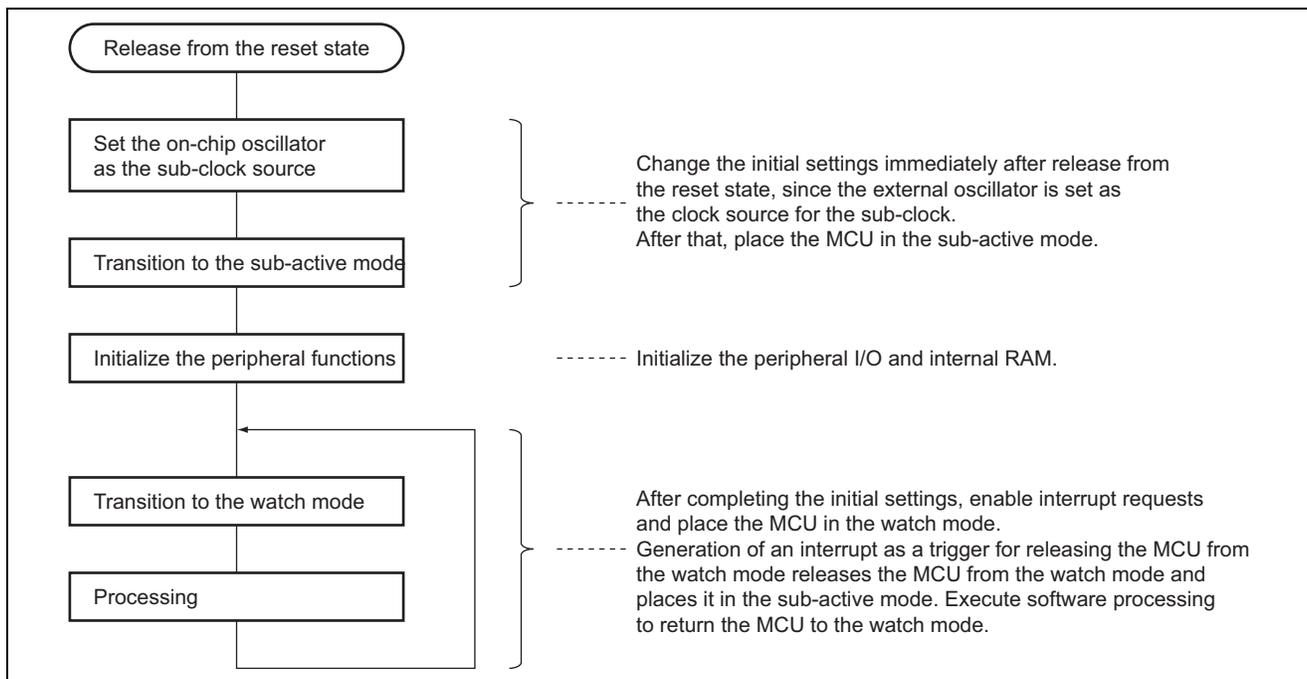- Flow which minimizes the current drawn by products for which the on-chip oscillator can be used as the sub-clock.



3. Reference Documents

1. Datasheet
 STEP-UP, PWM CONTORL or PWM/PFM SWITCHABLE BUILT-IN TRANSISTOR SWITCHING
 REGULATOR S-8353/8354 Series:
 Seiko Instruments Inc.
2. Datasheet
 ULTRA-LOW VOLTAGE OPERATON CHARGE PUMP IC FOR STEP-UP DC-DC CONVERTER STARTUP
 S-882Z Series:
 Seiko Instruments Inc.

Website and Support

Renesas Technology Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

csc@renesas.com

Revision Record

Rev.	Date	Description	
		Page	Summary
1.00	Mar.15.07	—	First edition issued

Notes regarding these materials

1. This document is provided for reference purposes only so that Renesas customers may select the appropriate Renesas products for their use. Renesas neither makes warranties or representations with respect to the accuracy or completeness of the information contained in this document nor grants any license to any intellectual property rights or any other rights of Renesas or any third party with respect to the information in this document.
2. Renesas shall have no liability for damages or infringement of any intellectual property or other rights arising out of the use of any information in this document, including, but not limited to, product data, diagrams, charts, programs, algorithms, and application circuit examples.
3. You should not use the products or the technology described in this document for the purpose of military applications such as the development of weapons of mass destruction or for the purpose of any other military use. When exporting the products or technology described herein, you should follow the applicable export control laws and regulations, and procedures required by such laws and regulations.
4. All information included in this document such as product data, diagrams, charts, programs, algorithms, and application circuit examples, is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas products listed in this document, please confirm the latest product information with a Renesas sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas such as that disclosed through our website. (<http://www.renesas.com>)
5. Renesas has used reasonable care in compiling the information included in this document, but Renesas assumes no liability whatsoever for any damages incurred as a result of errors or omissions in the information included in this document.
6. When using or otherwise relying on the information in this document, you should evaluate the information in light of the total system before deciding about the applicability of such information to the intended application. Renesas makes no representations, warranties or guaranties regarding the suitability of its products for any particular application and specifically disclaims any liability arising out of the application and use of the information in this document or Renesas products.
7. With the exception of products specified by Renesas as suitable for automobile applications, Renesas products are not designed, manufactured or tested for applications or otherwise in systems the failure or malfunction of which may cause a direct threat to human life or create a risk of human injury or which require especially high quality and reliability such as safety systems, or equipment or systems for transportation and traffic, healthcare, combustion control, aerospace and aeronautics, nuclear power, or undersea communication transmission. If you are considering the use of our products for such purposes, please contact a Renesas sales office beforehand. Renesas shall have no liability for damages arising out of the uses set forth above.
8. Notwithstanding the preceding paragraph, you should not use Renesas products for the purposes listed below:
 - (1) artificial life support devices or systems
 - (2) surgical implantations
 - (3) healthcare intervention (e.g., excision, administration of medication, etc.)
 - (4) any other purposes that pose a direct threat to human life

Renesas shall have no liability for damages arising out of the uses set forth in the above and purchasers who elect to use Renesas products in any of the foregoing applications shall indemnify and hold harmless Renesas Technology Corp., its affiliated companies and their officers, directors, and employees against any and all damages arising out of such applications.
9. You should use the products described herein within the range specified by Renesas, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas shall have no liability for malfunctions or damages arising out of the use of Renesas products beyond such specified ranges.
10. Although Renesas endeavors to improve the quality and reliability of its products, IC products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Please be sure to implement safety measures to guard against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other applicable measures. Among others, since the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
11. In case Renesas products listed in this document are detached from the products to which the Renesas products are attached or affixed, the risk of accident such as swallowing by infants and small children is very high. You should implement safety measures so that Renesas products may not be easily detached from your products. Renesas shall have no liability for damages arising out of such detachment.
12. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written approval from Renesas.
13. Please contact a Renesas sales office if you have any questions regarding the information contained in this document, Renesas semiconductor products, or if you have any other inquiries.