

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

R8C/2D Group

LED Table Lighting Application on Renesas Starter Kit

Introduction

This application note is to describe how to use the Renesas Starter Kit for R8C/2D to implement LED lighting with PFM (Pulse Frequency Modulation) controlling LED current. It is also controlled by key input, sound and CDS (Cadmium-Sulfide) sensor. The brightness can be adjusted smoothly by key, and be turned on/off by sound from a clap or button. With CDS sensing, it can automatically adjust lighting to constant luminance depending on lighting altitude. The board converts 12V DC to constant current for LED with PFM output of MCU; the MCU could share other tasks such as sound sensing, key control, CDS sensing etc.

Target Device

The target device is R8C/2D series.

Contents

1. The Configuration of The System	2
2. Hardware Specification	3
3. Reference Schematics	6
4. Program Flow Chart	9
5. Website and Support.....	13

1. The Configuration of the System

The configuration of the system is shown in Figure 1. R8C/2D generates the PFM output signal according to the A/D sense signals are generated after the PFM signals dimming the LED lamps brightness. CDS (Cadmium-Sulfide) sensor, MIC and Key provide different dimming condition to affect LED on/off and dimming.

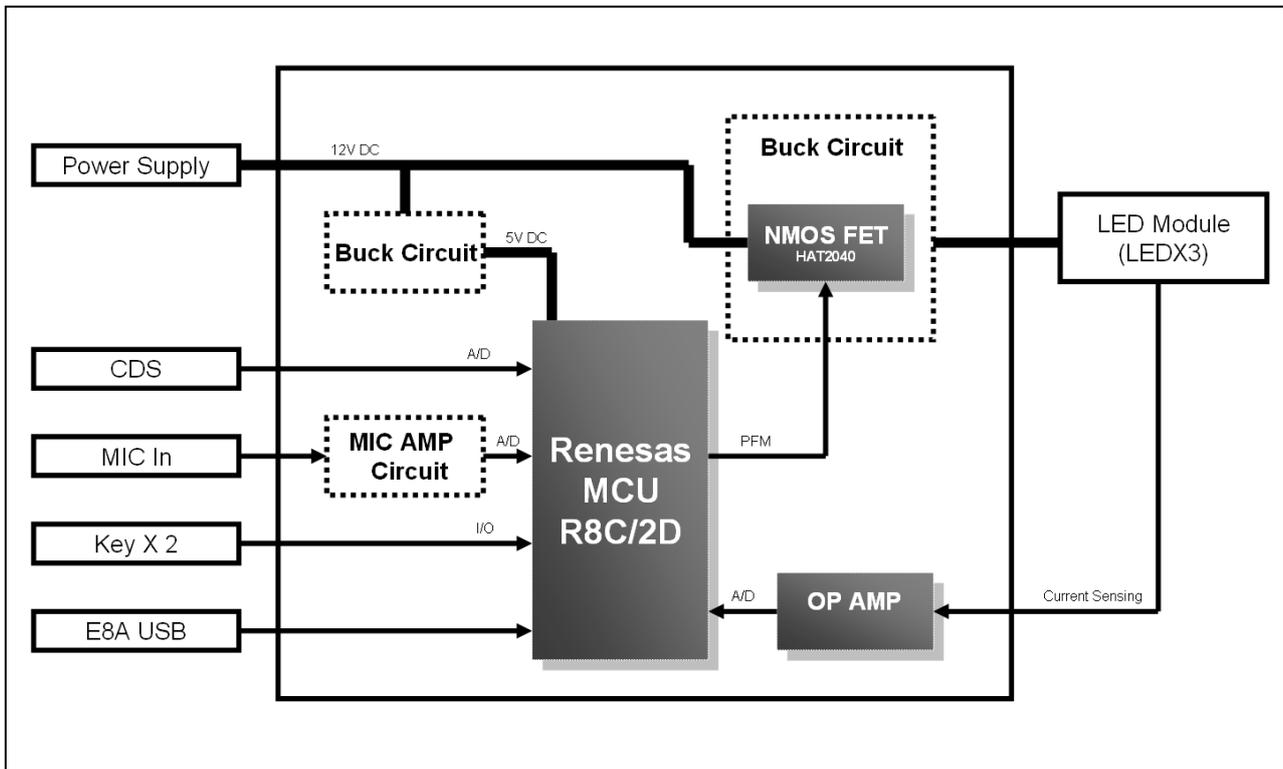


Figure 1 the configuration of the system

The block diagram above displays the LED table lighting function with Renesas R8C series MCU. It uses 3 ADCs to detect voltage and current. Auto dimming is based on CDS (Cadmium-Sulfide) sensing the lighting variation, then ADC captures the changes of A/D and sending value back to MCU to control PFM output. Sound control according to Miniature Condenser Microphone to receive sound and transfer voltage signal to ADC of MCU to on/ off LED module. Current sensing is supplied by amplifier, and the amplifier can get the current signal from LED Module. This function can help to provide feedback of the current status of LED to compensation current requirement of PFM control. Key functions are operated by I/O pin. The main purpose is to create power on/off key and manual dimming. Power supply is from 12V DC adapter and down to 5V DC to supply the MCU. Another one goes through DC-DC buck circuit to 9V DC and controlled current by PFM signal for brightness dimming. For this total solution is applicable for home lighting such as LED table lighting.

2. Hardware Specification

2.1 Implement LED table lighting application on Renesas Starter Kit for R8C/2D

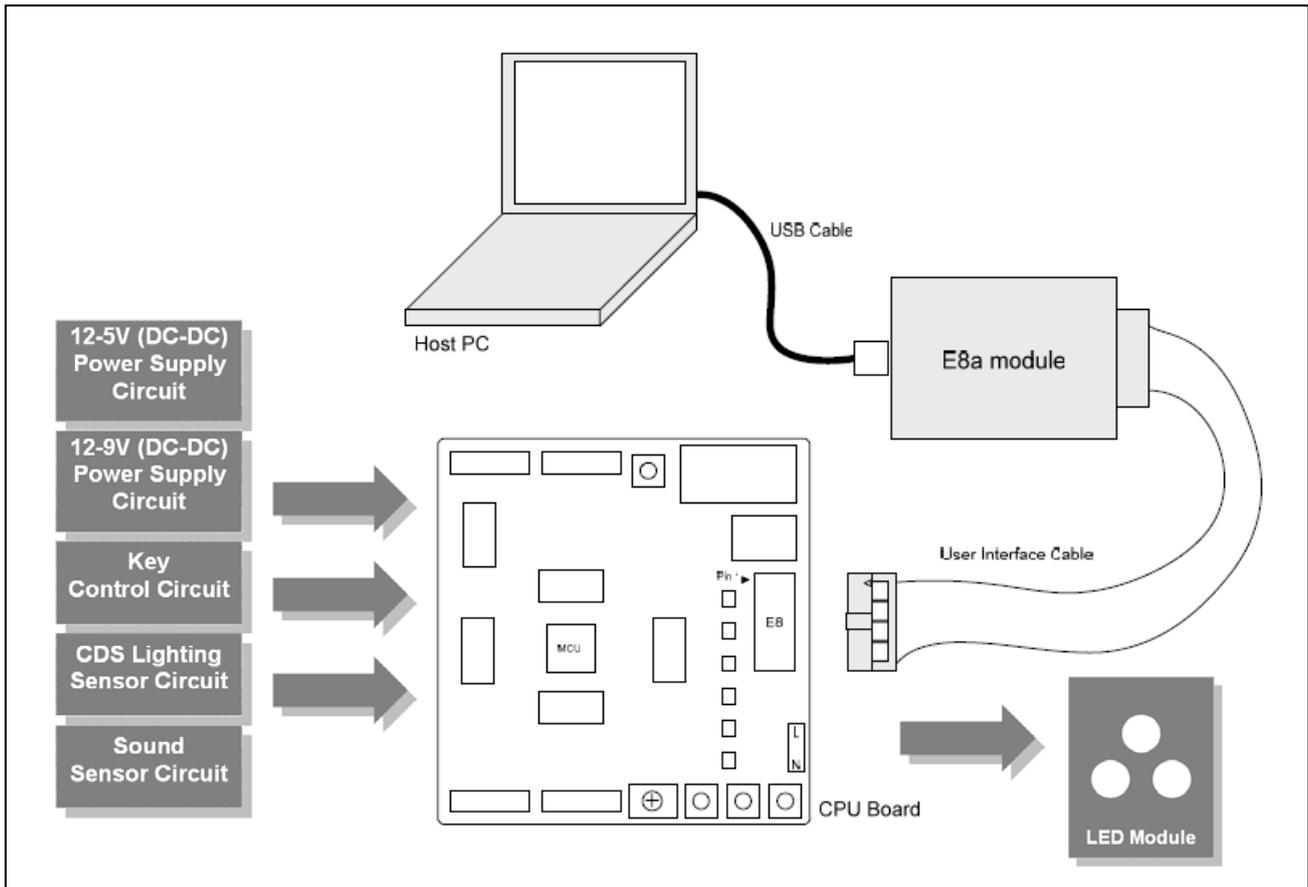


Figure 2 Implement LED table lighting application on RSK R8C/2D

RSK (Renesas Starter Kit) CPU board for R8C/2D is a useful platform which can implement LED table lighting conveniently. In Figure 2 illustrates the extra circuit block diagram for expansion on RSK. The detail schematics will be point out in next chapter “Reference Schematics”. The power supply of 12-5V DC-DC circuit block includes system 12V DC and the function of drop down 12V DC to 5V DC. The 5V DC is supplied to MCU operation. The second one is 12-9V power supply circuit. This buck circuit converts voltage from 12-9V DC, the power is provided to LED module, current control of LED Module is generated by PFM of MCU. Key control circuit connects to I/O pin of MCU for manual dimming. Another key function is connected with interrupt pin for power on/off control. CDS lighting sensor circuit contain CDS component which provides lighting- voltage conversion function. After ADC sensing the lighting- voltage is converted from CDS. MCU will adjust the PFM output for dimming automatically. Sound sensor includes MIC and amplifier circuit to capture the signal which is converted by sound to voltage. LED module has lamps current sensing circuit to feedback current status of lighting lamps. All of signal sensing, such as key (voltage detect), CDS (voltage detect), Sound (Voltage detect), LED module (current detect) are inputted to ADC of MCU thus according to these value to dim the brightness.

2.2 Timer RF and PFM Control

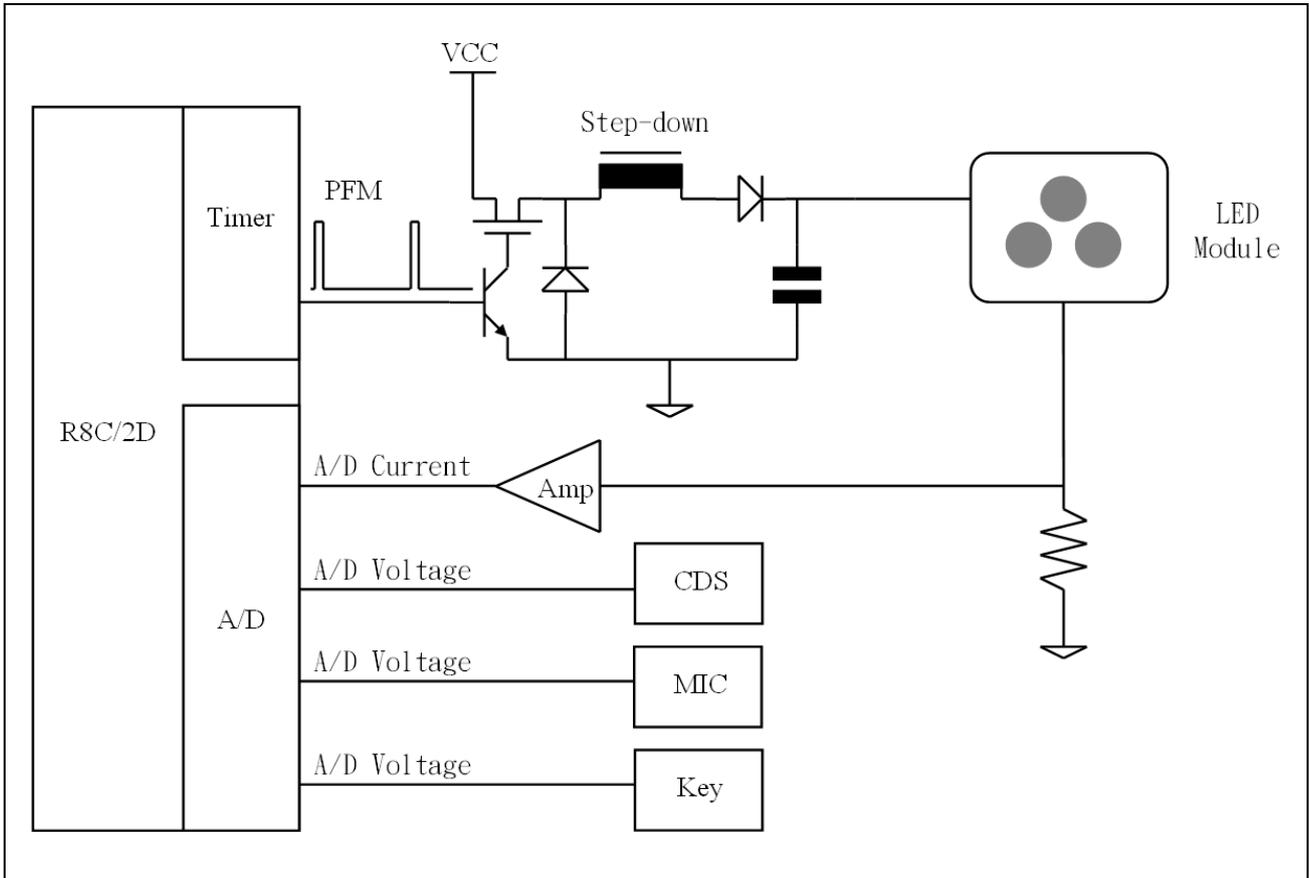


Figure 3 R8C/2D Timer RF out PFM Circuit

Figure 3 shows basic PFM and buck connection circuit. Figure 4 indicates PFM off, voltage keeps on high level and LED turn off. The output period of waveform is increase when dimming decrease and decrease when dimming increase. Timer RF of R8C/2D setting to PFM output mode. All of sensing signals capture by ADC then MCU change period for dimming.

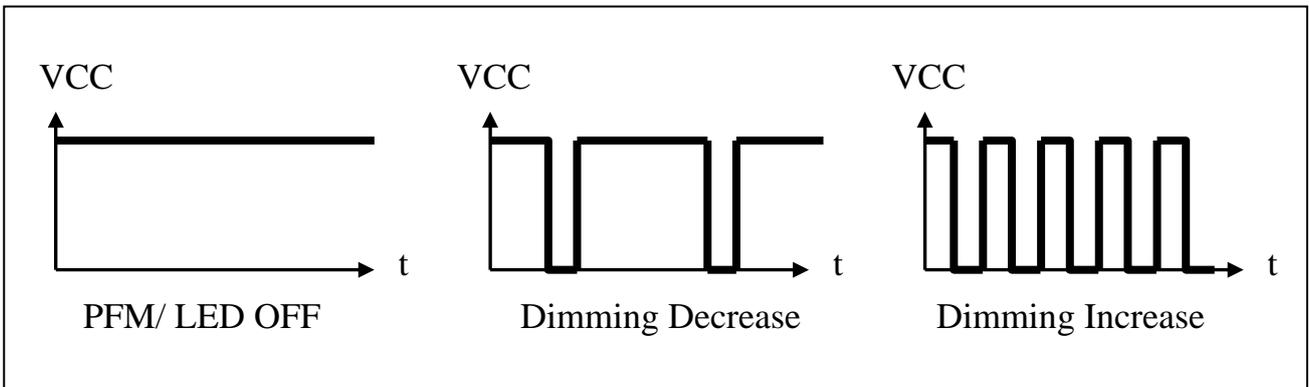


Figure 4 PFM Dimming Signals

2.3 Pin Usage on Renesas Starter Kit for R8C/2D

■ **Pin Usage on R8C/2D**

Pin No.	Pin Label	Function
42	TRFO00	Using Timer RF for PFM output
79	P3_7	I/O pin for key input (manual dimming)
44	INT0n	Interrupt pin for key input (power on/ off)
57	AN8	Analog to Digital Converter for MIC in voltage detection
56	AN9	Analog to Digital Converter for LED current detection (PFM control for dimming)
55	AN10	Analog to Digital Converter for CDS in voltage detection

Table 1 Pin Usage on R8C/2D

■ **Pin reference connect point on Renesas Starter Kit for R8C/2D**

Usage Pin Label	Connector on RSK R8C/2D	Pin No. in Connector of RSK
TRFO00	RSK R8C/2D CPU Board: J3	Pin 2
P3_7	RSK R8C/2D CPU Board: JA2	Pin 11
INT0n	RSK R8C/2D CPU Board: JA2	Pin 7
AN8	RSK R8C/2D CPU Board: JA5	Pin 9
AN9	RSK R8C/2D CPU Board: JA5	Pin 10
AN10	RSK R8C/2D CPU Board: JA5	Pin 11

Table 2 Reference connect point on RSK

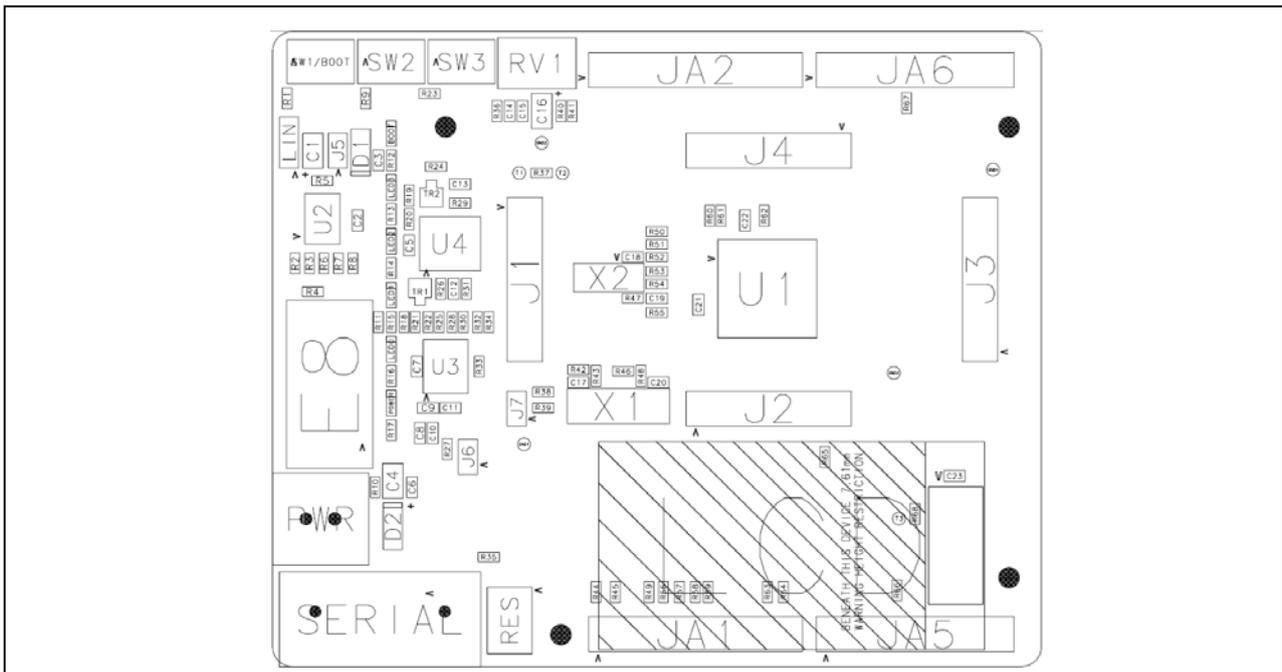


Figure 5 Connectors placement of Renesas Starter Kit CPU Board for R8C/2D

3. Reference Schematics

3.1 R8C/2D Control Schematics

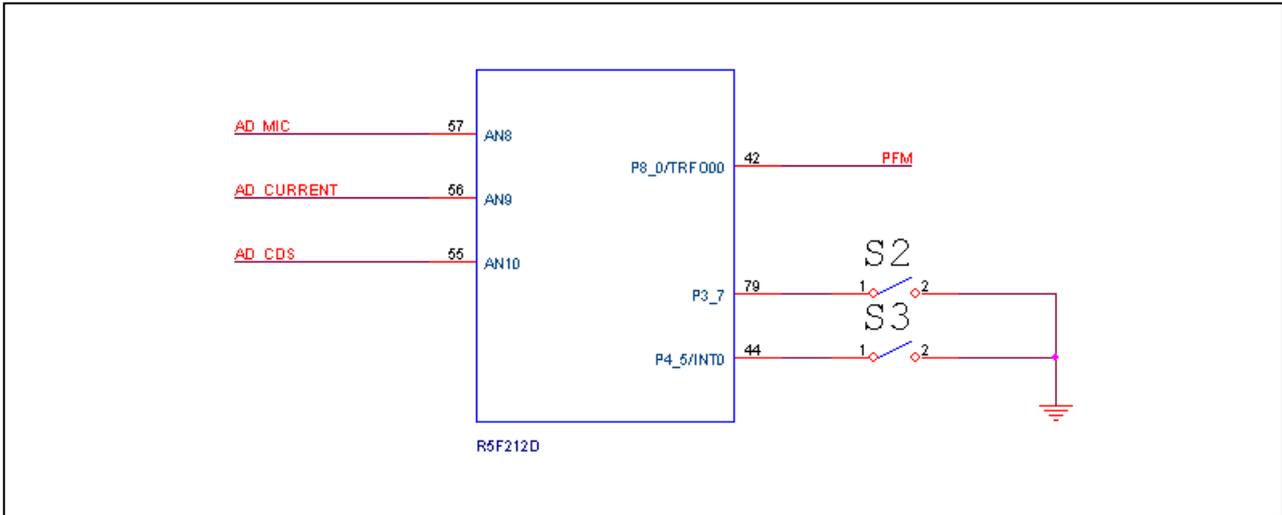


Figure 6 R8C/2D Control Schematics

3.2 12V and 5V DC Power Supply

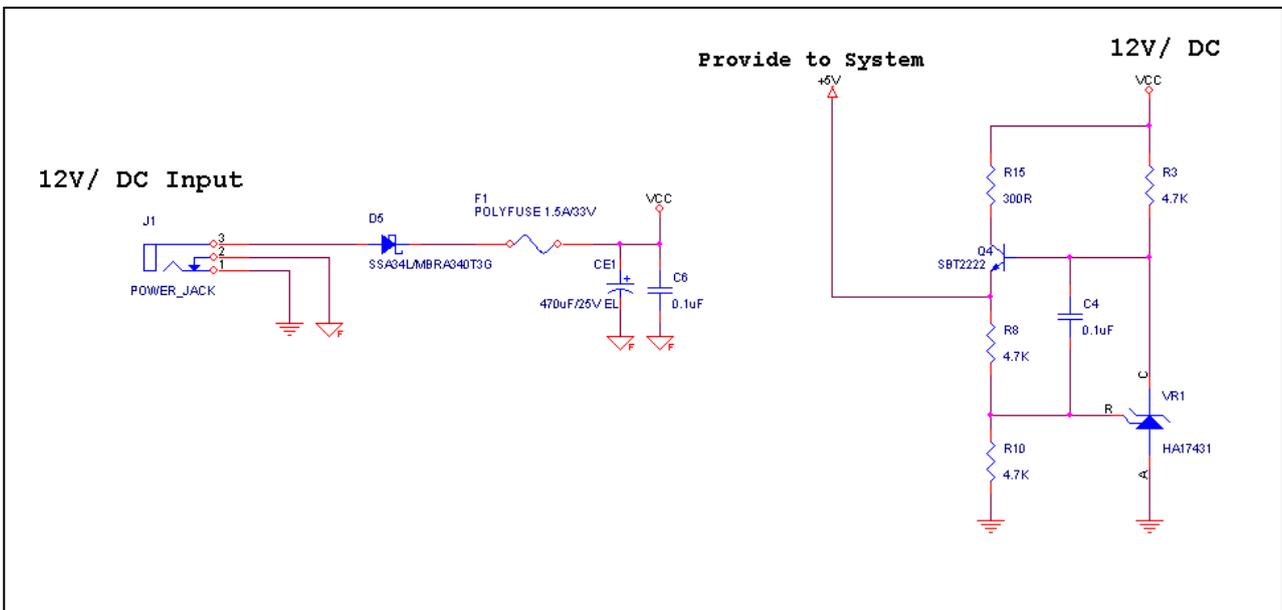


Figure 7 System Power Supply

3.3 LED Power Supply and PFM Control

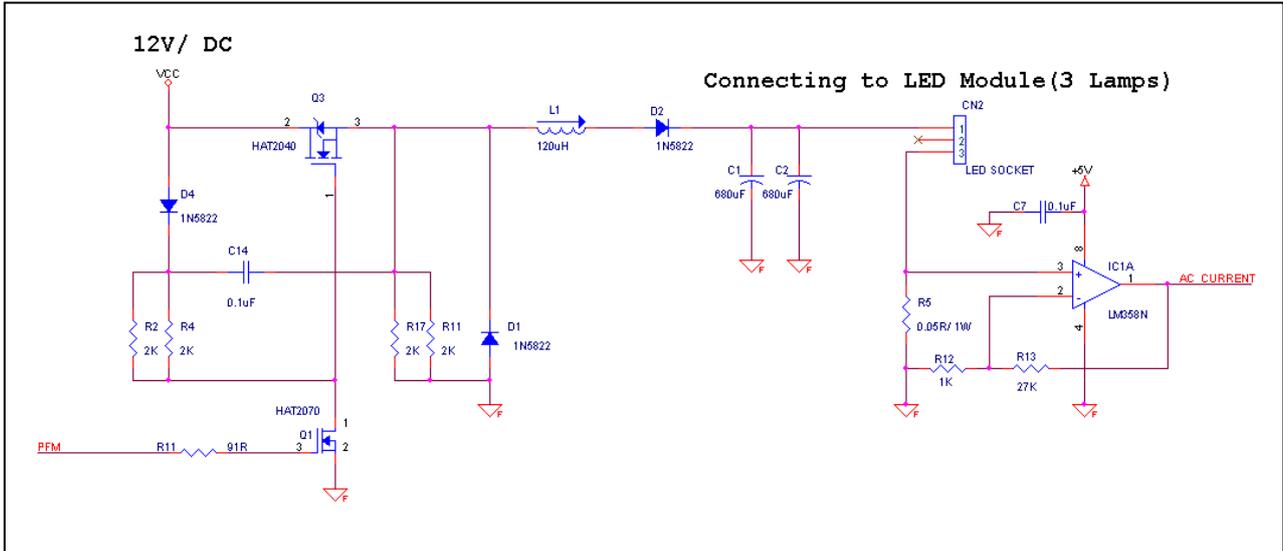


Figure 8 PFM Control Circuit

3.4 Sound Sensor Control

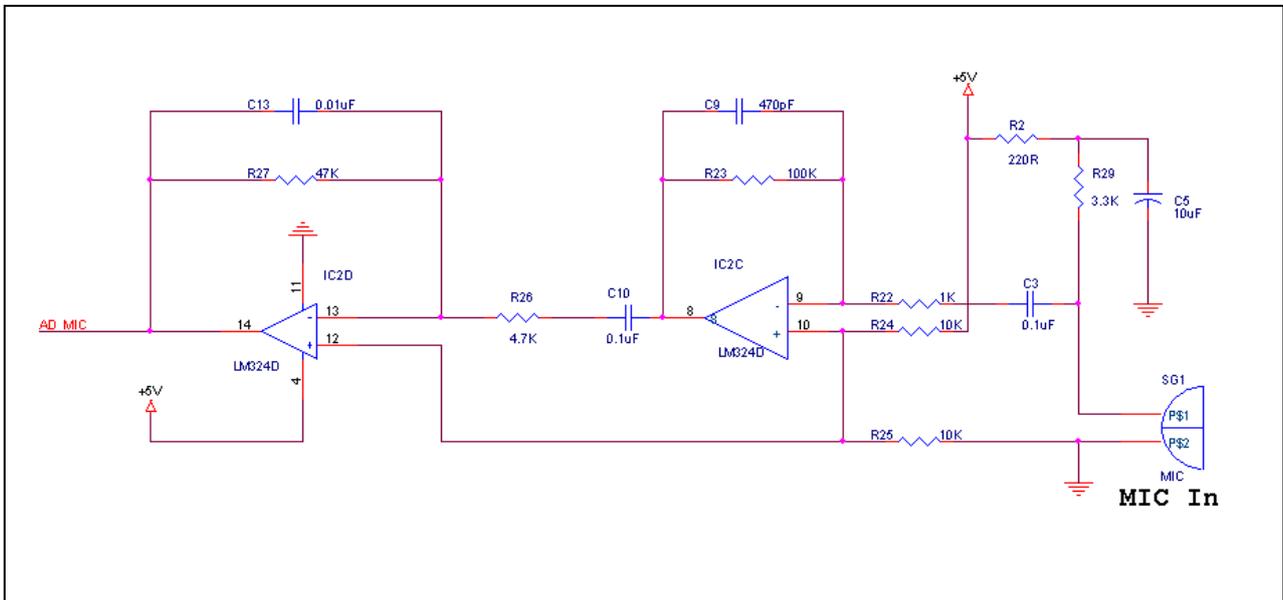


Figure 9 MIC in Sensing Circuit

3.5 LED Power Supply and PFM Control

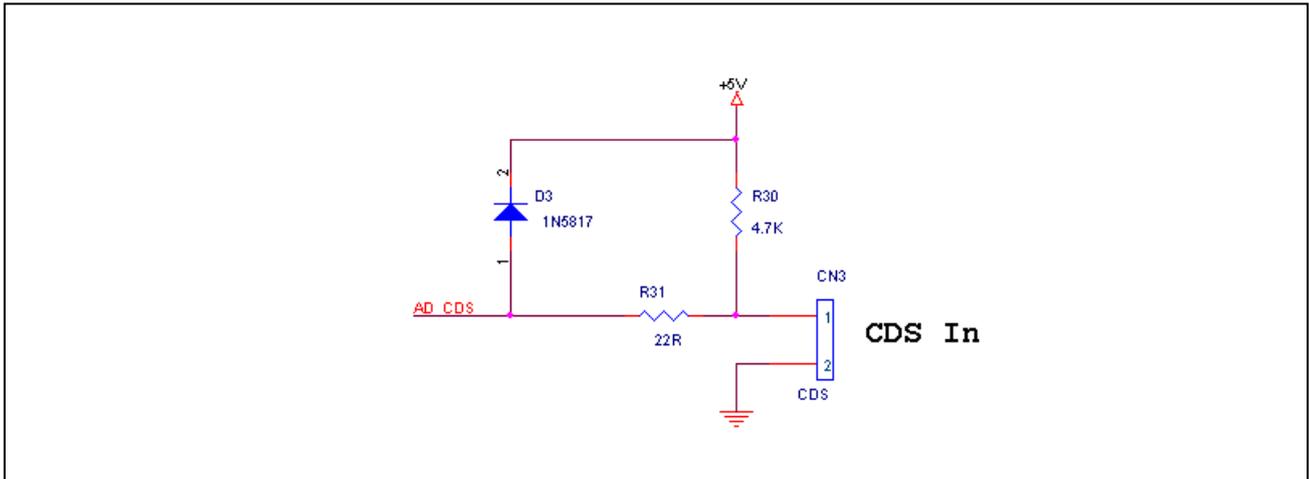


Figure 10 CDS Sensing Circuit

4 Program Flow Chart

■ Program flow chart of main() : System main routine

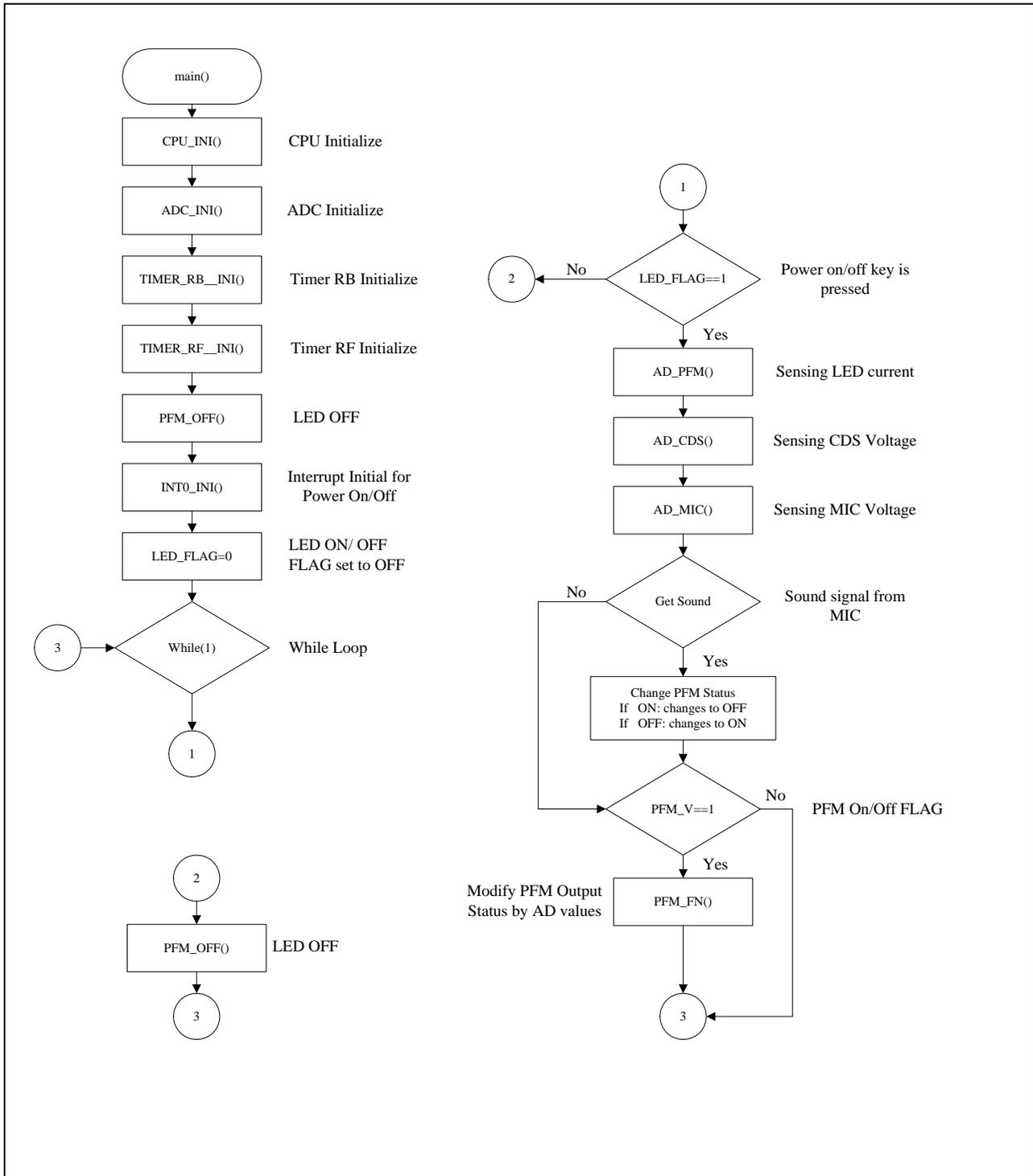


Figure 11 Program flow chart of main()

■ Program flow chart of into_int(): Power on/ off control

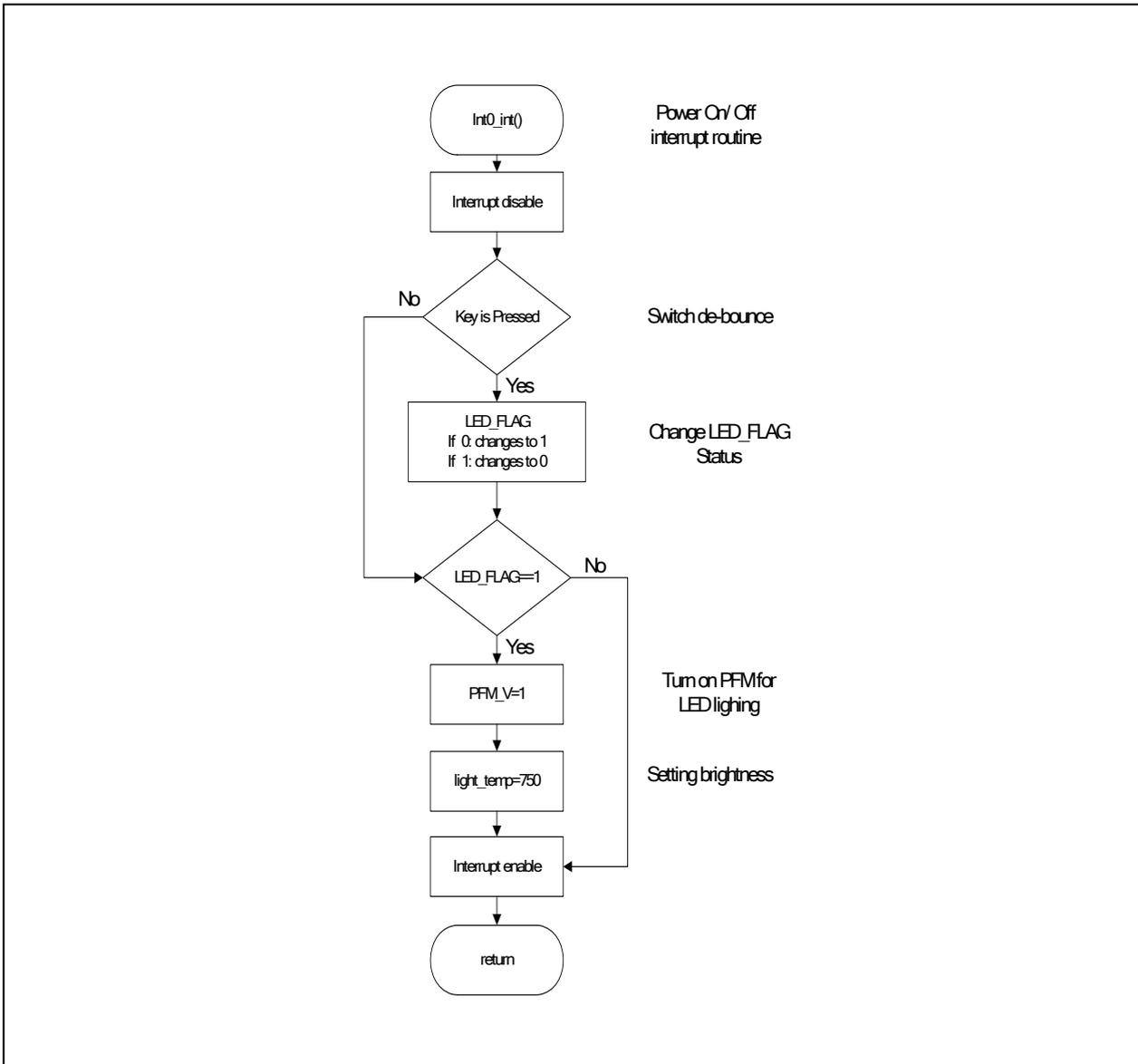


Figure 12 Program flow chart of int0_int ()

■ Program flow chart of PFM_FN(): PFM control for dimming- 1/2

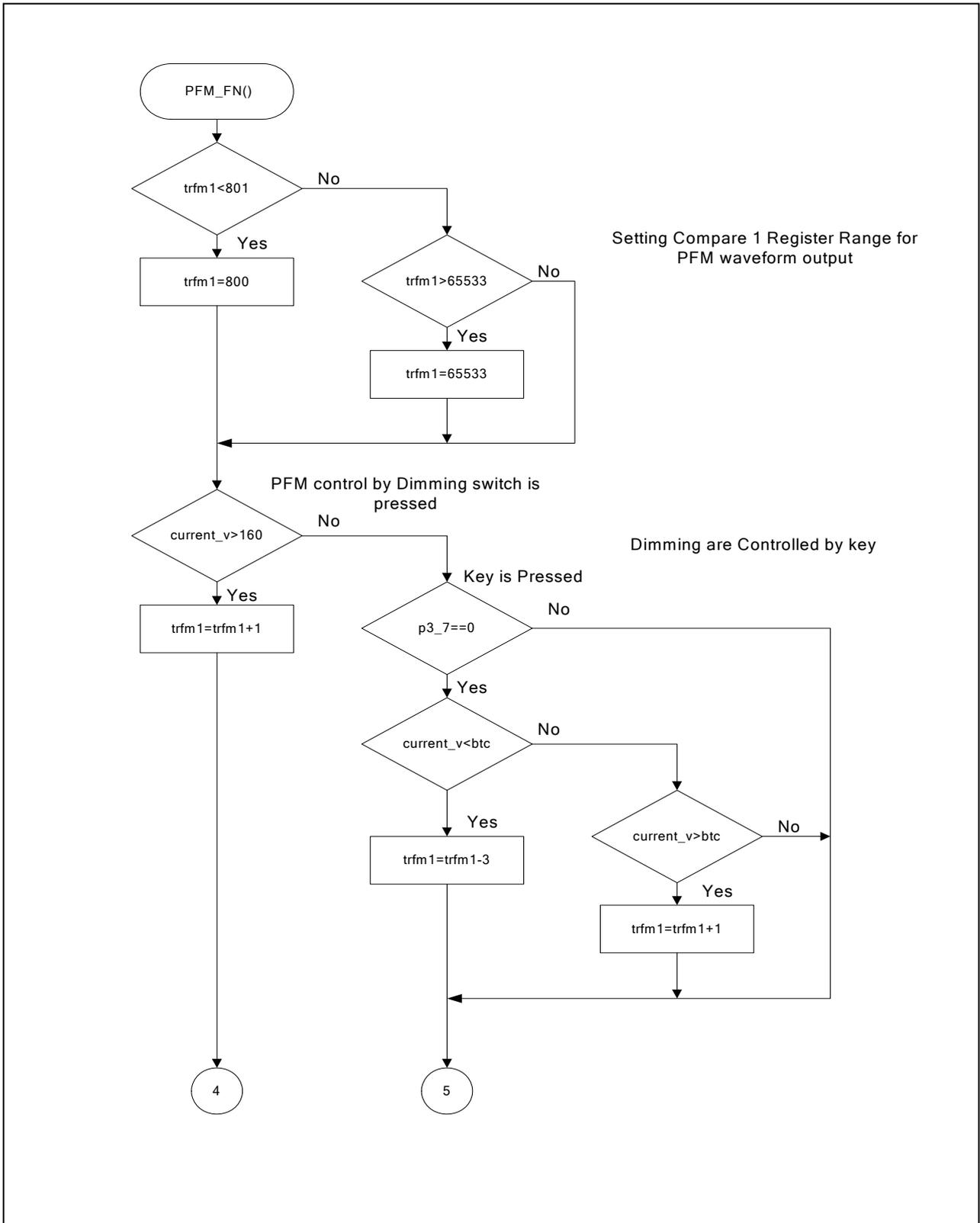


Figure 13 Program flow chart of PFM_FN() -1/2

■ Program flow chart of PFM_FN(): PFM control for dimming- 2/2

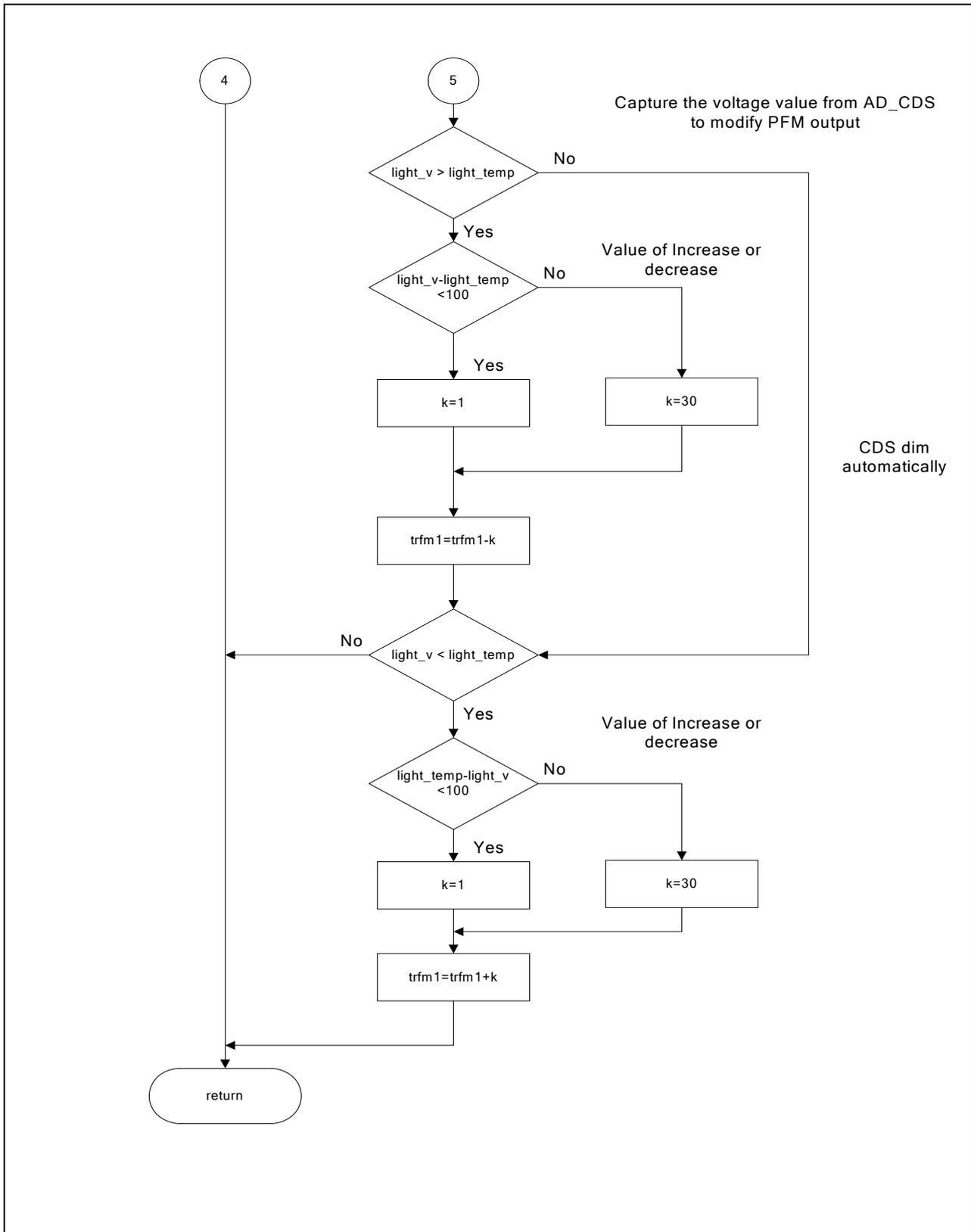


Figure 14 Program flow chart of PFM_FN () -2/2

5 Website and Support

Renesas Technology Website

<http://www.renesas.com/>

Inquiries

<http://www.renesas.com/inquiry>

csc@renesas.com

Revision Record

Rev.	Date	Description	
		Page	Summary
1.00	Mar.31.10	—	First edition issued

All trademarks and registered trademarks are the property of their respective owners.

Notes regarding these materials

1. This document is provided for reference purposes only so that Renesas customers may select the appropriate Renesas products for their use. Renesas neither makes warranties or representations with respect to the accuracy or completeness of the information contained in this document nor grants any license to any intellectual property rights or any other rights of Renesas or any third party with respect to the information in this document.
2. Renesas shall have no liability for damages or infringement of any intellectual property or other rights arising out of the use of any information in this document, including, but not limited to, product data, diagrams, charts, programs, algorithms, and application circuit examples.
3. You should not use the products or the technology described in this document for the purpose of military applications such as the development of weapons of mass destruction or for the purpose of any other military use. When exporting the products or technology described herein, you should follow the applicable export control laws and regulations, and procedures required by such laws and regulations.
4. All information included in this document such as product data, diagrams, charts, programs, algorithms, and application circuit examples, is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas products listed in this document, please confirm the latest product information with a Renesas sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas such as that disclosed through our website. (<http://www.renesas.com>)
5. Renesas has used reasonable care in compiling the information included in this document, but Renesas assumes no liability whatsoever for any damages incurred as a result of errors or omissions in the information included in this document.
6. When using or otherwise relying on the information in this document, you should evaluate the information in light of the total system before deciding about the applicability of such information to the intended application. Renesas makes no representations, warranties or guaranties regarding the suitability of its products for any particular application and specifically disclaims any liability arising out of the application and use of the information in this document or Renesas products.
7. With the exception of products specified by Renesas as suitable for automobile applications, Renesas products are not designed, manufactured or tested for applications or otherwise in systems the failure or malfunction of which may cause a direct threat to human life or create a risk of human injury or which require especially high quality and reliability such as safety systems, or equipment or systems for transportation and traffic, healthcare, combustion control, aerospace and aeronautics, nuclear power, or undersea communication transmission. If you are considering the use of our products for such purposes, please contact a Renesas sales office beforehand. Renesas shall have no liability for damages arising out of the uses set forth above.
8. Notwithstanding the preceding paragraph, you should not use Renesas products for the purposes listed below:
 - (1) artificial life support devices or systems
 - (2) surgical implantations
 - (3) healthcare intervention (e.g., excision, administration of medication, etc.)
 - (4) any other purposes that pose a direct threat to human life
 Renesas shall have no liability for damages arising out of the uses set forth in the above and purchasers who elect to use Renesas products in any of the foregoing applications shall indemnify and hold harmless Renesas Technology Corp., its affiliated companies and their officers, directors, and employees against any and all damages arising out of such applications.
9. You should use the products described herein within the range specified by Renesas, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas shall have no liability for malfunctions or damages arising out of the use of Renesas products beyond such specified ranges.
10. Although Renesas endeavors to improve the quality and reliability of its products, IC products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Please be sure to implement safety measures to guard against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other applicable measures. Among others, since the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
11. In case Renesas products listed in this document are detached from the products to which the Renesas products are attached or affixed, the risk of accident such as swallowing by infants and small children is very high. You should implement safety measures so that Renesas products may not be easily detached from your products. Renesas shall have no liability for damages arising out of such detachment.
12. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written approval from Renesas.
13. Please contact a Renesas sales office if you have any questions regarding the information contained in this document, Renesas semiconductor products, or if you have any other inquiries.

© 2010. Renesas Technology Corp., All rights reserved.