

Instrumentation Amplifiers

Working with the ISL2853x and ISL2863x High-Precision Instrumentation Amplifiers

Abstract

The ISL2853x and the ISL2863x are zero-drift instrumentation amplifiers (INAs) with nine programmable gain settings and rail-to-rail inputs and outputs. Their low offset, low noise, low gain error, and high CMRR makes these amplifiers ideal for high precision applications over the full industrial temperature range.

Both amplifiers possess the same programmable input stage, whose output terminals, VA+ and VA-, allow for the sensing of the input common-mode voltage. Their outputs, however, differ. The ISL2853x provides a single-ended output and an uncommitted zero-drift op-amp (Figure 1), while the ISL2863x offers a fully differential output (Figure 2).

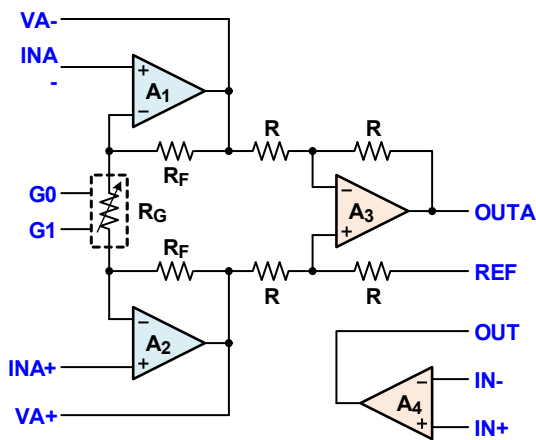


Figure 1. ISL2853x with Single Output and Uncommitted Zero-Drift Op-Amp

 


Figure 2. ISL2863x with Differential Output

Contents

- 1. The Input Stage ..... 3
  - 1.1 Internal Saturation Caution ..... 4
- 2. The Single Output Stage of the ISL2853x ..... 5
- 3. Applications Utilizing the Uncommitted Op-Amp ..... 6
  - 3.1 Buffer for Weak Voltage Reference ICs ..... 6
  - 3.2 Buffer for a Supply-Derived Reference Voltage ..... 7
  - 3.3 Active Filter Buffer for a Supply-Derived Reference Voltage ..... 7
  - 3.4 Feedback Integrator for Ultra-Low Input Bandwidth Limit ..... 8
  - 3.5 Single-Ended to Differential Output Converter ..... 9
- 4. Summary ..... 10
- 5. The Differential Output Stage of the ISL2863x ..... 10
- 6. Conclusion ..... 12
- 7. Revision History ..... 12

List of Figures

- Figure 1. ISL2853x with Single Output and Uncommitted Zero-Drift Op-Amp ..... 1
- Figure 2. ISL2863x with Differential Output ..... 1
- Figure 3. Differential Input Stage ..... 3

---

Figure 4.	1k $\Omega$ Symmetrical Strain Gauge Sensor . . . . .	5
Figure 5.	$V_{ID} = \pm 17\text{mV}$ Over $\pm 10\Omega$ Resistance Change . . . . .	5
Figure 6.	ISL2853x Output Stage . . . . .	5
Figure 7.	In a Dual-Supply Design Connect REF to GND . . . . .	6
Figure 8.	In a Single-Supply Design Make $V_{REF} = V_{CC}/2$ . . . . .	6
Figure 9.	Buffering a Voltage Reference that Lacks Current Sinking Capability . . . . .	6
Figure 10.	Proper Reference Buffering for High PSRR in Ratio-Metric Applications. . . . .	7
Figure 11.	Improved Reference Buffering with Second-Order Active Low-Pass Filter . . . . .	7
Figure 12.	Feedback Integrator with A4 Achieves Extremely Low Cut-Off Frequencies with DC-Coupled Inputs. . . . .	8
Figure 13.	Differential Output Configuration with A4 Doubles Signal Dynamic Range . . . . .	9
Figure 14.	Differential Output Stage of ISL2863x . . . . .	11
Figure 15.	Evaluation Board Schematic . . . . .	12

## Related Literature

For a full list of related documents, visit our website:

- [ISL28533](#), [ISL28534](#), [ISL28535](#), [ISL28633](#), [ISL28634](#), [ISL28635](#) device pages

## 1. The Input Stage

An instrumentation amplifier amplifies a small differential input signal,  $V_{ID}$ , that is superimposed on a much larger common-mode voltage,  $V_{CM}$ . To avoid output saturation, its differential input stage must have two distinguished gain factors, one for common-mode signals,  $G_{CM}$ , and one for differential signals,  $G_{Diff}$ .

 


Figure 3. Differential Input Stage

Signal convention assigns each input the common-mode component and half the differential signal component:

$$(EQ. 1) \quad V_{INA+} = V_{CM} + V_{ID}/2 \quad \text{and} \quad V_{INA-} = V_{CM} - V_{ID}/2$$

The difference between the input voltages is the differential input voltage,  $V_{ID}$ :

$$(EQ. 2) \quad V_{INA+} - V_{INA-} = V_{CM} + V_{ID}/2 - (V_{CM} - V_{ID}/2) = V_{ID}$$

Due to op-amp action, the signals at the non-inverting inputs of the amplifier also appear at their inverting inputs. If  $V_{ID} = 0V$ ,  $V_{CM}$  appears at the inverting inputs across  $R_G$ , which means no current is flowing through the  $R_F$ - $R_G$  resistor network. This also means that  $V_{CM}$  is present at  $VA+$  and  $VA-$ , indicating zero differential output.

The input gain for common-mode signals is therefore 1:  $G_{CM} = 1$ .

If  $V_{INA+}$  is larger than  $V_{INA-}$ , the resulting positive  $V_{ID}$  also occurs across  $R_G$ , causing a current,  $I_1$ , to flow from  $VA+$  to  $VA-$ :

$$(EQ. 3) \quad I_1 = \frac{V_{INA+} - V_{INA-}}{R_G} = \frac{V_{ID}}{R_G}$$

The differential output voltage due to this current is:

$$(EQ. 4) \quad V_{OD1} = V_{VA+} - V_{VA-} = I_1(R_G + 2R_F)$$

Inserting [Equation 3](#) into [Equation 4](#) and solving for differential output-to-input change gives the differential gain:

$$(EQ. 5) \quad \frac{V_{OD1}}{V_{ID}} = G_{DIFF} = 1 + \frac{2R_F}{R_G}$$

While standard instrumentation amplifiers require the use of precision resistors to minimize gain error, the ISL2853x and ISL2863x provide up to nine on-chip programmable gain settings, listed in [Table 1](#).

**Table 1. Programmable Gain Settings**

G1	G0	Gain (V/V)		
		ISL28533 ISL28633	ISL28534 ISL28634	ISL28535 ISL28635
0	0	1	1	1
0	Z	2	2	100
0	1	4	10	120
Z	0	5	50	150
Z	Z	10	100	180
Z	1	20	200	200
1	0	40	300	300
1	Z	50	500	500
1	1	100	1000	1000

**Note:** Ground = 0, VCC = 1, and Z = floating.

The three states of the gain setting logic can be accomplished through pin-strapping the G0 and G1 inputs to either of the supply rails (Ground for 0, VCC for 1) and floating for Z (high-impedance). Internal high-impedance pull-up and pull-down resistors ensure the validity of the high-impedance state. If G0 and G1 are controlled by a microcontroller, the high-impedance state is accomplished by switching an output port into input mode while disabling the internal pull-up and pull-down resistors of the controller.

### 1.1 Internal Saturation Caution

To prevent instrumentation from internal saturation, it is good to know the absolute voltages at VA+ or VA-. This allows for determining the available signal headroom, which is the distance between the common-mode potential and the upper and lower supply rails, and therefore the calculation of the maximum allowable gain setting.

The absolute voltages at VA+ and VA- are easily found when considering their corresponding input voltages,  $V_{INA+}$  and  $V_{INA-}$ , in [Equation 1 on page 3](#). The common-mode component,  $V_{CM}$ , is amplified by the common-mode gain,  $G_{CM} = 1$ , and the differential signal component,  $V_{ID}/2$ , is amplified by the differential gain,  $G_{Diff}$ , which results in:

$$(EQ. 6) \quad V_{VA+} = V_{CM} + \frac{V_{ID}}{2} G_{Diff} \quad \text{and} \quad V_{VA-} = V_{CM} - \frac{V_{ID}}{2} G_{Diff}$$

To avoid internal saturation, the voltage at VA+ must equal to or smaller than the positive supply voltage,  $V_+$ , and the voltage at VA- must be equal to or greater than the negative supply voltage,  $V_-$ . Then, substituting  $V_{VA+}$  and  $V_{VA-}$  in [Equation 6](#) with  $V_+$  and  $V_-$  respectively, and solving for  $G_{Diff}$ , yields the maximum allowable gain setting:

$$(EQ. 7) \quad G_{Diff} \leq 2 \frac{V_+ - V_{CM}}{V_D} \quad \text{and} \quad G_{Diff} \leq 2 \frac{V_{CM} - V_-}{V_D}$$

**Calculation Example 1:**

Figure 4 depicts a symmetrical strain gauge sensor with 1kΩ base resistance with a maximum change in resistance of ΔR = ±10Ω. Due to bridge symmetry, the V<sub>CM</sub> of the bridge = 1.65V.

 


Figure 4. 1kΩ Symmetrical Strain Gauge Sensor

 


Figure 5. V<sub>ID</sub> = ±17mV Over ±10Ω Resistance Change

Powered by a single 3.3V system supply, the ±10Ω span creates a V<sub>ID</sub> span of ±17mV (Figure 5). Using Equation 7, the maximum gain setting is:

$$G_{Diff} \leq 2 \frac{3.3V - 1.65V}{17mV} = 194 V/V$$

Table 1 shows that of the three single-output instrumentation amplifiers, the amplifier with the closest lower gain setting is the ISL28355 with 180V/V. This gain setting allows G0 and G1 to be floating.

Using Equation 6, we can calculate the absolute voltages at VA+ and VA- to ensure they are within the supply rails:

$$V_{VA+} = 1.65V + \frac{17mV}{2} \cdot 180 = 3.18V \quad \text{and} \quad V_{VA-} = 1.65V - \frac{17mV}{2} \cdot 180 = 0.12V$$

**2. The Single Output Stage of the ISL2853x**

The output stage of the ISL2853x is a difference amplifier that removes the input common-mode voltage, V<sub>CM</sub>, amplifies the differential output of the input stage, and then adds a common-mode voltage in the form of V<sub>REF</sub> to the output voltage at OUTA (Figure 6).

 


Figure 6. ISL2853x Output Stage

To derive its transfer function, we derive the voltages at the inverting and non-inverting of the inputs op-amp with:

$$V_n = \frac{V_{A-} + V_{OUTA}}{2} \quad \text{and} \quad V_p = \frac{V_{A+} + V_{REF}}{2}$$

Due to op-amp action, V<sub>n</sub> = V<sub>p</sub>, it follows that V<sub>A-</sub> + V<sub>OUTA</sub> = V<sub>A+</sub> + V<sub>REF</sub>, and solving for V<sub>OUTA</sub> gives:

(EQ. 8) 
$$V_{OUTA} = V_{A+} - V_{A-} + V_{REF}$$

From [Equation 5](#) we derive that  $V_{VA+} - V_{VA-} = G_{DIFF} \cdot V_{ID}$  and inserting this term into [Equation 8](#) gives:

$$(EQ. 9) \quad V_{OUTA} = G_{DIFF} \cdot V_{ID} + V_{REF}$$

Therefore, the INA output voltage is the differential input voltage amplified by the differential gain setting plus the added common-mode voltage,  $V_{REF}$ .

In dual supply applications, REF is usually connected to ground ([Figure 7](#)). In a single-supply design however,  $V_{REF}$  should be set to  $V_{CC}/2$  to allow for a symmetrical output swing of  $V_{OUTA}$  ([Figure 8](#)).

 


Figure 7. In a Dual-Supply Design Connect REF to GND

 


Figure 8. In a Single-Supply Design Make  $V_{REF} = V_{CC}/2$

**Note:** For clarity, any decoupling capacitors have been omitted. With regards to [Figure 8](#), some applications show the output of a voltage reference IC (VREF) buffered by an op-amp. This is usually not necessary but only required if the reference circuit lacks current drive or the capability of sinking current. VREFs are specially designed to provide a stable, low-noise voltage source with low source impedance.

However, there are applications where the reference input of the INA is not driven by a VREF, but with an op-amp in various amplifier configurations. In these cases, the uncommitted op-amp, A4, of the ISL2853x is extremely useful.

### 3. Applications Utilizing the Uncommitted Op-Amp

#### 3.1 Buffer for Weak Voltage Reference ICs

[Figure 9](#) depicts the op-amp as a buffer for weak voltage reference ICs. Here, weak means the IC lacks in output current drive, or in the ability of sinking current.


 


Figure 9. Buffering a Voltage Reference that Lacks Current Sinking Capability

 

The signal diagram on the right in [Figure 9](#) shows that the input current to the REF terminal of the INA changes with the output voltage. A robust VREF can supply this current directly into the REF terminal. In the case of a weak VREF however, the op-amp provides the required current drive as well as sinking capability, while the output current of the VREF is reduced to leakage level.

### 3.2 Buffer for a Supply-Derived Reference Voltage

Ratio-metric circuits derive their reference voltage from the system supply to ensure that  $V_{REF} = V_S/2$ , independently of the absolute supply voltage. [Figure 10](#) shows the level of  $V_{REF}$  being established with a high-impedance voltage divider to minimize current loading on the supply.

To maintain a high PSRR, a large 100µF capacitor,  $C_{IN}$ , is connected parallel to  $R_2$ . This capacitor, in combination with the parallel circuit of  $R_1$  and  $R_2$ , forms a low-pass filter for the supply voltage ripples. Its -3dB frequency is calculated with  $f_{-3dB} = 1/(2\pi R_1 || R_2 C_{IN})$ . For the circuit below,  $f_{-3dB} = 32\text{mHz}$ .


 


Figure 10. Proper Reference Buffering for High PSRR in Ratio-Metric Applications

Although the op-amp operates at unity-gain, a feedback resistor,  $R_F$ , is required to minimize the input offset due to bias currents. Its value should match the parallel combination of  $R_1$  and  $R_2$ :  $R_F = R_1 || R_2$ . The small capacitor,  $C_F$ , minimizes resistor noise.
 
### 3.3 Active Filter Buffer for a Supply-Derived Reference Voltage

A more elegant solution, using much smaller capacitor values, is the second-order active low-pass filter in [Figure 11](#). Making  $C_2 = 2 C_1$  increases the quality factor to  $Q = \sqrt{C_2/4C_1} = 0.707$ , generating a sharper pass-to-stop band transition. Despite the large difference in capacitance, both circuits provide a PSRR of about -60dB at 20Hz.




Design Equations  
 $C_2 = 2C_1$   
 $R_3 = 1/(2\pi f_c \sqrt{C_1 C_2})$   
 $R_1, R_2 = 2R_3$

Figure 11. Improved Reference Buffering with Second-Order Active Low-Pass Filter

### 3.4 Feedback Integrator for Ultra-Low Input Bandwidth Limit

Medical sensors often require the lower bandwidth limit of less than 0.2Hz. Configuring A4 as a simple integrator and placing it into the feedback loop between the output of INA, OUTA, and its reference terminal, REF, transforms the lower bandwidth limit of the inputs of INA to very low frequencies (Figure 12). The -3dB cutoff frequency is determined by the R-C time constant of the integrator with  $f_{-3dB} = 1/(2\pi R_F C_F)$ .

**Note:** In this 5V application, the DC-bias voltage of the integrator is  $V_B = V_{CC}/2 = 2.5V$ .

 

**Figure 12. Feedback Integrator with A4 Achieves Extremely Low Cut-Off Frequencies with DC-Coupled Inputs**

In the standard single-supply configuration of Figure 8, the output voltage of the INA is

$V_{OUTA} = V_{ID} \cdot G_{DIFF} + V_{REF}$ , (see Equation 9) with  $V_{REF} = V_S/2$  as a fixed DC-bias potential. In this application however,  $V_{REF}$  is the output voltage of the integrator and therefore, frequency dependent:

$V_{REF} = V_B (1 + X_{CF}/R_F) - V_{OUTA} X_{CF}/R_F$ . Inserting this new  $V_{REF}$  term into Equation 9 and solving for  $V_{OUTA}$  gives:

$$V_{OUTA} = V_{ID} \cdot G_{DIFF} + V_B (1 + X_{CF}/R_F) - V_{OUTA} X_{CF}/R_F$$

Then, collecting terms yields:

$$V_{OUTA} (1 + X_{CF}/R_F) = V_{ID} \cdot G_{DIFF} + V_B (1 + X_{CF}/R_F)$$

And solving for  $V_{OUTA}$  results in:

$$V_{OUTA} = V_{ID} \cdot \frac{G_{DIFF}}{1 + X_{CF}/R_F} + V_B \cdot \frac{1 + X_{CF}/R_F}{1 + X_{CF}/R_F}$$

or

$$V_{OUTA} = V_{ID} \cdot G_{DIFF} \cdot \frac{1}{1 + X_{CF}/R_F} + V_B$$

This equation confirms that the actual DC-bias voltage ( $V_B$ ), remains frequency independent.

To express the output voltage as a function of the -3dB cutoff frequency, we substitute  $X_{CF}$  with  $1/(j\omega C)$ , which turns the above fraction into:

$$\frac{1}{1 + X_{CF(f)}/R_F} = \frac{jf/f_C}{1 + jf/f_C} \quad \text{with} \quad f_C = \frac{1}{2\pi R_F C_F}$$



Then, insert this term into the output voltage equation:

$$(EQ. 10) \quad V_{OUTA(f)} = V_{ID(f)} \cdot G_{DIFF} \cdot \frac{jf/f_C}{1 + jf/f_C} + V_B$$

Therefore, the total differential gain is:

$$(EQ. 11) \quad \frac{\Delta V_{OUTA(f)}}{\Delta V_{ID(f)}} = G_{DIFF} \cdot \frac{jf/f_C}{1 + jf/f_C}$$

or in dB terms:

$$(EQ. 12) \quad \left| \frac{V_{OUTA(f)} - V_B}{V_{ID(f)}} \right| (dB) = 20 \log_{10} \left( G_{DIFF} \cdot \frac{f/f_C}{\sqrt{1 + (f/f_C)^2}} \right)$$

Plotting Equation 12 over frequency yields the gain response of Figure 12. This shows that the total differential signal gain is 0V/V at DC, and only the bias voltage,  $V_B$ , is present at OUTA. Then, with rising frequency, the gain increases until it reaches the initial  $G_{DIFF}$  value at  $f_C$ .

The benefit of this solution is that it requires only small capacitor values to achieve extremely low input bandwidth limits, while leaving the INA inputs DC-coupled. The conventional approach of AC-coupling the inputs, requires much larger capacitor values of 100µF and more to achieve the same low-frequency cutoff.

### 3.5 Single-Ended to Differential Output Converter

Configuring A4 as a simple integrator and placing it into the feedback loop between the output of INA, OUTA, and its reference terminal, REF, converts an INA with a single output into an INA with a differential output. The purpose of this solution is to double the dynamic output signal range of the INA; therefore increasing the resolution of the amplified input signal (Figure 13).

 


Figure 13. Differential Output Configuration with A4 Doubles Signal Dynamic Range

For better understanding, we compare the output dynamic range of the single output with the one of the differential output solution. The output dynamic range of the INA with single output is:

$$(EQ. 13) \quad V_{OUTA} = G_{DIFF} \cdot V_{ID} + V_{REF}$$

[Figure 13](#) depicts the positive terminal of the differential output as  $V_{OUTA}$ , and the negative terminal as  $\overline{V_{OUTA}}$ . The difference amplifier, operating at unity gain, buffers the difference between  $V_{OUTA}$  and  $V_S$  and drives the REF terminal of the INA and the negative output terminal:

$$(EQ. 14) \quad V_{REF} = \overline{V_{OUTA}} = V_S - V_{OUTA}$$

Inserting this  $V_{REF}$  term into the single output equation and solving for  $V_{OUTA}$  gives:

$$(EQ. 15) \quad V_{OUTA} = \frac{G_{DIFF} \cdot V_{ID}}{2} + \frac{V_S}{2}$$

Due to [Equation 14](#), this makes the negative output voltage:

$$(EQ. 16) \quad \overline{V_{OUTA}} = -\frac{G_{DIFF} \cdot V_{ID}}{2} + \frac{V_S}{2}$$

[Equations 15](#) and [16](#) show that the signal dynamic of both,  $V_{OUTA}$  and  $\overline{V_{OUTA}}$ , is only half that of the single output amplifier; therefore, yielding only half of the possible output differential range,  $V_{OD}$ . This is indicated by the dotted waveforms in [Figure 13](#), in comparison to the red waveform of the single output INA.

To use the full dynamic range of each output, the programmable gain,  $G_{DIFF}$ , must be doubled to yield:

$$(EQ. 17) \quad V_{OUTA} = \frac{V_S}{2} + G_{DIFF} \cdot V_{ID} \quad \text{and} \quad \overline{V_{OUTA}} = \frac{V_S}{2} - G_{DIFF} \cdot V_{ID}$$

The resulting differential output voltage is twice the dynamic range of the single output INA:

$$(EQ. 18) \quad V_{OD} = V_{OUTA} - \overline{V_{OUTA}} = 2G_{DIFF} \cdot V_{ID}$$


## 4. Summary

The uncommitted op-amp (A4) of the ISL2853x family of single output INAs is a nice little tool, which, as demonstrated, can help satisfy a wide variety of signal conditioning requirements.

## 5. The Differential Output Stage of the ISL2863x

[Figure 14](#) depicts the differential output stage of the ISL2863x family of INAs with programmable gain settings. The output of the first stage,  $V_{OD1}$ , is the input for the differential output stage. To find the equations for the differential and the individual output voltages, we define the three key voltages,  $V_{n3}$ ,  $V_{n4}$ , and  $V_{n5}$ :

$$V_{n3} = \frac{V_{A-} + V_{OUTA+}}{2} \quad V_{n4} = \frac{V_{A+} + V_{OUTA-}}{2} \quad V_{n5} = \frac{V_{OUTA+} + V_{OUTA-}}{2}$$

 

**Figure 14. Differential Output Stage of ISL2863x**

Due to op-amp action,  $V_{n3} = V_{n4}$  and  $V_{n5} = V_{REF}$ , which results in:

$$(EQ. 19) \quad \frac{V_{A-} + V_{OUTA+}}{2} = \frac{V_{A+} + V_{OUTA-}}{2}$$

and

$$(EQ. 20) \quad V_{REF} = \frac{V_{OUTA+} + V_{OUTA-}}{2}$$

Solving [Equation 19](#) for the differential output voltage gives:

$$(EQ. 21) \quad V_{OUTA+} - V_{OUTA-} = V_{A+} - V_{A-}$$

Because  $V_{OUTA+} - V_{OUTA-} = V_{OD2}$  and  $V_{A+} - V_{A-} = V_{OD1} = G_{DIFF} \cdot V_{ID}$ , the differential output voltage is:

$$(EQ. 22) \quad V_{OD2} = G_{DIFF} \cdot V_{ID}$$

To determine the actual voltage at OUT+, we solve [Equation 20](#) for  $V_{OUTA-}$ , insert the result into [Equation 21](#), and solve for  $V_{OUTA+}$ :

$$(EQ. 23) \quad V_{OUTA+} = V_{REF} + \frac{V_{A+} - V_{A-}}{2} = V_{REF} + G_{DIFF} \cdot \frac{V_{ID}}{2}$$

Applying the same steps to  $V_{OUTA-}$  yields:

$$(EQ. 24) \quad V_{OUTA-} = V_{REF} - G_{DIFF} \cdot \frac{V_{ID}}{2}$$

As a final check, we calculate the difference between the two output voltages and receive:

$$V_{OUTA+} - V_{OUTA-} = V_{OD2} = V_{REF} + G_{DIFF} \cdot \frac{V_{ID}}{2} - \left( V_{REF} - G_{DIFF} \cdot \frac{V_{ID}}{2} \right) = G_{DIFF} \cdot V_{ID}$$

This result confirms the correctness of [Equation 22](#).

## 6. Conclusion

The ISL2853x and ISL2863x are high-performance low-noise auto-zero instrumentation amplifiers with on-chip programmable gain settings. The ISL2853x family offers a single output and an uncommitted op-amp that can be configured either as a reference buffer for ratio-metric applications, as a feedback integrator enabling ultra-low cutoff frequencies for DC-coupled inputs, or as a single-to-differential output converter. The ISL2863x family has a differential output, providing you with the widest possible output dynamic range for a high signal resolution.

Hardware circuit development is supported by the ISL2853xEV2Z and ISL2863xEV2Z evaluation boards with associated user guides and board design files. [Figure 15](#) shows the evaluation board schematic.

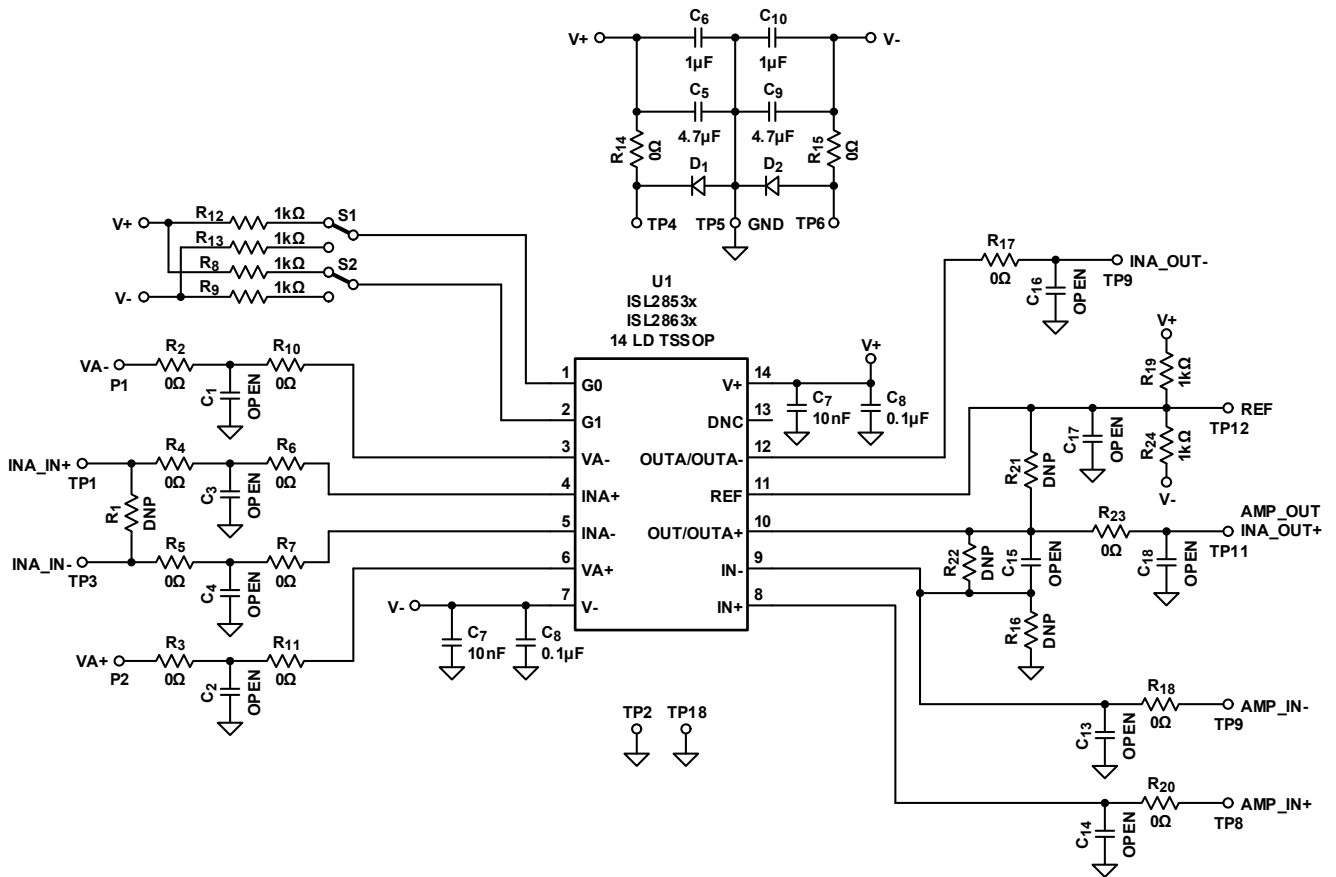


Figure 15. Evaluation Board Schematic

## 7. Revision History

Rev.	Date	Description
1.00	Apr.7.20	Initial release

## IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES (“RENESAS”) PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Rev.1.0 Mar 2020)

### Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan  
[www.renesas.com](http://www.renesas.com)

### Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:  
[www.renesas.com/contact/](http://www.renesas.com/contact/)

### Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.