

Renesas RA Family

Design Guide for Sub-Clock Circuits

Introduction

The sub-clock oscillation circuit has low gain to reduce power consumption. Due to the low gain, there is a risk that noise may cause the MCU to operate erroneously. This document describes how to minimize this risk when using a low capacitive load (CL) resonator.

Target Devices

RA MCU Series

Contents

1. Component Selection.....	2
1.1 External Crystal Resonator selection	2
1.2 Load Capacitor Selection	3
2. Board Design.....	4
2.1 Component Placement.....	4
2.2 Routing – Best Practices	4
2.2.1 XCIN and XCOOUT Routing	4
2.2.2 Ground Shield.....	8
2.2.3 Bottom Ground.....	10
2.2.3.1 Multilayered Boards at Least 1.2 mm Thick	10
2.2.3.2 Multilayered Boards Less than 1.2 mm Thick.....	13
2.2.4 Other Points.....	14
2.2.5 Main Clock Resonator	15
2.3 Routing – Errors to Avoid	16
2.4 Reference Oscillation Circuit Constants and Verified Resonator Operation.....	17
Revision History.....	20

1. Component Selection

Component selection is critical to ensure correct operation of the sub-clock circuit with RA MCU devices. The following sections provide guidance to aid in component selection.

1.1 External Crystal Resonator selection

An external crystal resonator may be used as the sub-clock oscillator source. The external crystal resonator is connected across the XCIN and XCOU pins of the MCU. The frequency of the external crystal resonator for the sub-clock oscillator must be exactly 32.768 kHz. Refer to the Electrical Characteristics section of the MCU Hardware User’s Manual for specific details.

For most RA microcontrollers, an external crystal resonator may be used as the main clock source. The external crystal resonator is connected across the EXTAL and XTAL pins of the MCU. The frequency of the main clock external crystal resonator must be in the frequency range of the main clock oscillator. This document focuses on the sub-clock oscillator, but these selection and design guidelines can also apply to design of the main clock source using an external crystal resonator.

Selection of a crystal resonator will be largely dependent on each unique board design. Due to the large selection of crystal resonators available that may be suitable for use with RA MCU devices, carefully evaluate the electrical characteristics of the selected crystal resonator to determine the specific implementation requirements.

Figure 1 shows a typical example of a crystal resonator connection for the sub-clock source.

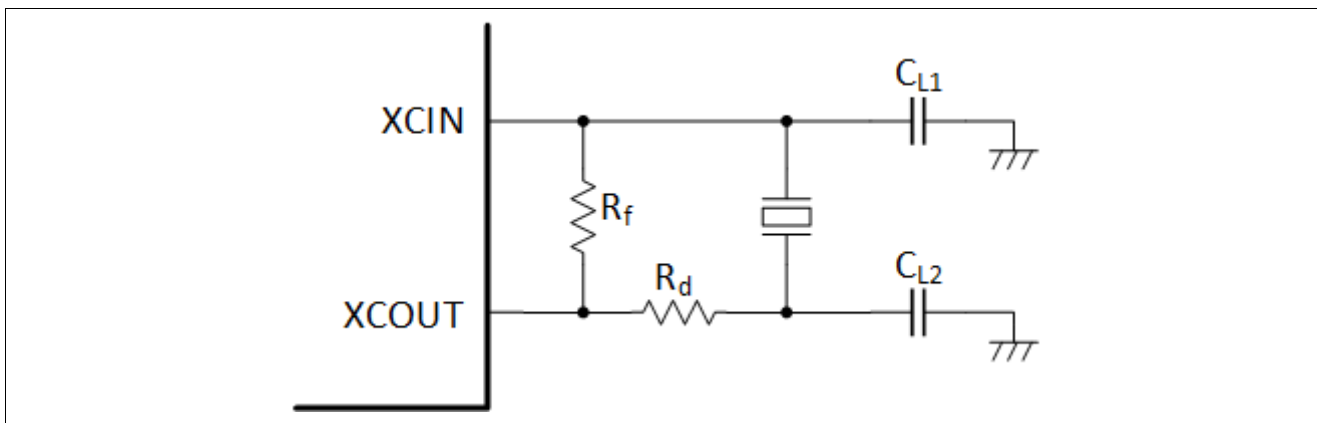


Figure 1. Example Crystal Resonator Connection for the Sub-clock

Figure 2 shows an equivalent circuit for the crystal resonator on the sub-clock circuit.

 


Figure 2. Equivalent Circuit for the Sub-clock Crystal Resonator

Figure 3 shows a typical example of a crystal resonator connection for the main clock source.

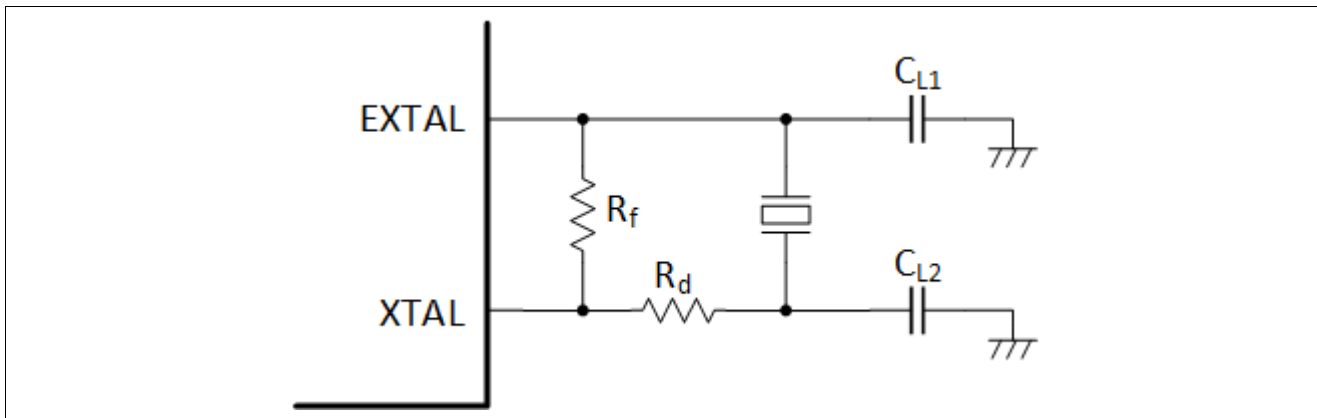


Figure 3. Example Crystal Resonator Connection for the Main Clock

Figure 4 shows an equivalent circuit for the crystal resonator on the main clock circuit.

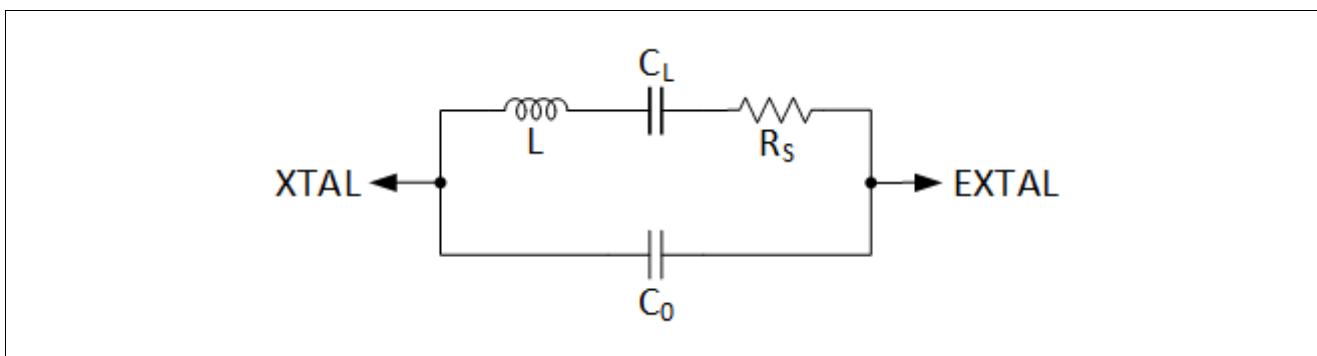


Figure 4. Equivalent Circuit of the Main Clock Crystal Resonator

Careful evaluation must be used when selecting the crystal resonator and the associated capacitors. The external feedback resistor (R_f) and damping resistor (R_d) may be added if recommended by the crystal resonator manufacturer.

Selection of the capacitor values for C_{L1} and C_{L2} will affect the accuracy of the internal clock. To understand the impact of the values for C_{L1} and C_{L2} , the circuit should be simulated using the equivalent circuit of the crystal resonator in the figures above. For more accurate results, also take in to account the stray capacitance associated with the routing between the crystal resonator components.

Some crystal resonators may have limits on the maximum current provided by the MCU. If the current provided to these crystal resonators is too high, the crystal may be damaged. A damping resistor (R_d) may be added to limit the current to the crystal resonator. Refer to the crystal resonator manufacturer to determine the value of this resistor.

1.2 Load Capacitor Selection

Crystal resonator manufacturers will typically provide a load capacitance (C_L) rating for each crystal resonator. For proper operation of the crystal resonator circuit, the board design must match the C_L value of the crystal.

There are several methods to calculate the correct values for the load capacitors C_{L1} and C_{L2} . These calculations take into account the values of the load capacitors and the stray capacitance (C_s) of the board design, which includes the capacitance of the copper traces and the device pins of the MCU.

One equation to calculate C_L is:

$$C_L = \frac{C_{L1} \times C_{L2}}{C_{L1} + C_{L2}} + C_s$$

As an example, if the crystal manufacturer specifies $C_L = 14$ pF, and the board design has a C_S of 5 pF, the resulting C_{L1} and C_{L2} would be 18 pF. Section 2.4 in this document provides details for some verified resonator selections and the associated circuit constants for proper operation.

There are other factors that will affect the performance of the crystal. Temperature, component aging, and other environmental factors may change the performance of a crystal over time and should be accounted for in each specific design.

To ensure proper operation, each circuit should be tested under the expected environmental conditions to guarantee correct performance.

2. Board Design

2.1 Component Placement

Placement of the crystal oscillator, load capacitors, and optional resistors can have a significant impact on the performance of the clock circuit.

For reference within this document, “component side” refers to same side of the PCB design as the MCU, and “solder side” refers to the opposite side of the PCB design from the MCU.

It is recommended to place the crystal resonator circuit as close as possible to the MCU pins on the component side of the PCB. The load capacitors and optional resistors should also be placed on the component side and should be placed between the crystal resonator and the MCU. An alternate placement is to place the crystal resonator between the MCU pins and the load capacitors, but additional ground routing will need to be considered.

Low C_L crystal oscillators are sensitive to fluctuations in temperature, which can affect the stability of the sub-clock circuit. To reduce the influence of temperature on the sub-clock circuit, keep other components which may produce excessive heat away from the crystal oscillator. If copper areas are used as a heat sink for other components, keep the copper heat sink away from the crystal oscillator.

2.2 Routing – Best Practices

This section describes key points on proper layout of a crystal resonator circuit for RA MCU devices.

2.2.1 XCIN and XCOOUT Routing

The following list describes points on routing for XCIN and XCOOUT. Figure 5, Figure 6, and Figure 7 show examples of preferred trace routing for XCIN and XCOOUT. Figure 8 shows an alternate example of trace routing for XCIN and XCOOUT. Identification numbers in the Figures refer to this list.

1. Do not cross the XCIN and XCOOUT traces with other signal traces.
2. Do not add an observation pin or test point to XCIN or XCOOUT traces.
3. Make the XCIN and XCOOUT trace width between 0.1 mm and 0.3 mm. The trace length from the MCU pins to the crystal resonator pins should be less than 10 mm. If 10 mm is not possible, make the trace length as short as possible.
4. The trace connected to the XCIN pin and the trace connected to the XCOOUT pin should have as much space between them (at least 0.3 mm) as possible.
5. Connect external capacitors as close together as possible. Connect the traces for the capacitors to the ground trace (hereinafter referred to as the “ground shield”) on the component side. For details on the ground shield, refer to section 2.2.2. When the capacitors cannot be placed using the preferred placement, use the placement shown in Figure 8.
6. In order to decrease the parasitic capacitance between XCIN and XCOOUT, include a ground trace between the resonator and the MCU.

 


Figure 5. Example of Preferred Placement and Routing for XCIN and XCOU, LQFP Packages

 


Figure 6. Example of Preferred Placement and Routing for XCIN and XCOU, LGA Packages

 


Figure 7. Example of Preferred Placement and Routing for XCIN and XCOU, BGA Packages

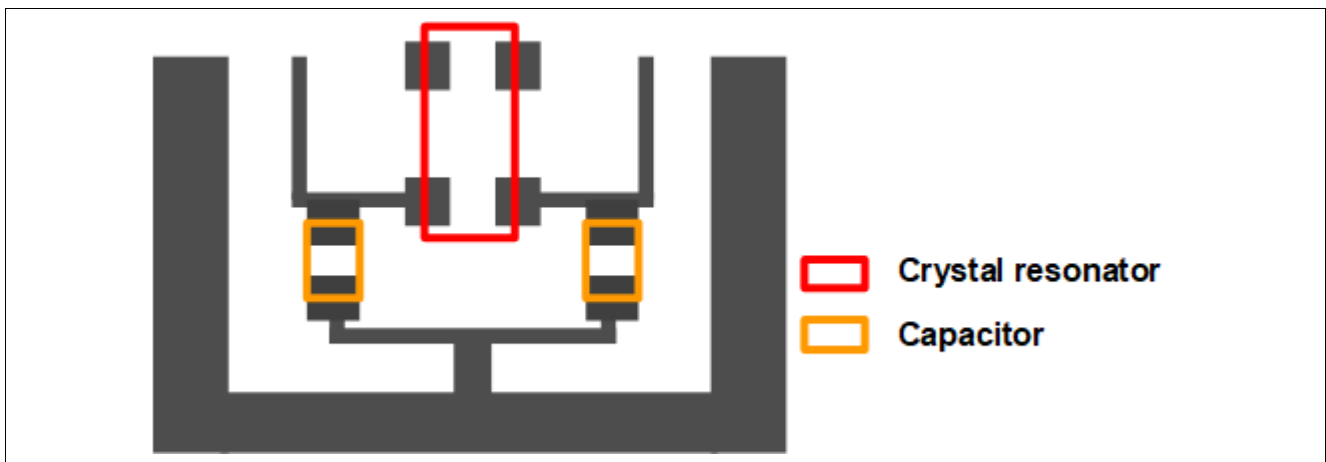


Figure 8. Example of Alternate Placement and Routing for XCIN and XCOU

2.2.2 Ground Shield

Shield the crystal resonator with a ground trace. The following list describes the points regarding the ground shield. Figure 9, Figure 10, and Figure 11 show routing examples for each package. Identification numbers in each figure refer to this list.

1. Lay out the ground shield on the same layer as the crystal resonator trace routing.
2. Make the ground shield trace width at least 0.3 mm and leave a 0.3 to 2.0 mm gap between the ground shield and other traces.
3. Route the ground shield as close to the VSS pin on the MCU as possible and ensure that the trace width is at least 0.3 mm.
4. To prevent current through the ground shield, branch the ground shield and the ground on the board near the VSS pin on the board.

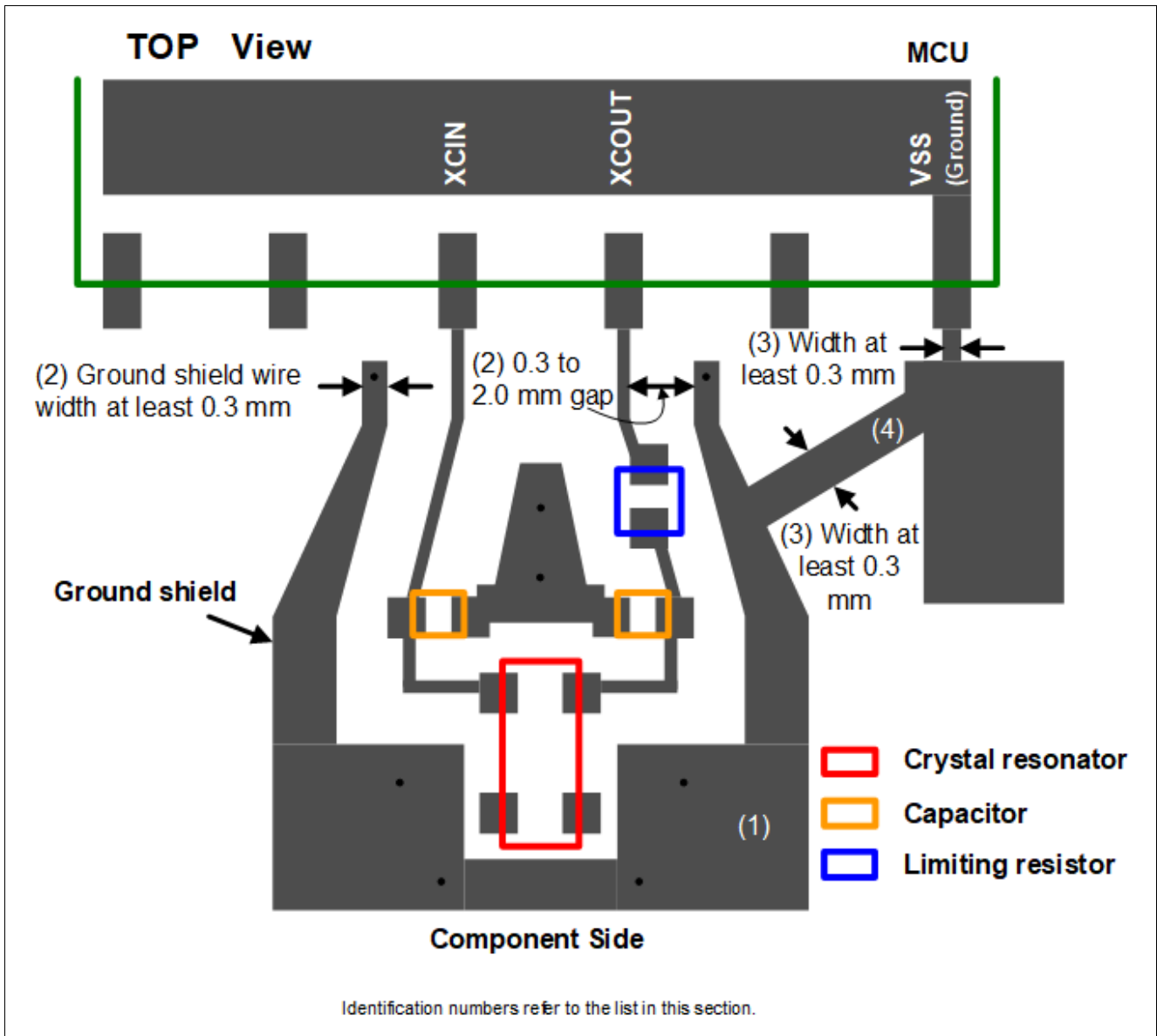


Figure 9. Trace Example for the Ground Shield, LQFP Packages

 


Figure 10. Trace Example for the Ground Shield, LGA Packages

 


Figure 11. Trace Example for the Ground Shield, BGA Packages

2.2.3 Bottom Ground

2.2.3.1 Multilayered Boards at Least 1.2 mm Thick

For boards that are at least 1.2 mm thick, lay out a ground trace on the solder side (hereinafter referred to as bottom ground) of the crystal resonator area.

The following list describes points when making a multilayered board that is at least 1.2 mm thick. Figure 12, Figure 13, and Figure 14 show routing examples for each package type. Identification numbers in each figure refer to this list.

1. Do not lay out any traces in the middle layers of the crystal resonator area. Do not lay out power supply or ground traces in this area. Do not pass signal traces through this area.
2. Make the bottom ground at least 0.1 mm bigger than the ground shield.
3. Connect the bottom ground on the solder side only to the ground shield on the component side before connecting it to the VSS pin.

Additional notes:

- For LQFP and TFLGA packages, only connect the ground shield to the bottom ground of the component side of the board. Connect the bottom ground to the VSS pin through the ground shield. Do not connect the bottom ground or the ground shield to a ground other than the VSS pin.

- For LFBGA packages, connect the bottom ground directly to the VSS pin. Do not connect the bottom ground or the ground shield to a ground other than the VSS pin.

 


Figure 12. Routing Example When a Multilayered Board is at Least 1.2 mm Thick, LQFP Packages

 


Figure 13. Routing Example When a Multilayered Board is at Least 1.2 mm Thick, LGA Packages

 


Figure 14. Routing Example When a Multilayered Board is at Least 1.2 mm Thick, BGA Packages

2.2.3.2 Multilayered Boards Less than 1.2 mm Thick

The following describes points when making a multilayered board that is less than 1.2 mm thick. Figure 15 shows a routing example.

- Do not lay out any traces to layers other than the component side for the crystal resonator area. Do not lay out power supply and ground traces in this area. Do not pass signal traces through this area.

 


Figure 15. Routing Example When a Multilayered Board is Less Than 1.2 mm Thick, LQFP Packages

2.2.4 Other Points

The following list describes other points to consider, and Figure 16 shows a routing example when using an LQFP package. The same points apply to any package type. Identification numbers in the figure refer to this list.

1. Do not place the XCIN and XCOU traces near traces that have big changes in current.
2. Do not route the XCIN and XCOU traces parallel to other signal traces, such as those for adjacent pins.
3. Traces for pins that are adjacent to the XCIN and XCOU pins should be routed away from the XCIN and XCOU pins. Route the traces toward the center of the MCU first, then route the traces away from the XCIN and XCOU pins. This is recommended to avoid routing of traces parallel to the XCIN and XCOU traces.

4. Lay out as much of the ground trace on the bottom side of the MCU as possible.

 


Figure 16. Routing Example for Other Points, LQFP Package Example

2.2.5 Main Clock Resonator

This section describes points on routing the main clock resonator. Figure 17 shows a routing example.

- Shield the main clock resonator with a ground.
- Do not connect the ground shield for the main clock resonator to the ground shield for the sub-clock. If the main clock ground shield is connected directly to the sub-clock ground shield, there is a possibility that noise from the main clock resonator may transfer through and affect the sub-clock.
- When placing and routing the main clock resonator, follow the same guidelines as explained for the sub-clock oscillator.

 


Figure 17. Routing Example When Shielding the Main Clock Resonator with a Ground Shield

2.3 Routing – Errors to Avoid

When routing the sub-clock circuit, be cautious to avoid any of the following points. Routing the traces with any of these issues may cause the low C_L resonator to not oscillate correctly. Figure 18 shows a routing example and points out the routing errors. Identification numbers in the figure refer to this list.

1. XCIN and XCOUT traces cross other signal traces. (Risk of erroneous operation.)
2. Observation pins (test points) are attached to XCIN and XCOUT. (Risk of oscillation stopping.)
3. XCIN and XCOUT wires are long. (Risk of erroneous operation or decreased accuracy.)
4. The ground shield does not cover the entire area, and where there is a ground shield, the routing is long and narrow. (Easily affected by noise, and there is a risk that accuracy will decrease from the ground potential difference generated by the MCU and external capacitor.)
5. Ground shield has multiple VSS connections in addition to the VSS pin. (Risk of erroneous operation from MCU current flowing through the ground shield.)
6. Power supply or ground traces are under the XCIN and XCOUT traces. (Risk of losing the clock or oscillation stopping.)
7. A trace with a large current is routed nearby. (Risk of erroneous operation.)
8. Parallel traces for adjacent pins are close and long. (Risk of losing the clock or oscillation stopping.)
9. The middle layers are used for routing. (Risk of oscillation characteristics decreasing or signals operating erroneously.)

 


Figure 18. Routing Example Showing a High Risk of Erroneous Operation Due to Noise

2.4 Reference Oscillation Circuit Constants and Verified Resonator Operation

Table 1 lists the reference oscillation circuit constants for the verified crystal resonator operation. Figure 1 at the beginning of this document shows an example circuit for the verified resonator operation.

Table 1. Reference Oscillation Circuit Constants for Verified Resonator Operation

Manufacturer	Series	SMD/ Leaded	Frequency (kHz)	C _L (pF)	C _{L1} (pF)	C _{L2} (pF)	R _d (kΩ)
Kyocera	ST3215S B	SMD	32.768	12.5	22	22	0
				9	15	15	0
				6	9	9	0
				7	10	10	0
				4	1.8	1.8	0

Note that not all RA MCU devices are listed on the Kyocera website, and sub-clock oscillator recommendations are not listed for most RA MCU devices. Data in this table includes recommendations for other comparable Renesas MCU devices.

The verified resonator operation and reference oscillation circuit constants listed here are based on information from the resonator manufacturer and are not guaranteed. As reference oscillation circuit constants are measurements surveyed under fixed conditions by the manufacturer, values measured in the user system may vary. To achieve optimum reference oscillation circuit constants for use in the actual user system, inquire with the resonator manufacturer to perform an evaluation on the actual circuit.

The conditions in the figure are conditions for oscillating the resonator connected to the MCU and are not operating conditions for the MCU itself. Refer to the specifications in the electrical characteristics for details on the MCU operating conditions.

Website and Support

Visit the following URLs to learn about key elements of the RA family, download components and related documentation, and get support.

RA Product Information	www.renesas.com/ra
RA Product Support Forum	www.renesas.com/ra/forum
RA Flexible Software Package	www.renesas.com/FSP
Renesas Support	www.renesas.com/support

Revision History

Rev.	Date	Description	
		Page	Summary
1.00	Jan.7.2022	—	Initial release

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.

Contact information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/.