

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

High-Speed CMOS Logic IC HD74HC Series

Application Note

1. Input Protection Circuit

An Si-gate process is applied to Renesas's high-speed CMOS logic ICs. They have a thinner gate oxide compared to conventional Al-gate CMOS logic ICs and are composed into finer patterns.

Therefore, an input protection circuit is necessary for the gate to be protected from surges at the input pins.

Since Al-gate CMOS logic ICs use a diffusion resistor as the input protection resistor (as shown in Figure 1a), input over-current flows directly to the power supply and the destruction of the protection diode may occur.

On the other hand, using polysilicone as its input protection resistor (shown in Figure 1b), high-speed CMOS logic ICs take the role of a current limiter to counter input over voltage.

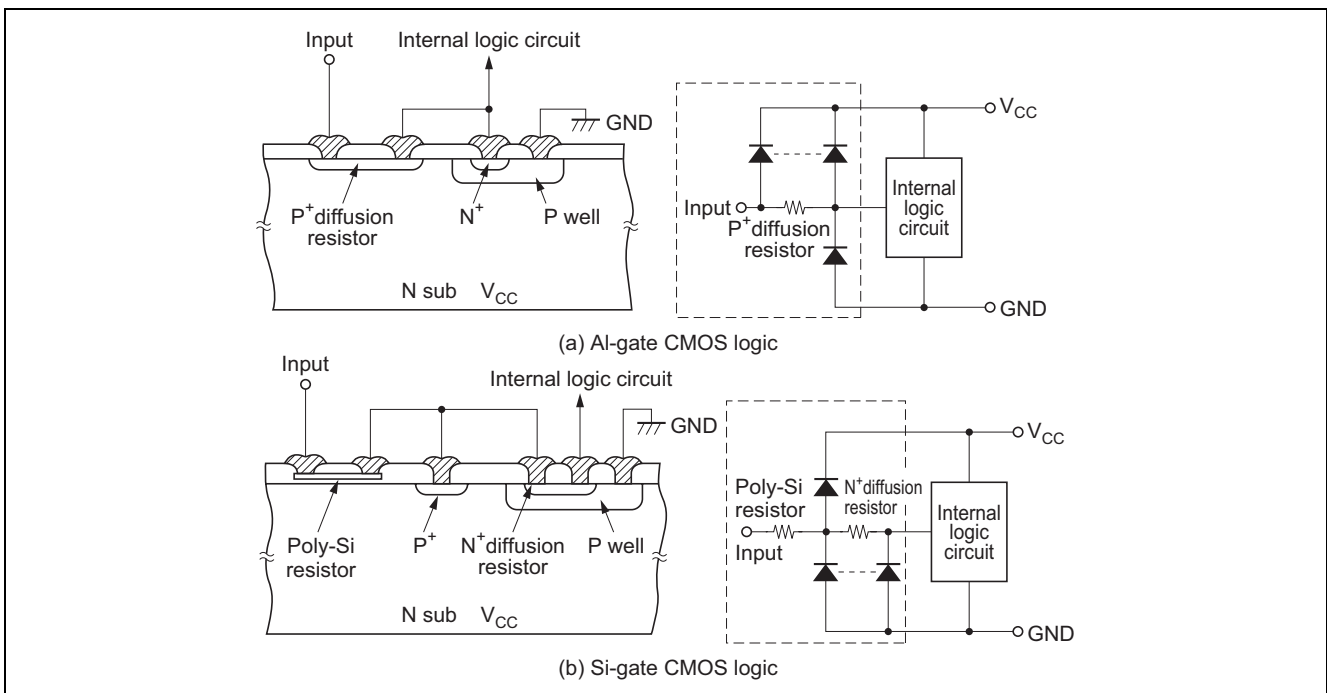


Figure 1 Input Protection Device and Equivalent Circuit

2. Electric Static Discharge Immunity (ESD Immunity)

ESD immunity is evaluated by the capacitor discharge method shown in the test circuit of Figure 2. The capacitor is 200 pF, accounting for the electrostatic capacitance of human bodies. Figure 3 shows an example of ESD immunity of integrated circuits for each products series.

The ESD for high-speed CMOS logic is over ± 200 V, which is the same level or better than LS-TTL.

 


Figure 2 ESD Immunity Test Circuit

 


Figure 3 ESD Immunity for Each Series

3. Latch-Up

3.1 Latch-up

Latch-up is an inevitable phenomenon occurring from the basic structure of CMOS logic ICs.

Since CMOS has PMOS and NMOS on one chip, NPN and PNP transistors are made. These two types of transistors are combined into a PNP structure, in which a parasitic thyristor is formed (see Figure 4).

If excessive noise is applied to the input or output pins when the IC is operating, the parasitic thyristor will turn on and the abnormal current will flow through the power supply pin to ground.

If the power supply is turned off, the IC will be restored to its normal state, however, the internal AI wiring of the IC may melt thus causing the IC to be destroyed.

There are countermeasures to prevent latch-up as listed below

- (1) Separate PMOS from NMOS.
- (2) Shut down electrical paths between PNP and NPN transistors which form parasitic thyristors by its layout pattern.
- (3) Isolate each MOS transistor with an insulator to prevent the formation of parasitic thyristors.

Renesas's high-speed CMOS logic utilizes method (2)

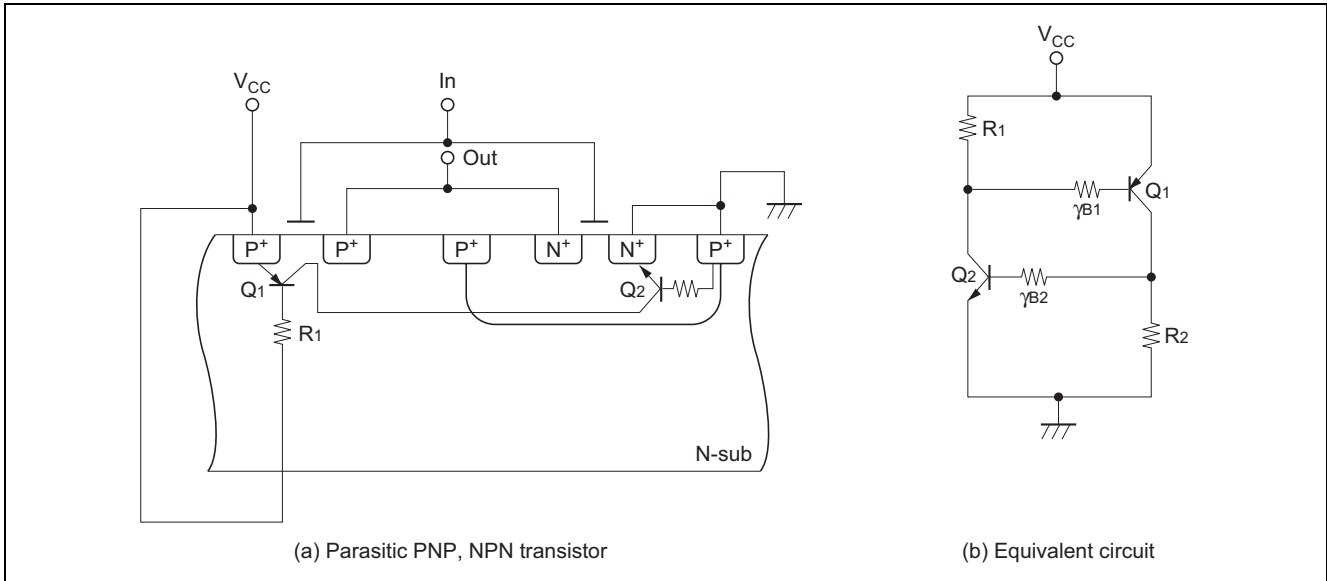


Figure 4 Parasitic Thyristor

3.2 Latch-Up immunity

Latch-up immunity is evaluated by the test circuit shown in Figure 5.

Table 1 lists the test results of latch-up immunity of Renesas’s high-speed CMOS logic.

The starting voltage of high-speed CMOS logic is over ± 300 V which causes almost no problems for practical use.

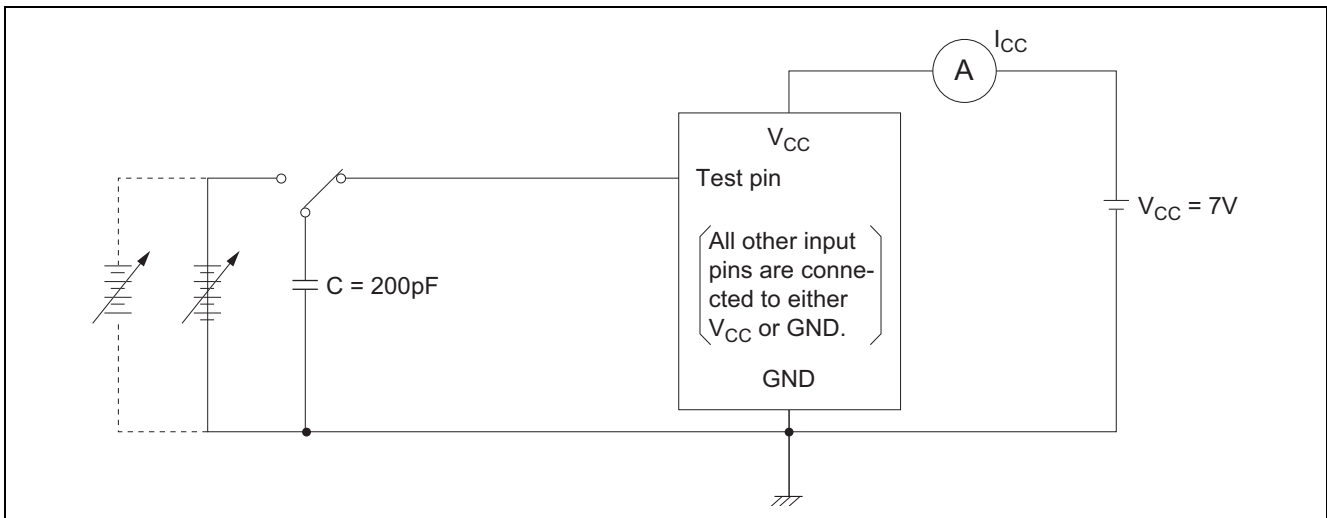


Figure 5 Latch-Up Immunity Test Circuit

Table 1 Latch-Up Starting Voltage Test Results

	Latch-up starting voltage
Positive	Over 300 V
Negative	Over 300 V

4. Electrical Characteristics

4.1 DC characteristics

(1) Logic threshold voltage (V_{TH})

The Logic threshold voltage (V_{TH}) of Renesas's high-speed CMOS logic ICs (HD74HC Series) is at half the level of V_{CC} in order to set up the widest noise margin possible.

(2) Output current characteristics

Reenas's high-speed CMOS logic ICs have symmetrical characteristics between I_{OH} and I_{OL} . Thus, the balance between t_{PLH} and t_{PHL} is mostly kept even when connecting with a comparatively large load capacitance.

Figures 7 and 8 show the output current characteristics.

 


Figure 6 Output Voltage vs Input Voltage

 


Figure 7 Output Current vs Voltage (Low Level)

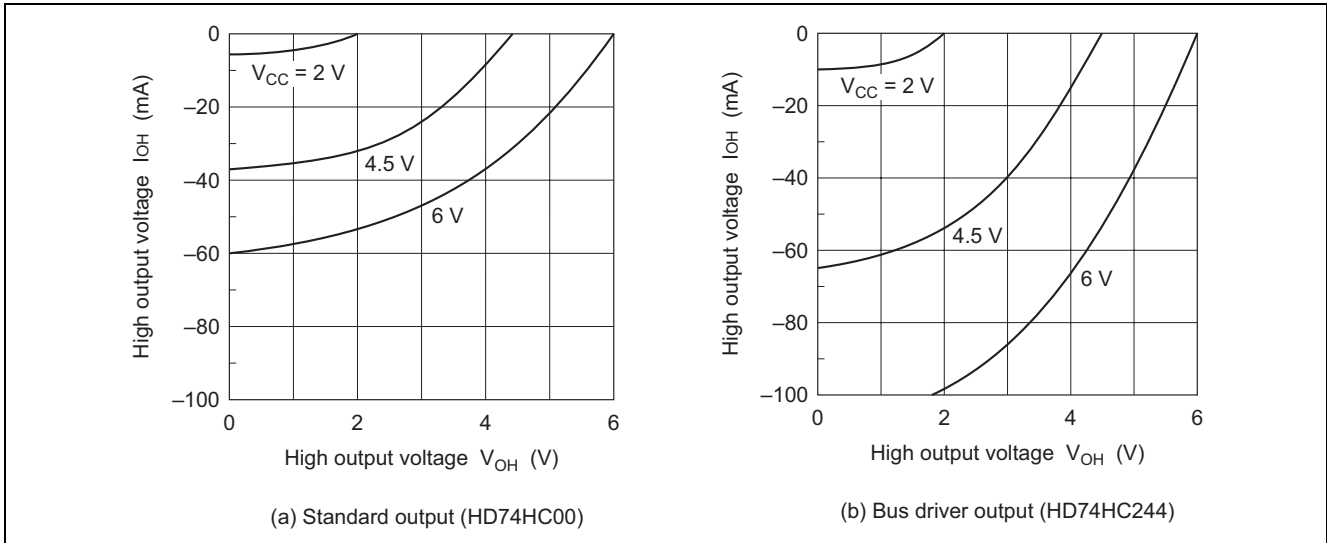


Figure 8 Output Current vs Voltage (High Level)

4.2 AC characteristics

t_{PLH} and t_{PHL} of Renesas's high-speed CMOS logic ICs are set up to be about the same to simplify system timing design.

(1) Propagation delay time, output rise and fall time vs supply voltage characteristics.

 


Figure 9 Propagation Delay Time vs Supply Voltage

 


Figure 10 Output Rise and Fall Time vs Supply Voltage

(2) Propagation delay time, output rise and fall time vs load capacitance characteristics.

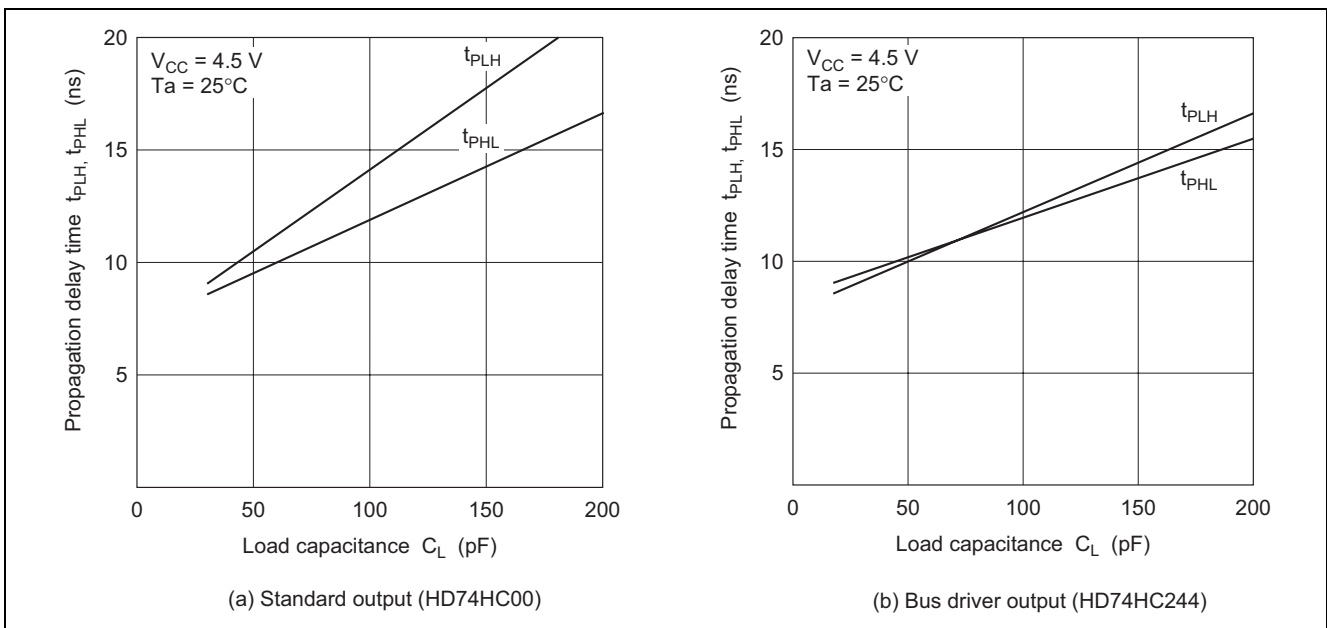


Figure 11 Propagation Delay Time vs Load Capacitance

 


Figure 12 Output Rise and Fall Time vs Load Capacitance

5. Power Dissipation

5.1 Calculating the power dissipation

The power dissipation P_T of high-speed CMOS logic can be calculated by (1). From this equation, the power dissipation depends on the load capacitance, frequency and supply voltage.

$$P_T = (C_L + C_{PD}) \cdot f \cdot V_{CC}^2 \quad (1)$$

Figure 13 shows examples of the operating frequency with the power supply current.

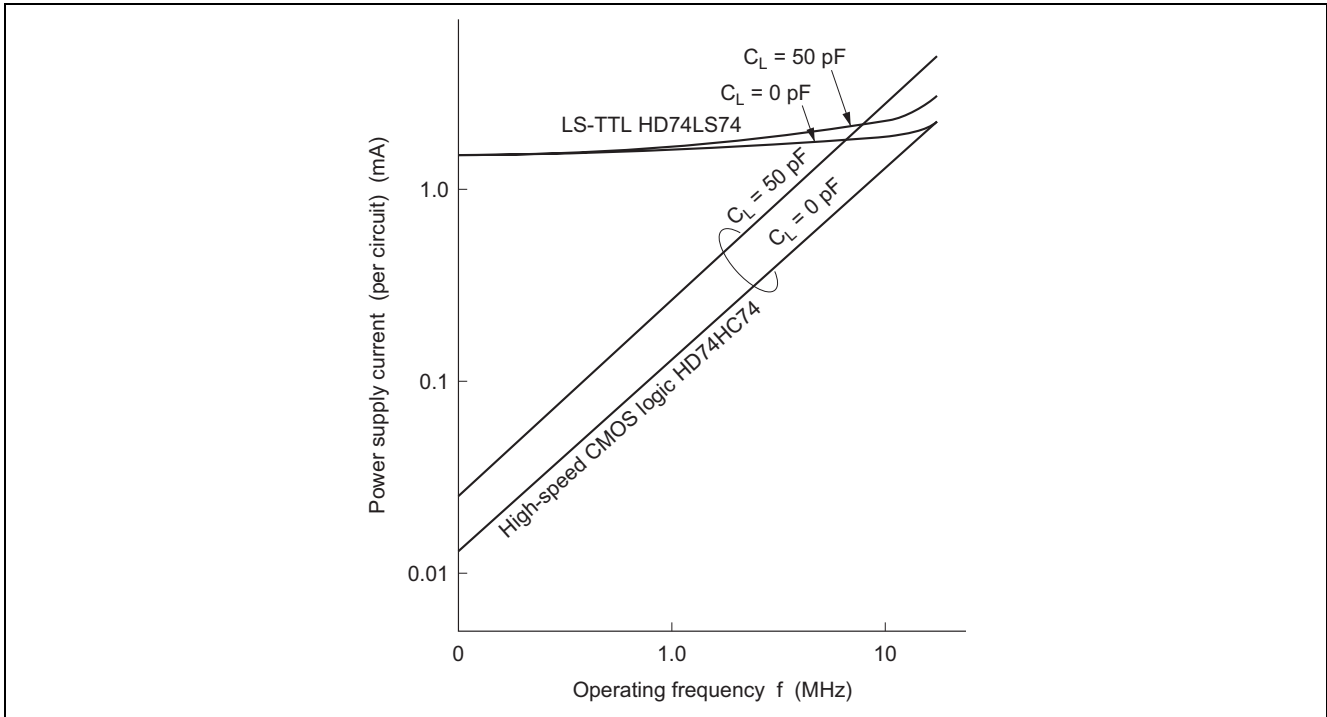


Figure 13 Operating Frequency vs Power Supply Current

5.2 Power dissipation capacitance

Power dissipation capacitance (C_{pd}) can be calculated by the following equations,

$$P_{T1} = C_{PD} \cdot V_{CC}^2 \cdot f_1 = I_{CC1} \cdot V_{CC} \quad (2)$$

$$P_{T2} = C_{PD} \cdot V_{CC}^2 \cdot f_2 = I_{CC2} \cdot V_{CC} \quad (3)$$

therefore,

$$\begin{aligned} C_{pd} &= \frac{P_{T2} - P_{T1}}{V_{CC}^2 \times (f_2 - f_1)} \\ &= \frac{I_{CC2} - I_{CC1}}{V_{CC} \times (f_2 - f_1)} \end{aligned} \quad (4)$$

then,

- I_{CC1} : Supply current at frequency f_1
- I_{CC2} : Supply current at frequency f_2

Table 2 lists the power dissipation capacitance of Renesas's high-speed CMOS logic.

Furthermore, the power dissipation capacitance differs according to the input conditions.

Table 3 shows typical examples.

Table 2 Power Dissipation Capacitance of High-Speed CMOS

Function		Product part no.	Note 1	Power dissipation capacitance typ. (pF)
Gate		HD74HC00	*	27
		HD74HC04	*	24
Flip-Flop	D-type	HD74HC74	*	41
	J-K-type	HD74HC76	*	49
COMPARATOR		HD74HC85	P	48
DECORDER		HD74HC138	P	90
COUNTER		HD74HC161	P	57
BUFFER		HD74HC240	*	42
MULTIPLEXER		HD74HC258	P	78
LATCH		HD74HC373	P	57

Notes: 1. *:Per circuit; P: Per package.

2. Measurement circuit is shown in figure 14.

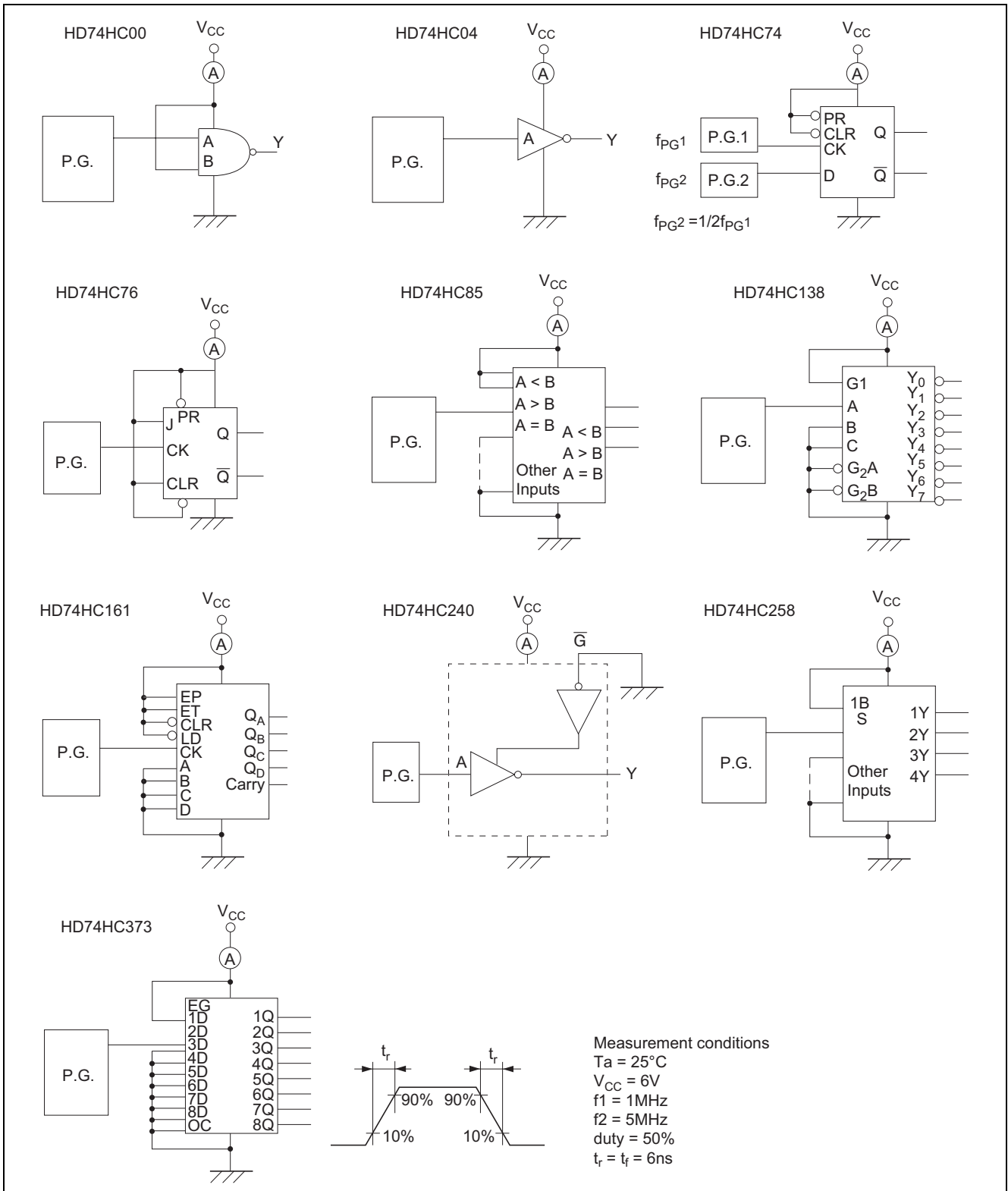
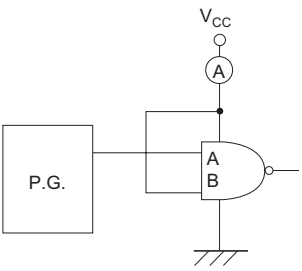
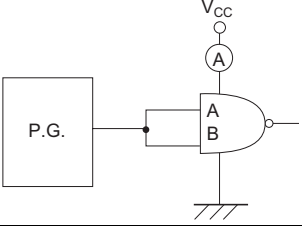
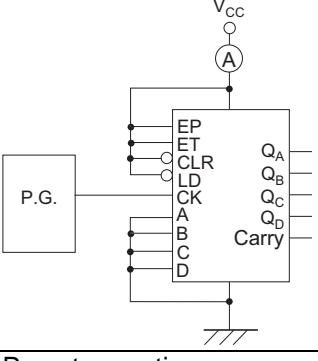
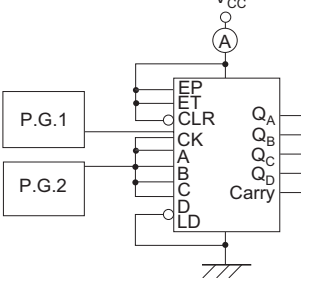


Figure 14 Measurement Circuits for Dynamic Power Supply Current

Table 3 Power Dissipation Capacitance by Input Conditions

Product part no.	Input conditions	Power dissipation capacitance (pF)
HD74HC00	Single input 	27
	Double input 	27
HD74HC161	Counting operation 	57
	Preset operation 	113

6. Decoupling

CMOS logic ICs have current spikes when switching. These spikes are produced by the repeated charging and discharging of the output capacitance when charging the output level from low to high or high to low.

Because of the current spikes the potentials of V_{CC} and GND change, and large current spikes flow when switching. Therefore ringing is produced at the output. (See Figure 15 a.)

To prevent this, decoupling capacitors must be provided externally between V_{CC} and GND.

This is proven to be useful in instantly absorbing the current and ringing at the output as shown in Figure 15 b.

 


Figure 15 HD74HC00 Spike Current Waveform

7. Precautions on Board Design

High-speed CMOS logic has different electrical characteristics, such as switching speed and output current drivability, from the conventional standard logics (AI-gate CMOS, LS-TTL). The system design requires an application technique for high-speed CMOS logic.

Here an interfacing technique between high-speed CMOS logic and LS-TTL will be explained.

7.1 Transmission line reflection

(1) Analysis of transmission signals by the Bergeron diagram The Bergeron diagram is commonly used for the analysis of transmission signals in high-speed digital systems.

Figure 17 is the analysis result of an actual transmission model which is shown in Figure 16.

As for the analysis conditions, $Z_0 = 125 \Omega$ considering the standard system board, and the wiring length (l) is 1.5 m. The output impedance of the HD74HC04, which operates as a driver becomes the $I_{OH} - V_{OH}$ characteristic curve when the output is high, and the input impedance of the HD74LS04 which operates as a receiver becomes the $I_{IH} - V_{IH}$ characteristic curve.

On the other hand, when the output level of the HD74HC04 is low, the output impedance becomes the $I_{OL} - V_{OL}$ characteristic curve and the input impedance becomes the $I_F - V_F$ characteristic curve.

The drawing of load line Z_0 as these input/output impedance curves enables the reflection of the transmission signal to be analyzed.

The intersection coordinates in Figure 17 shows the voltage and current values at the drive end of $2T$ (T being the propagation delay from the driver end to the receiver end) intervals when the coordinates are even numbers ($2T, 4T$) or zero, or the voltage and current values at the receiver end when the coordinates are odd numbers ($T, 3T, 5T$).

Figure 18 shows the analysis result of the voltage waveform at the receiver end.

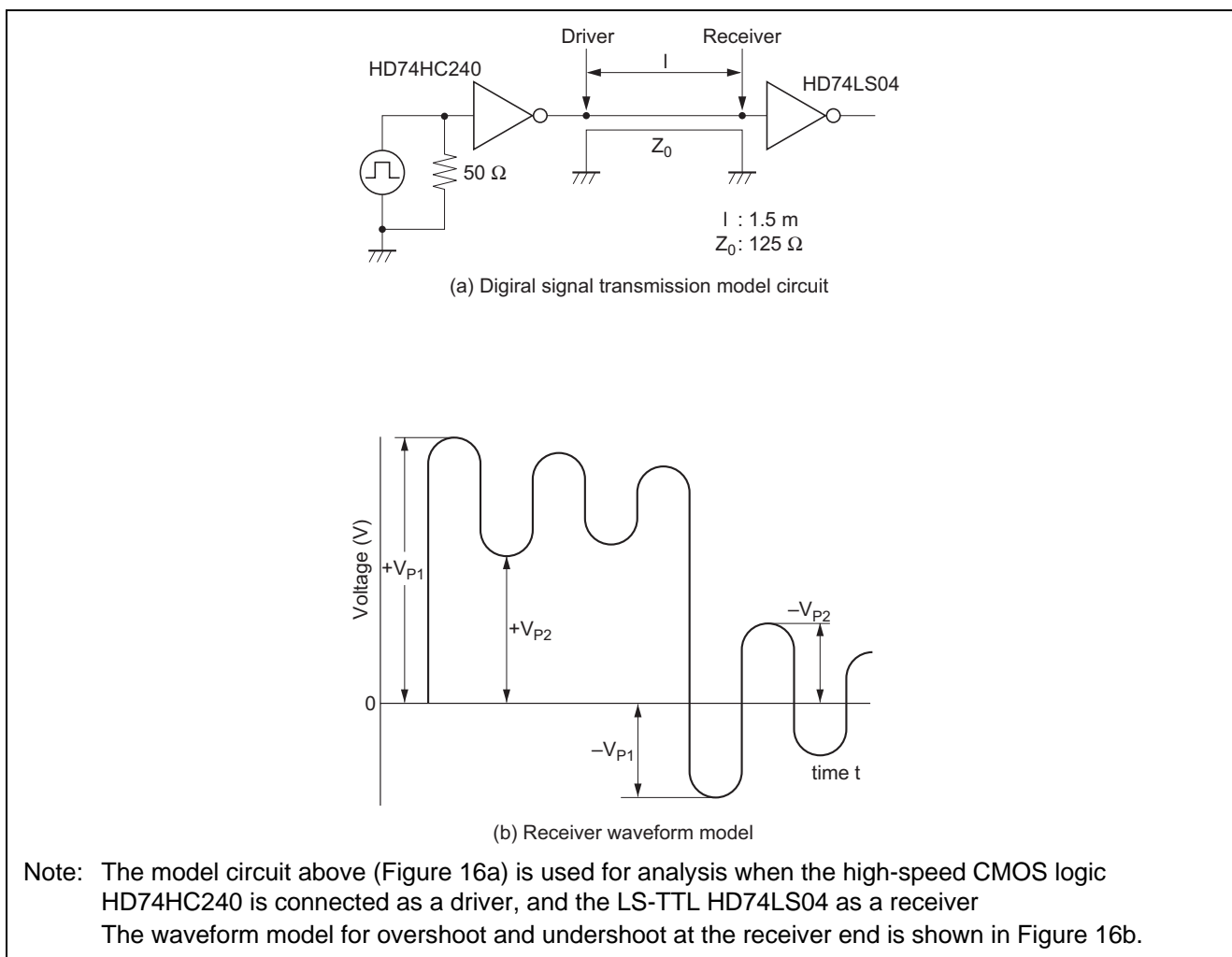


Figure 16 Digital Signal Transmission

 


Figure 17 Bergeron Diagram Analysis of the Transmission Model

 


Figure 18 Analysis Results of the Waveform at the Receiver End

(2) An example for measuring the reflection on the transmission line Figure 19 shows the measured results of the reflection of the transmission line using three types of transmission line media such as 1) coaxial cable ($Z_0 = 50 \Omega$), 2) twisted pair cable ($Z_0 = 120 \Omega$), and 3) single lead wire ($Z_0 = 150$ to 200Ω).

Figure 19 shows that the drivers and receivers operate normally with a wiring length of up to 2 m.

However, careful precautions should be taken when considering impedance in practical system designing.

 
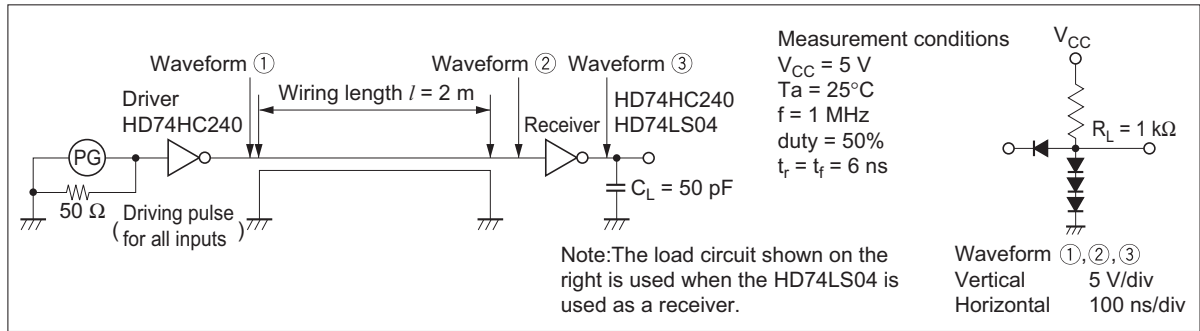


Figure 19 Reflection Ringing Waveforms (Driver: HD74HC240)

7.2 Crosstalk

Crosstalk is the capacitive coupling of signals from one line to another.

Figure 20 shows an example of crosstalk noise levels using a twisted pair cable.

Figure 20 also shows that the wiring length beyond 1 m causes malfunction.

Careful precautions should be taken especially when the spacing between circuits is narrow.

 
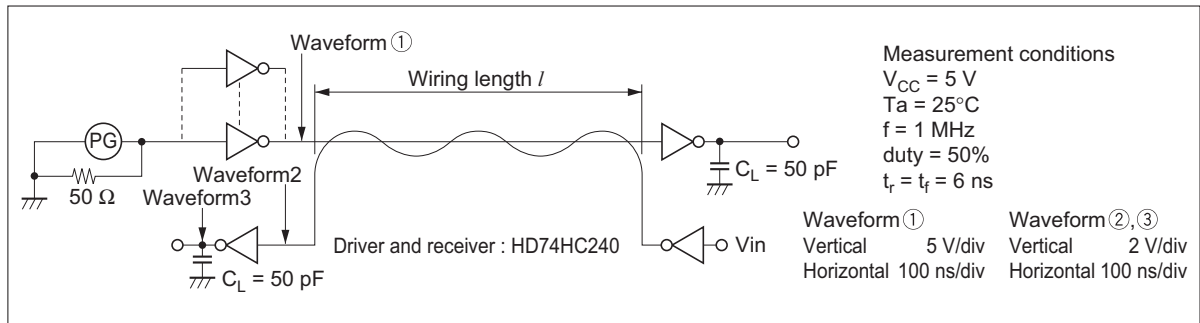


Figure 20 Crosstalk Noise Waveform (Driver: HD74HC240)

8. Interfacing

Renesas's high-speed CMOS logic has two types of input voltage levels, 74HC and 74HCT.

The 74HC has a CMOS-type input level and the 74HCT has a TTL-type input level.

Interfacing from high-speed CMOS logic to LS-TTL

Since the output level of high-speed CMOS logic is of CMOS, the use of an interfacing circuit is not necessary.

This is the same case for a microcomputer and memory IC with TTL input levels.

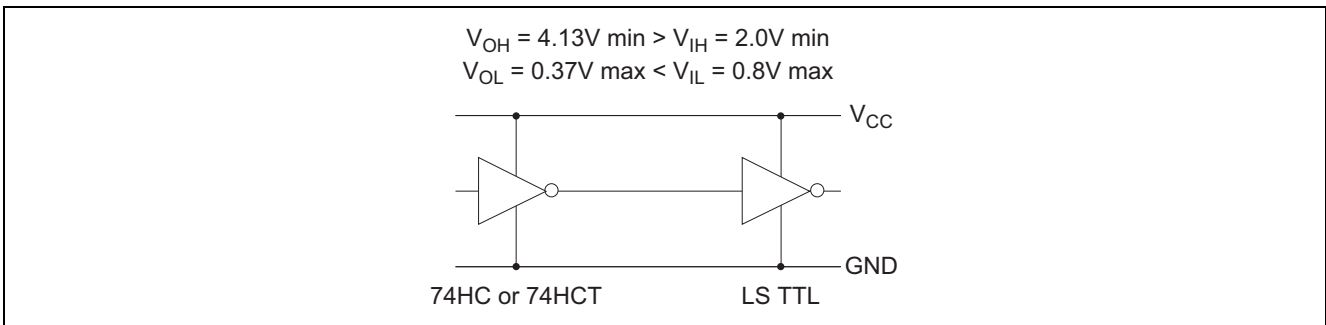


Figure 21 Interfacing HS-CMOS to LS-TTL

Interfacing from LS-TTL to high-speed CMOS logic (74HCT type)

An interfacing circuit is not necessary.

This is the same case for a microcomputer and memory IC with TTL output levels.

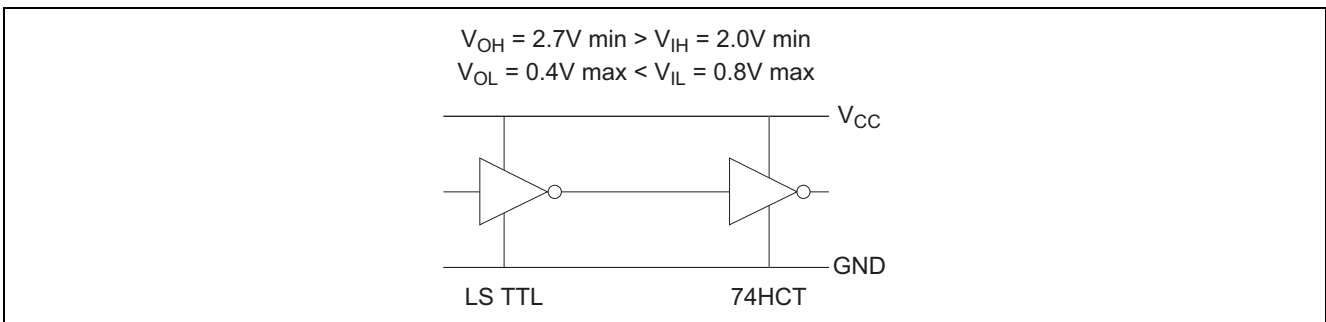


Figure 22 Interfacing LS-TTL to 74HCT

Interfacing from LS-TTL to high-speed CMOS logic (74HC type)

A pull-up resistor should be added as shown in Figure 25.

The output voltage of LS-TTL (V_{OH}) is 2.7 V (min), where as the input voltage of 74HC (V_{IH}) is 3.15 V (min.).

This implies that LS-TTL cannot drive 74HC types directly.

This is the same case for a microcomputer and memory ICs with TTL output levels.

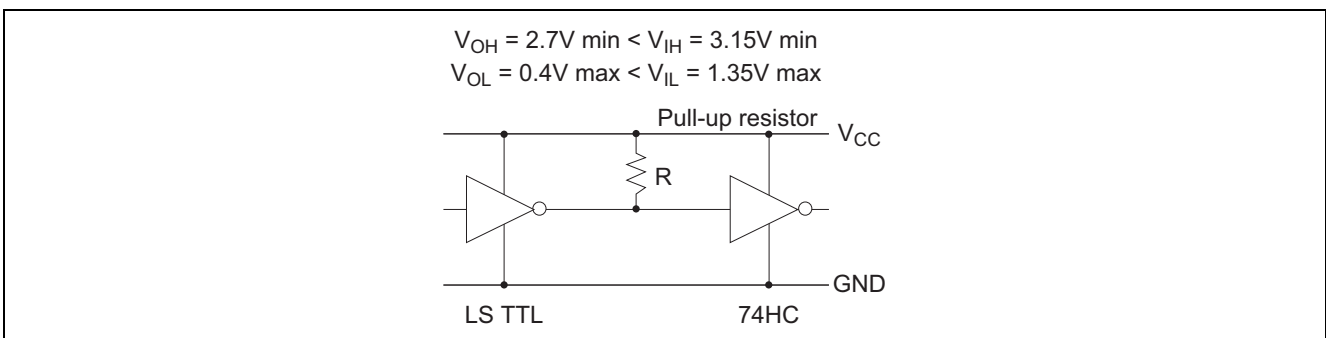


Figure 23 Interfacing LS-TTL to 74HC

Interfacing from LS-TTL with 3-state output to high-speed CMOS logic.

A pull-up or pull-down resistor should be added as shown in Figure 26.

When the output of a LS-TTL is in the high-impedance state, the input of the high-speed CMOS becomes unstable.

This is the same case for all devices with a tri-state output structure.

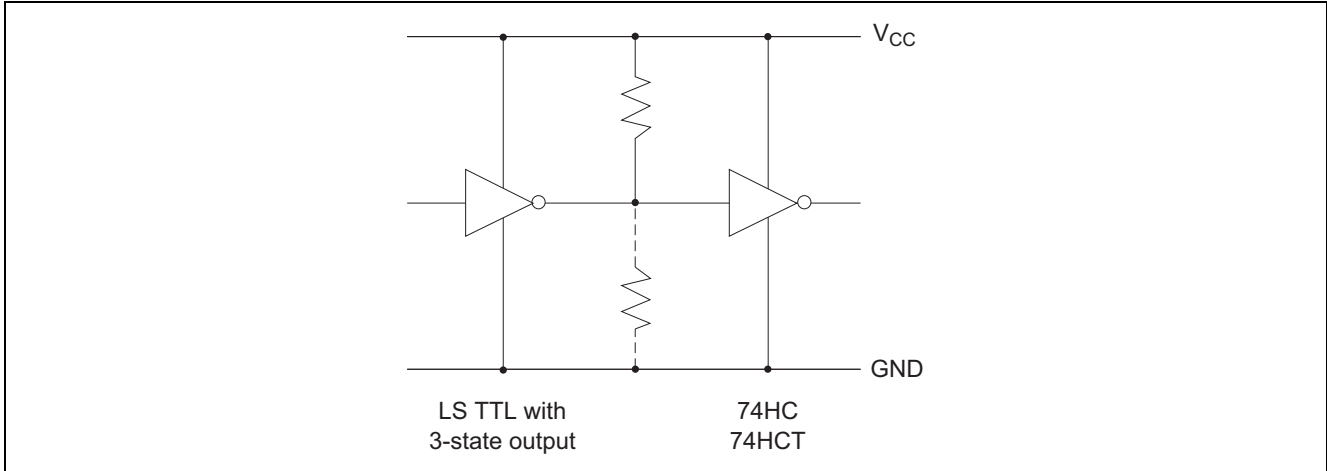


Figure 24 Interfacing LS-TTL with 3-state Output to 74HC or 74HCT

9. Surface Mount Package

9.1 Mounting small outline packages (SOP, TSSOP)

The explanation on the mounting of SOPs describes the characteristics and reliabilities of the small IC package.

(1) Dip Soldering

Initially, the package is temporarily fixed on to the board by an adhesive.

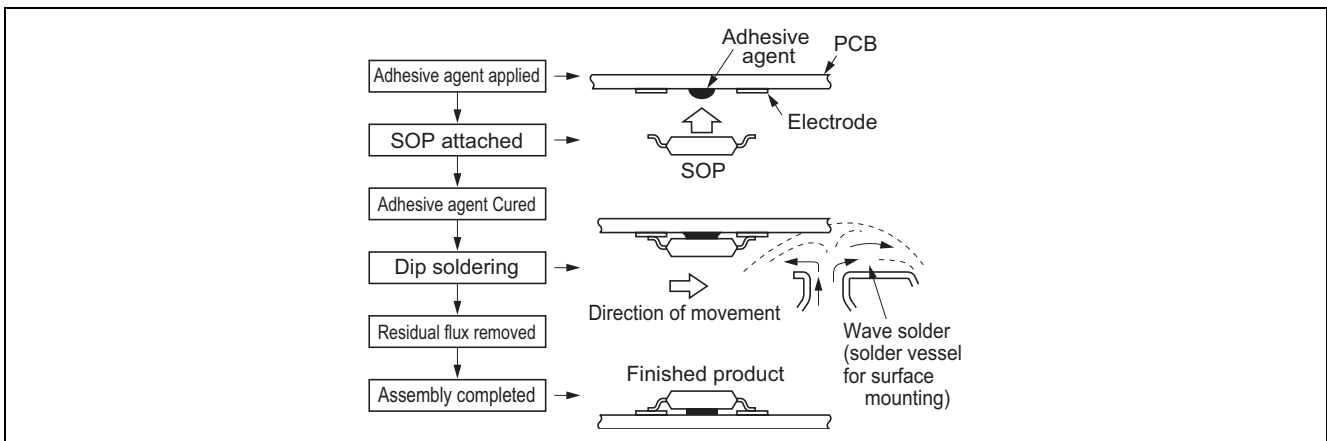


Figure 25 Process Flow for Dip Soldering SOP

With the component side of the board downward, the package is then passed through molten solder. Figure 27 depicts the process flow for dip soldering SOP. As compared with reflow methods, this method exerts an extremely high thermal stress on the semiconductor chips. The adverse effects from this thermal should be avoided by providing a preheating zone to lessen the thermal shock and by minimizing the soldering time. Figure 28 shows a typical temperature profile for dip soldering.

The dip soldering temperature is 260°C maximum at a period of 10 seconds maximum (2 to 4 seconds is recommended).

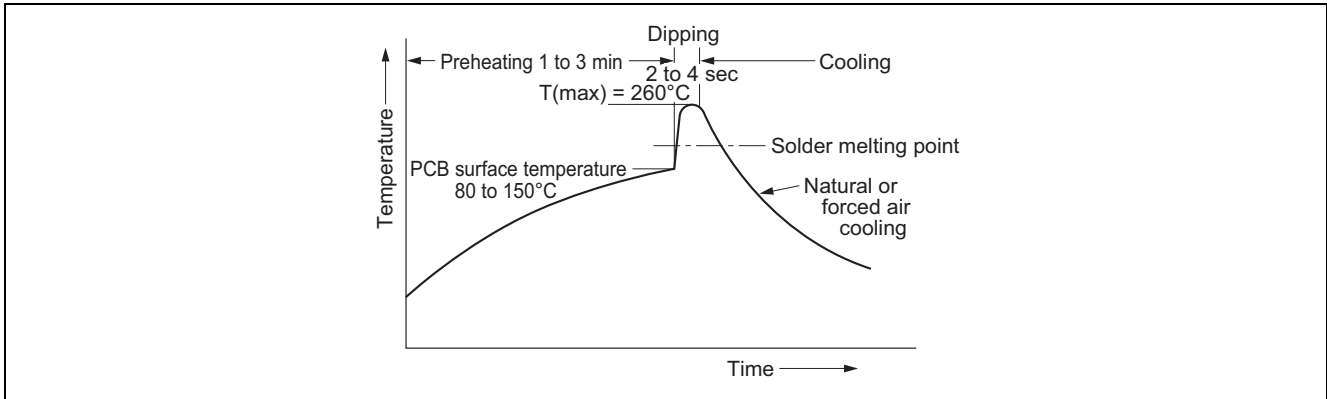


Figure 26 Temperature Profile of Dip Soldering

(2) Reflow Soldering

Reflow soldering is the basic method of mounting the SOP on to a board.

The solder composition to be used is Sn63/Pb37 or Sn62/Pb36/Ag2 with a melting point of 183°C to 193°C.

A recommended pasty flux is solder cream SP210-2 by Tamura Kaken. A pasty flux and organic solvent are also used during the process.

Be careful to reflow solder at a low temperature for short periods of time. The recommended conditions are shown below. The allowable board temperature is 230°C maximum and the maximum heating time is 15 sec.

(3) Footprint dimension vs solderability

The failure rate of soldering is affected by footprint dimensions. Figure 29 shows the soldering failure with the footprint dimension.

The recommended dimensions are within the safety zone of this figure.

When reflow soldering SOPs, the recommended thickness of a footprint is 0.2 mm min.


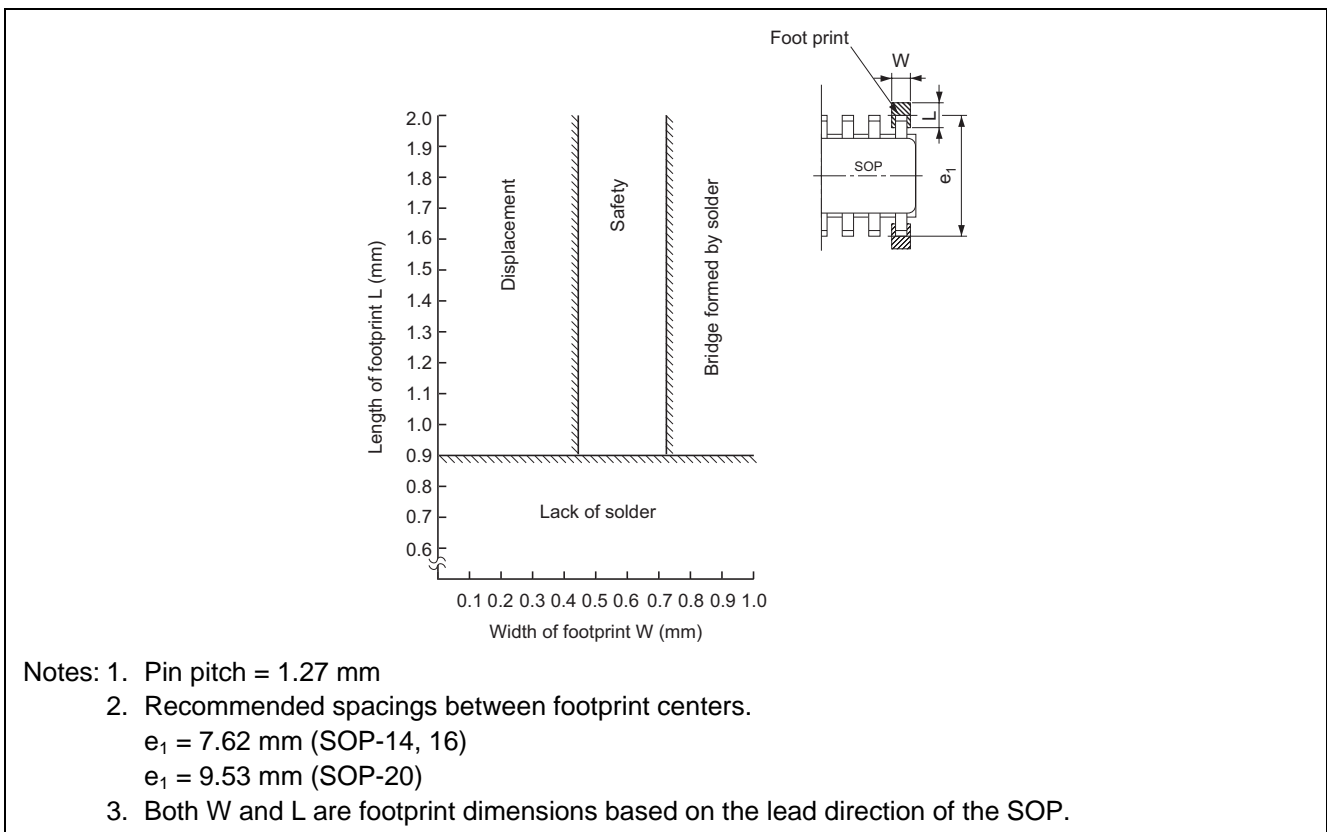


Figure 27 Recommended Dimension of Footprint

(4) Thermal Resistance of SOP

Figure 30 shows the derating curves for SOPs of high-speed CMOS logic, and Table 6 lists the thermal resistance (θ_{j-a}) for SOPs.

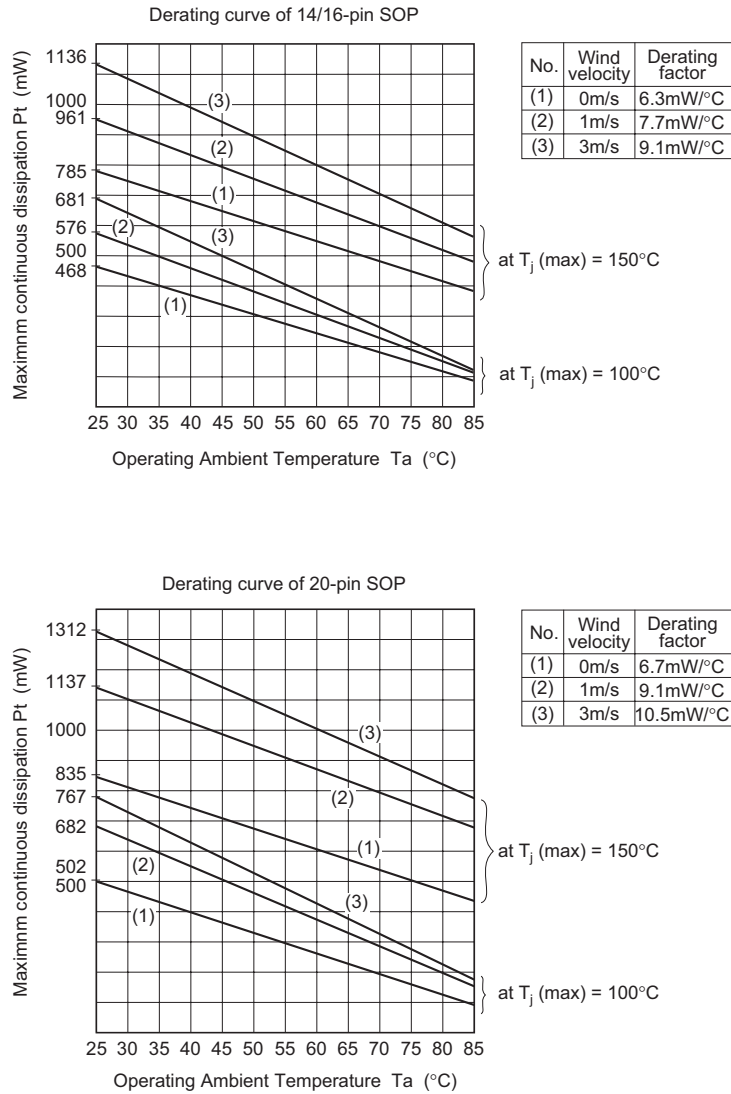

Note: When T_a is below 25°C , P_T becomes the same value as at $T_a = 25^\circ\text{C}$ being independent of T_a .
 The data above was measured by using the ΔV_{BE} method on a glass-epoxy board ($40 \times 40 \times 1.0$ mm) with wiring density of 10%.
 Careful considerations are required for input and load conditions, T_a , cooling, etc., during actual use.

Figure 28 Derating Curves of SOP

Table 6 Thermal Resistance of SOPs

Number of pins	Wind velocity	Derating factor	Thermal resistance	Maximum continuous dissipation $T_a = 25^\circ\text{C}$	
				$T_j(\text{max}) = 150^\circ\text{C}$	$T_j(\text{max}) = 100^\circ\text{C}$
14	0 m/s	6.3 mW/°C	160°C/W	785 mW	468 mW
16	1 m/s	7.7 mW/°C	130°C/W	961 mW	576 mW
	3 m/s	9.1 mW/°C	110°C/W	1136 mW	681 mW
20	0 m/s	6.7 mW/°C	150°C/W	835 mW	502 mW
	1 m/s	9.1 mW/°C	110°C/W	1137 mW	682 mW
	3 m/s	10.5 mW/°C	95°C/W	1312 mW	787 mW

(5) Thermal Resistance of TSSOP

Figure 29 shows the derating curve of TSSOP with HD74BC/AC/HC devices, table 7 shows the thermal resistance (θj-a) and figure 30 shows the mounting method.

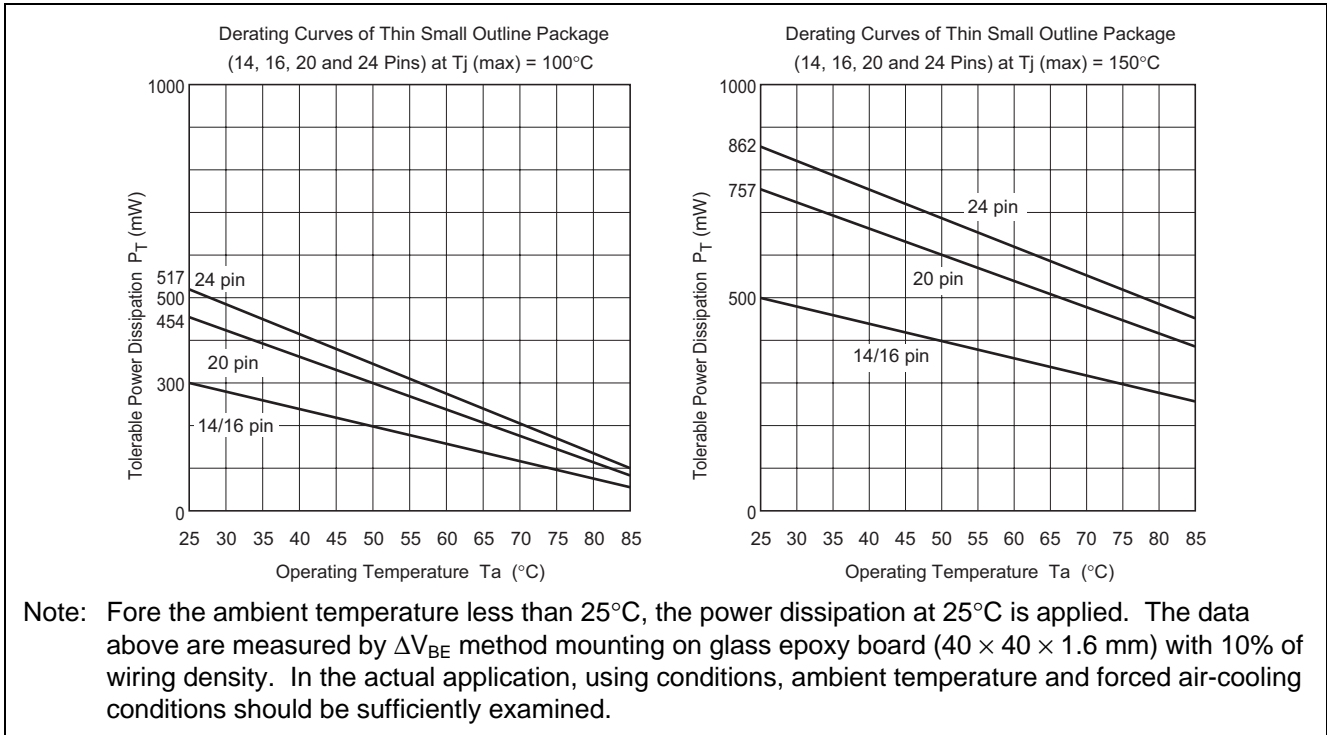


Figure 29 Derating Curve of TSSOP

Table 7 Thermal Resistance of TSSOP Package

Number of pins	Wind velocity	Derating factor	Thermal resistance	Tolerable power dissipation	
				at Tj(max) = 150°C	at Tj(max) = 100°C
14, 16	0 m/s	4.0 mW/°C	250°C/W	500 mW	300 mW
20	0 m/s	6.1 mW/°C	165°C/W	757 mW	454 mW
24	0 m/s	6.9 mW/°C	145°C/W	862 mW	517 mW

(6) TSSOP Solder Mounting


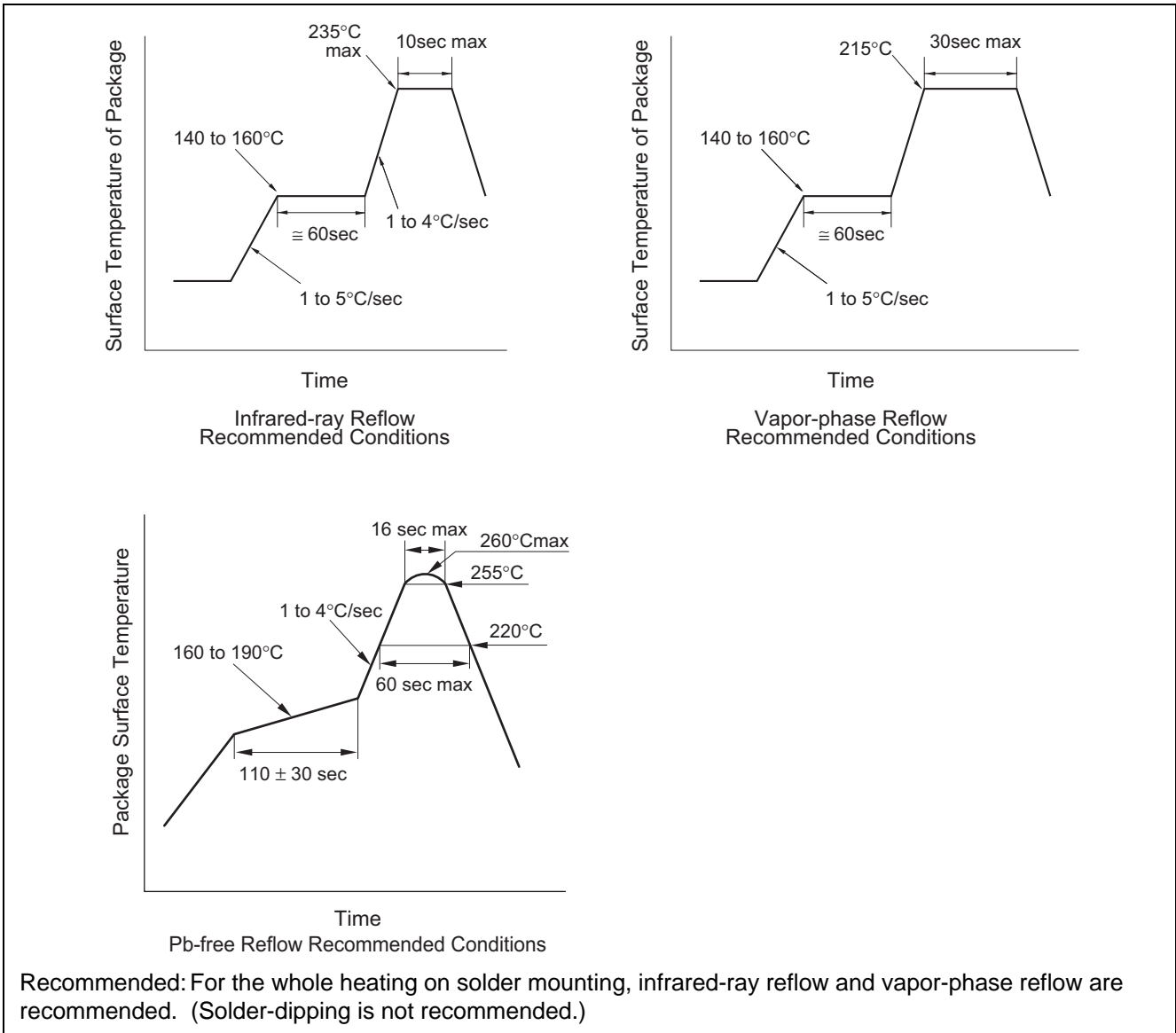


Figure 30 Mounting Method of TSSOP

(7) Marking on Package

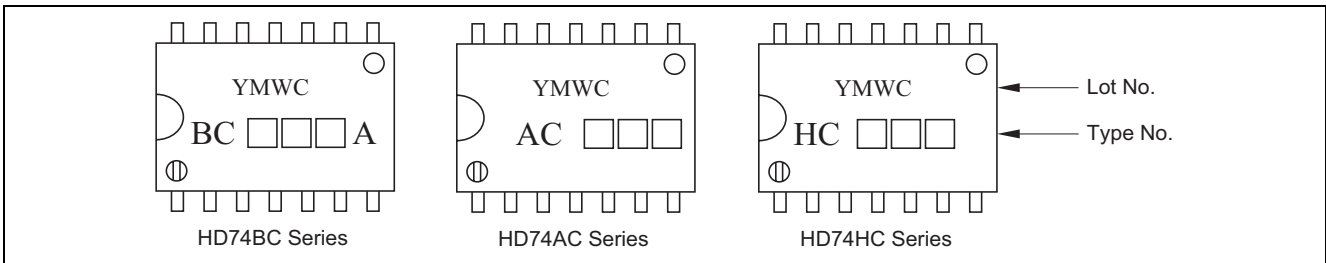(a) Small outline Package (EIAJ) 14, 16, 20 pins



(b) Small outline Package (JEDEC) 14, 16, 20 pins

The diagrams show two packages. The left package is labeled 'HD74AC Series' and has 'YMWC' and 'AC' followed by three squares. The right package is labeled 'HD74HC Series' and has 'YMWC' and 'HC' followed by three squares. Arrows point to the top-right corner for 'Lot No.' and the bottom-right corner for 'Type No.' on the HD74HC package.

Note: Meaning of marking on package example device name:
HD74AC245RP
 Y: Year code (the last digit of year)
 M: Month code
 W: Week code
 C: Control code
 Type No.: delete HD74 and package code (RP) from device name

(c) Thin Shrink Small outline Package 14, 16, 20 pins

The diagrams show three packages. The first is 'HD74BC Series' with 'YMWC', 'B C', and 'A' followed by three squares. The second is 'HD74AC Series' with 'YMWC', 'A C', and three squares. The third is 'HD74HC Series' with 'YMWC', 'H C', and three squares. Arrows point to the top-right corner for 'Lot No.' and the bottom-right corner for 'Type No.' on the HD74HC package.

Note: Meaning of marking on package example device name:
HD74BC245AT
 Y: Year code (the last digit of year)
 M: Month code
 W: Week code
 C: Control code
 Type No.: delete HD74 and package code (T) from device name

Revision Record

Rev.	Date	Description	
		Page	Summary
1.00	Jul.09.04	—	First edition issued

Keep safety first in your circuit designs!

1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage.
Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.
2. Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information before purchasing a product listed herein.
The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.
Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (<http://www.renesas.com>).
4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
5. Renesas Technology Corp. semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
6. The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials.
7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
8. Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.