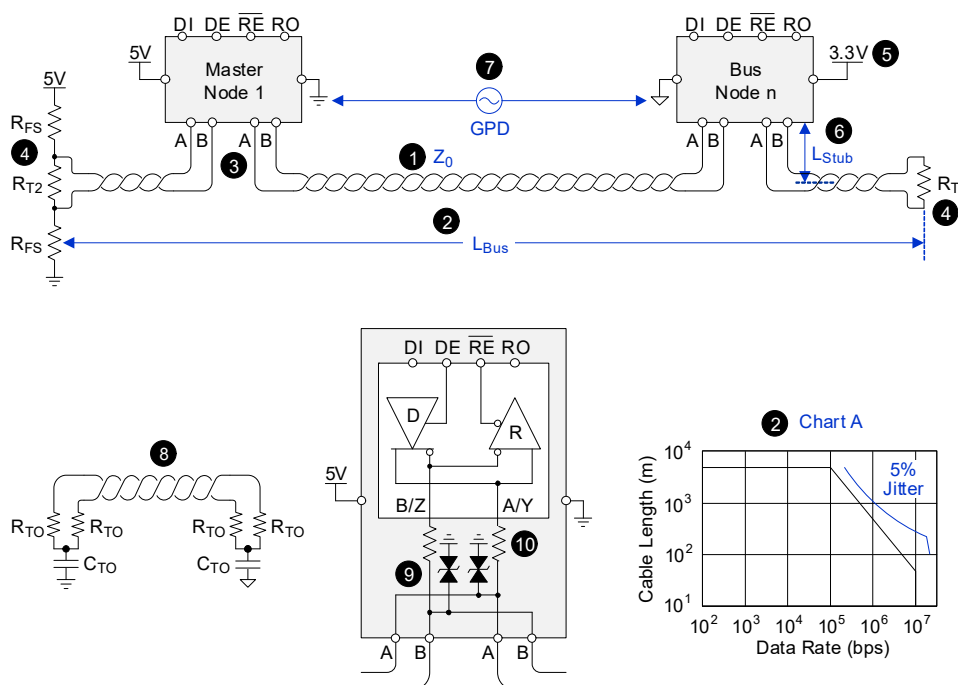


RS-485 Design Tips

This tutorial provides recommendations for quickly starting the design process with compatible RS-485 devices.



Ten Best Design Tips

Note: Each tip is referenced in the diagram by number.

- Use the twisted-pair cable with the following: $Z_0 = 120\Omega$ or 100Ω
- Determine maximum cable length, L_{Bus} , with Chart A.
- Connect the bus nodes with the Daisy-chain.
- Terminate one cable end with the following: $R_{T1} = Z_0$
Apply the failsafe biasing to the other end with the following:

$$R_{FS} = \left(\frac{V_{CC-min}}{V_{AB-idle}} + 1 \right) \cdot k$$

$$k = 27.8\Omega \text{ for } Z_0 = 120\Omega$$

$$k = 23.4\Omega \text{ for } Z_0 = 100\Omega$$
 Terminate this end with the following:

$$R_{FS} = \frac{R_{FS} \cdot Z_0}{R_{FS} - Z_0}$$
- You can operate 3V and 5V transceivers on the same bus.
- Make the stub length no longer than the following:

$$L_{Stub} < 3 \cdot 10^{-4} \cdot t_r \cdot v$$

$$L_{Stub} = \text{stub length (m)}$$

$$t_r = \text{driver rise time (ns)}$$

$$v = \text{signal velocity in cable (\%)}$$
- For GPD = ± 7 , use ISL315xE or RAA78815x
For GPD > $\pm 15V$, use ISL324xx
For higher GPDs, use ISL31xxE + optocouplers
- Terminate unused conductors with the following:
 $R_{TO} = Z_0/2$ and $C_{TO} = 1\mu F$
- For ESD, EFT, and Surge protection:
Use SM712 or read AN1976, AN1977, AN1978, and AN1979.
- Limit transient current into the transceiver with the following:
20 Ω carbon-composite or MELF resistors

Revision History

| Revision | Date | Description |
|----------|-------------|------------------|
| 1.00 | Nov 8, 2023 | Initial release. |

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.0 Mar 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.