## Old Company Name in Catalogs and Other Documents

On April 1<sup>st</sup>, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <a href="http://www.renesas.com">http://www.renesas.com</a>

April 1<sup>st</sup>, 2010 Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (http://www.renesas.com)

Send any inquiries to <a href="http://www.renesas.com/inquiry">http://www.renesas.com/inquiry</a>.



#### Notice

- 1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
- Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights
  of third parties by or arising from the use of Renesas Electronics products or technical information described in this document.
  No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights
  of Renesas Electronics or others.
- 3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
- 4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
- 5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
- 6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
- 7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
  - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
  - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
  - "Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
- 8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
- 9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
- 10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- 11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



# **HD74LS194A**

## 4-bit Bidirectional Universal Shift Register

REJ03D0456-0300 Rev.3.00 Jul.15.2005

The bidirectional shift register is designed to incorporate virtually all of the features a system designer may want in a shift register. The circuit contains 46 equivalent gates and features parallel inputs, parallel outputs, right-shift and left-shift serial inputs. Operating-mode-control inputs, and a direct overriding clear line. The register has four distinct modes of operation, namely;

- Parallel (broadside) load
- Shift right (in the direction Q<sub>A</sub> toward Q<sub>D</sub>)
- Shift left (in the direction  $Q_D$  toward  $Q_A$ )
- Inhibit clock (do nothing)

Synchronous parallel loading is accomplished by applying the four bits of data and taking both mode control inputs,  $S_0$  and  $S_1$ , high. The data are loaded into the associated flip-flops and appear at the outputs after the positive transition of the clock input. During loading, serial data flow is inhibited. Shift right is accomplished synchronously with the rising edge of the clock pulse when  $S_0$  is high and  $S_1$  is low. Serial data for this mode is entered at the shift-right data input. When  $S_0$  is low and  $S_1$  is high, data shifts left synchronously and new data is entered at the shift-left serial input.


Clocking of the flip-flop is inhibited when both mode control inputs are low.

• Ordering Information

Part Name	Package Type	Package Code (Previous Code)	Package Abbreviation	Taping Abbreviation (Quantity)
HD74LS194AP	DILP-16 pin	PRDP0016AE-B (DP-16FV)	Р	_
HD74LS194AFPEL	SOP-16 pin (JEITA)	PRSP0016DH-B (FP-16DAV)	FP	EL (2,000 pcs/reel)

Note: Please consult the sales office for the above package availability.

## Pin Arrangement

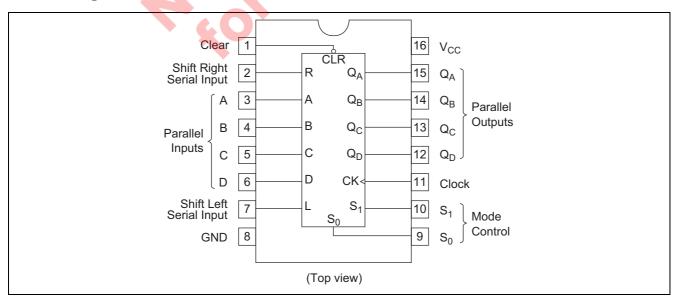


#### **Function Table**

				Inp	uts						Out	puts	
Clear	Мо	ode	Clock	Se	rial		Para	allel		0	0	0	0
Clear	S <sub>1</sub>	S <sub>0</sub>	Clock	Left	Right	Α	В	С	D	$Q_A$	Q <sub>B</sub>	Qc	$Q_D$
L	Х	Х	Х	Х	Х	Х	Х	Х	Х	L	L	L	L
Н	Х	Х	L	Х	Х	Х	Х	Х	Х	$Q_{A0}$	$Q_{B0}$	Q <sub>C0</sub>	$Q_{D0}$
Н	Н	Н	1	Х	Х	а	b	С	d	а	b	С	d
Н	L	Н	1	Х	Н	Х	Х	Х	Х	Н	Q <sub>An</sub>	$Q_{Bn}$	Q <sub>Cn</sub>
Н	L	Н	1	Х	L	Х	Х	Х	Х	L	Q <sub>An</sub>	$Q_{Bn}$	Q <sub>Cn</sub>
Н	Н	L	1	Н	Х	Х	Х	Х	Х	$Q_{Bn}$	Q <sub>Cn</sub>	$Q_{Dn}$	Н
Н	Н	L	1	L	Х	Х	Х	Х	Х	$Q_{Bn}$	Q <sub>Cn</sub>	$Q_{Dn}$	L
Н	L	L	Х	Х	Х	Х	Х	Х	Х	$Q_{Ao}$	$Q_{Bo}$	$Q_{Co}$	$Q_{Do}$

Notes: 1. H; high level, L; low level, X; irrelevant

- 2. 1; transition from low to high level
- 3. a to d; the level of steady-state input at inputs A, B, C, or D, respectively
- 4. Q<sub>A0</sub> to Q<sub>D0</sub>; the level of Q<sub>A</sub>, Q<sub>B</sub>, Q<sub>C</sub>, or Q<sub>D</sub>, respectively before the indicated steady-state input conditions were established.
- 5.  $Q_{An}$  to  $Q_{Dn}$ ; the level of  $Q_A$ ,  $Q_B$ ,  $Q_C$ , or  $Q_D$ , respectively before the most-recent  $\uparrow$  transition of the clock.

#### **Block Diagram**

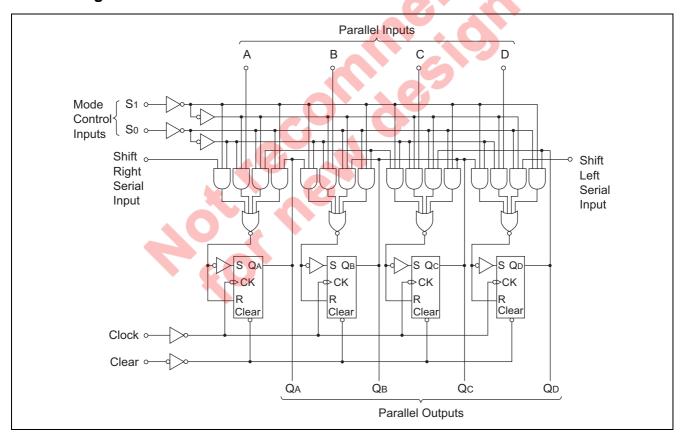

### **Absolute Maximum Ratings**

Item	Symbol	Ratings	Unit
Supply voltage	V <sub>CC</sub>	7	V
Input voltage	V <sub>IN</sub>	7	V
Power dissipation	P <sub>T</sub>	400	mW
Storage temperature	Tstg	-65 to +150	°C

Note: Voltage value, unless otherwise noted, are with respect to network ground terminal.

## **Recommended Operating Conditions**

	Item	Symbol	Min	Тур	Max	Unit
Supply voltage	Э	V <sub>CC</sub>	4.75	5.00	5.25	V
Output current	•	I <sub>OH</sub>	_	_	-400	μΑ
Output current	L	I <sub>OL</sub>	_	_	8	mA
Operating tem	perature	T <sub>opr</sub>	-20	25	75	°C
Clock frequen	су	fclock	0	_	25	MHz
Clock pulse width		t <sub>w (CK)</sub>	20	- )	_	ns
Clear pulse wi	dth	t <sub>w (CLR)</sub>	20	- 0	_	ns
	Mode Control		30		_	ns
Setup time	A, B, C, D, R, L	t <sub>su</sub>	20		<u> </u>	ns
Cotap time	CLR (inactive state)	-su	25	- 6	<u> </u>	ns
Hold time		t <sub>h</sub>	0		<b>/</b> –	ns

## **Electrical Characteristics**

 $(Ta = -20 \text{ to } +75 \text{ }^{\circ}\text{C})$ 

Item	Symbol	min.	typ.*	max.	Unit	Condition
Input voltage	V <sub>IH</sub>	2.0	<u> </u>	4	V	
Input voltage	$V_{IL}$	4		0.8	V	
Output voltage	V <sub>OH</sub>	2.7	Z		V	$V_{CC} = 4.75 \text{ V}, V_{IH} = 2 \text{ V}, V_{IL} = 0.8 \text{ V}, \\ I_{OH} = -400  \mu\text{A}$
Output voltage	Vol	_		0.4	V	$I_{OL} = 4 \text{ mA}$ $V_{CC} = 4.75 \text{ V}, V_{IH} = 2 \text{ V},$
	VOL	+		0.5	v	$I_{OL} = 8 \text{ mA}$ $V_{IL} = 0.8 \text{ V}$
	I <sub>IH</sub>		_	20	μΑ	$V_{CC} = 5.25 \text{ V}, V_{I} = 2.7 \text{ V}$
Input current	l <sub>IL</sub>	(	_	-0.4	mA	$V_{CC} = 5.25 \text{ V}, V_{I} = 0.4 \text{ V}$
	l <sub>l</sub>	_	_	0.1	mA	$V_{CC} = 5.25 \text{ V}, V_{I} = 7 \text{ V}$
Short-circuit output current	I <sub>OS</sub>	-20		-100	mA	V <sub>CC</sub> = 5.25 V
Supply current**	I <sub>CC</sub>	_	15	23	mA	V <sub>CC</sub> = 5.25 V
Input clamp voltage	$V_{IK}$	_	_	-1.5	V	$V_{CC} = 4.75 \text{ V}, I_{IN} = -18 \text{ mA}$

Notes:  $*V_{CC} = 5 \text{ V}$ ,  $Ta = 25^{\circ}C$ 

### **Switching Characteristics**


 $(V_{CC} = 5 \text{ V}, \text{ Ta} = 25^{\circ}\text{C})$ 

Item	Symbol	Inputs	Outputs	min.	typ.	max.	Unit	Condition
Maximum clock frequency	$f_{\sf max}$			25	36	_	MHz	
	t <sub>PHL</sub>	Clear			19	30	ns	$C_L = 15 pF$ ,
Propagation delay time	t <sub>PLH</sub>	Clock	Q	_	14	22	ns	$R_L = 2 k\Omega$
	t <sub>PHL</sub>	Clock		_	17	26	ns	




<sup>\*\*</sup> With all outputs open, inputs A through D grounded, and 4.5 V applied to  $S_0$ ,  $S_1$ , clear and the serial inputs,  $I_{CC}$  is tested with a momentary GND, then 4.5 V, applied to clock.

### **Count Sequences**

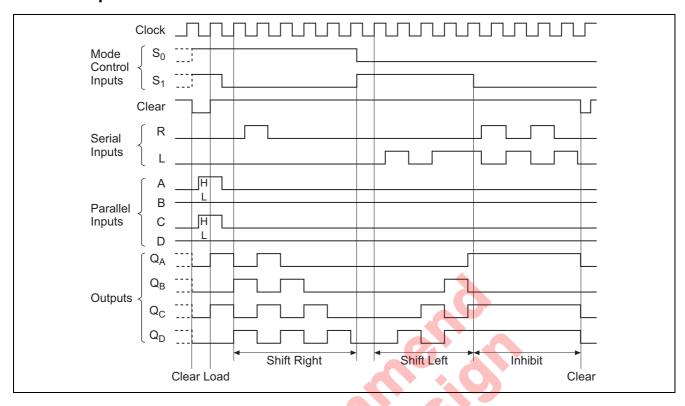

## **Testing Method**

#### **Test Circuit**

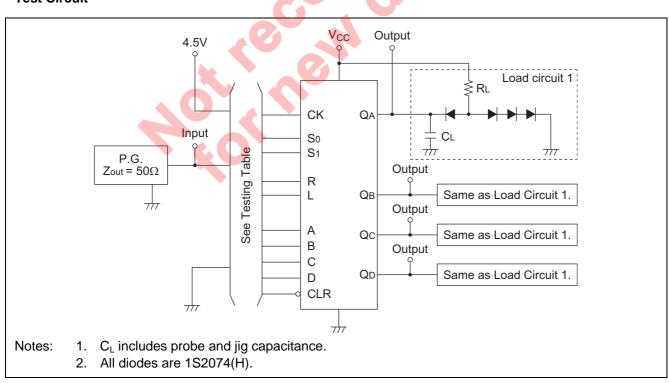


#### **Testing Table**

Item	From input to output					Inp	uts				
item	From input to output	CLR	S <sub>1</sub>	S <sub>0</sub>	СК	L	R	Α	В	С	D
£	right-shift	4.5V	4.5V	GND	IN	4.5V	IN	GND	GND	GND	GND
fmax	left-shift	4.5V	GND	4.5V	IN	IN	4.5V	GND	GND	GND	GND
	Clear→Q	IN	4.5V	4.5V	IN	GND	GND	4.5V	4.5V	4.5V	4.5V
t <sub>PLH</sub>	Clock→Q	4.5V	4.5V	GND	IN	4.5V	IN	GND	GND	GND	GND
t <sub>PHL</sub>	CIUCK→Q	4.5V	4.5V	GND	IN	IN	4.5V	GND	GND	GND	GND


Item	From input to output		Out	puts	
itein	From input to output	$\mathbf{Q}_{A}$	Q <sub>B</sub>	Q <sub>C</sub>	$\mathbf{Q}_{D}$
£	right-shift	OUT	OUT	OUT	OUT
J max	left-shift	OUT	OUT	OUT	OUT
	Clear→Q	OUT	OUT	OUT	OUT
t <sub>PLH</sub>	Clock→Q	OUT	OUT	OUT	OUT
t <sub>PHL</sub>	CIOCK→Q	OUT	OUT	OUT	OUT

#### Waveforms 1

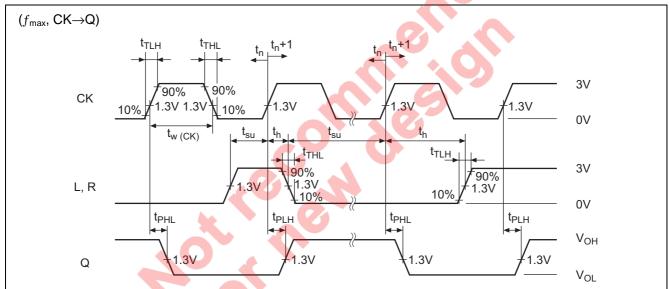



Notes: 1. Right-shift is measured with Q<sub>A</sub> at t<sub>n+1</sub>, Q<sub>B</sub> at t<sub>n+2</sub>, Q<sub>C</sub> at t<sub>n+3</sub>, and Q<sub>D</sub> at t<sub>n+4</sub>. Left-shift is measured with Q<sub>A</sub> at t<sub>n+4</sub>, Q<sub>B</sub> at t<sub>n+3</sub>, Q<sub>C</sub> at t<sub>n+2</sub>, and Q<sub>D</sub> at t<sub>n+1</sub>.

#### Waveforms 2

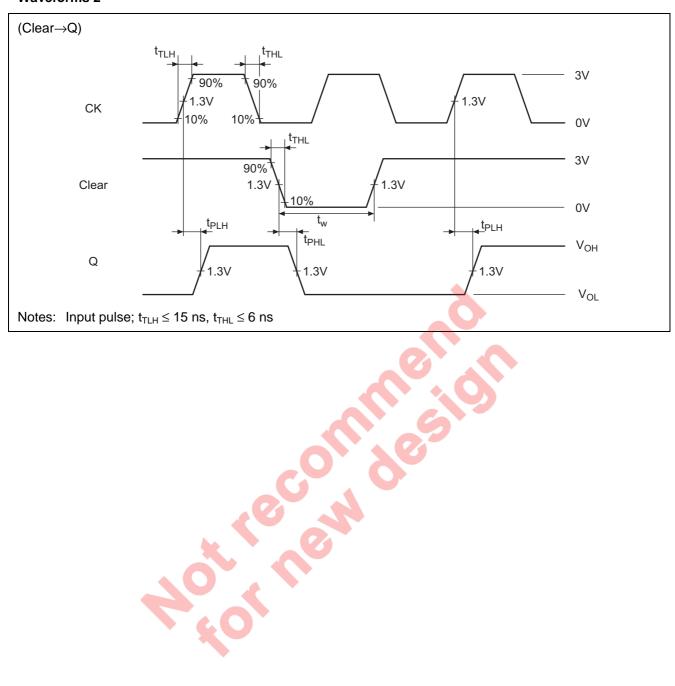

### **Package Dimensions**

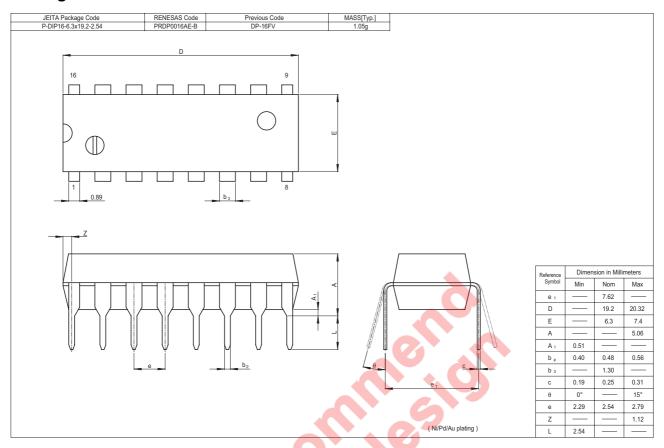

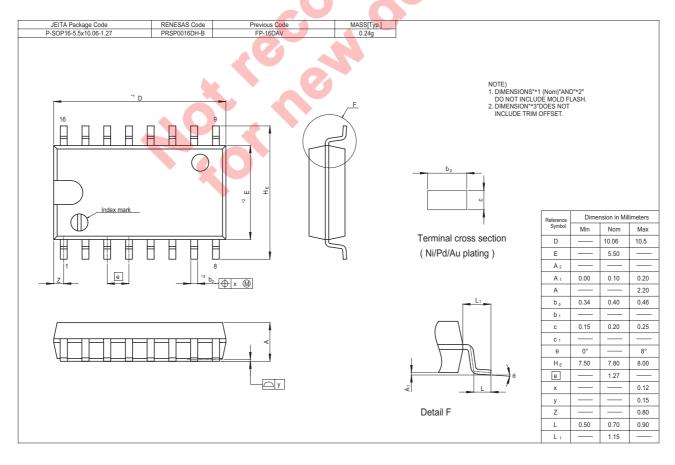

Renesas Technology Corp. Sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

Keep safety first in your circuit designs!

1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal righty, fire or property damage.

Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

Notes regarding these materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.

2. Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.

3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information before purchasing a product listed herein.

The information described here may contain technical inaccuracies or typographical errors.

Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.

Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (http://www.renesas.com).

A. When using any or all of the information published by reclievas recliniogy Corp. by various nitears, including the Reflexas Technology Corp. Semiconductor home page (http://www.renesas.com).
 When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. sensional products are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
 The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials.
 If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.

Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
 Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.



**RENESAS SALES OFFICES** 

http://www.renesas.com

Refer to "http://www.renesas.com/en/network" for the latest and detailed information.

Renesas Technology America, Inc. 450 Holger Way, San Jose, CA 95134-1368, U.S.A Tel: <1> (408) 382-7500, Fax: <1> (408) 382-7501

Renesas Technology Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: <44> (1628) 585-100, Fax: <44> (1628) 585-900

Renesas Technology Hong Kong Ltd.

7th Floor, North Tower, World Finance Centre, Harbour City, 1 Canton Road, Tsimshatsui, Kowloon, Hong Kong Tel: <852> 2265-6688, Fax: <852> 2730-6071

**Renesas Technology Taiwan Co., Ltd.** 10th Floor, No.99, Fushing North Road, Taipei, Taiwan Tel: <886> (2) 2715-2888, Fax: <886> (2) 2713-2999

Renesas Technology (Shanghai) Co., Ltd. Unit2607 Ruijing Building, No.205 Maoming Road (S), Shanghai 200020, China Tel: <86> (21) 6472-1001, Fax: <86> (21) 6415-2952

Renesas Technology Singapore Pte. Ltd.

1 Harbour Front Avenue, #06-10, Keppel Bay Tower, Singapore 098632 Tel: <65> 6213-0200, Fax: <65> 6278-8001

**Renesas Technology Korea Co., Ltd.**Kukje Center Bldg. 18th Fl., 191, 2-ka, Hangang-ro, Yongsan-ku, Seoul 140-702, Korea Tel: <82> 2-796-3115, Fax: <82> 2-796-2145

Renesas Technology Malaysia Sdn. Bhd. Unit 906, Block B, Menara Amcorp, Amcorp Trade Centre, No.18, Jalan Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia Tel: <603> 7955-9390, Fax: <603> 7955-9510

- 1
- 1