

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - "Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

4552 Group

Timer 1, Timer 2 (PWM Signal Output Control: Remote-Control Carrier Wave Output Control)

1. Abstract

The following article introduces and shows an application example of the PWM signal (remote-control carrier wave) output from CNTR pin by Timer 1 or Timer 2 of the 4552 Group.

2. Introduction

The explanation of this issue is applied to the following condition:

- Applicable MCU: 4552 Group
- Oscillation frequency: 3.64 MHz
- Operation mode: Frequency/4 mode

3. Contents

3.1 Application Example of PWM Signal Output Control

Outline

- Generate the PWM signal (remote-control carrier wave) by Timer 2.
- Control the output of the PWM signal to the CNTR pin by Timer 1.
- Switch the ON/OFF of the output of the CNTR pin every Timer 1 underflow.
- Timer 1 count source: PWM signal
Change the interval of ON/OFF of the output of the CNTR pin by change of the Timer 1 set value.
- Even when the output of the PWM signal to the CNTR pin is not performed, the PWM signal is generated internally.

Specifications

- PWM signal : 37.9 kHz, Duty 1/3
- CNTR output: Standard interval $T = 0.55$ ms, $8T$ output ON - $4T$ output OFF - T output ON

Figure 1 shows the auto-control of CNTR output by Timer 1, and Figure 2 shows the connection of Timer and the dividing ratio.

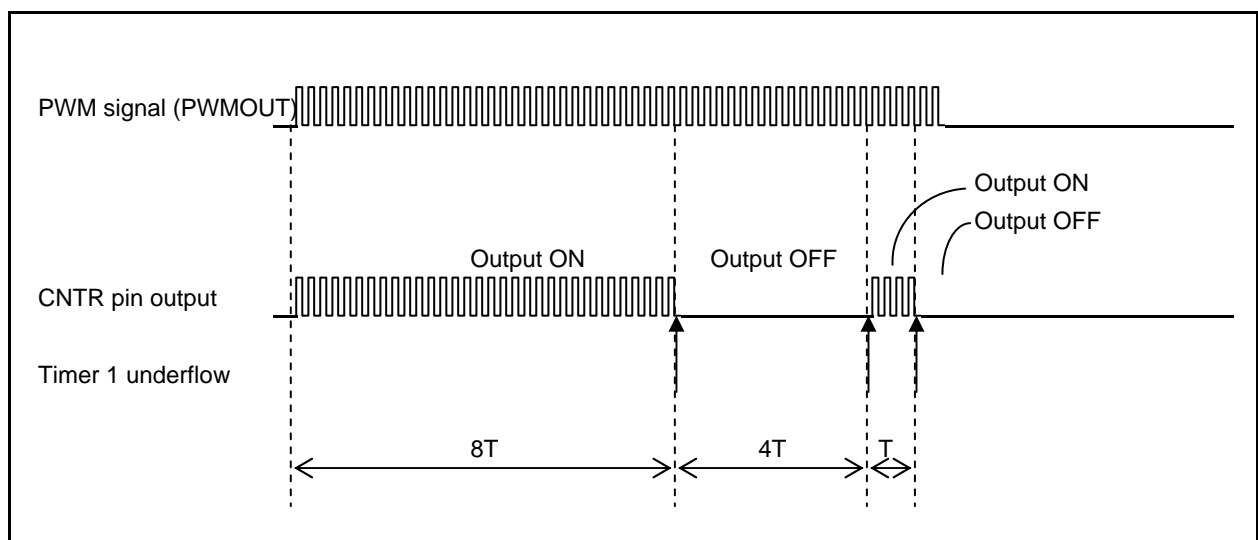


Figure 1 Auto-Control of CNTR Output by Timer 1

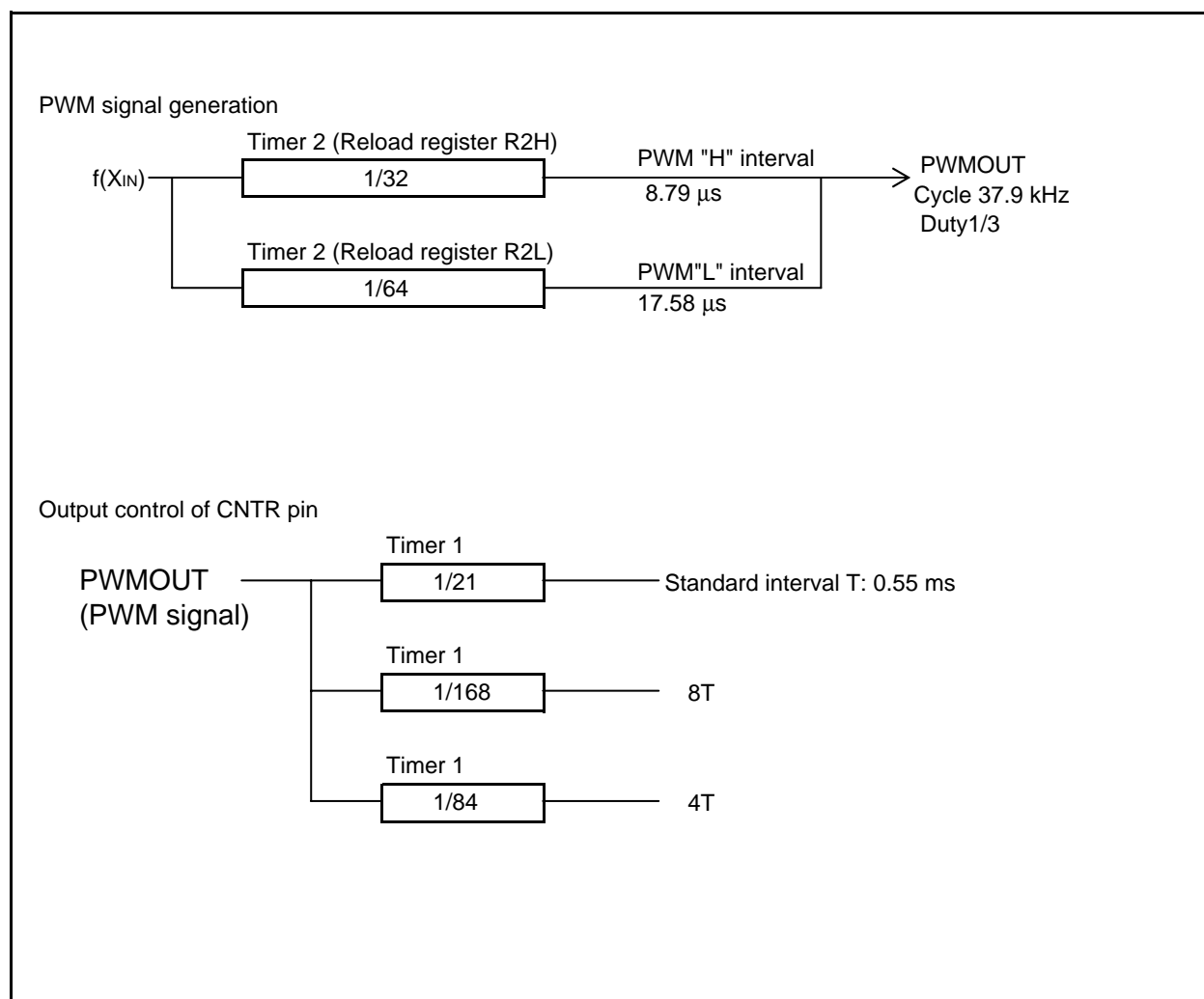


Figure 2 Connection Diagram of Timer and Dividing Ratio

3.2 Relevant Register Setting

Figure 3 shows the relevant register setting.

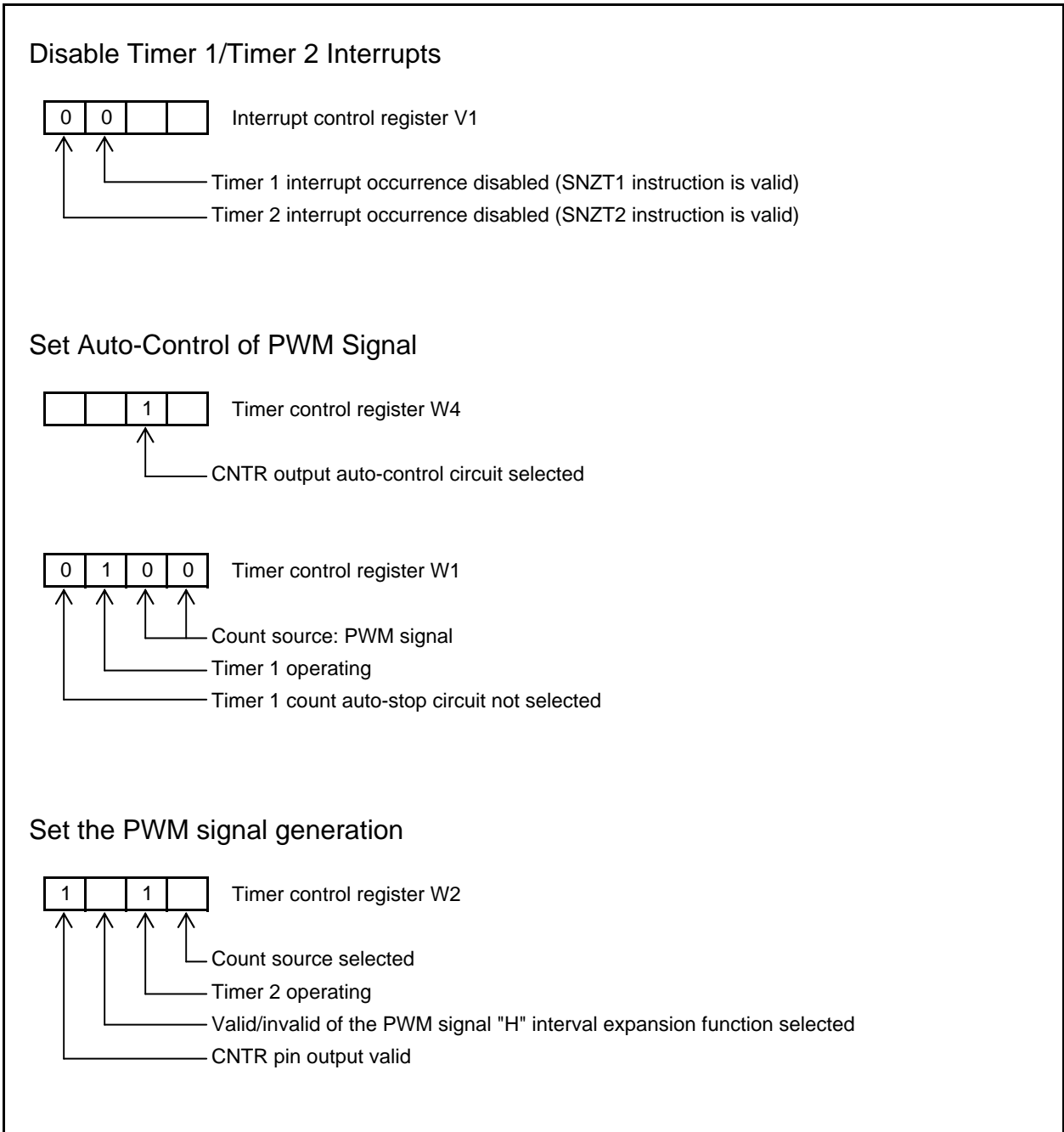


Figure 3 Relevant Register Setting

3.3 Control Procedure

Figure 4 and Figure 5 show the control procedure.

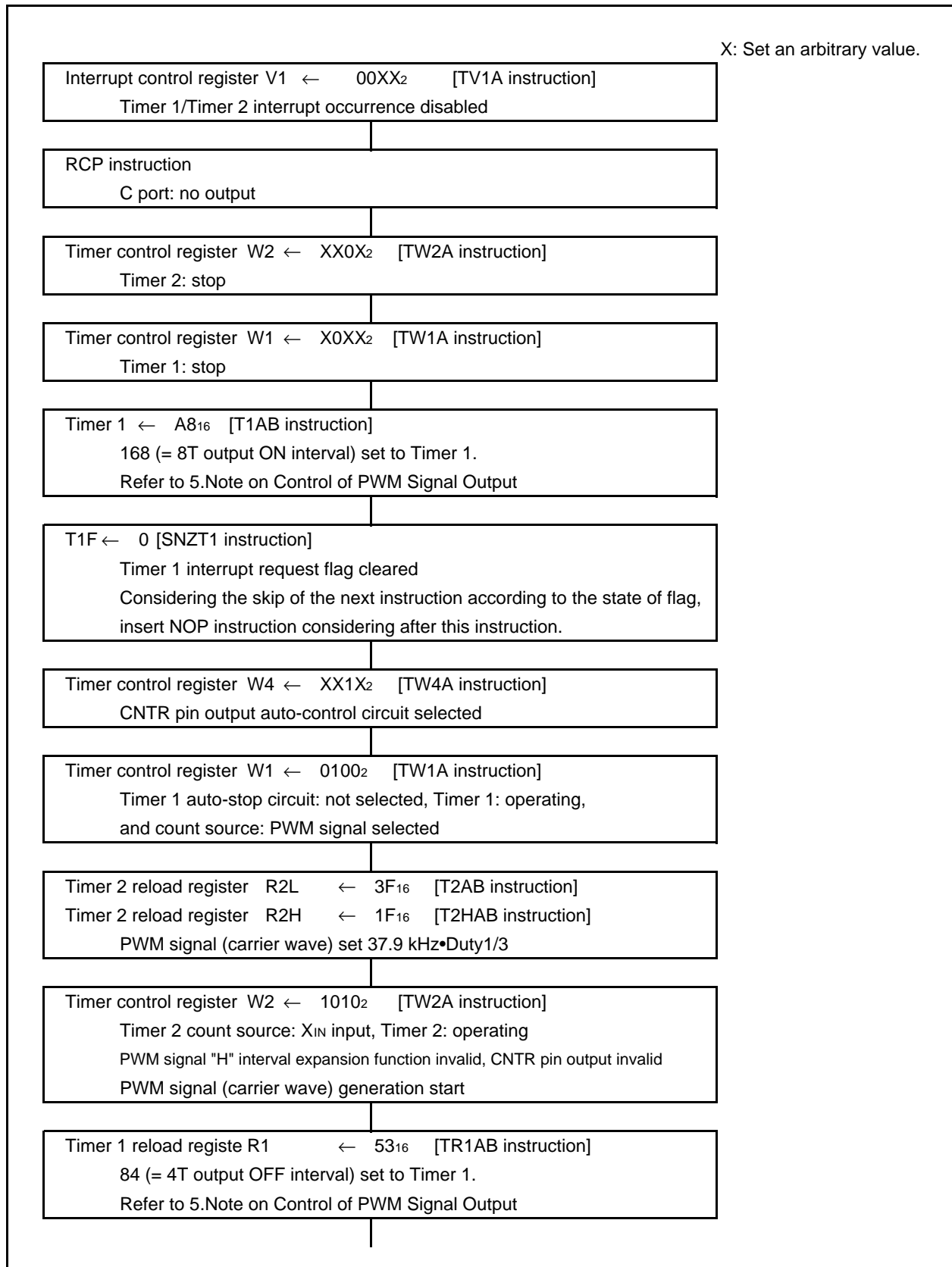


Figure 4 Control Procedure (1)

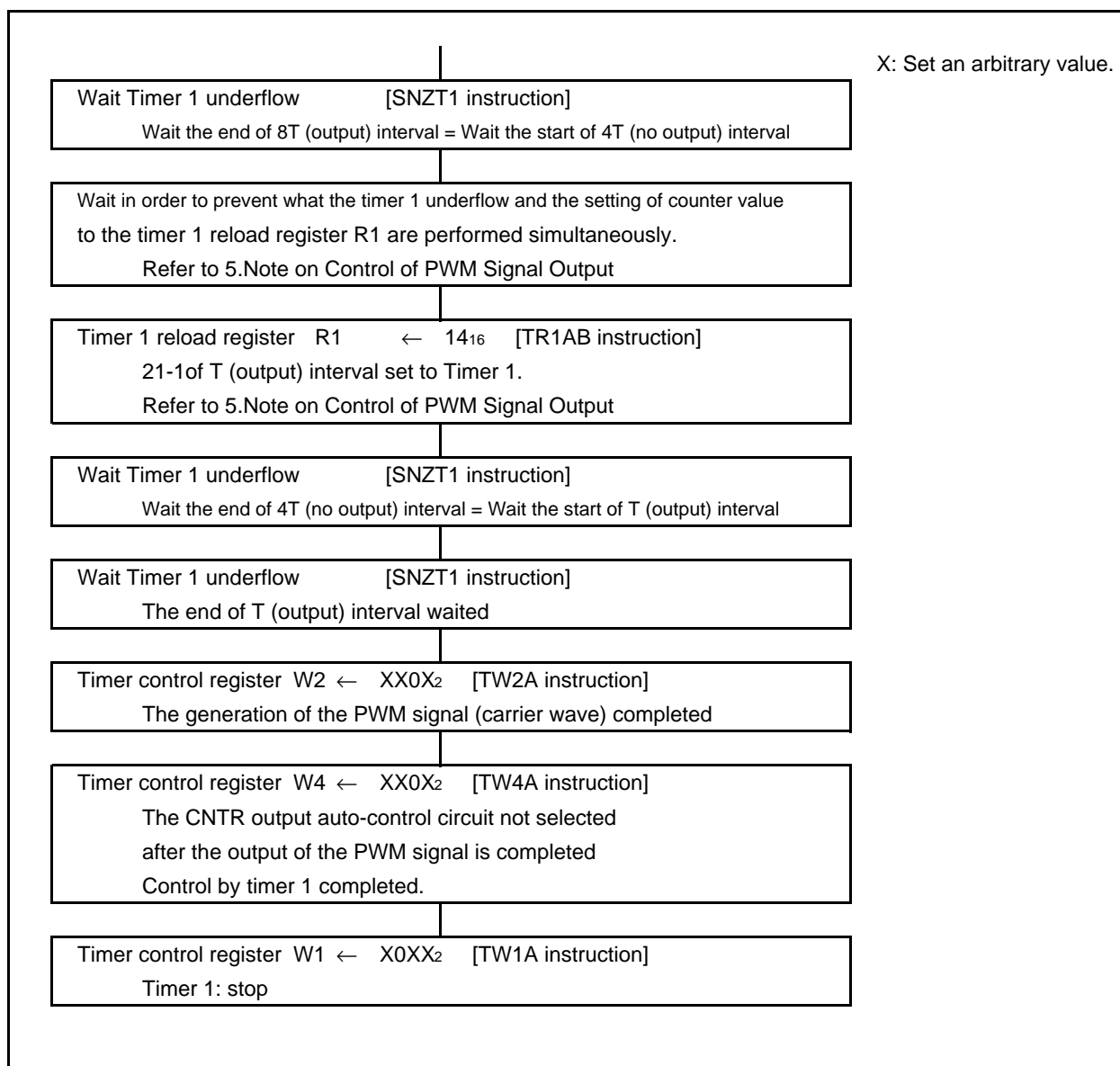


Figure 5 Control Procedure (2)

4. Sample Programming Code

Figure 6 and Figure 7 show the sample programming code.

| | | | |
|----------|-------|-------|--|
| EX_CNTR: | LA | 0000b | ; Disable Timer 1 • Timer 2 interrupts |
| | TV1A | | ; Set 0 to bit 2 of register V1 to use SNZT1 instruction |
| | RCP | | ; C/(CNTR) no output |
| | | | ; * Even if CNTR is used, H output function of port C is valid |
| | LA | 0000b | ; CNTR output: invalid • PWM signal "H" interval expansion function: invalid • |
| | TW2A | | ; Timer 2: stop |
| | LA | 0000b | ; Switch the Timer 1 auto-stop circuit from "not select state" to "selected state" |
| | TW1A | | |
| | LA | 0Ah | ; Set the counter value for the first output interval 4.4 ms (8T) |
| | TBA | | |
| | LA | 08h | ; As T is carrier wave 21 counts, |
| | T1AB | | ; 21 X 8 = 168 = A8h |
| | SNZT1 | | ; Clear Timer 1 underflow (interrupt request) flag |
| | NOP | | |
| | LA | 0010b | ; In order that the CNTR output auto-control circuit is selected state, |
| | TW4A | | ; set 1 to bit 1 of register W4. |
| | LA | 0100b | ; Timer 1 auto-stop circuit: not selected • Timer 1: operating • |
| | | | ; Count source: PWM signal |
| | TW1A | | ; Start operation of Timer 1 for the output control first |
| | LA | 03h | ; Set for the waveform of the PWM signal |
| | TBA | | ; L • 64 counts |
| | LA | 0Fh | ; (3Fh = 64–1) |
| | T2AB | | ; 64/3.64 MHz = 17.58 μs |
| | LA | 01h | ; H • 32 count |
| | TBA | | ; (1Fh = 32–1) |
| | LA | 0Fh | ; 32/3.64 MHz = 8.79 μs |
| | T2HAB | | |
| | LA | 1010b | ; Timer 2 • CNTR output: valid • "H" interval expansion: invalid |
| | TW2A | | ; Timer 2: operating • Count source: X _{IN} |
| | | | ; PWM signal cycle 17.58 μs + 8.79 μs = 26.37 μs ∴ 37.92 kHz |
| | | | ; X _{IN} /96 Duty1/3 |

Figure 6 Sample Programming Code (1)

```

LA      05h      ; Set the counter value for the no output interval 2.2 ms (4T)
TBA                                ; of the next PWM signal is set to reload register R1.
LA      03h      ; As T is carrier wave 21 counts,
TR1AB                                ; 21 X 4 = 84 = 54h = 53h + 1

WAIT_NH: SNZT1                                ; Wait the output interval 4.4 ms of the PWM signal
BL      WAIT_NH                                ; Wait more than one cycle of the PWM signal
NOP                                ; One cycle of PWM signal (26.37 μs) ≤ Wait time (3.30 μs X 8 = 26.40 μs)
NOP
NOP

LA      01h      ; Set the counter value for the output interval 0.55 ms (T)
TBA                                ; of the next PWM signal to reload register R1.
LA      04h      ; As T is carrier wave 21 counts,
TR1AB                                ; 21 = 15h = 14h + 1

WAIT_L:  SNZT1                                ; Wait the end of the no output interval 2.2 ms of the PWM signal
BL      WAIT_L

WAIT_END: SNZT1                                ; Wait the end of the output interval 0.55 ms of the PWM signal
BL      WAIT_END

LA      0000b    ; Stop Timer 2 (PWM signal generating side)
TW2A

NOP
NOP                                ; Wait more than one cycle of the PWM signal
NOP                                ; One cycle of PWM signal (26.37 μs) ≤ Wait time (3.30 μs X 8 = 26.40 μs)
NOP
NOP
NOP
NOP

LA      0000b    ; In order that the CNTR output auto-control circuit is unselected state,
TW4A                                ; set 0 to bit 1 of register W4

LA      0000b    ; Stop Timer 1 (CNTR output control side)
TW1A

```

Figure 7 Sample Programming Code (2)

5.Note on Control of PWM Signal Output

- The port C “H” output function is valid even when CNTR (output) pin is valid.
Clear "0" to the output latch of port C with the RCP instruction before the PWM signal is output.
- When the CNTR output auto-control by timer 1 is performed, set the frequency division to Timer 1 at the first time.
Set (frequency division - 1) to the reload register R1 after second times.
Also, the PWM signal is started at output, and it becomes the no-output state by the first Timer 1 underflow.
- Even when the CNTR pin output is set to be invalid by the CNTR pin output signal selection bit W23,
the generation of the PWM signal is not stopped internally by timer 2 until the end of the one cycle of the PWM signal.
- When writing data to the reload register R1 with the TR1AB instruction while Timer 1 is operating, avoid a timing when Timer 1 underflows.
In particular, wait one cycle or more of the timer 1 count source after underflow, and then,
set a value to the reload register R1.
Note is especially required when the cycle of the count source is longer than the machine cycle.

6. Reference

Data Sheet

4552 Group Data sheet

Before using this material, please visit our website to verify that this is the most updated document available.

Renesas Technology Corporation Semiconductor Home Page

<http://www.renesas.com>

E-mail Support

E-mail: support_apl@renesas.com

Revision Record

4552 Group (PWM signal output control)
APPLICATION NOTE

| Rev. | Date | Description | |
|------|------------|-------------|----------------------|
| | | Page | Summary |
| 1.00 | 2005.03.25 | - | First edition issued |
| | | | |
| | | | |
| | | | |
| | | | |

Keep safety first in your circuit designs!

1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (I) placement of substitutive, auxiliary circuits, (II) use of non-flammable material or (III) prevention against any malfunction or mishap.

Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.
2. Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information before purchasing a product listed herein.
The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss arising from these inaccuracies or errors.
Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (<http://www.renesas.com>).
4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
5. Renesas Technology Corp. semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
6. The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials.
7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
8. Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.