Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: http://www.renesas.com

April 1st, 2010 Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (http://www.renesas.com)

Send any inquiries to http://www.renesas.com/inquiry.



Notice

- 1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
- Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights
 of third parties by or arising from the use of Renesas Electronics products or technical information described in this document.
 No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights
 of Renesas Electronics or others.
- 3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
- 4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
- 5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
- 6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
- 7. Renesas Electronics products are classified according to the following three quality grades: "Standard", "High Quality", and "Specific". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as "Specific" without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as "Specific" or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is "Standard" unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - "Specific": Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
- 8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
- 9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
- 10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- 11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majorityowned subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



M51348AVP

VIF/SIF for Low Supply Voltage

REJ03F0062-0100Z Rev.1.0 Sep.19.2003

Description

The M51348 is a low supply voltage, low power semiconductor IC for compact TV sets which includes Video Intermediate Frequency (VIF), Sound Intermediate Frequency (SIF), and Synchronous Separation (Sync. Sep.) functions.

An IF amplifier. Video detector (with simultaneous sound detector), IF AGC, RF AGC (forward type), AFT, SIF limiter amplifier, FM detector electronic volume, and synchronous separation function are provided.

The package is of the 24-pin mini-flat type.

The M513848AFP has better DG and DP but less VIF input sensitivity than the M51348FP.

Features

• This IC can be used with very low supply voltage and low power and it comes in a mini-flat package to suit the compact TV or compact TV tuner.

Minimum operating power voltage 3V

Consuming current 16mA (when used with 4.5V supply voltage)

- Current automatically decreases to ensure power saving when a strong signal is received, when the electronic volume control is at its lowest.
- There are separate GND pins for the VIF/Sync. Sep. circuit and for the SIF circuit so that cross-interference is reduced.
- It is possible to adjust the video detector output amplitude by controlling the 24-pin voltage externally.
- The AGC works fast because of the 2-stage AGC filter.
 - AGC has high stability against outside noise due to the AGC noise canceller.
- Emitter input circuit is used in Sync. Sep. Output is taken from the Sync. Positive polarity.


Application

Portable B/W, color TV

Recommend Operating Condition


Supply voltage range 3.0V to 6.0V

Rated supply voltage 4.5V

 




Block diagram &Pin configuration

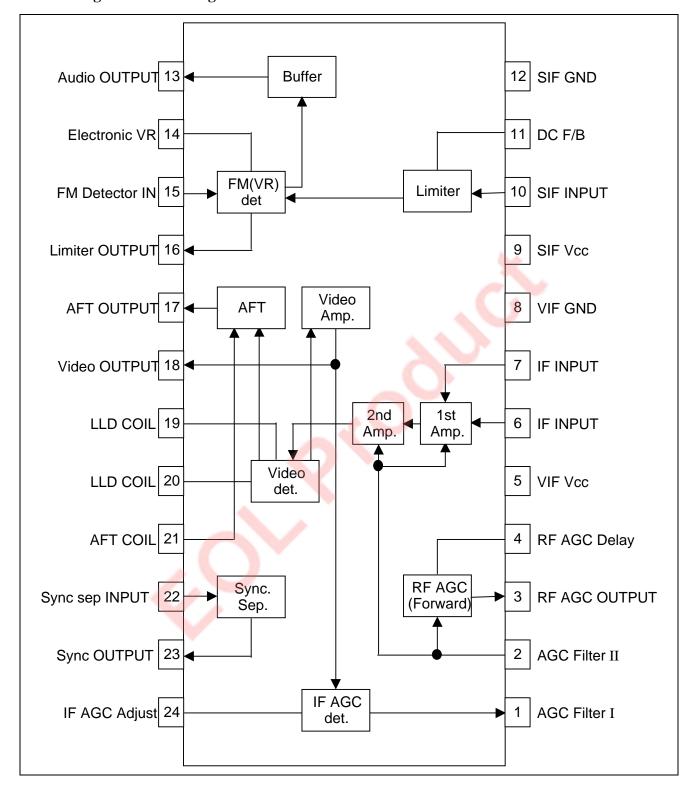

Absolute maximum ratings

(Ta=25°C,unless otherwise noted.)

Parameter	Symbol	Ratings	Unit	Note
Supply Voltage(1)	Vcc(5)	7.5	V	
Supply Voltage(2)	Vcc(9)	7.5	V	
Power Dissipation	Pd	360	mW	
Operating Temperature	Topr	- 20 to +75	°C	
Storage Temperature	Tstg	- 40 to +125	°C	

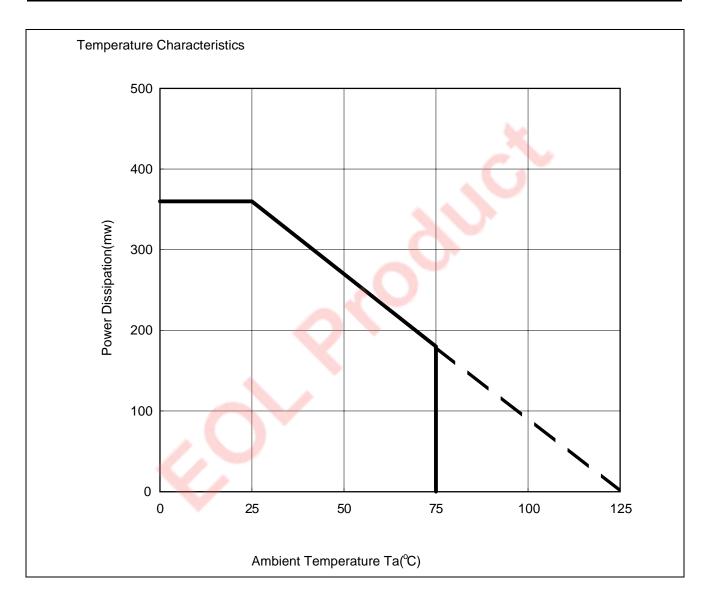

Electrical Characteristics

AC Characteristic (VIF)


(Ta = 25° C, unless otherwise noted.)

	Те		Test	est			Limits		
No	Parameter	symbol	point	Input	Test conditions	min	Тур.	max	Unit
1	Circuit current	I _{VIE}	(5)	_	Input current with 4.5V in 5	10	15	20	mA
2	Video detector output	Vodet	18	SG1 90dBμ	Output amplitude.	0.7	0.9	1.1	Vp- p
3	Input sensitivity	Vinmin	18	SG1 Variable	Input level when output amplitude reaches 3dB less than Vo det.	_	45	55	dBμ
4	Maximum allowable input	Vinmax	18	SG1 Variable	Input level when output amplitude reaches 3dB more than Vo det.	100	111		dBμ
5	Video frequency characteristic	BW	18	SG2	BW is defined as f1- f2 whenoutput amplitude reaches - 3dB less than when f1- f2=1MHz.	6	7	_	MHz
6	RF AGC maximum voltage	V_{3H}	3	SG4 90dBμ	Output DC voltage with 4.5V in 4.5V	3.2	3.7	_	Vo- p
7	RF AGC minimum voltage	V_{3L}	3	SG4 90dBμ	Output DC voltage with 2V in ④	_	0	0.2	Vo- p
8	AFT detector sensitivity	μ	17	SG5 90dBμ	Refer to note1	30	50	_	mV /KHz
9	DC voltage at AFT mute ON	V _{M17}	17	SG5 90dBμ	Output DC voltage with 0V in 21).	2	2.25	2.5	V
10	AFT center voltage	V_{AC}	17	- /	Output DC voltage with 0V in 2	0.5	1.4	2.5	V
11	Sync.Sep.output voltage	Vsync	23	SG1 90dBµ	Output amplitude.	3.5	3.8	4.1	Vp-p
12	Operating voltage	V _{VIF}	5	SG1 90dBµ	Must be operated.	3	_	6	V
13	Video detector output at high or low voltage	VoHdet	18	SG1 90dBμ	Output amplitude with 6.0V or 3.0V in 5	0.95	1.25	1.55	Vp-p

AC Characteristic (SIF)


			Test			Limits	5		
No	Parameter	symbol	point	Input	Test conditions	min	Тур.	max	Unit
1	Circuit current	I _{SIF}	9	_	Input current with 4.5V in 9	2.2	3.2	4.2	mA
2	Detector output• voltage	Vo _{AF}	13	SG6 90dBμ	Output amplitude.	200	240	280	mVrms
3	Input limiting sensitivity	Vimin	13	SG6 Variable	Input level when input amplitude reaches - 3dB below Vo _{AF} .	_	32	49	dBμ
4	AM rejection ratio	AMR	13	SG7 90dBμ	Where V_{AM} denotes output amplitude, $AMR = 20log \frac{Vo_{AF}(mVrms)}{V_{AM}(mVrms)}$	40	53	_	dB
5	Bandwidth	BW(s)	13	SG8 90dBμ	Refer to note2.	100	130	_	kHz
6	Electronic volume	VR1	13	SG6	Ratio of output amplitude	3.0	3.9	4.8	dB
	control characteristic	VR2	-	90dBμ	and Vo _{AF} when (4) is changed from 4.0V to 1.0v.	N	-53	-45	-
7	Distortion	THD	13	SG9 90dBμ	Measured by distortion meter.	-	0.4	1.0	%
8	Operating voltage	V _{SIF}	9	SG6 90dBμ	Must be operated.	3	_	6	V
9	Detector output	VoH _{AF}	13	SG6	Output amplitude with 6.0V	380	430	480	mVrms
	voltage at high or low voltage	VoL _{AF}	_	90dBμ	or 3.0V in(9)	53	64	75	-

Test Circuit

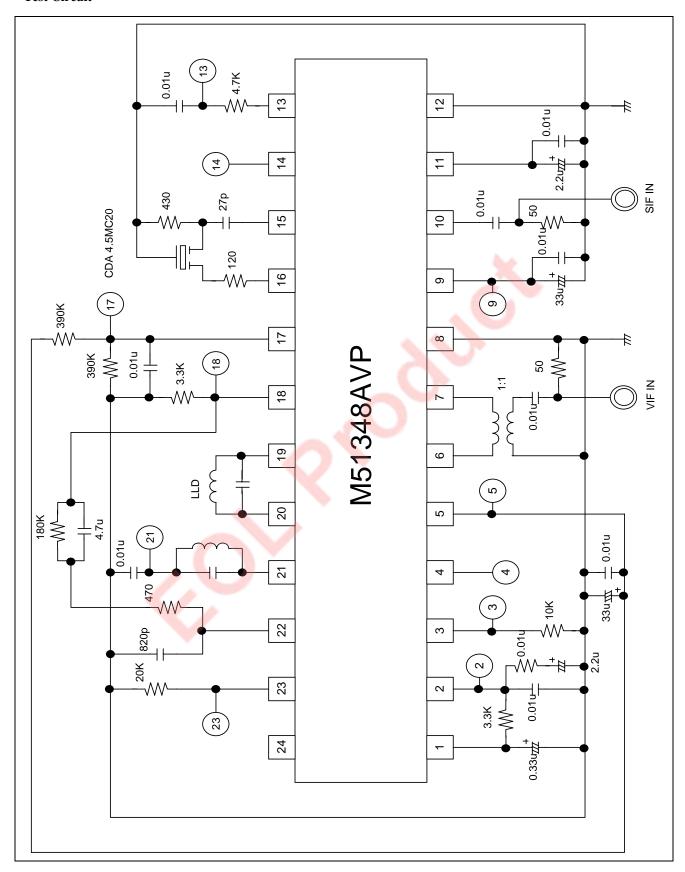

Precaution concerning electical charactristics

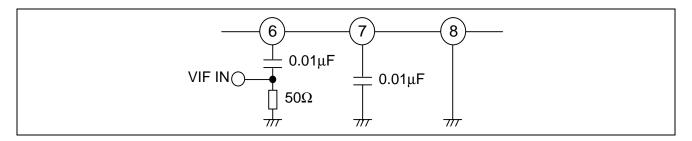
- 1) Voltage Supplied (pins 5 and 9)is 4.5V unless otherwise noted in the conditions column.
- 2) VIF input amplitude (Vin)is the amplitude of VFI IN in the circuit below. Feed SG1 90dB μ signal into the circuit below, and measure the DC voltage V2 at 2)Set the circuit for AC voltage measurement and adjust the input amplitude, monitoring DC voltage at 2), until it reaches the level of V2.90dB μ is defined as the input amplitude at that time.




2)	1 .	. 1		1	1 1
3)	Innut	signals	are	shown	below.
~,	111				0010

SG1	fo=58.75MHz	fm=20KHz	77.8%AM
SG2	f1=58.75MHz	Vi=90dBµ	CW
	f2=53 ±5MHz	$Vi=70dB\mu$	CW
SG3	fo=58.75MHz	Linearity 10step signal	
		(87.5% Video modulation	1)
SG4	fo=58.75MHz		CW
SG5	fo=58.75 ±5MHz		CW(SWEEP)
SG6	fo=4.5MHz	FM 25KHz dev	fm=400Hz
SG7	fo=4.5MHz	AM 30%	fm=400Hz
SG8	fo=4.5MH• ±200KH•	FM 7.5KHz dev	fm=400Hz
SG9	fo=4.5MH•	FM 7.5KHz dev	fm=400Hz

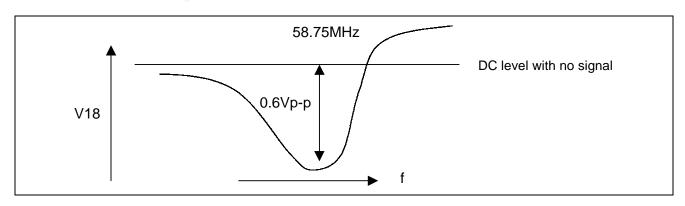
- 4) Adjustment of LLD coil
 - 1. Feed SG5 Vi=90dBµ into VIF IN.
 - 2. AFT coil must be shifted to detuned condition.
 - 3. Feed outside voltage to 2 and check tank response at (8) as shown in the figure below.
 - 4. Adjust LLD coil so that peak comes at 58.75MHz.



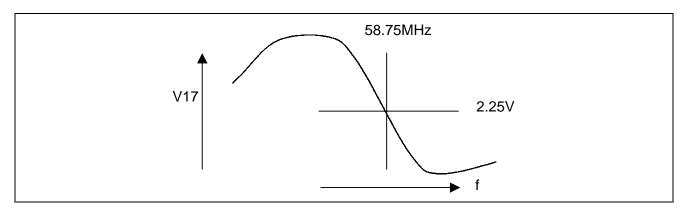- 5) Adjustment of AFT coil
 - 1. Feed SG5 Vi=90dBµ in VIF IN.
 - 2. Measure the voltage at pin ① and adjust AFT coil as shown in the figure below.



Note1 AFT detector sensitivity " μ "

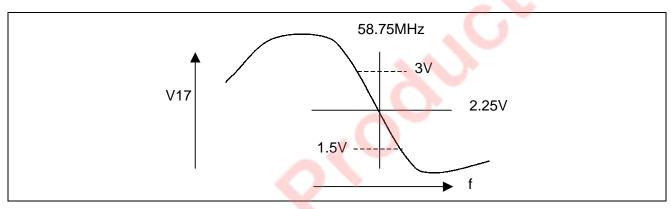

Where f_A denotes a frequency at A and f_B at B.

$$\mu$$
= 1500mV
 $f_B(kHz)-f_A(kHz)$


Note2 Bandwidth "BW(s)"

First, define Vo(DET)FM as the output amplitude when the signal fo=4.5MHz, fm=400Hz and fdev= $\pm 7.5KHz$ is given to SIF IN.

Decrease and increase the frequency to until the output amplitude reaches - 3dB than Vo(DET)FM. These are defined as fo L and fo H respectively. Bandwidth is defined as

BW(s) = foH-foL

Package Dimensions

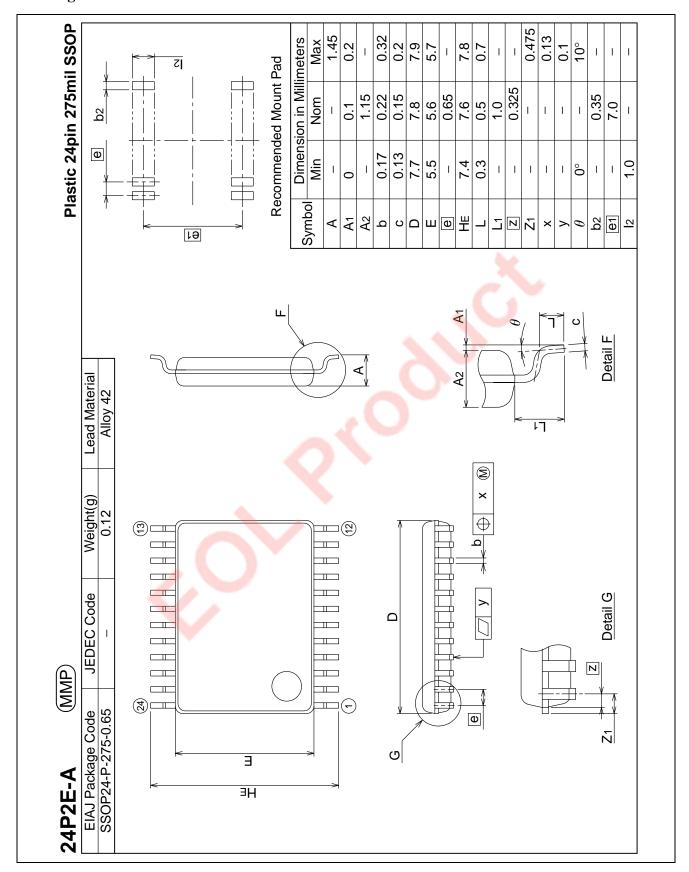

Renesas Technology Corp. Sales Strategic Planning Div. Nippon Bldg., 2-6-2, Ohte-machi, Chiyoda-ku, Tokyo 100-0004, Japan

Keep safety first in your circuit designs!

1. Renesas Technology Corp. puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage.

Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corp. product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corp. or a third party.

2. Renesas Technology Corp. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.

3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corp. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corp. or an authorized Renesas Technology Corp. product distributor for the latest product information described here may contain technical inaccuracies or typographical errors.

Renesas Technology Corp. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.

Please also pay attention to information published by Renesas Technology Corp. by various means, including the Renesas Technology Corp. Semiconductor home page (http://www.renesas.com).

4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corp. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.

5. Renesas Technology Corp. semiconductors are not designed or manufactured for use in a device or system that is used

- use.

 6. The prior written approval of Renesas Technology Corp. is necessary to reprint or reproduce in whole or in part these materials.

 7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.

 Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.

 8. Please contact Renesas Technology Corp. for further details on these materials or the products contained therein.



RENESAS SALES OFFICES

http://www.renesas.com

Colophon 1.0

Renesas Technology America, Inc. 450 Holger Way, San Jose, CA 95134-1368, U.S.A Tel: <1> (408) 382-7500 Fax: <1> (408) 382-7501

Renesas Technology Europe Limited.

Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, United Kingdom Tel: <44> (1628) 585 100, Fax: <44> (1628) 585 900

Renesas Technology Europe GmbH Dornacher Str. 3, D-85622 Feldkirchen, Germany Tel: <49> (89) 380 70 0, Fax: <49> (89) 929 30 11

Renesas Technology Hong Kong Ltd. 7/F., North Tower, World Finance Centre, Harbour City, Canton Road, Hong Kong Tel: <852> 2265-6688, Fax: <852> 2375-6836

Renesas Technology Taiwan Co., Ltd. FL 10, #99, Fu-Hsing N. Rd., Taipei, Taiwan Tel: <886> (2) 2715-2888, Fax: <886> (2) 2713-2999

Renesas Technology (Shanghai) Co., Ltd. 26/F., Ruijin Building, No.205 Maoming Road (S), Shanghai 200020, China Tel: <86> (21) 6472-1001, Fax: <86> (21) 6415-2952

Renesas Technology Singapore Pte. Ltd.
1, Harbour Front Avenue, #06-10, Keppel Bay Tower, Singapore 098632 Tel: <65> 6213-0200, Fax: <65> 6278-8001