

To our customers,

Old Company Name in Catalogs and Other Documents

On April 1st, 2010, NEC Electronics Corporation merged with Renesas Technology Corporation, and Renesas Electronics Corporation took over all the business of both companies. Therefore, although the old company name remains in this document, it is a valid Renesas Electronics document. We appreciate your understanding.

Renesas Electronics website: <http://www.renesas.com>

April 1st, 2010
Renesas Electronics Corporation

Issued by: Renesas Electronics Corporation (<http://www.renesas.com>)

Send any inquiries to <http://www.renesas.com/inquiry>.

Notice

1. All information included in this document is current as of the date this document is issued. Such information, however, is subject to change without any prior notice. Before purchasing or using any Renesas Electronics products listed herein, please confirm the latest product information with a Renesas Electronics sales office. Also, please pay regular and careful attention to additional and different information to be disclosed by Renesas Electronics such as that disclosed through our website.
2. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
3. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part.
4. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
5. When exporting the products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations. You should not use Renesas Electronics products or the technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations.
6. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
7. Renesas Electronics products are classified according to the following three quality grades: “Standard”, “High Quality”, and “Specific”. The recommended applications for each Renesas Electronics product depends on the product’s quality grade, as indicated below. You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application categorized as “Specific” without the prior written consent of Renesas Electronics. Further, you may not use any Renesas Electronics product for any application for which it is not intended without the prior written consent of Renesas Electronics. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for an application categorized as “Specific” or for which the product is not intended where you have failed to obtain the prior written consent of Renesas Electronics. The quality grade of each Renesas Electronics product is “Standard” unless otherwise expressly specified in a Renesas Electronics data sheets or data books, etc.
 - “Standard”: Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots.
 - “High Quality”: Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; safety equipment; and medical equipment not specifically designed for life support.
 - “Specific”: Aircraft; aerospace equipment; submersible repeaters; nuclear reactor control systems; medical equipment or systems for life support (e.g. artificial life support devices or systems), surgical implantations, or healthcare intervention (e.g. excision, etc.), and any other applications or purposes that pose a direct threat to human life.
8. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
9. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or system manufactured by you.
10. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
11. This document may not be reproduced or duplicated, in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.

(Note 1) “Renesas Electronics” as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.

(Note 2) “Renesas Electronics product(s)” means any product developed or manufactured by or for Renesas Electronics.

M16C/62

Using the M16C/62 CRC

1.0 Abstract

The register sets of the M16C/62 devices contain a Cyclic Redundancy Check (CRC) calculating peripheral. This gives the user the ability to quickly calculate a CRC given a stream of data.

2.0 Introduction

This article will not only explain how to use the CRC circuitry provided by the M16C, it will also explain the theory behind CRC and provide some helpful hints when developing with this error detection algorithm.

The CRC calculation circuit detects an error in data blocks. The microcomputer uses a generator polynomial of CRC_CCITT $X^{16} + X^{12} + X^5 + 1$ to generate CRC code.

The CRC code is a 16-bit code generated for a block of a given data length in multiples of 8 bits. The CRC code is set in a CRC data register each time one byte of data is transferred to a CRC input register after writing an initial value into the CRC data register. Generation of CRC code for one byte of data is completed in two machine cycles.

3.0 A Lesson in CRC and the CCITT Polynomial

In hardware, the CRC circuitry is quite easy to implement. It consists of 16 D-type flip-flop and some XOR gates. In CRC, new 8-bit values are shifted in order to manipulate the existing 16-bit value representing the current CRC result up until that point. For the CRC_CCITT polynomial, $X^{16} + X^{12} + X^5 + 1$ (or $X^{16} + X^{12} + X^5 + X^0$), the power X is raised to represents the bit location that needs to be Exclusive OR-ed with the bit that will become the overflow bit each time a new bit is shifted in.

For a refresher of the truth table for an Exclusive OR, see Table 1.

Table 1 Exclusive OR Truth Table

IN1	IN2	OUT
0	0	0
0	1	1
1	0	1
1	1	0

For a visual representation of the CRC_CCITT hardware, see Figure 1.

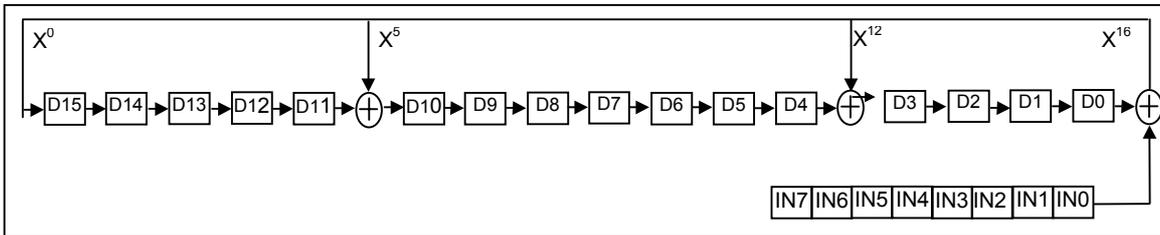


Figure 1 CRC_CCITT Hardware

Using the example in the data sheet for the M16C, the CRC data register is initialized to 0x0000 and a 0x01 is written to the CRC input register; the internal workings of the CRC_CCITT circuitry would be as shown in Table 2. The result shown in the last line would be in the CRC data register after the calculation is complete.

Table 2 CRC Data Register Example 1

D15	D14	D13	D12	D11	D10	D9	D8	D7	D6	D5	D4	D3	D2	D1	D0	X ¹⁶	IN
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1
1	0	0	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	0	0	0	1	0	0	0	0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1	0	0	0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	1	1	0	0	0	1	0	0	1	0	0	0	0	0
0	1	0	0	0	1	1	0	0	0	1	0	0	1	0	0	0	0
0	0	1	0	0	0	1	1	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	1	1	0	0	0	1	0	0	1	x	x
1				1				8				9					

x = don't care

The specification then continues the example by showing a 0x23 as the next input. The result is shown in Table 3.

Table 3 CRC Data Register Example 2

D15	D14	D13	D12	D11	D10	D9	D8	D7	D6	D5	D4	D3	D2	D1	D0	X ¹⁶	IN
0	0	0	1	0	0	0	1	1	0	0	0	1	0	0	1	0	1
0	0	0	0	1	0	0	0	1	1	0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	0	0	1	1	0	1	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	1	1	0	1	0	1	1	0
1	0	1	0	0	1	0	0	0	0	0	1	0	0	1	0	0	0
0	1	0	1	0	0	1	0	0	0	0	0	1	0	0	1	0	1
0	0	1	0	1	0	0	1	0	0	0	0	0	1	0	0	0	0
0	0	0	1	0	1	0	0	1	0	0	0	0	0	1	0	0	0
0	0	0	0	1	0	1	0	0	1	0	0	0	0	0	1	X	x
0				A				4				1					

4.0 LSB versus MSB CRC

For our CRC hardware, values are always shifted in Least Significant Bit (LSB) first, there is no option to allow MSB first. If Most Significant Bit (MSB) first CRC_CCITT is required, reverse-bit order your data (make D0-D7 = D7-D0) before you write it to the CRC register; then reverse-bit order the resulting data.

5.0 Reference

Renesas Technology Corporation Semiconductor Home Page

<http://www.renesas.com>

E-mail Support

support_apl@renesas.com

Data Sheets

- M16C/62 datasheets, 62aeds.pdf

6.0 Software Code

6.1 Calculating CCITT Using the M16C CRC Registers

The M16C provides two SFR registers for CRC_CCITT calculations:

- **CRC Data Register** – This is the 16-bit register that holds the current CRC result.
- **CRC Input Register** – This is the 8-bit register where data is fed to.

Therefore, the device firmware needed to represent the example above would be as follows:

```
unsigned int answer;
crcd = 0x0000;      /* Initialize data register to 0 */
crcin = 0x01;       /* add in first byte */
crcin = 0x23;       /* add in second byte */
answer = crcd;      /* answer will now equal 0x0A41 */
```

6.2 Software Algorithm for Deriving CCITT

The following is a software implementation of the CCITT polynomial. You may want to use this to create a program that will calculate the CRC_CCITT for your data so that you may incorporate the correct result into your firmware program.

```
unsigned int crc_buff = 0; /* init our buffer to 0 */
unsigned char input = 0x01; /* our first input will be 1 */
int i;
unsigned int x16;          /* we'll use this to hold the XOR mask */

for (i=0; i<8; i++) {
    /* XOR current D0 and next input bit to determine x16 value */
    if( (crc_buff & 0x0001) ^ (input & 0x01) )
        x16 = 0x8408;
    else
        x16 = 0x0000;

    /* shift crc buffer */
    crc_buff = crc_buff >> 1;

    /* XOR in the x16 value */
    crc_buff ^= x16;

    /* shift input for next iteration */
    input = input >> 1;
}
```

At the end of this for loop, `crc_buff` will equal 0x1189.

Keep safety first in your circuit designs!

- Renesas Technology Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

- These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corporation product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corporation or a third party.
- Renesas Technology Corporation assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
- All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor for the latest product information before purchasing a product listed herein.
The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corporation assumes no responsibility for any damage, liability, or other loss arising from these inaccuracies or errors.
Please also pay attention to information published by Renesas Technology Corporation by various means, including the Renesas Technology Corporation Semiconductor home page (<http://www.renesas.com>).
- When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corporation assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
- Renesas Technology Corporation semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
- The prior written approval of Renesas Technology Corporation is necessary to reprint or reproduce in whole or in part these materials.
- If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
- Please contact Renesas Technology Corporation for further details on these materials or the products contained therein.