

Choose a Digitally-Controlled Potentiometer Instead of a DAC?

There are two options for designers wishing to translate digital information into its analog corollary—a DCP or a DAC.

Traditional wisdom chooses a DAC when resolution or temperature stability is the reigning concern. That same wisdom selects a DCP when cost, memory, or flexibility with references is needed. Neither the DAC or DCP suppliers were content with small pieces of the market. DAC suppliers countered with smaller packages and smaller prices. DCP manufacturers capitalized on improvements in process technology to provide comparable temperature performance. As both camps jockey for your business, let's take a look at the state of the art.

Table 1 offers a side-by-side comparison of available attributes of DCPs and DACs. A few attributes such as package type are omitted because the two are so similar.

The prominent difference in Table 1 is in component resolution. Most DACs provide fixed resolutions; you can purchase 8-bit, 10-bit, 12-bit... up to 20-bit versions. That means the output voltage spans between the supply voltages (or close) in 256, 1024, or 2[#] bit steps. DCPs, on the other hand, are currently limited to 1024 taps (or 10 bits) by process steps that dictate the size of transistor switches and matched resistor structures. The hidden benefit, though, is the freedom to set the voltage on the ends of the potentiometer. If the ends are set at the rails, then the resolution of the output is equal to the number of taps. However, if the ends are set to a span of half the supply, then the output resolution also benefits by that same factor of two. In this way, the resolution of the DCP can be improved for a given application by simply adding resistance in series. The DCP won't feasibly reach 24 bits like some DACs, but the flexibility to vary the voltage across the fixed resistance provides different benefits.

There are many aspects to the flexibility of a DCP. Since the DCP doesn't need to be tied to fixed voltages, it can be easily used in the feedback path of an amplifier. Some DCPs, like the X9C103, incorporate charge pumps so that the output can

swing between dual supplies while the input remains between a single supply and ground. Others, like the AD5280, are designed to operate on a single +1.5 volt supply or ±5 volts.

Another issue is memory. Often, we would like the system to store information. The traditional solution for both a DAC and DCP is to include a separate EEPROM IC, so critical information would not be lost in case of a power disruption or failure. Most DACs do not include memory. The DCPs that have no integrated memory are labelled as “volatile”. Many DCPs now include non-volatile memory. With a minimum amount of EEPROM cells, basic information like wiper position can be stored. If additional EEPROM memory is included within the DCP package, then identification, calibration information, test conditions and more can be stored.

As for temperature stability, first glance gives preference to the DAC, with 5ppm/°C appearing 10 times better than a typical DCP. While it is true that the full-scale resistance of a DCP used to exhibit 600ppm/°C, the recent generations of process technologies provide 50ppm/°C of change in the total end-to-end resistance of a DCP. However, very few DCPs are used in this manner. More commonly, they are used as a voltage divider. When the resistances are relative (as in a voltage divider), it is the relative differences versus temperature that become most important. In this manner, the temperature performance is nearly 4ppm/°C and no longer a performance limitation in DCPs. In regard to DAC temperature performance, be careful when reading the datasheet. Many DACs choose to report a simple, small number like 5ppm/°C as the gain error only. There are many other aspects that will contribute to overall performance versus temperature. A few of these are integral non-linearity, reference tempco and long-term stability on top of the DAC's gain error. High accuracy designs can corral the overall temperature coefficient to about 20ppm/°C, while low-cost versions can easily exceed 1000ppm/°C.

TABLE 1. COMPARISON OF DCP AND DAC OPTIONS

TYPICAL PARAMETERS	DCP	DAC
Maximum Resolution	1024 taps (10-bit) within variable max/min	24-bit, fixed
Full-Scale Voltage	Supplies or Variable	Supplies/V _{REF}
Memory	Volatile and non-volatile available, up to 16k additional memory	None
Reported Temperature Stability	± 50ppm/°C full scale, ±4ppm/°C relative match	± 5ppm/°C typical (Gain Error)
Steps	Linear or Logarithmic	Linear
Output Drive	Resistive or Current - Some have output buffer to allow for current drive	Voltage or Current - Includes output buffer to drive low load impedance
Control Interface	Serial SPI, I ² C, up/down, push-button	Serial or parallel I ² C, SPI, QSPI, MICROWIRE, etc.

The final three aspects in Table 1 highlight more similarities between the DAC and DCP rather than the differences. Truly, both provide linear output steps. The DCP can also be chosen with logarithmic steps, making it the perfect selection for audio systems. The outputs of either the DAC or DCP can be found with an output buffer to drive small impedance loads, but it is more common to find a DCP in its “natural form” with a simple resistance at the output. The control interface can take a variety of forms. The DAC can offer parallel or serial input while the DCP can offer up/down or push-button controls. Both readily include SPI or I²C interfaces. Although straightforward, these options help govern the best choice for your application.

An example application will best illuminate the benefits of using a DCP. In base station applications (Figure 1), a DCP (ISL22343) is used as a voltage divider to adjust the gate bias on the power transmitter. It sets the amplifier bias current through the buffer and low-pass filter to optimize transmit range. The gate bias is very sensitive—if it's too small, the transmit range is sacrificed and if it's too large, distortion occurs. Setting the initial gate bias is accomplished with a voltage reference. Preserving gate bias is even more difficult in the presence of the large temperature gradients caused by heating of the output transistors. Therefore, the optimum value of gate bias is a function of multiple parameters. A DCP can store its own calibration information, directly set the gate bias for proper function, and dynamically make adjustments to incorporate information from alternate sources like temperature sensors. DACs are more precise, but have yet to incorporate so many different functions.

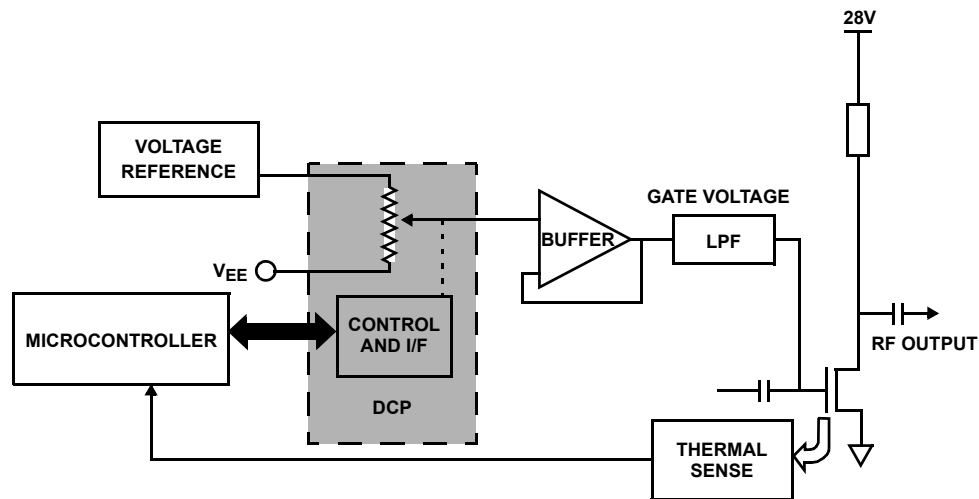


FIGURE 1. BLOCK DIAGRAM OF BASE STATION APPLICATION USING A DCP FOR THERMAL STABILITY

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.

"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.

Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
- (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338